



C. Willard Sharratt  
615 N. Lake St

**Library**  
of the  
**University of Wisconsin**

7F-9

ROBT. B. BOHMAN



**ADVANCED LABORATORY PRACTICE  
IN  
ELECTRICITY AND MAGNETISM**

*McGraw-Hill Book Co. Inc*

PUBLISHERS OF BOOKS FOR

Electrical World ∇ Engineering News-Record  
Power ∇ Engineering and Mining Journal-Press  
Chemical and Metallurgical Engineering  
Electric Railway Journal ∇ Coal Age  
American Machinist ∇ Ingenieria Internacional  
Electrical Merchandising ∇ Bus Transportation  
Journal of Electricity and Western Industry  
Industrial Engineer

**ADVANCED  
LABORATORY PRACTICE  
IN  
ELECTRICITY  
AND  
MAGNETISM**

BY  
**EARLE MELVIN TERRY, Ph.D.**  
ASSOCIATE PROFESSOR OF PHYSICS, UNIVERSITY OF WISCONSIN

**FIRST EDITION**

**McGRAW-HILL BOOK COMPANY, Inc.**  
**NEW YORK: 370 SEVENTH AVENUE**  
**LONDON: 6 & 8 BOUVERIE ST., E. C. 4**  
**1922**

**COPYRIGHT, 1922, BY THE  
MCGRAW-HILL BOOK COMPANY, INC.**

**THE MAPLE PRESS - YORK PA**



Engr

372482

2399499

LL  
.T27  
.5

ac

## PREFACE

In preparing this book, the author has had in mind particularly the needs of those students who have at their disposal only one year to devote to the study of electricity and magnetism in addition to the work covered in an elementary course in general physics. It has been his aim to include, in addition to the usual work in electrical measurements, a sufficient study of the discharge of electricity through gases, radio activity, and thermionics to enable those who cannot pursue special courses to gain an idea of the fundamentals of these newer branches.

The subject matter covers the work given to third year students in electrical engineering at the University of Wisconsin. Following the elementary work of the first nine chapters, a number of the complex bridge methods for precise measurements of inductance and capacitance are discussed, together with descriptions of the various sources of alternating currents which have been developed in recent years for energizing bridge circuits. A discussion of the more modern instruments for detecting the balance condition of bridges, together with their individual merits, has been included. This is preceded by an elementary study of "transients," in which the fundamental phenomena of reactance, necessary for an understanding of bridge methods, are set forth.

The electron tube, because of the multiplicity of its uses, finds many applications, not only in the art of radio communication, but also in engineering practice and in the general research laboratory. Considerable space has been devoted to this device, as well as to the fundamentals of the electron theory and the passage of electricity through gases.

The author is a firm believer in the laboratory method of instruction, and each exercise is preceded by a discussion of the theories involved sufficient to enable the student to understand clearly the relation of each experiment to the general field in which it lies. It is believed that with the material given in the text and the references to standard works, which have been included, the student can pursue the subject without the aid of

5 July 49 D. W. M. G. F. E.

formal lectures, although at the present time the writer is devoting one hour per week to a lecture-conference. Experience shows that the average student performs fourteen of these exercises per semester and the topics herewith presented accordingly permit of some little choice.

In selecting material, advantage has been taken not only of the original sources, but also of the standard texts in the special fields represented. Being a collection of laboratory exercises, this book makes no claim to originality of the subject matter included, and the author hereby acknowledges his indebtedness to the many books and special articles referred to in the footnotes throughout the text. He is indebted, also, to the Leeds-Northrup Company, J. G. Biddle Company, Queen & Company, General Radio Company, Tinsley & Company, and other manufacturers of electrical apparatus for supplying the cuts which have been used. In particular, he wishes to express his gratitude to Dr. H. B. Wahlin and L. L. Nettleton, instructors in physics at the University of Wisconsin, who have read the entire manuscript and made many valuable suggestions during its preparation.

E. M. TERRY.

UNIVERSITY OF WISCONSIN,  
MADISON, WIS.  
*June, 1922.*

# CONTENTS

|  | PAGE |
|--|------|
| PREFACE  | v    |
| CHAPTER I.—GENERAL DIRECTIONS—ELECTRICAL UNITS . . . . .   | 1    |
| Preparation—Connections—Keys and Switches—Rheostats—<br>Switch Board—Care of Apparatus—Notebooks—Electrostatic<br>System of Units—Electromagnetic System of Units—Practical<br>System of Units—Ratios of the Electrical Units—Rationalized<br>Practical System of Units. |      |
| CHAPTER II.—GALVANOMETERS. . . . .   | 17   |
| Thomson Galvanometer—D'Arsonval Galvanometer—Galvano-<br>meter Sensitivity—Figure of Merit—Ballistic Galvanometer—<br>Constant of Ballistic Galvanometer—Flux Meter—Checking<br>Devices.   |      |
| CHAPTER III.—MEASUREMENT OF RESISTANCE . . . . .   | 35   |
| Ohm's Law—Specific Resistance—Temperature Coefficient of<br>Resistance—Wheatstone Bridge—Measurement of Low Resistance<br>—Measurement of High Resistance—Internal Resistance of Cells—<br>Battery Test.   |      |
| CHAPTER IV.—MEASUREMENT OF POTENTIAL DIFFERENCE. . . . .   | 55   |
| Description of Potentiometer—Direct Reading Potentiometer—<br>Leeds and Northrup Potentiometer—Wolff Potentiometer—<br>Tinsley Potentiometer—Weston Standard Cell—Volt Box.  |      |
| CHAPTER V.—MEASUREMENT OF CURRENT . . . . .  | 70   |
| Kelvin's Balance—Siemen's Electrodynamometer—Ammeters and<br>Voltmeters—Adjustment of Ammeters and Voltmeters—Measure-<br>ment of Current by the Potentiometer.  |      |
| CHAPTER VI.—MEASUREMENT OF POWER . . . . .   | 82   |
| Wattmeters, Types of—Compensation of Wattmeters—Calibra-<br>tion of an Indicating Wattmeter.   |      |
| CHAPTER VII.—MEASUREMENT OF CAPACITANCE. . . . .   | 86   |
| Condensers—Grouping of Condensers—Standard Condensers—<br>Comparison of Condensers—Flemming and Clinton Commutator.  |      |
| CHAPTER VIII.—MAGNETISM . . . . .  | 95   |
| Strength of Pole—Strength of Field—Magnetic Moment—<br>Magnetic Induction—Permeability and Susceptibility—<br>Demagnetization due to Ends of a Bar Magnet—Magnetic<br>Circuit—Magnetic Units—Magnetization Curves—Hysteresis.  |      |

|  | PAGE |
|--|------|
| CHAPTER IX.—SELF AND MUTUAL INDUCTANCE . . . . .   | 117  |
| General Principles—Definition of Units of Inductance—Standards of Inductance—Measurement of Self-inductance—Measurement of Mutal Inductance.   |      |
| CHAPTER X.—ELEMENTARY TRANSIENT PHENOMENA . . . . .  | 126  |
| Time Constant—Circuit Containing Resistance and Inductance—Circuit Containing Resistance and Capacitance—Circuit containing Resistance, Inductance and Capacitance—Non-oscillatory Discharge of a Condenser—Aperiodic Discharge of a Condenser—Oscillatory Discharge of a Condenser—Logarithmic Decrement—Harmonic E. M. F. acting on a Circuit Containing Resistance, Inductance, and Capacitance—Vector Diagrams—Series Resonance—Parallel Resonance—Measurement of Inductance and Capacitance by Resonance—Effective Value of an Alternating Current—Power Consumed by a Circuit Traversed by an Alternating Current. |      |
| CHAPTER XI.—SOURCES OF ELECTROMOTIVE FORCE AND DETECTING DEVICES FOR BRIDGE METHODS. . . . .   | 151  |
| Sechometer—Wire Interrupter—Motor Generator—Microphone Hummer—Audio Oscillator—Vreeland Osallator—Electron Tube Oscillator—Telephone Receiver—Thermo Galvanometer—Vibration Galvanometer—Alternating Current Galvanometer.   |      |
| CHAPTER XII.—ALTERNATING CURRENT BRIDGES . . . . .   | 168  |
| General Considerations—Maxwell's Bridge—Anderson's Modification of Maxwell's Bridge—Stroude and Oates' Bridge—Trowbridge's Method—Heydweiller's Network—Heavieside's Bridge—Maxwell's Bridge for Mutual Inductance—Mutual Inductance Bridge—Frequency Bridge—Circuits of Variable Impedance—Motional Impedance of a Telephone Receiver—Power Factor and Capacitance of Condensers—Resistance of Electrolytes.  |      |
| CHAPTER XIII.—CONDUCTION OF ELECTRICITY THROUGH GASES. . . . .   | 198  |
| Electrons—Conductivity of Gases—Structure of the Atom—Ionization Current—Resistance of a Discharge Tube—Phenomena of the Discharge Tube—Theory of the Discharge—Field Strength at Various Points in the Discharge—Cathode Rays—Velocity and Ratio of the Charge to the Mass of an Electron—Radioactive Substances—Alpha Rays—Beta Rays—Gamma Rays—Radio active Transformations—Ionization by Radio Active Substances.  |      |
| CHAPTER XIV.—ELECTRON TUBES . . . . .  | 218  |
| Free Electrons—Electron Emission—Two Element Electron Tube—Voltage Saturation—Space Charge—Characteristics of the Two Element Electron Tube—Three Element Electron Tube—Static Characteristics—Amplification Factor—Internal Resistance of Three Element Electron Tube—Tungar Rectifier.   |      |

*CONTENTS*

ix

|  | PAGE |
|--|------|
| CHAPTER XV.—PHOTOMETER AND OPTICAL PYROMETER. . . . .  | 239  |
| Intensity of Radiation—Photometers—Lummer-Brodhun Photo-<br>meter—Study of Incandescent Lamps—General Principles of<br>Radiation—Black Body Furnace—Distribution of Energy in the<br>Spectrum—Applications to Pyrometry—Optical Pyrometer. |      |
| APPENDIX . . . . .   | 252  |
| Calculation of Self Inductance—Calculation of Capacitance.   |      |
| INDEX . . . . .  | 259  |



## LIST OF EXPERIMENTS

|   | PAGE |
|---|------|
| ✓ 1. Specific Resistance of Materials .....   | 42   |
| 2. Temperature Coefficient of Resistance .....                                      | 45   |
| ✓ 3. Insulation Resistance by Leakage .....   | 48   |
| 4. Internal Resistance of Cells by Condenser Method .....                           | 52   |
| 5. Battery Test .....   | 53   |
| 6. Comparison of E.M.F. of Cells by the Potentiometer .....                         | 66   |
| 7. Calibration of a Voltmeter by the Potentiometer and Volt Box .....               | 68   |
| 8. Calibration of an Electro-dynamometer .....                                      | 73   |
| 9. Electrical Adjustment of an Ammeter and a Voltmeter .....                        | 77   |
| 10. Calibration of an Ammeter by the Potentiometer and Standard<br>Resistance ..... | 80   |
| 11. Calibration of a Wattmeter .....  | 84   |
| 12. Comparison of Capacitances by the Bridge Method .....                           | 92   |
| 13. Capacitance by the Fleming and Clinton Method .....                             | 93   |
| 14. Magnetization Curves by Hopkinson's Bar and Yoke .....                          | 108  |
| 15. Magnetization Curves by the Rowland Ring Method .....                           | 113  |
| 16. Hysteresis Curves .....   | 114  |
| 17. Comparison of Self Inductances by the Bridge Method .....                       | 122  |
| 18. Mutual Inductance by Carey-Foster's Method .....                                | 124  |
| 19. Measurement of Inductance and Capacitance by Resonance .....                    | 148  |
| 20. Maxwell's Bridge for Self Inductance .....                                      | 171  |
| 21. Stroude and Oate's Bridge for Self Inductance .....                             | 174  |
| 22. Trowbridge's Method for Self Inductance .....                                   | 177  |
| 23. Heydweiller's Method for Mutual Inductance .....                                | 179  |
| 24. Heaviside's Bridge for Self Inductance .....                                    | 182  |
| 25. Maxwell's Bridge for Mutual Inductance .....                                    | 184  |
| 26. Comparison of Mutual Inductances .....  | 185  |
| 27. Bridge Method for Measuring Frequency .....                                     | 187  |
| 28. Motional Impedance of a Telephone Receiver .....                                | 191  |
| 29. Phase Difference and Capacitance of a Condenser .....                           | 193  |
| 30. Resistance of Electrolytes .....  | 197  |
| 31. Resistance of a Discharge Tube .....  | 202  |
| 32. Variation of Field Strength along the Discharge .....                           | 207  |
| 33. Measurement of $\frac{e}{m}$ and Velocity of an Electron .....                  | 211  |
| 34. Ionization by Radio Active Substances .....                                     | 216  |
| 35. Characteristics of the Two Element Electron Tube .....                          | 224  |
| 36. Static Characteristics of a Three Element Electron Tube .....                   | 226  |
| 37. Amplification Factor of a Three Element Electron Tube .....                     | 231  |
| 38. Plate-Filament Resistance of a Three Element Electron Tube .....                | 235  |
| 39. Study of the Tungar Rectifier .....   | 237  |
| 40. Study of Incandescent Lamps .....   | 243  |
| 41. The Optical Pyrometer .....   | 250  |





# ADVANCED LABORATORY PRACTICE

IN

## ELECTRICITY AND MAGNETISM

### CHAPTER I

#### GENERAL DIRECTIONS—ELECTRICAL UNITS

**1. Preparation.**—If one is to make the best use of his time in the laboratory, he must understand thoroughly what is to be done and then proceed in a systematic manner to do it. This can be accomplished only when preparation for the task has been made before taking up the experimental work. Assignments accordingly will be made one week in advance, and the student is expected to enter the laboratory with the following preparation:

1. An understanding of the theory of the experiment.
2. A knowledge of the working principles of the instruments to be used.
3. A schedule according to which the data are to be taken. In order to facilitate the work of the first few periods, the following general directions should be carefully read:

**2. Connections.**—A large portion of the trouble in performing electrical measurements arises from imperfect connections. All instruments, to which wires are to be attached, are provided with binding posts. To secure good contact, remove the insulation about an inch from the end of the wire, scrape it clean, wrap it two-thirds around the binding post, and then screw down the nut. If the wire is too short to reach between the points desired, join two or more wires with connectors, having first scraped the ends clean. Never join wires by twisting their ends together, as connections of this sort, unless soldered, are entirely unreliable. Do not coil wires about a rod or a pencil, since then they cannot be used again. Cut wires to the proper length, thus avoiding a complicated tangle difficult to trace, which, through leaks,

furnishes a source of constant trouble. Never allow one wire to rest upon another, even though both are covered with insulation.

Before attempting a set-up, make a rough sketch of connections, arranging the apparatus in a compact and orderly manner. This will be of great service later in checking connections and locating faults. In many cases, especially in complicated networks, a little forethought in the arrangement will save much time and inconvenience in the performance of the test. Always make the connection with the source of current supply last, having first assured yourself as to the correctness of the connections by comparison with the sketch, or by consultation with your instructor. As a further precaution, close the main switch at first only an instant, opening it at once to see if there are any indications of a short circuit. This is especially important where the source is a dynamo or a storage battery.

**3. Keys and Switches.**—Always open and close a switch quickly, to avoid burning it at the point of contact. If the

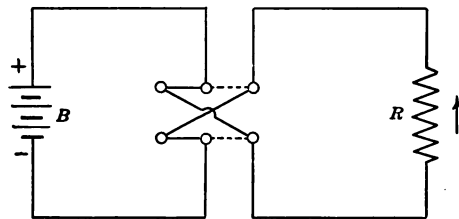


FIG. 1.—Reversing switch.

circuit includes mercury cups and connecting links, it should be broken by means of a knife switch, not by removing the link, as mercury is especially likely to arc. Ordinary contact keys should be used only where a small current is to be carried, and where variations in the resistance of the circuit introduce no serious error; as, for example, the galvanometer circuit of a Wheatstone bridge.

The device generally employed for reversing the current through any portion of a circuit is the Pohl's commutator, which consists of a double pole double throw switch with two cross wires, as shown in Fig. 1. It will be seen that when the switch is closed, as shown by the heavy lines, the current through  $R$  flows upwards, but is reversed when the switch is thrown towards the right. Since the cross wires in such a commutator are frequently

placed under the block, a double pole double throw switch should be examined carefully before it is connected in circuit, as the cross wires of the commutator may produce short circuits, resulting in serious injury to the apparatus.

**4. Rheostats.**—A rheostat is a variable resistance capable of carrying considerable current. It is used primarily as a controlling device and its value, in general, need not be accurately known. When connected in series with a source of electrical

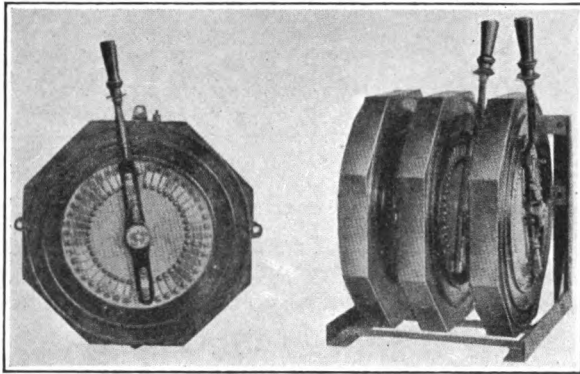


FIG. 2.—Rheostat with fixed steps.

power, the current supplied to any circuit may be varied and brought to any desired value, within certain definite limits, by changing the resistance of the rheostat. Since the energy consumed by a rheostat always appears in the form of heat, the current carrying capacity for a given resistance depends upon the provision made for dissipating heat either by conduction, convection, or radiation.

Many different forms of rheostats are in use and only a few of the more common types will be mentioned here. Figure 2 illustrates one that is frequently used for controlling relatively large currents. It consists of a number of copper lugs between which are connected units of high resistance metal in the form of a thin ribbon to give as much heat irradiating surface as possible. They are bent back and forth in a zig-zag shape and embedded in sand. With this arrangement the resistance varies by steps. By connecting two in series, one having large and the other small steps, a fairly smooth variation in current may be obtained.

Another common form of rheostat is shown in Fig. 3. A high resistance wire is wound on an insulating tube. Binding posts are connected to each end of the wire, and as the sliding contact is moved along, the resistance between it and one end of the wire changes from zero to a maximum. Wires of various sizes are frequently wound on the same tube thus giving two or more

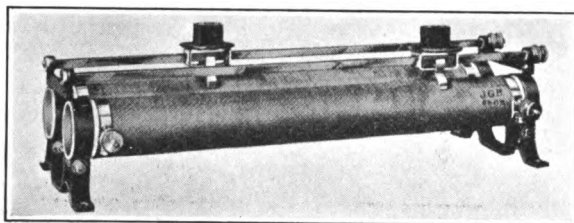


FIG. 3.—Tube rheostat.

ranges for one instrument. For carrying large currents, the ends of the tube are closed and cooling water is passed through. Such rheostats are generally wound with a ribbon to improve the thermal contact between the wire and tube. The figure shows a high resistance instrument, which may also be used as a potential divider. If the E.M.F. to be divided is connected across the end binding posts, any desired fraction of this voltage may be

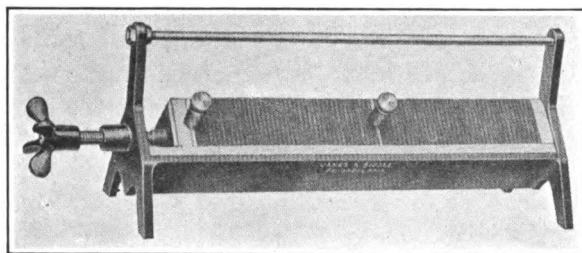


FIG. 4.—Carbon compression rheostat.

obtained by “picking off” between one end and the slider, and moving the latter back and forth.

Another device for controlling current makes use of the fact that the resistance between two carbon surfaces varies with the pressure. An instrument of this sort is shown in Fig. 4. It consists of series of rectangular carbon plates placed in a trough and arranged in such a way that they can be subjected to variable pressures by means of an adjusting screw. Rheostats of this

type are useful where low voltage currents are to be controlled. They have the disadvantage of requiring frequent readjustment since the tension changes with variations of the temperature of both the carbon plates and metal parts.

**5. Switch Board.**—A switch board is a necessary adjunct to any electrical laboratory and is used to distribute electrical power of different types and voltage to the various working circuits of the laboratory, and to connect the different circuits with one another. It consists of a panel of insulating material, usually marble, on which is mounted a series of pairs of sockets. The various laboratory and power circuits are joined to these sockets on the back of the board and connections between them are made at the front by means of flexible connectors, often called "jumpers," to the ends of which are attached plugs which fit snugly into the sockets. Power circuits are distinguished by the word "Volts." With the exception of the A.C. circuits, each terminal is labeled plus or minus. If, for example, 10 volts are desired on circuit 91, connect the positive of a 10 volt set with the positive of 91, and similarly for the negative, when the polarity at the laboratory end will be found as indicated. If some voltage is desired, e.g., 16 volts, for which there is no separate set, connect two or more sets in series, joining plus to minus as though connecting cells on a table; then, considering the group as a single set, connect to the laboratory terminals as above. If a current larger than the normal rated capacity of the storage battery is desired, use the dynamo or connect in parallel two or more sets of equal voltage. To do the latter, join all the positive terminals, similarly the negatives, and then connect to the laboratory terminals as above. Before making switch board connections, be sure that the circuit switch in the laboratory is open. Connect the "dead" ends first, and, before pushing in the final plug closing the circuit, tap it cautiously against the socket, quickly withdrawing it. If a spark is seen, some error in connection has been made which must be located before the circuit is closed. Never connect in parallel on a battery with some one else without first obtaining his permission.

**6. Care of Apparatus.**—Electrical apparatus is delicate and expensive, and it is necessary to proceed with the utmost caution. If an instrument is provided with a shunt, use the smallest resistance first; or, if protected by a series resistance, use the largest value first decreasing it until the desired value has been

reached. If an instrument fails to work, do not replace it in the case and get another, but report at once to the instructor. Resistance boxes are most frequently injured by carrying too large currents. Before closing the main switch, look over the connections and make a rough calculation of the current that will flow in each box. In no case should the power consumed by a single coil, given by  $I^2R$ , be more than four watts. Plugs should be seated by a gentle pressure, accompanied by a twisting motion, heavy pressure being unnecessary.

Never move galvanometers from one place to another without first making sure that the weight of the moving system has been removed from the suspension by means of the arrestment which is always provided. Standard cells should never be tipped up for purposes of inspection or otherwise, and should not be used as a source of current, but merely for balancing potentials; and even here, a large series resistance should at first be included and cut out as a balance is approached. Ammeters are instruments for measuring the total current flowing, and should be connected in series with the circuit, analogous to a water meter. They are most frequently injured by the passage of too large currents. If the arrangement of the apparatus is not such that the current can approximately be calculated before the circuit is closed, a sufficiently large rheostat should be included and cautiously cut out, the instrument being watched in the meantime. Voltmeters are electrical pressure gauges, indicating the difference of potential between the points to which their terminals are attached, and are accordingly connected in parallel with the circuit. Most voltmeters are provided with two scales; and in such cases, one should use the larger first, transferring to the smaller one if the voltage is found to be less than the lower full scale reading. Before leaving the laboratory, return all apparatus to its proper place in the cases. Wires less than a foot long should be thrown in the waste box, and the others returned to their hooks in the wire cabinet. Switch board connectors should be pulled and returned to the proper hooks. Leave the laboratory as tidy as you found it.

**7. Notebooks.**—All data, as they are taken during an experiment, should be recorded in tabular form in a rough notebook with bound leaves. Ascertain from the instructor specific directions regarding the form in which the final report is to be made, and in its preparation observe the following outline:

1. Give name of experiment and references.
2. Enumerate apparatus used, giving number of each piece.
3. Make a sketch (not a picture) including all instruments, resistance boxes, switches, etc., which will show the actual path of the current. (Use a ruler and dividers.)
4. Give the theory of the experiment as fully as possible, deriving all formulae used.
5. Outline briefly the method of procedure, mentioning special precautions to be taken and difficulties to be overcome.
6. Tabulate your data, arranging it in compact form. State the units in which your results are expressed.
7. Plot curves showing your results graphically, using as ordinates the dependent variable. Choose scales such that the curves will cover as nearly as possible the entire sheet, labeling axes and putting the scale along each. Draw in a smooth curve, striking an average between outstanding points.
8. Give a brief discussion of results, including estimates of accuracy and sources of error.
9. Answer all questions asked under special directions at the end of each experiment.

#### ELECTRICAL AND MAGNETIC UNITS

**8. Systems of Units.**<sup>1</sup>—There are two distinct systems of units used in the measurement of electrical quantities; the electrostatic and the electromagnetic. In the former, the fundamental unit is determined by means of the repulsion between two similar charges of electricity, while in the latter, it is based upon the repulsion of two similar magnetic poles. Both of these systems may properly be termed “absolute” since all the quantities involved are directly expressible in terms of the fundamental units of length, mass, and time. The ratio between corresponding units of these two systems is some power of the velocity of light. In actual practice, however, neither of these systems is used, since, in general, the quantities therein defined are not of such magnitudes as to be convenient working units. A third system, known as the “practical system,” has accordingly been devised, in which all the units are decimal multiples of the corresponding electromagnetic units. The units of this system are

<sup>1</sup> EVERETT, The C. G. S. System of Units, chap. X, XI.  
Electrical Meterman's Handbook, chap. II.

the only ones to which names have been given, and it has been the custom of the international conferences by which they have been defined, to honor scientists, famous in the fields in which the units lie, by giving to them their names. Electrical quantities, expressed in the electrostatic and electromagnetic systems, are designated by the letters E.S.U. and E.M.U., respectively.

#### FUNDAMENTAL ELECTRICAL UNITS

**9. Magnetic Units.** *Magnetic Pole Strength.*—The unit magnetic pole is a pole of such strength that it repels a like pole at a distance of one centimeter, in air, with a force of one dyne.

*Magnetic Field Strength.*—A magnetic field of unit intensity is a field that acts upon a unit magnetic pole placed in it, with a force of one dyne.

**10. Electrostatic Units.** *Quantity.*—The electrostatic unit of quantity is of such a magnitude that it repels a like quantity at a distance of one centimeter, in air, with a force of one dyne.

*Current.*—The electrostatic unit of current exists when an electrostatic unit of quantity flows past any plane in a conductor per second.

*Potential Difference.*—Unit electrostatic difference of potential exists between two points when the amount of work required to carry an electrostatic unit of quantity from one to the other is one erg.

*Resistance.*—A conductor possesses the electrostatic unit of resistance if, when carrying the electrostatic unit of current, the difference of potential across its terminals is one electrostatic unit.

*Capacitance.*—A condenser possesses an electrostatic unit of capacitance if the electrostatic unit of potential difference across its terminals gives to it the electrostatic unit of charge.

*Inductance.*—A coil possesses an electrostatic unit of inductance if, when the inducing current is changing at the rate of one electrostatic unit per second, the induced electromotive force is one electrostatic unit. This applies both to self and mutual induction.

**11. Electromagnetic Units.** *Current.*—The electromagnetic unit of current is a current such that, when flowing through an arc of one centimeter length of a circle of one centimeter radius, it produces, at the center, a unit magnetic field.

*Quantity.*—The electromagnetic unit of quantity is that quan-



tity which passes, per second, any plane of a conductor in which the electromagnetic unit of current is flowing.

*Potential Difference.*—The electromagnetic unit of potential difference exists between two points when the amount of work required to carry the electromagnetic unit of quantity from one to the other is one erg.

*Resistance.*—A conductor possesses the electromagnetic unit of resistance, if, when carrying the electromagnetic unit of current, the difference of potential across its terminals is one electromagnetic unit.

*Capacitance.*—A condenser possesses the electromagnetic unit of capacitance if the electromagnetic unit of potential difference across its terminals gives to it one electromagnetic unit of charge.

*Inductance.*—A coil possesses an electromagnetic unit of inductance if, when the inducing current varies at the rate of one electromagnetic unit per second, the induced electromotive force is one electromagnetic unit.

**12. Practical Units.** *Current.*—An ampere is one-tenth of an electromagnetic unit of current.

*Quantity.*—The coulomb is the quantity of electricity which passes per second any plane of a conductor in which the current is one ampere.

*Potential Difference.*—The difference of potential between two points is one volt when the amount of work required to carry one coulomb from one to the other is one joule.

*Resistance.*—A conductor possesses a resistance of one ohm if, when carrying a current of one ampere, the difference of potential across its terminals is one volt.

*Capacitance.*—A condenser possesses a capacitance of one farad if a difference of potential of one volt across its terminals gives it a charge of one coulomb.

*Inductance.*—Two coils possess a mutual inductance of one henry if, when the primary current is changing at the rate of one ampere per second, the electromotive force induced in the secondary is one volt.

A coil possesses one henry of self-inductance if, when the current through it is varying at the rate of one ampere per second, the induced counter electromotive force is one volt. One milli-henry equals 0.001 henry.

*Magnetic Flux.*—The total flux in a magnetic circuit is one maxwell when it possesses one magnetic line of induction.

*Magnetic Induction.*—The induction in a magnetic circuit is one gauss when the flux density is one maxwell per square centimeter.

*Magnetomotive Force.*—The magnetomotive force of a magnetic circuit is one gilbert if the work required to carry a unit magnetic pole once around the circuit is one erg.

*Field Strength.*—A magnetic field possesses unit strength if the magnetomotive force is one gilbert per centimeter. (This definition is identical with that previously given for field strength.)

*Reluctance.*—A magnetic circuit possesses a reluctance of one oersted if a magnetomotive force of one gilbert produces a flux of one maxwell.

**13. Legal Definitions of the Practical Units.**—At the last International Conference on Electrical Units and Standards, which met in London, in 1908, the following resolutions were adopted, which have served as the basis for legislation in the different countries of the world for fixing the legal definitions of the fundamental electrical units now in force. The full report of this Conference, in which 21 different nations were represented, may be found in *The Electrical Review*, vol. 63, (1908), page 738.

#### RESOLUTIONS

I. The Conference agrees that as heretofore the magnitude of the fundamental electric units shall be determined on the electromagnetic system of measurements with reference to the centimeter as the unit of length, the gram as the unit of mass, and the second as the unit of time.

These fundamental units are (1) the ohm, the unit of electric resistance which has the value of 1,000,000,000 in terms of the centimeter and second; (2) the ampere, the unit of electric current which has the value of one-tenth (0.1) in terms of the centimeter, gram, and second; (3) the volt, the unit of electromotive force which has the value of 100,000,000 in terms of the centimeter, the gram, and the second; (4) the watt, the unit of power, which has the value of 10,000,000 in terms of the centimeter, the gram, and the second.

II. As a system of units representing the above and sufficiently near to them to be adopted for the purpose of electrical measurements and as a basis for legislation, the Conference recommends

the adoption of the International ohm, the International ampere, and the International volt, defined according to the following definitions.

III. The ohm is the first primary unit.

IV. The International ohm is defined as the resistance of a specified column of mercury.

V. The International ohm is the resistance offered to an unvarying electric current by a column of mercury at the temperature of melting ice, 14.4521 grams in mass, of a constant cross-sectional area and of a length of 106.300 cm.

To determine the resistance of a column of mercury in terms of the International ohm, the procedure to be followed shall be that set out in specification I, attached to these resolutions.

VI. The ampere is the second primary unit.

VII. The International ampere is the unvarying electric current which, when passed through a solution of nitrate of silver in water, in accordance with the specification II, attached to these resolutions, deposits silver at the rate of 0.00111800 of a gram per second.

VIII. The International volt is the electrical pressure which, when steadily applied to a conductor whose resistance is one International ohm, will produce a current of one International ampere.

IX. The International watt is the energy expended per second by an unvarying electric current of one International ampere under an electric pressure of one International volt.

The Conference recommends the use of the Weston Normal Cell as a convenient method of measuring both electromotive force and current, and when set up under the conditions specified in schedule C, may be taken, provisionally, as having, at a temperature of 20° C., an E.M.F. of 1.0184 volts.

**14. The New Value of the Weston Standard Cell.**—Since the meeting of the London Conference, a large amount of research has been carried on at the Bureau of Standards at Washington on the Weston Cell and the electrochemical equivalent of silver; and it has been found that the electromotive force of this cell, in terms of the International ohm and International ampere, is, within one part in 10,000,

$$E = 1.0183 \text{ International volts at } 20^{\circ} \text{ C.},$$

and this value was adopted by the Bureau of Standards Jan. 1,

1911. The formula for the temperature coefficient of the Weston Cell adopted by the London Conference, based on the investigations of the Bureau of Standards, is as follows:

$$E_t = E_{20} - .0000406 (t - 20^\circ) - .00000095 (t - 20)^2 + .00000001 (t - 20)^3 \quad (1)$$

**15. Ratios of the Electrical Units.**—For convenience of comparison the dimensions of the electrostatic and electromagnetic units are given below. The dimensions of the dielectric constant and the permeability are unknown and are inserted in the formula as  $\kappa$  and  $\mu$ , respectively. All that is known concerning the nature of these quantities is that  $\frac{1}{\sqrt{\kappa\mu}}$  equals  $v$ , equals  $3 \times 10^{10}$  cm. per second, the velocity of light in free space. The last column gives the ratio of the corresponding units in the two systems, in terms of  $v$ .

| Unit            | Electro-magnetic                   | Electro-static                        | Electro-magnetic                   | E. M. U. |
|-----------------|------------------------------------|---------------------------------------|------------------------------------|----------|
|                 |                                    |                                       | Electro-static                     | E. S. U. |
| Quantity.....   | $[M^{1/2}L^{1/2}\mu^{-1/2}]$       | $[M^{1/2}L^{3/2}T^{-1}\kappa^{1/2}]$  | $[L^{-1}T\kappa^{-1/2}\mu^{-1/2}]$ | $v$      |
| Current.....    | $[M^{1/2}L^{1/2}T^{-1}\mu^{-1/2}]$ | $[M^{1/2}L^{3/2}T^{-2}\kappa^{1/2}]$  | $[L^{-1}T\kappa^{-1/2}\mu^{-1/2}]$ | $v$      |
| Pot. diff.....  | $[M^{1/2}L^{3/2}T^{-2}\mu^{1/2}]$  | $[M^{1/2}L^{1/2}T^{-1}\kappa^{-1/2}]$ | $[LT^{-1}\kappa^{1/2}\mu^{1/2}]$   | $v^{-1}$ |
| Resistance..... | $[LT^{-1}\mu]$                     | $[L^{-1}T\kappa^{-1}]$                | $[L^2T^{-2}\kappa\mu]$             | $v^{-2}$ |
| Capacity.....   | $[L^{-1}T^2\mu^{-1}]$              | $[L\kappa]$                           | $[L^{-2}T^2\kappa^{-1}\mu^{-1}]$   | $v^2$    |
| Inductance..... | $[L\mu]$                           | $[L^{-1}T^2\kappa^{-1}]$              | $[L^2T^{-2}\mu\kappa]$             | $v^{-2}$ |

The following table gives the practical units in terms of the corresponding units of both the electromagnetic and the electrostatic systems:

|              |   |            |            |   |                              |            |
|--------------|---|------------|------------|---|------------------------------|------------|
| 1 Ampere     | = | $10^{-1}$  | E. M. U.'s | = | $3 \times 10^9$              | E. S. U.'s |
| 1 Coulomb    | = | $10^{-1}$  | E. M. U.'s | = | $3 \times 10^9$              | E. S. U.'s |
| 1 Volt       | = | $10^8$     | E. M. U.'s | = | $\frac{1}{3 \times 10^2}$    | E. S. U.'s |
| 1 Ohm        | = | $10^9$     | E. M. U.'s | = | $\frac{1}{9 \times 10^{11}}$ | E. S. U.'s |
| 1 Farad      | = | $10^{-9}$  | E. M. U.'s | = | $9 \times 10^{11}$           | E. S. U.'s |
| 1 Microfarad | = | $10^{-15}$ | E. M. U.'s | = | $9 \times 10^6$              | E. S. U.'s |
| 1 Henry      | = | $10^9$     | E. M. U.'s | = | $\frac{1}{9 \times 10^{11}}$ | E. S. U.'s |

## THE RATIONALIZED PRACTICAL SYSTEM OF UNITS

**16. Advantages of the Rationalized System.**—In the discussion of the practical system it was pointed out that our present working units are decimal multiples of the corresponding units of the electromagnetic system. In fixing these ratios the international conferences have selected values in such a way that the electrical quantities commonly measured are expressed by numbers of ordinary magnitude. This, in reality, constitutes a mixed system of units, and, as a result, many of the formulæ used in every day calculations contain factors such as  $10^{-1}$ ,  $10^8$ ,  $10^9$ , etc. Again, a system based upon the unit magnetic pole and the unit electric charge as given in paragraphs 9 and 10, respectively, inevitably leads to many formulæ in which the factor  $4\pi$  appears.

It has been pointed out by Perry<sup>1</sup> and by Fessenden<sup>2</sup> that by properly choosing new units for magnetomotive force and field strength, and by submerging the factor  $4\pi$  in the arbitrary constants defining the dielectric and magnetic properties of materials, that these objectionable factors may be eliminated, and all that Heaviside sought to accomplish by his "Rationalized System of Units," realized. In an admirable paper entitled "A Digest of the Relations between the Electrical Units and the Laws underlying the Units," Bennett<sup>3</sup> has carried out the suggestions of Perry and Fessenden and has developed a consistent series of defining equations and working formulæ in which the objectionable factors are suppressed, and has clearly set forth the relations between the units of the different systems. In this treatment, a new unit of force, the "Dyne-seven" (equal to  $10^7$  dynes) has been introduced. The advantage of this unit is obvious, since, when acting through one centimeter, it performs one joule of work.

**17. Definitions.** 1. *Unit Quantity of Electricity.*—The method followed here is similar to that of the electrostatic system in that the unit of charge is taken as the fundamental unit, and its magnitude is arrived at by an application of Coulomb's law, namely,

$$F = \frac{Q_1 Q_2}{kd^2}$$

<sup>1</sup> PERRY, *Electrician*, vol. 27, 1891, p. 355.

<sup>2</sup> FESSENDEN, *Electrical World*, vol. 34, 1899, p. 901.

<sup>3</sup> Bull. 880, Univ. of Wisconsin.

Where  $Q_1$  and  $Q_2$  are two charges of electricity placed  $d$  cm. apart. The quantity  $k$  is a constant depending upon the medium in which the charges are placed, and for free space is arbitrarily put equal to  $\frac{1}{9 \times 10^{11}}$ . If  $Q_1 = Q_2 = 1$  and  $d = 1$ , then  $F = 9 \times 10^{11}$  dyne sevens. Accordingly the coulomb is that quantity of electricity which repels a similar quantity at a distance of one centimeter in a vacuum with a force of  $9 \times 10^{11}$  dyne sevens. The coulomb, as thus defined, is identical with that defined in the practical system of Art. 12.

2. *Permittivity of a Medium.*—The factor  $k$  in the expression for Coulomb's law is called the dielectric constant of the medium.

Since in many formulæ the factor  $\frac{k}{4\pi}$  appears, it is expedient to replace  $k$  by a new medium constant defined by the relation

$$p = \frac{k}{4\pi}$$

and Coulomb's law is then written

$$F = \frac{Q_1 Q_2}{4\pi p d^2}$$

The quantity  $p$  is called the permittivity of the medium, and for free space has the numerical value

$$p = \frac{k}{4\pi} = \frac{1}{4\pi \cdot 9 \times 10^{11}} = 8.84 \times 10^{-14}$$

The relative permittivity of a substance is the ratio of the permittivity of the substance to the permittivity of free space, and is thus numerically equal to the dielectric constant or specific inductance capacity as ordinarily defined.

3. *Unit of Current; the Ampere.*—A current of one ampere is flowing in a circuit if the quantity passing any plane in the circuit per second is one coulomb.

4. *Unit of Potential Difference; the Volt.*—A difference of potential of one volt exists between two points if the work required to carry one coulomb from one point to the other is one joule.

5. *Unit of Resistance; the Ohm.*—A conductor has a resistance of one ohm if a difference of potential between its terminals of one volt maintains a current of one ampere.

6. *Unit of Capacitance; the Farad.*—A condenser has a capacitance of one farad if a charge of one coulomb produces differences of potential between its plates of one volt.

7. *Unit of Inductance; the Henry.*—A coil has an inductance of one henry if a current through it, changing at the rate of one ampere per second, induces within it an E.M.F. of one volt.

8. *Line of Magnetic Intensity.*—By a line of magnetic intensity or a line of force in a magnetic field is meant any line which is traced out by the center point of a small plane direction-finding coil,<sup>1</sup> as the coil is moved in the direction pointed out by its normal axis. Such lines are always found to be closed loops, which either link with electric currents or pass through magnets.

9. *Magnetic Flux Density.*—The magnetic flux density,  $B$ , at a point in a magnetic field is defined as a vector quantity whose direction is the positive direction along the line of magnetic intensity passing through the point, and whose magnitude is equal to the force upon a straight wire one centimeter in length carrying a current of one ampere, the direction of the wire making a right angle with a line of magnetic intensity through the point.

*Unit of Flux Density.*—The Weber per square centimeter.—If a wire one centimeter in length carrying a current of one ampere, in a direction at right angles to the lines of magnetic intensity is acted upon by a force of one dyne seven, the flux density is one weber per square centimeter. One weber per square centimeter equals  $10^8$  gauss.

10. *Relation Between the Magnetic Flux Density and the Current Causing the Field.*—Experimental measurements show that at any point in a field, free from iron, the value of the magnetic flux density,  $B$ , is directly proportional to the value of the current producing the field. For the special case of an annular ring uniformly wound with a coil of  $N$  turns, carrying a current  $I$ , experimental measurements show that the lines of magnetic intensity are circles lying within the ring as illustrated in Fig. 57 and that the value of the flux density,  $B$ , is uniform along each circle and has the value

$$B = \mu \frac{NI}{L}$$

<sup>1</sup> A direction-finding coil is a small plane circular coil carrying a continuous current. The coil is so mounted on gimbals that its normal axis is free to take any direction. The normal axis is a line perpendicular to the plane of the coil at its center. The positive direction along the normal axis is defined to bear the same relation to the direction of the current around the coil that the direction of advance of a right-hand screw bears to its direction of rotation. This is called the right-hand screw convention.

in which  $L$  is the length of the circle.  $\mu$  is a constant having the value  $1.257 \times 10^{-8}$  for all except ferromagnetic materials.

11. *Permeability*.—The constant  $\mu$ , which appears in the equation expressing the relation between the flux density and the current, is called the permeability of the medium in which the magnetic field is set up. It is a constant analogous to conductivity in the conducting field and to permittivity in the electric field. This unit is called the weber per ampere turn per centimeter and is equal to  $4\pi \times 10^{-9}$  units of permeability as defined in the unrationalized practical system.

12. *Magnetic Intensity*.—The defining equation of (10) may be written in the form

$$\frac{B}{\mu} = \frac{NI}{L}$$

The expression  $\frac{B}{\mu}$  appears in so many calculations dealing with magnetic fields that, for the sake of convenience, the name “magnetic intensity” or “strength of field” is given to it. It is seen to be equal to the number of ampere turns per centimeter. This unit of field strength is called the ampere turn per centimeter and is equal to  $\frac{10}{4\pi}$  gilberts per centimeter.

13. *Magneto-motive Force*.—The line integral  $\int Hdl$  for any closed magnetic circuit is called the magneto-motive force for that circuit. For the simple circuit of Fig. 57 we have  $\int Hdl = HL = NI$ . The unit of magneto-motive force is the “Ampere Turn” and is equal to  $\frac{4\pi}{10}$  gilberts.

14. *Reluctance, Ampere Turn per Weber*.—A magnetic circuit possesses a reluctance of one ampere turn per weber if a magneto-motive force of one ampere turn produces a flux of one weber. One ampere turn per weber equals  $\frac{10^9}{4\pi}$  oersteds.



## CHAPTER II

### GALVANOMETERS<sup>1</sup>

**18. Description of a Galvanometer.**—A galvanometer is an instrument for the detection and measurement of very small electric currents. Strictly speaking, when used merely for the detection of an electric current, as, for example, in determining the balance condition for a Wheatstone bridge or a potentiometer, it should be called a galvanoscope, and the term galvanometer restricted to the case in which it is standardized and used for the accurate measurement of currents. The fundamental principle upon which all galvanometers operate is the reaction between a current and a magnetic field, one of which is fixed and the other movable. There are two types of instruments, named after their originators, and known respectively as the Thomson and the D'Arsonval types.

**19. Thomson Galvanometer.**—The Thomson galvanometer was invented by William Thomson (Lord Kelvin) and was first used as a detecting instrument in connection with the trans-Atlantic cable. It uses fixed coils and moving magnets, the axes of which are placed at right angles to the fields produced by the current in the coils. A high sensitivity requires, among other things, that the restoring torque on the moving system should be as small as possible. This is accomplished by use of the so-called astatic system which is illustrated in Fig. 5. A rigid rod, *BC*, usually a slender glass tube, is suspended by a very fine quartz fibre *AB*. This rod carries two systems of magnets *NS* placed with their planes accurately parallel, but with polarities reversed. If the magnetic moments of the two groups of magnets are equal, then when the system

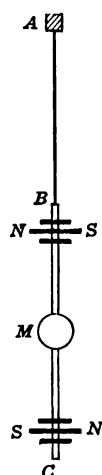


FIG. 5.  
Astatic  
needle  
system.

<sup>1</sup> LAWS, *Electrical Measurements*, chap. I.

BROOKS and POYSER, *Magnetism and Electricity*, chap. XIX.

HADLEY, *Magnetism and Electricity*, chap. XVI.

is placed in a uniform magnetic field, it will remain in any position in which it is placed, since the torque on one group of magnets is balanced by that on the other.

The fixed coils which carry the current to be measured are wound in opposite directions so that the reactions of their fields upon the magnets of the moving system give torques in the same direction. By making the system very light, e.g., a few milligrams, and by using a very fine quartz fibre for suspension, it is possible, with this type of instrument, to measure currents of the order of  $10^{-12}$  amperes. Since the fields due to currents of such magnitudes are very weak, slight gradients in the external field produce relatively large differences in the torques upon the upper and lower magnet systems, and unsteadiness of the zero position results. Galvanometers of this type must, therefore, be carefully shielded magnetically.

Magnetic shields<sup>1</sup> may be either spherical or cylindrical in shape, but since no openings may be permitted without serious reduction in effectiveness, the latter form is usually employed. It has been found that if the iron is all concentrated in a single cylindrical shell having an outside diameter five times that of the inner, the effectiveness is 98 per cent of that of a shield having an infinite thickness. Furthermore, for a given amount of iron, the effectiveness is greatly increased by using several concentric cylinders. For extreme sensitivity, Thomson galvanometers are made very small, and the coils are often mounted in a solid iron container made by splitting a soft iron rod longitudinally and drilling small holes in each half to receive the coils.

**20. D'Arsonval Galvanometer.**—The D'Arsonval galvanometer consists of a fixed, permanent horse-shoe magnet and a light coil suspended between the pole pieces by a fine phosphor-bronze ribbon, the plane of the coil being parallel to the direction of the field. The current is led to the coil by the supporting ribbon and away by a helix of the same material attached at the bottom. While this type of instrument cannot be made as sensitive as the Thomson, it has the following special advantages: (a) The deflections are but little affected by variations in the external magnetic field; (b) the instrument may face in any direction; (c) the moving system may be made aperiodic, thus avoiding loss of time in waiting for it to come to rest. For these reasons, except where extreme sensitivity is required, the D'Arsonval

<sup>1</sup> WILLS, *Physical Review*, vol. 24, 1907, p. 243.

galvanometer has practically replaced the Thomson for general laboratory work.

There are two distinct purposes for which galvanometers are used: (a) The measurement of small currents, and (b) the measurement of small quantities of electricity, such as are obtained by the discharge of condensers. When designed for the first purpose, they are called "current galvanometers" and for the second, "ballistic galvanometers."

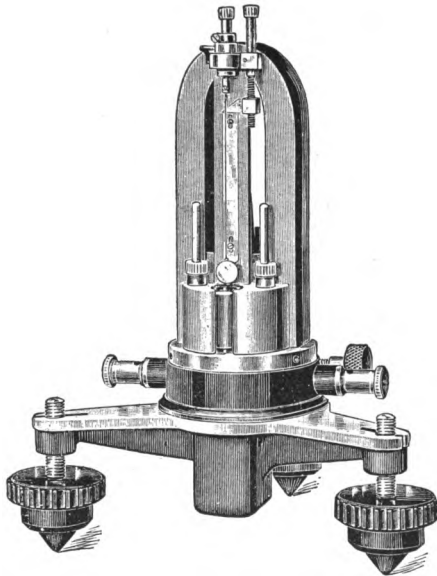


FIG. 6.—High sensitivity galvanometer with cover removed.

**21. The Current Galvanometer.**—Figure 6 shows a high sensitivity current galvanometer manufactured by the Leeds and Northrup Company. The permanent magnet is mounted in a vertical position and is provided with pole tips shaped so as to give a nearly cylindrical gap between them. Coaxial with this gap is placed a cylinder of soft iron and the coil rotates in the annular space thus formed. The suspension is carried on a rod supported by a bracket from the magnet. A set screw permits a vertical adjustment of the coil and the knurled head, which projects through the top of the case, gives a rough adjustment for zero position on the scale. A slow motion screw at the base of the instrument gives the final zero setting. The axis of the coil

is made to coincide with that of the gap by means of three leveling screws which support the instrument. These screws are turned by heavy vulcanite nuts which give, at the same time, good insulation from ground. The right hand screw at the top operates an arresting device by means of which the weight of the coil may be taken off the suspension when the instrument is being moved. A cylindrical case, provided with a window to pass light to and from the mirror, protects the system against air currents.

**22. Galvanometer Sensitivity.**—If several galvanometers, selected at random, are connected in series and a definite current is sent through them, it will be found that there are marked differences in the response made by the individual instruments. Those showing greater responses are said to have higher sensitivities. The indication of a galvanometer is usually read by means of a beam of light reflected from a mirror, attached to the moving system, on a fixed scale. Obviously, for a given motion of the system, the indication will be proportional to the distance from mirror to scale, and so it is customary, when comparing galvanometers, to place the scale at a distance of one meter, and to read the deflection in millimeters. The sensitivity of galvanometers is defined in a number of ways among which the following are the most common:

(a) *Microampere Sensitivity.*—This is defined as the deflection in millimeters of a spot of light on a scale one meter from the mirror when the deflecting current is one microampere.

(b) *Microvolt Sensitivity.*—By this is meant the deflection in millimeters of a spot of light on a scale one meter from the mirror when an E.M.F. of one microvolt is impressed across the terminals of the galvanometer.

(c) *Megohm Sensitivity.*—By this is understood the number of megohms which must be placed in the galvanometer circuit in order that with an impressed E.M.F. of one volt there results a deflection of one millimeter on the scale whose distance is one meter.

The dependence of the sensitivities, as just defined, upon the constants of the instrument and the relations between them may be understood from the following considerations. It will be assumed that the coil is rectangular in shape and that it is so supported as to be capable of rotation about a vertical axis of symmetry. It will also be assumed that the field is radial,

uniform and horizontal, as shown in Fig. 7. A field of this sort is obtained by means of a cylindrical core between properly shaped pole pieces, and has the advantage that, for a constant current through the coil, the torque is independent of its angular position.

Let  $l$  be the length of the coil;  $b$  its width;  $n$  the number of turns; and  $H$  the strength of the field in which it is placed. Calling  $T$  the torque on the coil when the current flowing through it is  $i$ , we have, if  $c, g, s$  units are used,

$$T = Hinlb \tag{1}$$

The quantity  $nlb$ , that is, the product of the number of turns and the area of the coil, is frequently called the "equivalent winding surface." Designating this by  $E$  we have

$$T = HiE = Ci \tag{2}$$

where  $C$ , equal to  $HE$ , is the torque for unit current and is called the "Dynamic Constant" for the instrument.

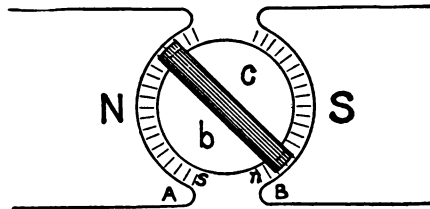


FIG. 7.—Diagram of moving coil galvanometer.

As the coil rotates, it twists the supporting metallic ribbon which exerts an elastic counter torque proportional to the angle of twist, and the coil takes an equilibrium position such that the two torques balance each other. Designating by  $\tau$  the constant of the suspension, that is, the restoring torque when it is twisted through an angle of one radian, the angular deflection  $\theta$  for a given current  $i$  satisfies the relation

$$\tau\theta = Ci \tag{3}$$

Letting  $A$  equal the angular displacement resulting from unit current we have

$$A = \frac{C}{\tau} = \frac{HE}{\tau} \tag{4}$$

$A$  is the angular displacement in radians resulting from one C.G.S. unit of current and is, accordingly, the current sensitivity in C.G.S. units. The microampere sensitivity, as defined above, may be obtained from eq. (4) in the following manner: For

small deflections, the angular displacement of the system is proportional to the linear displacement of the spot of light along the scale. Moreover, the angular displacement of the reflected beam is twice that of the reflecting mirror. Accordingly, a deflection  $A$  in radians is equivalent to a deflection  $2,000A$  when expressed as the deflection in millimeters of a spot of light along a scale at a distance of one meter from the mirror.

Again, if the current is measured in microamperes instead of C.G.S. units, it follows, since 1 microampere is  $10^{-7}$  C.G.S. units, that the right-hand member of eq. (4) must be divided by  $10^7$  for this case. Therefore, replacing  $A$  by its value  $S$  divided by 2,000, where  $S$  is the deflection in millimeters due to one microampere, we have

$$S = \frac{C}{\tau} \times 2 \times 10^{-4} \quad (5)$$

This is the microampere sensitivity and is seen to be .0002 times the ratio of the dynamic constant to the suspension constant.

It is easily seen that the megohm sensitivity defined above is numerically equal to the microampere sensitivity just discussed. For, if  $S$  is the deflection in millimeters due to one microampere, then the current in amperes required for a deflection of millimeter is  $\frac{1}{S \cdot 10^6}$ . Let  $M$  be the megohm sensitivity; that is, the number of megohms placed in series such that the deflection is 1 millimeter when the E.M.F. is 1 volt. By Ohms law,

$$i = \frac{1}{S \cdot 10^6} = \frac{1}{M \cdot 10^6} \text{ whence } M = S \quad (6)$$

To obtain the relation between the microampere and the microvolt sensitivity, let it be supposed that a difference of potential of 1 microvolt is impressed across the galvanometer. The current  $i$  in microamperes is given by

$$i = \frac{1}{R} \quad (7)$$

where  $R$  is the resistance of the galvanometer. The resulting deflection  $V$ , or the microvolt sensitivity is, accordingly,

$$V = Si = \frac{S}{R} \quad (10)$$

Thus the microvolt sensitivity is obtained by dividing the microampere sensitivity by the resistance of the coil.

**23. Figure of Merit.**—While the definitions of galvanometer sensitivity given above are convenient for distinguishing the

properties of one galvanometer from another, they are not well suited to the practical case in which the instrument is to be standardized and used for the measurement of currents. Here it is simpler to use the relation

$$i = \frac{\tau\theta}{C} = Fd \tag{11}$$

If  $d$  is the deflection in millimeters at a meter distance and  $i$  is in amperes,  $F$  is called the "figure of merit" or simply the "constant" of the galvanometer and is defined as the current in amperes required to produce a deflection of 1 millimeter at a distance of 1 meter. The smaller  $F$ , the greater is the sensitivity of the instrument.

To determine the figure of merit of a galvanometer it is merely necessary to pass known currents through the instrument and measure the deflections they produce. These currents may be supplied through a standardized variable resistance by a cell of known E.M.F., and computed by Ohm's law. Since, for most galvanometers, the required current is very small, the arrangement shown in Fig. 8 is generally employed. By making  $P$  small, usually 10 or 100 ohms, and  $Q$  large, 1,000 or 10,000 ohms, only a small fraction of the E.M.F. of the cell is effective in sending a current to the galvanometer  $G$ , and this current may be still further reduced by making  $R$  large. If  $R + G$  is large in comparison to  $P$ , the fall of potential across  $P$  is

$$e = \frac{P}{P + Q} E \tag{12}$$

where  $E$  = E.M.F. of cell read by the voltmeter  $VM$ . The current  $i$  through the galvanometer is

$$i = \frac{e}{R + G} = \frac{P}{P + Q} \frac{E}{R + G} \tag{13}$$

and the constant  $F$  is given by

$$F = \frac{PE}{(P + Q)(R + G)} \frac{1}{d} \tag{14}$$

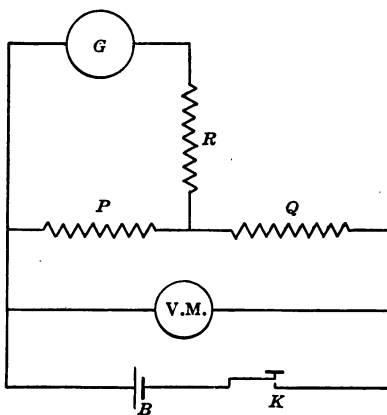


FIG. 8.—Connection for figure of merit.

Since, in no galvanometer, is the deflection strictly proportional to current, it is necessary, in making a standardization, to use currents giving deflections over the entire range for which the instrument is to be used, determining from each a value of  $F$  which, when plotted as ordinates against  $d$ , as abscissas, gives a working curve showing  $F$  as a function of the deflections.

**24. The Ballistic Galvanometer.**—The ballistic galvanometer, which may be of either the moving coil or the moving magnet type, differs from the current galvanometer in that its moving system has a large moment of inertia, giving it a long period of vibration. If, while the system is at rest, a small quantity of electricity, such as a condenser charge, is suddenly passed through it, during the small interval of time that this electricity is flowing, there will be a torque acting on the system. This torque must be of very short duration as compared with the time required for the complete swing of the instrument, and is called an impulsive torque. The system is thus given an angular velocity, and an application of the laws of mechanics shows that the amplitude of the first ballistic throw is a measure of the impulsive torque applied, and hence of the quantity of electricity that has passed. The ballistic galvanometer is, then, an integrating rather than an indicating instrument. The rotational energy of the moving system is consumed in two ways: (a) The air surrounding the system is set in motion; (b) the relative motion of the coil and magnet induces a current in the coil, if the circuit is closed. Since the system is thus losing energy, each succeeding swing is less than the preceding one, the instrument comes gradually to rest, and the motion is said to be “damped.” If the resistance across the galvanometer terminals is very large, the system will make several swings before coming to rest. If the resistance is small, the system will not vibrate at all, but will come to rest slowly. If, however, it is of the proper value, the motion may be just aperiodic; that is, it will not swing past zero, but will return to zero in the shortest time. The instrument is then said to be “critically” damped, and the resistance required is called the “critical resistance.” In many instruments, the moving coil is wound on a closed copper form in which currents are induced as it swings, thus making it nearly aperiodic on open circuit.

**25. Constant of a Ballistic Galvanometer.**—A study of the equation of motion of the ballistic galvanometer shows that, no matter what the damping may be, whether zero or so great that



the motion is aperiodic, the first throw is proportional to the quantity of electricity discharged through it, the only limitation being that this discharge must take place before the system moves appreciably from its zero position. If the throw is small, so that the tangent is proportional to the angle, this fact may be expressed thus

$$Q = Kd \quad (15)$$

where  $Q$  is the quantity of electricity,  $d$  the deflection as read by a mirror and scale, and  $K$  a constant depending upon the sensitiveness of the instrument, numerically equal to the quantity necessary to give unit deflection. The smaller  $K$ , the greater is the sensitiveness of the instrument. If, then,  $K$  is known, we have a means of measuring small quantities of electricity

**26. Theory of the Undamped Ballistic Galvanometer.**—It will be assumed that the galvanometer is of the D'Arsonval type and that the field in which the coil moves is radial and uniform. It will also be assumed that the duration of the discharge is short compared to the time required for the first ballistic throw to take place. The conditions under consideration, then, are these: A small quantity of electricity, such as the charge of a condenser, is passed through the coil. While the current is flowing, the reaction between the current and the field produces a torque on the coil which starts it rotating. Although the duration of this torque is very short, the coil has, nevertheless, acquired a certain kinetic energy, and its motion is opposed only by the counter torque of the suspension, since we are neglecting damping. It will continue to rotate until its energy has been transferred to the suspension where it is stored as potential energy of elastic deformation. The coil then starts swinging in the reverse direction and when it passes through its zero position, it again possesses the same kinetic energy that it had originally, and will continue to oscillate indefinitely.

Let  $I$  be the moment of inertia of the coil,  $\omega$  its angular velocity,  $\alpha$  its angular acceleration, and  $\theta$  its angular deflection at any instant. As in the discussion of the current galvanometer, let  $C$  be the coil constant, that is, the torque produced by unit current, and let  $\tau$  be the suspension constant, that is, the counter torque for a twist of one radian. At any instant during the discharge, the equation of motion for the system is

$$Ci - \tau\theta = I\alpha \quad (16)$$

Since we are assuming that the discharge takes place before the coil swings appreciably from its zero position, the second term on the left hand side may be neglected; and, writing for  $\alpha$  its value,  $\frac{d^2\theta}{dt^2}$ , we have

$$Ci = I \frac{d^2\theta}{dt^2} \quad (17)$$

Let  $t'$  be the time required for the discharge to take place. Then

$$C \int_0^{t'} i dt = I \int_0^{t'} \frac{d^2\theta}{dt^2} dt \quad (18)$$

Carrying out this integration and letting  $\omega'$  be the angular velocity at the time  $t'$ , we have

$$CQ = I\omega' \quad (19)$$

Where  $Q$  is the quantity of electricity which passed through the coil. The kinetic energy thus acquired by the coil is

$$\text{Energy} = \frac{1}{2}I\omega'^2 = \frac{1}{2} \frac{C^2Q^2}{I} \quad (20)$$

If the coil swings through an angle  $\theta_1$ , the potential energy of elastic deformation is

$$\overline{W} = \tau \int_0^{\theta_1} \theta d\theta = \frac{1}{2}\tau\theta_1^2 \quad (21)$$

Since this is equal to the initial kinetic energy of rotation, there results

$$\frac{C^2Q^2}{I} = \tau\theta_1^2$$

whence

$$Q = \frac{\sqrt{\tau I}}{C} \theta_1 \quad (22)$$

Inasmuch as the quantities in the coefficient of  $\theta_1$  are not readily determined, it is simpler to express this quantity in terms of the figure of merit of the galvanometer and its period of oscillation  $T$ . Since the coil executes an angular harmonic motion, its period is given by

$$T = 2\pi\sqrt{\frac{I}{\tau}} \quad (23)$$

Substituting from (23) and (11) in (22) there results

$$Q = \frac{T}{2\pi} Fd \quad (24)$$

The constant  $K$  of eq. (15) is thus seen, for the undamped

ballistic galvanometer, to be  $\frac{T}{2\pi}$  times its figure of merit when used as a current measuring instrument.

The ideal condition, i.e., zero damping, cannot be realized in practice. Moreover, it would be exceedingly cumbersome to use, because of the difficulty in bringing the coil to zero and maintaining it in this position while adjusting other parts of the apparatus in preparation for an observation. Since a certain amount of damping must necessarily be present, it is usually most convenient to increase the damping until the motion is just aperiodic. In this case, the galvanometer deflects to a certain point and then returns to zero in the quickest time; and, barring external disturbances, remains in this position indefinitely.

The theory of the damped ballistic<sup>1</sup> galvanometer is somewhat involved and is beyond the scope of this book. It may be shown, however, that when damping exists, the quantity of electricity passed through is given by

$$Q = \frac{T}{2\pi} F \left( 1 + \frac{\lambda}{2} \right) d \tag{25}$$

where  $\lambda$  is called the "logarithmic decrement" and is defined as the Naperian logarithm of the ratio of any deflection to the next one succeeding it in the same direction. It is thus seen that damping reduces the ballistic sensitivity of a galvanometer. Further, if the galvanometer is standardized under conditions such that the damping is different from what it is in use, the decrement must be determined in both cases and the difference allowed for by eq. (25).

**27. Determination of the Constant of a Ballistic Galvanometer.**—The standardi-

zation of a ballistic galvanometer consists in passing known quantities of electricity through it and measuring the deflec-

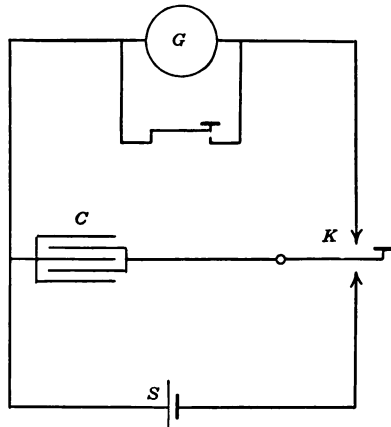


FIG. 9.—Condenser and standard cell method for obtaining constant of ballistic galvanometer.

<sup>1</sup> O. M. STEWART, *Phys. Rev.*, vol. XVI, 1903, p. 158.

LAWS, *Electrical Measurements*, chap. II.

tions they produce. Two methods are in common use, known respectively as the "condenser and standard cell method" and the mutual inductance or "standard solenoid method."

1. *The Condenser and Standard Cell Method.*—This method consists in charging a condenser of known capacity by means of a standard cell, and then discharging this quantity through the galvanometer. The apparatus is arranged as shown in Fig. 9, where  $G$  is the galvanometer to be standardized,  $C$  a standard condenser,  $K$  a charge and discharge key, and  $S$  a standard cell. If  $V$  is the E. M. F. of the cell, the quantity stored in the condenser when the key is pressed down is

$$Q = CV \quad (26)$$

and since

$$Q = Kd \quad (27)$$

we have

$$K = \frac{CV}{d} \quad (28)$$

If  $C$  is a subdivided condenser, several different values should be used, a curve plotted using  $Q$  as abscissas and  $d$  as ordinates, and the constant computed from the slope of the straight line. If  $C$  is expressed in farads,  $V$  in volts, and  $d$  in centimeters,  $K$  will be given in coulombs per centimeter; but if  $C$  is in micro-farads,  $K$  will be given in micro-coulombs per centimeter.

2. *The Standard Solenoid Method.*—This method is especially applicable to cases in which the galvanometer is used on low resistance circuits where the damping is large. The known quantity of electricity discharged through the galvanometer is obtained from the secondary of a standard mutual inductance when a measured change in the primary current is produced. The connections are shown in Fig. 10 where  $AD$  is the primary of the mutual inductance,  $SS'$  the secondary coil, and  $G$  the galvanometer to be calibrated.

Let  $Q$  = quantity of electricity discharged through the galvanometer.

$i$  = instantaneous current in galvanometer.

$e$  = instantaneous E.M.F. in secondary coil.

$I$  = value of primary current.

$R$  = total resistance of secondary circuit.

$M$  = mutual inductance between  $AD$  and  $SS'$ .

$T$  = time required for discharge to take place.

Then, from the above,

$$Q = Kd = \int_0^T idt \tag{29}$$

But

$$i = \frac{e}{R} \text{ and } e = M \frac{dI}{dt} \text{ from definition} \tag{30}$$

Hence,

$$Kd = \int_0^T \frac{M}{R} \frac{dI}{dt} dt = \frac{M}{R} \int_0^I dI = \frac{MI}{R} \tag{31}$$

or

$$K = \frac{MI}{R} \frac{1}{d} \tag{32}$$

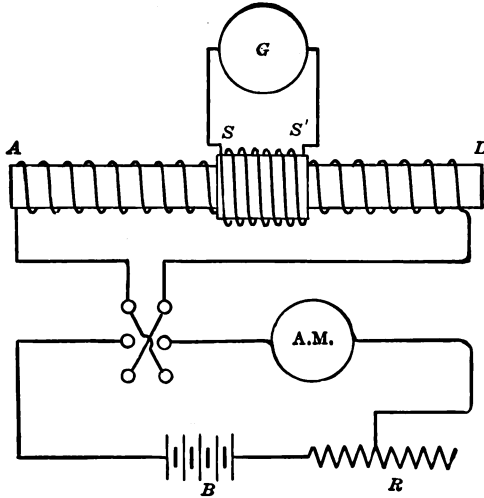


FIG. 10.—Standard solenoid method for ballistic galvanometer constant.

If one of the coils is uniformly wound and has a length great in comparison to its diameter, as the primary AD of Fig. 10, it is called a standard solenoid. The mutual inductance may then be calculated from the dimensions of the solenoid, and the number of turns on the coils, as follows:

- Let  $A$  = area of standard solenoid
- $L$  = length of standard solenoid
- $N$  = number of turns on standard solenoid
- $H$  = field strength in standard solenoid
- $\phi$  = total flux in standard solenoid
- $n$  = turns on secondary of standard solenoid.

The coefficient of mutual inductance may be defined, in electromagnetic units, as the number of magnetic linkages through the secondary when unit current is flowing in the primary, where, by linkages is understood the product of the number of turns and the total flux. As the secondary coil surrounds the standard solenoid, we have

$$M = n\phi = nHA \quad (33)$$

$$= \frac{4\pi NnA}{L} \text{ electromagnetic units} \quad (34)$$

Since, however, we wish  $M$  expressed in henries, we must divide by  $10^9$ , the number of E.M.U's. required for one henry. Accordingly, our equation becomes

$$K = \frac{4\pi NnA}{RL10^9} \frac{I}{d} \quad (35)$$

It is customary to reverse the current through the primary of the standard solenoid instead of merely "making" it as implied in the above derivation. The limits of integration in equation (31) should then be  $-I$  and  $+I$  instead of  $0$  and  $I$ , in which case our formula becomes

$$K = \frac{8\pi NnA}{RL10^9} \frac{I}{d} \quad (36)$$

In the above derivation, we have assumed that the field strength at the center of the standard solenoid is given by the formula

$$H = \frac{4\pi NI}{10L} \quad (37)$$

which is true only for an infinitely long solenoid. If the length of the standard solenoid is fifty times the diameter, the error, which is due to the demagnetizing effects of the ends, is less than one-half of one per cent. We have further assumed that there is no magnetic leakage between primary and secondary coils, a condition which is never realized. Our value for  $M$ , computed above, is, therefore, too large; and for very accurate work, a correction should be made. If we call  $f$  the demagnetization and leakage factor, our corrected formula for  $K$  becomes

$$K = \frac{8\pi NnA}{RL10^9} \frac{I}{d} (1 - f) \quad (38)$$

In practice, it is customary to obtain a series of deflections using different values of  $I$ , then plot  $I$  as abscissas and  $d$  as ordinates, and obtain the ratio  $\frac{I}{d}$  from the slope of the line. If

practical units of electrical quantities are used throughout,  $K$  will be expressed in coulombs per centimeter.

**28. The Fluxmeter.**—It was pointed out above, as a necessary condition that the ballistic galvanometer should give indications proportional to the quantity of electricity passed through it, that this passage must be completed before the moving system swings

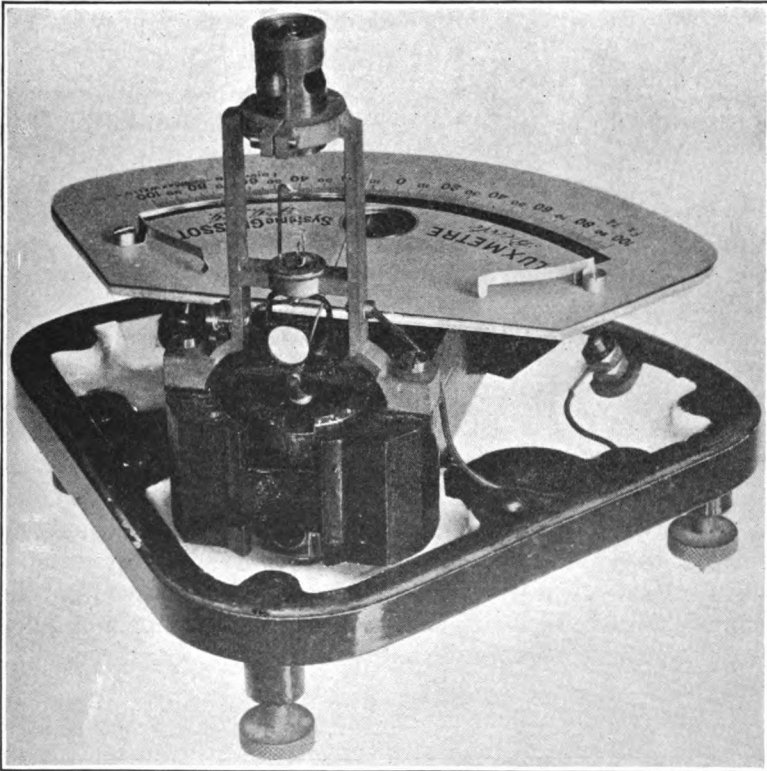


Fig. 11.—Grassot Flux Meter.

appreciably from its zero position. In certain instances, as, for example, the testing of iron possessing magnetic viscosity, the induced current which is passed through the galvanometer persists too long, and hence the ordinary instrument cannot be used. The Grassot fluxmeter is a modified ballistic galvanometer of the moving coil type, in which this difficulty is overcome. The coil is suspended by a fine silk fibre and is practically free from restoring forces, the current being led in and out by

means of fine helical springs. It is rectangular in shape and is placed in a field as nearly radial as possible, with respect to its axis of rotation, the parts involved being similar to those of the Weston ammeter. The torque, for a given current, is practically independent of the position of the coil. When connected to a resistance equal to or less than its critical resistance, the coil is stationary in any position. When a given quantity of electricity is discharged through it, it moves to a new position and the change in position is proportional to the quantity that passed, no matter how long a time was required. It is standardized and used as an ordinary ballistic galvanometer, except that some means must be provided for bringing it back to its zero position. Figure 11 shows the construction of an instrument of this type.

**29. Theory of the Fluxmeter.**<sup>1</sup>—As originally designed, the fluxmeter was intended as an instrument for the direct measurement of magnetic flux density. For this purpose, coils are constructed which consist of a definite number of turns wound on a plate of nonmagnetic material, the area of which must be carefully measured. These coils are made very thin so that they may be inserted in a narrow air gap such as exists between the armature and pole pieces of a dynamo. The measurement of an unknown flux density consists then in connecting the test coil by flexible leads directly to the fluxmeter and placing it at right angles to the flux to be measured. The instrument is brought to zero by some suitable device. The test coil is then withdrawn from the flux and the accompanying deflection of the instrument, multiplied by its constant, measures directly the change in flux through the test coil.

The direct proportionality between change of flux through the coil and deflection of the instrument may be shown as follows:

- Let  $\phi$  = flux through the exploring coil  
 $N$  = number of turns in exploring coil  
 $L$  = inductance of exploring and galvanometer coils  
 $R$  = resistance of exploring and galvanometer coils  
 $C$  = constant of galvanometer coil =  $HnIb$   
 $I$  = moment of inertia of galvanometer coil

<sup>1</sup> LAWS, *Electrical Measurements*, p. 124.

M. E. GRASSOT, Fluxmètre, *Journal de Physique*, 4th series, vol. 3, 1904, p. 696.



- $\omega$  = angular velocity of galvanometer coil
- $i$  = instantaneous current in galvanometer coil
- $\theta$  = angular deflection due to change of flux

As the test coil is withdrawn from the flux, there is induced in it an E.M.F. given by  $\frac{d\phi}{dt}$ . This is opposed by the counter E.M.F.,  $L \frac{di}{dt}$  due to the inductance of the galvanometer coil, and also by an E.M.F.  $C\omega$  due to the motion of this coil through the field of the instrument. Accordingly, the current at any instant is

$$i = \frac{N \frac{d\phi}{dt} - L \frac{di}{dt} - C\omega}{R} \tag{39}$$

The motion of the coil is given by

$$Ci = I \frac{d\omega}{dt} = \frac{CN}{R} \frac{d\phi}{dt} - \frac{CL}{R} \frac{di}{dt} - \frac{C^2\omega}{R} \tag{40}$$

Integrating between the limits  $0$  and  $t$ , where  $t$  is the duration of the change of flux and consequent motion of the galvanometer coil, we have

$$\frac{CN}{R} \int_0^t \frac{d\phi}{dt} dt = I \int_0^t \frac{d\omega}{dt} dt + \frac{CL}{R} \int_0^t \frac{di}{dt} dt + \frac{C^2}{R} \int_0^t \omega dt \tag{41}$$

Remembering that at both limits the current and angular velocity are each zero and that  $\int \omega dt = \theta$ , we have

$$\phi_2 - \phi_1 = \frac{C}{N} \theta \tag{42}$$

The change of flux through the test coil is thus seen to be directly proportional to the angle  $\theta$  through which the coil rotates. This deflection may be read either by a pointer or a mirror and scale. The fluxmeter may be used for almost any purpose for which the ballistic galvanometer is suited, but has, in general, a somewhat lower sensitivity.

**30. Checking Devices.**—If a ballistic galvanometer is not critically damped, it is convenient to have some device to check its motion and to set it accurately at its zero position. If the instrument is of the D'Arsonval type, this may usually be accomplished simply by a short circuiting key. However, since most keys possess slight thermal E.M.F.'s, the zero with the key closed will usually be different from the normal zero with the key open. When the galvanometer is used on a closed circuit, the

device shown in Fig. 12 is much more satisfactory. It consists of a coil of wire through which a bar magnet may be moved. The coil is connected in series with the galvanometer and the motion of the magnet induces in it a small E.M.F., positive or negative,

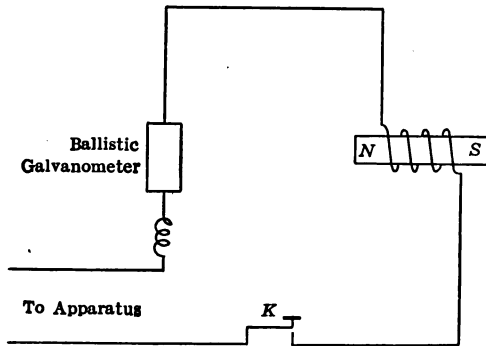


FIG. 12.—Checking device for ballistic galvanometer.

depending upon the direction of motion. The key must remain closed except when it is necessary to "get a new hold" on the galvanometer. With a little experience the instrument may, with this device, be set on zero very quickly and accurately.

## CHAPTER III

### MEASUREMENT OF RESISTANCE

**31. Ohm's Law.**—When a current of electricity is flowing from one point to another along a conductor, a difference of potential is found to exist between these points. The magnitude of the difference of potential depends upon the current and upon a property of the material in virtue of which it offers opposition to the passage of current. The relation between potential difference and current was first given by Ohm, and is known as Ohm's law. It states that, as long as the physical condition of a conductor remains unchanged, there is a constant ratio between the current and potential difference; or, in symbols,

$$I = \frac{E}{R} \quad (1)$$

where the proportionality factor  $R$  is called the resistance of the conductor. This law is a result of experiment and has been found to be true within the limits of the most refined measurements.

**32. Specific Resistance.**—For a uniform conductor, other conditions remaining the same, the resistance is proportional to the length and inversely proportional to the area of cross section. Hence, if  $l$  represents the length and  $a$  the cross section, we have

$$R = \rho \frac{l}{a} \quad (2)$$

where  $\rho$  is a constant depending upon the material of the conductor. Considering this as a defining equation for  $\rho$ , we see that, when  $l$  and  $a$  are unity,  $\rho$  equals  $R$ . The constant  $\rho$  is thus the resistance of a unit cube of the material, and is known as the Specific Resistance. In tabulating the resistivities of substances, the specific resistance is a convenient quantity to use, since knowing it, one can readily compute the resistance of a conductor of any length and cross section by means of eq. (2). The value of  $\rho$  depends upon the units employed for the measurement of length and resistance. Since the resistance of a unit cube of any metal is a very small quantity, it is customary to express the specific resistance in microhms per centimeter cube where a

microhm is one millionth of an ohm. Alloys, in general, have a much higher specific resistance than pure metals, and the presence of even a trace of another metal which, of itself, may be a good conductor, has a considerable effect upon the resistance; and hence, copper, for electrical purposes, should be pure.

**33. Temperature Coefficient of Resistance.**—The resistance of all conductors is found to change with the temperature. In the case of the pure metals, the resistance increases with increasing temperature, while for carbon and electrolytes, the opposite is true. The former are said to have a positive, and the latter a negative, temperature coefficient. Experiment shows that, over relatively large intervals of temperature, the resistance of a given conductor, at any temperature  $t$ , may be expressed by the equation

$$R_t = R_0(1 + \alpha t + \beta t^2 + \dots) \quad (3)$$

where  $R_0$  is the resistance at zero degrees and  $\alpha$  and  $\beta$  are constants depending upon the material and the temperature interval concerned. Over small ranges of temperature, the change in resistance is nearly proportional to the change in temperature, and may be represented by the linear relation

$$R_t = R_0(1 + \alpha t). \quad (4)$$

The coefficient  $\alpha$  is called the "Temperature Coefficient," and is the change in resistance per ohm per degree change in temperature. Some alloys, such as german silver and manganin, have a very small temperature coefficient, that of the latter being zero at some temperatures. Manganin is well suited, for this reason, for the construction of standard resistances.

**34. Measurement of Resistance.**—The independent or "absolute" determination of resistance, that is, measurement in terms of the fundamental units of length, mass, and time, is a matter of considerable difficulty; and so the establishment of primary standards is, at the present time, left almost entirely to government Bureaus of Standards, which are especially equipped for work of this character. On the other hand, the comparison of resistances, even to a high degree of accuracy, is relatively simple, and it is with work of this character only that we are concerned here.

**35. The Wheatstone Bridge.**—This is the usual method employed for comparing resistances of ordinary magnitudes, and its principle may be readily understood from Fig. 13. Four resistances are connected in the form of a diamond, with current

from the battery entering at *A*, where it divides in two parts which unite again at *B*. The galvanometer *G* is connected across the other corners of the diamond.

Since the points *P* and *Q* possess potentials intermediate between those of *A* and *B*, it must be possible to make *Q* have the same potential as *P* by suitably choosing  $R_3$  and  $R_4$ . When this condition has been established, no current flows through the galvanometer, as indicated by zero deflection, and the bridge is

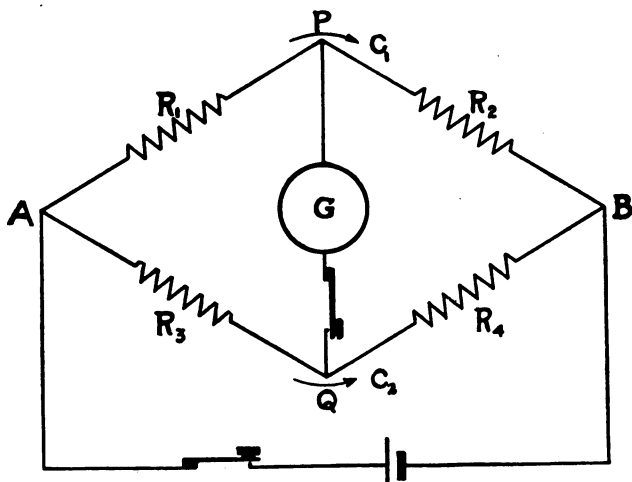


FIG. 13.—Wheatstone Bridge.

said to be balanced. Calling the current through  $R_1$  and  $R_2$ ,  $C_1$ , and that through  $R_3$  and  $R_4$ ,  $C_2$ , we have the

P.D. between *A* and *P* = P.D. between *A* and *Q* and

P.D. between *P* and *B* = P.D. between *Q* and *B*.

By Ohm's law

$$R_1 C_1 = R_3 C_2 \quad (5)$$

and

$$R_2 C_1 = R_4 C_2 \quad (6)$$

Whence

$$\frac{R_1}{R_2} = \frac{R_3}{R_4} \quad (7)$$

This is the law of the Wheatstone bridge, and it is clear that, if three of these resistances are known the fourth may be computed.

**36. The Slide Wire Bridge.**—If, in the above equation,  $R_1$  is an unknown and  $R_2$  a standard resistance, the former may be

expressed in terms of the latter by means of the ratio of  $R_3$  to  $R_4$ . It is obvious then that the actual values of  $R_3$  and  $R_4$  need not be known, their ratio being sufficient. Advantage is taken of this fact in the construction of the slide wire bridge, which is shown diagrammatically in Fig. 14 where the corresponding points of Fig. 13 are indicated by the same letters.  $R_3$  and  $R_4$  are replaced

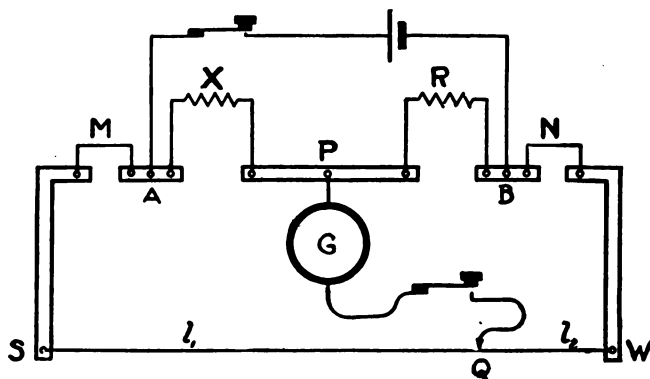


FIG. 14.—Slide wire bridge.

by portions of the slide wire  $SW$  and their magnitudes varied by moving the slider  $Q$ . Calling  $\rho$  the resistance of 1 cm. of the wire, we have

$$\frac{X}{R} = \frac{\rho l_1}{\rho l_2} \quad (8)$$

whence

$$X = \frac{l_1}{l_2} R. \quad (9)$$

In order to increase the accuracy of setting, and to reduce the relative errors in measuring  $l_1$  and  $l_2$ , especially where  $X$  and  $R$  have quite different values, resistances are introduced in place of the links  $M$  and  $N$ , which may be measured in terms of  $\rho$  and expressed, therefore, as a certain number of slide wire units to be added to  $l_1$  and  $l_2$ .

**37. The Post-office Box.**—A more compact form of Wheatstone bridge is shown in Fig. 15, which is known as the post-office box, from the fact that it was adopted at an early date by the British Post and Telegraph Office. The slide wire is replaced by two series of ratio coils,  $AQ$  and  $BQ$ , having resistances of 10, 100, 1,000 and 10,000 ohms each, while the third arm is a series

of coils, arranged as in the ordinary resistance box, frequently having a total of 100,000 ohms. The unknown  $X$  is connected between  $B$  and  $P$ . Since the ratio of  $X$  to  $R$  is thus a decimal number, no calculation is required. With the ratio coils set at

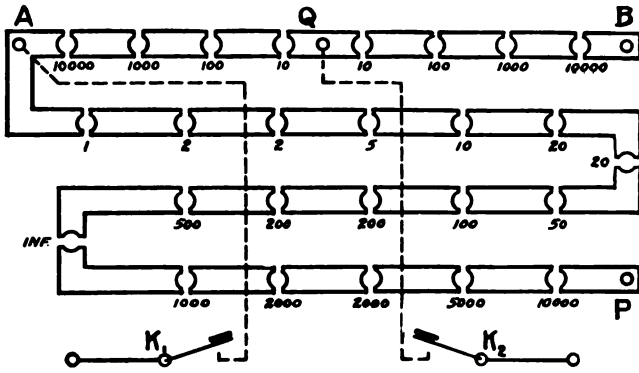


FIG. 15.—Post-Office box diagram.

1,000:1, resistances up to 100 megohms may be measured; while with the ratio reversed, resistances of the order of .001 may be detected. The range is thus great and its advantages are obvious. In using the box bridge, one should first use a 1:1 ratio, setting the coils at 100 ohms each, and obtain a rough balance, thus finding

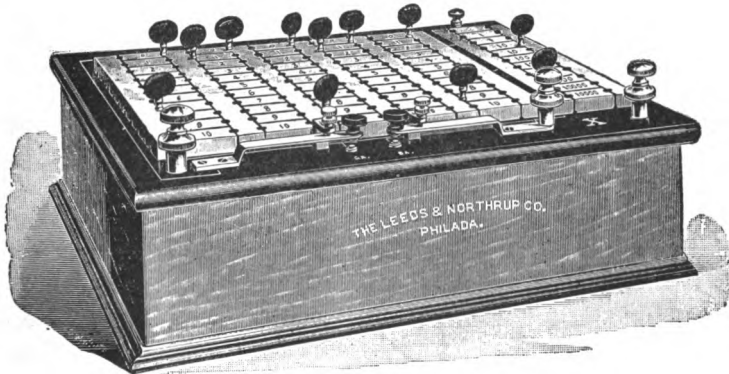


FIG. 16.—Post-office box.

the order of magnitude of the unknown. He should then choose such a ratio as will cause the balance setting of  $R$  to be as large as possible. For example, suppose  $C$  is found to be of the order of 45 ohms. By using a ratio of 1:1,000 a balance may be obtained

at 45,638, let us say, giving, as the value of the unknown, 45,638; while if a ratio of 1:100 had been used, the result would have been 45.64. The higher ratio thus increases the accuracy. Box bridges of the better class are provided with plugs for interchanging the ratio arms, by means of which inequalities in the internal connections of the bridge may be eliminated, and a check obtained upon the accuracy of the ratio coils. For accurate work, one should reverse the battery terminals in each case and re-balance, thus eliminating errors due to thermal and contact differences of potential. A convenient form of post-office box is shown in Fig. 16.

**38. Measurement of Low Resistance.<sup>1</sup> Kelvin's Double Bridge.**—For the measurement of extremely low resistances such as that of a few feet of trolley wire, cable, bus-bars, etc., the Wheatstone bridge is unsuited for two reasons: First, when the resistances to be compared are very low, the bridge becomes insensitive; and second, some sort of connectors must be used for

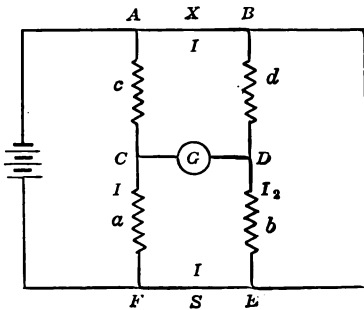


FIG. 17.—Diagram for Kelvin's double bridge.

joining the unknown to the bridge, and these may have a resistance comparable to that to be measured. The Kelvin double bridge avoids both of these difficulties. The general scheme of this circuit is shown in Fig. 17, where  $X$  and  $S$  are the unknown and standard resistances, respectively, through which a large current flows which need not necessarily be constant. There are four ratio

coils,  $a$ ,  $b$ ,  $c$ , and  $d$ , arranged in pairs, while the galvanometer is connected at the points  $C$  and  $D$ , between each pair. By properly adjusting the ratio coils,  $C$  and  $D$  may be brought to the same potential, when no current flows through the galvanometer and the currents in  $X$  and  $S$  are equal. When the balance has thus been obtained, let us call  $I$  the current through  $X$  and  $S$ ,  $I_1$  that through  $a$  and  $c$ , and  $I_2$  that through  $b$  and  $d$ . Then, by Ohm's law,

$$cI_1 = XI + dI_2 \text{ and } aI_1 = SI + bI_2 \tag{10}$$

<sup>1</sup> NORTHROP, Measurement of Resistance, chap. VI.  
LAWS, Electrical Measurements, chap. IV.



Whence

$$XI = cI_1 - dI_2 \text{ and } SI = aI_1 - bI_2 \tag{11}$$

$$XI = c\left(I_1 - \frac{d}{c}I_2\right) \quad SI = a\left(I_1 - \frac{b}{a}I_2\right) \tag{12}$$

By the construction of the instrument,

$$\frac{d}{c} = \frac{b}{a}$$

which gives, on dividing equations (12),

$$\frac{X}{S} = \frac{c}{a} \tag{13}$$

which is the working formula for the instrument. One form of this bridge devised by Leeds and Northrup, is shown in Fig. 18 where the points corresponding to those of the schematic diagram

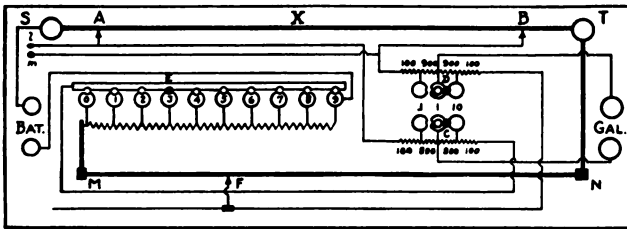


FIG. 18.—Laboratory form of Kelvin's double bridge

of Fig. 17, are lettered similarly. The unknown is represented as a heavy rod with potential taps at A and B, while the standard consists of the bar MN and the coils with posts numbered 0-9. Each of the coils, as well as the standard bar, has a resistance of .01 ohms, and the resistance being used as the standard S, is that between the slider F and the movable plug E. The standard thus has a range of 0 to .1 ohms by infinitesimal steps. The ratio coils are situated to the right of the standard coils and are connected to the galvanometer in different ways by means of the plugs C and D. A little study of the connections will show that three different ratios are possible; namely, 1:10, 1:1, and 10:1. The plugs C and D must be placed opposite one another, since a double ratio must be maintained as indicated by the equations; that is,

$$\frac{X}{S} = \frac{c}{a} = \frac{d}{b} \tag{14}$$

The resistance  $X$  is that portion of the rod between the points  $A$  and  $B$  only. When the resistance to be determined is of some other form than a rod, it must be provided with two sets of leads; a heavy pair for the current, which are joined to the bridge at  $S$  and  $T$ , and a light pair for the potential drop across it, joined at  $l$  and  $m$ . The bridge thus measures the resistance of the conductor between the points to which the potential leads are attached.

**39. Experiment 1. Specific Resistance of Materials.**—In this experiment, the specific resistance of three metals, copper, brass, and iron, is to be found. The metals are provided in the form of rods, which are to be clamped in the bridge at  $S$  and  $T$ . Make sure that good contact is obtained at  $A$  and  $B$  by polishing the bars at those points with emery cloth. Use, as a current supply, a ten-volt storage battery and include an ammeter and a reversing switch in this circuit, and a press key in the galvanometer circuit. Operate the bridge on 3 amperes. Measure the resistance of 50 cm. and 100 cm. lengths of each bar, reversing the current at each setting to eliminate errors due to thermal and contact potential differences within the instrument. Make at least four balances for each length approaching the balance point from both sides. Determine the diameter of the rod by means of a micrometer gauge, taking the average of ten measurements uniformly distributed over its length.

**Report.**— 1. Compute the specific resistance of each material in microms per centimeter cube.

2. Compare your results with the data given in one or two of the standard tables of physical constants to be found on the reference shelves. How do you account for the discrepancies?

**40. Carey-Foster Method for Comparing Two Nearly Equal Resistances.**—A very accurate method for comparing two resistances which are nearly equal to one another has been devised by Carey Foster.<sup>1</sup> It possesses the advantage that errors arising from the resistance of leads within the bridge, as well as those due to thermal and contact electromotive forces, providing they remain constant, are automatically eliminated. The wiring diagram is shown in Fig. 19. It consists of a slide wire bridge in which  $R_1$  and  $R_2$  are ratio coils and  $A$  and  $B$  are the resistances to be compared. Let  $r_1$  and  $r_2$  be the resistances of the internal bridge leads between the battery and slide wire

<sup>1</sup> *Phil. Mag.*, May, 1884.

connections on each side. Then if  $l_1$  and  $m_1$  are lengths of the bridge wire at balance, we have

$$\frac{R_1}{R_2} = \frac{A + r_1 + \rho l_1}{B + r_2 + \rho m_1} \tag{15}$$

where  $\rho$  is the resistance of the slide wire per unit length. Now let  $A$  and  $B$  exchange places, and let  $l_2$  and  $m_2$  be the corresponding lengths for a new balance. Then

$$\frac{R_1}{R_2} = \frac{B + r_1 + \rho l_2}{A + r_2 + \rho m_2} \tag{16}$$

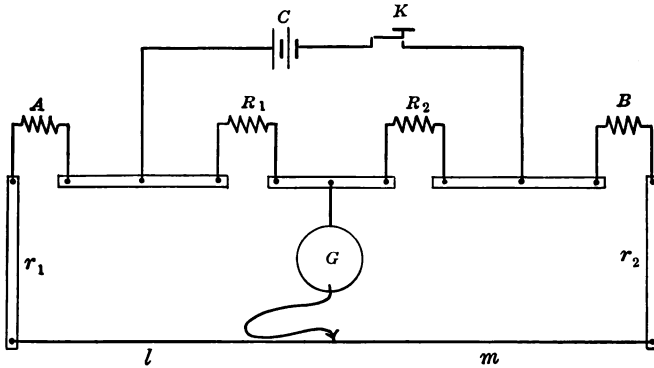


FIG. 19.—Wiring diagram for Carey-Foster bridge.

Equating the right hand members of equations (15) and (16) and taking the resulting equation by addition, we have

$$\frac{A + r_1 + \rho l_1 + B + r_2 + \rho m_1}{B + r_2 + \rho m_1} = \frac{B + r_1 + \rho l_2 + A + r_2 + \rho m_2}{A + r_2 + \rho m_2} \tag{17}$$

Since  $l_1 + m_1 = l_2 + m_2$ , the numerators of these fractions are equal; the denominators are therefore also equal, whence

$$\begin{aligned} B + r_2 + \rho m_1 &= A + r_2 + \rho m_2 \\ A - B &= \rho(m_1 - m_2) = \rho(l_2 - l_1) \end{aligned} \tag{18}$$

The difference in the resistance of the two coils,  $A$  and  $B$ , is thus seen to be equal to the resistance of the slide wire between the two points of balance, before and after the interchange of the coils. It is to be noted that this result is independent of the values of  $R_1$  and  $R_2$ .

The Carey-Foster bridge is usually employed for the comparison of coils whose temperature must be maintained constant and they are usually immersed in some sort of oil bath for this

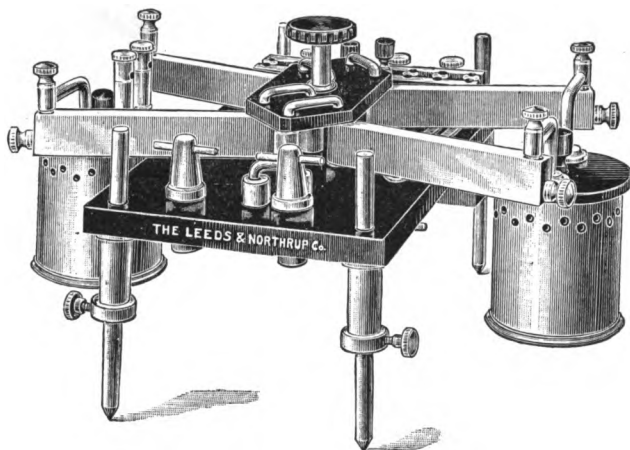


FIG. 20.—Coil interchanger for Carey-Foster bridge.

purpose. A convenient device therefore must be provided for interchanging them without removing them from their baths or producing any changes in contact resistances by handling them.

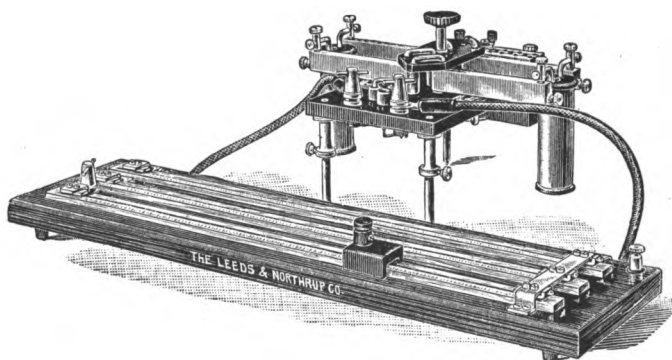


FIG. 21.—Complete Carey-Foster bridge.

Figure 20 shows an arrangement for this purpose. The coils are supported at the ends of heavy copper bars which swing so as to receive units of different sizes. Contact between resistance

terminals and bars as well as between bars and links of the commutator are made by boring cups in the bars and partially filling them with mercury. The interchange of the coils is effected by a half turn of the commutator at the center. Adjustable legs enable the coils to be lowered in the baths to the proper depth.

To adapt the bridge to the comparison of coils of high as well as low resistances and to secure at the same time a satisfactory sensitivity, it is important to have several slide wires of different resistances per unit length. Figure 21 shows a complete bridge in which any one of three slide wires may be used at will. To obtain the effect of a very low resistance slide wire, one of ordinary magnitude may be shunted. A link, seen at the front of the switch board is provided for this purpose.

**41. Determination of  $\rho$ .**—The Carey-Foster method requires that the slide wire be of uniform resistance, and that its resistance per unit length be accurately known. To measure  $\rho$ , the process of measurement above described may be inverted, using for  $A$  and  $B$  two equal coils of known resistance, one of which is shunted by a known variable resistance. By choosing appropriate values for the shunt, any desired difference between  $A$  and  $B$  may be obtained, and by changing  $R_1$  and  $R_2$  the balance points may be shifted to different positions along the slide wire. The constant  $\rho$  is obtained by substituting in eq. (18).

**42. Experiment 2. Measurement of Temperature Coefficient.**—The Carey-Foster method is particularly well adapted to the measurement of the variation of a resistance with temperature. The process consists in determining the difference between the resistances of two coils one of which is constant while the other is changed by holding it at different temperatures. The metal, whose coefficient is to be measured, is in the form of a wire wound on a frame which may be placed in an oil bath to secure a uniform temperature throughout. Place the container in an ice pack and measure the resistance at a temperature as near as possible to  $0^\circ\text{C}$ . Next place the container in a water bath heated by an electric heater. Obtain the resistance at  $10^\circ$  intervals up to  $80^\circ\text{C}$ . While each measurement is in progress, remove the heater and place the bath upon a wooden stand. Stir the oil continuously and read the thermometer frequently. Settings should be made as rapidly as possible to avoid temperature changes. After the highest temperature has been reached, allow the bath to cool and check the readings at three

points on the way down. The standard resistance should also be placed in an oil bath and its temperature maintained constant.

**Report.**— 1. Plot a resistance temperature curve using resistance as ordinates and temperature as abscissas. Draw a straight line through these points to strike an average, and from it determine the values for  $R_0$  and  $R_{35}$ . Compute the temperature coefficient  $\alpha$  from the equation

$$R_t = R_0(1 + \alpha t)$$

2. Consult a table of physical constants and see if you can identify the wire tested from the value of the temperature coefficient obtained.

**43. The Measurement of High Resistance.**<sup>1</sup>—In previous sections, methods for measuring resistances of ordinary magnitude and for very small resistances have been considered. The measurement of very high resistances, such as the insulation between the bus-bars of a switch board and the ground, the armature bars and core of an electrical machine, insulation of cables, etc., requires special consideration. A ready method commonly employed by engineers, which gives reliable results for resistances up to several tenths of a megohm, and even higher, is that in which a voltmeter of known resistance is employed, the unknown high resistance taking the place of the multiplier in the ordinary use of the instrument. Suppose a voltmeter, of resistance  $r$ , is connected across a source of E.M.F., and the voltage, which we will call  $V$ , is measured. Then let an unknown resistance  $R$  be connected in series with the instrument across the same source. Since the voltmeter measures the fall of potential across its own internal resistance, which we will call  $V_r$ , while the total voltage across  $R$  and  $r$  is that originally measured, *i.e.*,  $V$ , we may write, by Ohm's law,

$$\frac{V_r}{V} = \frac{r}{r + R} \quad (19)$$

Or,

$$\frac{V - V_r}{V_r} = \frac{R}{r} \quad (20)$$

Whence

$$R = \frac{r(V - V_r)}{V_r}. \quad (21)$$

<sup>1</sup> NORTHROP, Measurement of Resistance, chap. VIII.

CARHART and PATTERSON, Electrical Measurements, p. 92.

GRAY'S, Absolute Measurements in Electricity and Magnetism, p. 253.

If the resistance  $R$  is too large,  $V_r$  will be insignificant compared with  $V$ , and the method evidently will not yield satisfactory results. For resistances of such magnitude, e.g., several megohms, recourse is generally taken to some leakage method in which the high resistance is used as an insulator, and its magnitude estimated from the rate at which a known charge leaks through it. As an example, consider the case in which it is

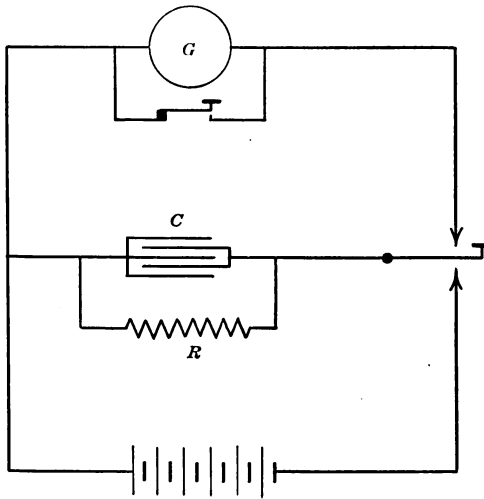


FIG. 22.—Insulation resistance by leakage.

desired to measure the resistance of the insulation of a given length of cable. The cable should be coiled up and placed in a tank of water, both ends being left outside. This arrangement may be considered a condenser, one plate of which is the water, the other the wire, while the insulation is the dielectric. Its electrical equivalent is shown in Fig. 22. If the wire and water are charged to a given potential difference and the insulation were perfect, the charge would remain constant; but, if the insulation possesses a slight conductivity, the charge will gradually leak through, reducing the potential difference of the condenser. The rate of leak may be estimated by measuring the residual charge after leakage has been going on for a definite time and comparing it with the original charge. The resistance is then calculated as follows:

Let  $C$  = capacity of the coil  
 $V_0$  = applied voltage  
 $R$  = insulation resistance in ohms  
 $V$  = instantaneous difference of potential  
 $I$  = instantaneous leakage current  
 $Q$  = instantaneous charge

The charge  $Q$  is given by

$$Q = CV \quad (22)$$

and

$$I = -\frac{dQ}{dt} = -C\frac{dV}{dt} = \frac{V}{R} \quad (23)$$

or

$$C\frac{dV}{dt} + \frac{V}{R} = 0 \quad (24)$$

Separating the variables

$$\frac{dV}{V} + \frac{dt}{CR} = 0 \quad (25)$$

Integrating

$$\log_e V + \frac{t}{CR} = K \quad (26)$$

where  $K$  is a constant of integration to be determined from the initial conditions. For this purpose, reckoning time from the instant when the leakage begins, the condition to be satisfied by the equation is, when  $t = 0$ ,  $V = V_0$ . Substituting these values in eq. (26), we have  $\log_e V_0 = K$ . Replacing  $K$  by this value, we have

$$\log_e V + \frac{t}{CR} = \log_e V_0 \quad (27)$$

or

$$\log_e V_0 - \log_e V = \frac{t}{CR} \quad (28)$$

Thus,

$$\log_e \frac{V_0}{V} = \frac{t}{CR} \quad (29)$$

Solving,

$$R = \frac{t}{C \log_e \frac{V_0}{V}} \quad (30)$$

**44. Experiment 3. Insulation Resistance by Leakage.**—Connect the apparatus as shown in Fig. 22 where  $G$  is a ballistic galvanometer,  $C$  the coil under test,  $B$  a storage battery, and  $K$  a well insulated charge and discharge key.  $B$  should have such



a voltage that the first throw of the galvanometer is about 15 cms. Since this is a leakage experiment, its success depends upon having all parts well insulated; the tank should be placed upon a glass plate or an insulated stand, and care be taken that no wires touch each other, the table, or other apparatus. Since the capacity of the coil does not change with time, the deflections of the galvanometer are proportional to the voltage across its terminals. Charge and discharge immediately thus obtaining a deflection proportional to  $V_0$ . Repeat this several times and take the average. Then charge and place the key on the point marked "Insulate" and, after allowing 15 seconds for leakage, again discharge and obtain a deflection proportional to  $V$ . Repeat the operation for the following times of leak: 0.5, 1, 2, 5, 7, 10, 20, 30 minutes. If, in computing the resistance, common logarithms are used, the modulus for changing to natural logarithms must be introduced. If  $t$  is in seconds, and  $C$  in farads,  $R$  will be expressed in ohms; but if  $C$  is in microfarads  $R$  will be in megohms. The formula becomes

$$R = \frac{t}{2.303 C \log_{10} \frac{d_0}{d}} \quad (31)$$

The capacitance  $C$  of the cable may be obtained from the relation

$$Q_0 = CV_0 = kd_0 \quad (32)$$

where  $k$ , the constant of the galvanometer, is to be obtained by charging a standard condenser with a standard cell and discharging through the galvanometer, as explained in Art. 27. Measure  $V_0$  by an ordinary voltmeter. Measure the resistance of the wire of the cable by the voltmeter-ammeter method, using for this purpose about 20 amperes. Determine also the diameter of the wire by means of a micrometer gauge.

**Report.**—1. Compute the resistance of the cable for each time of leak from eq. 31, and plot the insulation resistance in megohms as ordinates, and time of leak as abscissas. It will be found that the resistance is not constant but increases with the time during which it was subjected to a voltage, approaching asymptotically to a limiting value. This is characteristic of all insulators of this class, and, in stating their resistances, the time for which it was determined must always be specified.

2. From the data on the resistance and diameter of the wire, find, by means of a wire table, the length of the cable, and com-

pute the insulation resistance per mile for some selected time of leak. In making this calculation, remember that the insulation resistance is measured in the direction in which the leakage current flows, namely, radially from the wire to the outside, and that the longer the cable the less will be the total insulation resistance.

**45. The Internal Resistance of Cells.**<sup>1</sup>—It is a well-known experimental fact that when a cell is delivering current, the E.M.F. across its terminals is not the same as on open circuit but changes with the current, being less the larger the current. This is true not only for cells, but for all electrical generators containing internal resistance. Let a cell, having an E.M.F. of  $E$  volts and an internal resistance of  $r$  ohms, be connected to an external resistance of  $R$  ohms, and let  $I$  be the amperes flowing; then the rate at which energy is delivered by the cell is  $EI$  watts. Since the current must flow, not only through the external resistance, but also through the internal resistance of the cell, this energy will be consumed by both of these resistances;  $I^2R$  watts in the former, and  $I^2r$  watts in the latter. Accordingly we have

$$EI = (R + r)I^2 \quad (33)$$

or

$$E = RI + rI \quad (34)$$

This is an equation of E.M.F.'s which states that the total E.M.F. of the cell is equal to the external plus the internal potential drops. Putting the terminal P.D. equal to  $E'$ , we have

$$E - E' = rI \quad (35)$$

from which it is seen that the internal resistance may be computed if  $E$ ,  $E'$ , and  $I$  are known. In fact, this is the method generally employed for cells which are able to furnish a considerable current without polarization; for example, storage cells. Suppose such a cell, whose internal resistance is to be measured is connected as shown in Fig. 23, where  $AM$ ,  $R$ , and  $K$  are an ammeter, rheostat, and key, respectively. Let the voltmeter (V.M.) be an instrument taking no current, e.g., an electrostatic voltmeter, having an infinite resistance. When  $K$  is open, the voltmeter registers the total E.M.F. of the cell because there is no fall of potential across  $r$ , as no current is flowing. When  $K$  is closed, however, the voltmeter registers, not the total E.M.F.

<sup>1</sup> NORTHROP, Measurement of Resistance, chap. XI.

CARRHART and PATTERSON, Electrical Measurements, pp. 96-105.

as before, but the terminal P.D.  $E' = E - rI$ , the portion  $rI$  being consumed in sending the current through  $r$ . Reading now the current, the internal resistance may be computed from Eq. 35. In practice, an ordinary Weston voltmeter may be used without appreciable error since the resistance of the voltmeter is very large compared with that of the cell, and the  $ir$  drop within the cell, which is the quantity by which the indications of the instrument differ from the total E.M.F., is so small that it may be neglected,  $i$  being the current taken by the voltmeter.

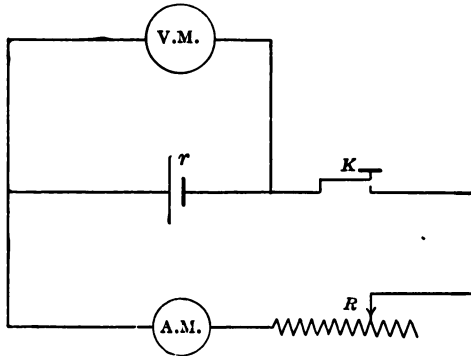


FIG. 23.—Voltmeter-ammeter method for internal resistance of cells.

If, however, the cell is one that polarizes rapidly, this method cannot be used, since  $E$  and  $E'$  will depend upon how long the current has been flowing. This difficulty may be overcome by using a known resistance  $R$  and taking the voltages so quickly that little or no polarization sets in. The current  $I$  is given by

$$I = \frac{E}{R + r} = \frac{E'}{R}. \quad (36)$$

Substituting either of these values for  $I$ , preferably the latter, in eq. (35), we have

$$E - E' = E' \frac{r}{R} \quad (37)$$

and solving for  $r$ , we have

$$r = R \frac{E - E'}{E'} \quad (38)$$

Since the right-hand member of this equation contains a ratio of voltages, it is not necessary to know actual values, relative values being sufficient; hence, any device giving indications

proportional to the voltage may be used in place of the voltmeter; for example, a condenser and ballistic galvanometer.

**46. Condenser and Ballistic Galvanometer Method.**—The basis for this method is that the first throw of the galvanometer is proportional to the quantity of electricity discharged through it, and that the charge of a condenser is proportional to the potential difference across its terminals; that is

$$Q = CE$$

where  $C$  is the capacity of the condenser. Accordingly, if the voltages  $E$  and  $E'$  are used to charge the condenser, and these charges are then passed through the ballistic galvanometer, the deflections are proportional to the voltages; that is

$$Q = K_1 d = CE$$

or

$$E = k_2 d \quad (39)$$

Substituting in (38), we have

$$r = \frac{R(E - E')}{E'} = R \frac{(d - d')}{d'} \quad (40)$$

**47. Experiment 4. Internal Resistance of a Cell by Condenser Method.**—Connect the apparatus as shown in Fig. 24, where

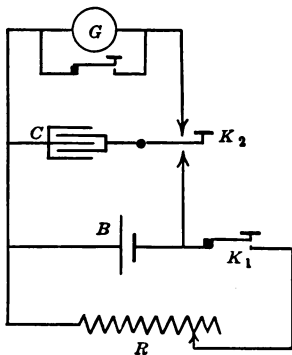


FIG. 24.—Condenser method for internal resistance of a cell.

$B$  is the cell to be tested,  $C$  a condenser,  $G$  a ballistic galvanometer,  $K_2$  a charge and discharge key, and  $R$  a known variable resistance. First, with  $K_1$  open, press down  $K_2$  thus charging the condenser to the total E.M.F. of the cell, and discharge by allowing  $K_2$  to rise, obtaining a deflection proportional to  $E$ . Take several readings in this manner and average. Then, having set  $R$  at a suitable value, close  $K_1$ , charge and discharge as above, opening  $K_1$  as quickly as possible to avoid polarizing the cell.

The average of several readings taken in this manner measures  $E'$ , whence  $r$  may be computed. It is well first to practice operations upon a cell other than the one to be tested, in order to become expert in manipulating the keys quickly and in their proper order. In carrying out this experiment, use the

following values for  $R$ : 10, 7, 5, 4, 3, 2, 1, .5 and .2 ohms. The current from the cell is given by—

$$I = \frac{E}{R + r} \quad (41)$$

where  $E$  is the total E.M.F. To obtain  $E$ , it is necessary to determine the voltage constant of the condenser and galvanometer system, which is, in reality, the constant of eq. 39. In other words, we must measure the voltage required to give unit deflection. For this purpose replace  $B$  by a standard cell and, with  $K_1$  open, charge and discharge several times. Substitute in eq. (39) and solve for  $k_2$ .

**Report.**—1. Compute the internal resistance for each different current drawn from the cell and plot the former as ordinates against the latter as abscissas.

2. How do you account for the fact that the internal resistance is not constant?

**48. Battery Test.**—When a primary battery is furnishing current, it polarizes; that is, hydrogen, which is one of the products of the reactions going on within, collects on the positive plate. This, together with other causes, diminishes the activity of the cell. Indeed, the polarization may become so great as to cause the E.M.F. to fall to zero. A chemical, called the depolarizer, is introduced to remove the hydrogen, or to prevent its being formed. Cells intended for open circuit work contain a depolarizing agent that acts very slowly; thus they polarize rapidly if left on closed circuit, but recover if left for a time on open circuit. Cells intended for closed circuit work should polarize very little, thus the depolarizing agent should act quickly. The deterioration of a cell, when left on open circuit, due to local action within the cell, is important, but can best be found by actual use, since it takes too long to test this in the laboratory. We might also run an efficiency test by working the cell to exhaustion; but this, too, is better found by actual use. What we are interested in, however, is the behavior of the cell when run on a closed circuit for a given time as the value of a cell is determined by the rate of its polarization and recovery as well as by its E.M.F. and internal resistance.

**49. Experiment 5. Battery Test.**<sup>1</sup>—Study in this experiment the time variation of: (a) Total E.M.F. on open circuit, (b) the terminal potential difference on closed circuit, (c) the internal

<sup>1</sup> CARHART, Primary Batteries.

resistance, (*d*) the current, and (*e*) the rate of recovery from polarization. The set-up is the same as in Exp. 4 and all quantities are to be measured by the methods there outlined. The difference here is that the key  $K_1$  is left closed all the time except for an instant when it is opened to charge the condenser for measuring the total E.M.F. As above, obtain the readings for the E.M.F. and terminal potential difference for the initial condition of the cell. Now close  $K_1$ , and at the end of a minute, charge the condenser and discharge it through the galvanometer, thus obtaining the value of the terminal potential difference on closed circuit after the cell has been delivering current for one minute. As soon as this is done, open  $K_1$  for an instant and charge the condenser; then set  $K_2$  on "insulate" and again close  $K_1$ . This key,  $K_1$ , must be opened and closed quickly, also these two readings, i.e., for total E.M.F. and terminal P.D., taken as nearly simultaneously as possible. As soon as the galvanometer comes to rest, discharge the condenser through it, obtaining a measure of the E.M.F. on open circuit after the cell had been furnishing current for one minute. This will give a measure of the polarization. Repeat these readings every minute for five minutes and then every five minutes for twenty-five minutes more. At the end of this time, open  $K_1$  and measure the E.M.F. of the cell as it recovers for another thirty minutes. As above, take readings at first every minute and then at intervals of five minutes. Find out from the instructor what resistance to use for  $R$ . Read Exp. 4 before attempting this one. Practice with another cell as there suggested.

**Report.**—1. Compute the total E.M.F. and terminal potential difference in volts, and internal resistance in ohms.

2. Plot on one sheet, with time as abscissas, the total E.M.F., the terminal potential difference, the internal resistance, and the current as ordinates.

3. Plot also on the same sheet the recovery curve, starting at the other end of the time axis, running the curve backwards.

## CHAPTER IV

### MEASUREMENT OF POTENTIAL DIFFERENCE

**50. Description of a Potentiometer.**<sup>1</sup>—There is, perhaps, no single electrical instrument which has so wide a field of usefulness and which gives, at the same time, such trustworthy results as the potentiometer. While comparing potentials primarily, it may, with proper accessories, be adapted to compare currents and resistances as well, and is so easy to manipulate as to be an effective instrument even in the hands of a novice. The funda-

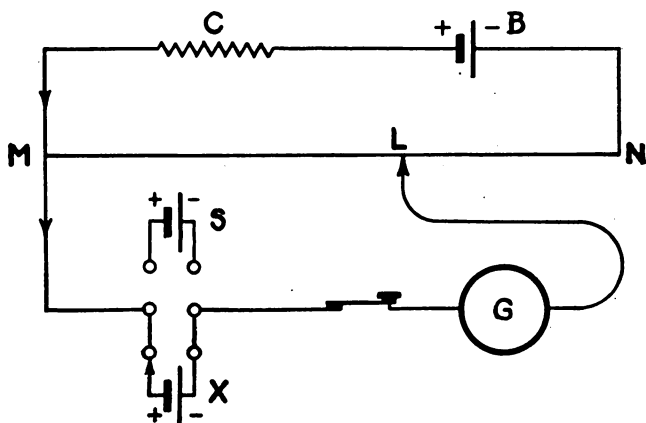


FIG. 25.—Simple Potentiometer circuit.

mental principle of the potentiometer may be illustrated by Fig. 25, where  $MN$  is a wire of uniform resistance, stretched along a scale with equal divisions and supplied with current from a battery  $B$ , whose E.M.F. must be larger than those to be compared. If the polarity of  $B$  is as shown,  $M$  will be at a higher potential than  $N$ , and the fall of potential per unit length will be the same all along the wire. If the difference of potential between  $M$  and  $N$  is known, the wire may be regarded as a potential measur-

<sup>1</sup> LAWS, *Electrical Measurements*, p. 271.

*Electrical Meterman's Handbook*, p. 208.

KARAPETOFF, *Experimental Engineering*, p. 74.

ing rod. To measure an unknown E.M.F., such as the battery  $X$  of the figure, an auxiliary circuit  $MXL$  is provided, containing a galvanometer and key. If the battery  $X$  were temporarily removed and a short circuiting wire substituted in its place, a portion of the current from  $B$  would flow in the shunt circuit from  $M$  to  $L$ , causing a deflection of the galvanometer in a particular direction. If, instead, the battery  $B$  were removed,  $X$  would cause a current to flow in the direction  $XMLG$ , giving a reverse deflection. If, however, both batteries are included, and the slider  $L$  is adjusted until the  $IR$  drop in the wire due to the current from  $B$  is exactly equal to the E.M.F. of  $X$ , no current will flow in the shunt, indicated by zero deflection of the galvanometer. The current in the circuit  $BNM$  is then just the same as though the shunt were disconnected. If the potential drop per unit length of the slide wire is known,  $X$  may be directly determined, for we have

$$X = \rho I l_1, \quad (1)$$

where  $\rho$  is the resistance per unit length, and  $l_1$  the length required for balance.  $\rho I$  may be determined by substituting for  $X$  a cell  $S$  of known E.M.F. and balancing as before. Let  $l_2$  be the length required for this balance. Then

$$S = \rho I l_2 \quad (2)$$

Whence

$$\rho I = \frac{S}{l_2} \quad (3)$$

and

$$X = S \frac{l_1}{l_2} \quad (4)$$

The unknown E.M.F. is thus obtained in terms of  $S$  by a direct comparison of the lengths  $l_1$  and  $l_2$ . If the fall of potential per unit length of wire were some decimal fraction of a volt, the unknown  $X$  could be read from the slide wire directly, thus avoiding the calculation indicated. The method of accomplishing this may be illustrated by the following example: Suppose the slide wire  $MN$  contains 200 divisions, and the fall of potential between  $M$  and  $N$  is 2 volts. The fall of potential per division is then .01 volt. Let the standard cell have an E.M.F. of 1.0185 volts. Set the slider at 101.85 divisions, include  $S$  in the shunt circuit, and obtain a balance, not by moving the slider, but by varying the control resistance  $C$ , thereby changing the current  $I$ . When a balance has been secured,  $\rho I = \frac{1.0185}{101.85}$



.01 volt per division. The potentiometer is now standardized. Substitute  $X$  for  $S$  and balance by moving  $L$ , leaving  $C$  unchanged. If this reading should be 145.63 divisions, the E.M.F. of the unknown cell would be 1.4563 volts. When used in this manner, the instrument is said to be a "Direct Reading Potentiometer."

To carry out comparisons with great accuracy, a very long wire, having a high degree of uniformity, is obviously necessary. Since such a wire is difficult to obtain, and inconvenient to use, it is customary to substitute for it two resistances, as shown in Fig. 26. If the sum of  $R_1$  and  $R_2$  is kept constant, they together

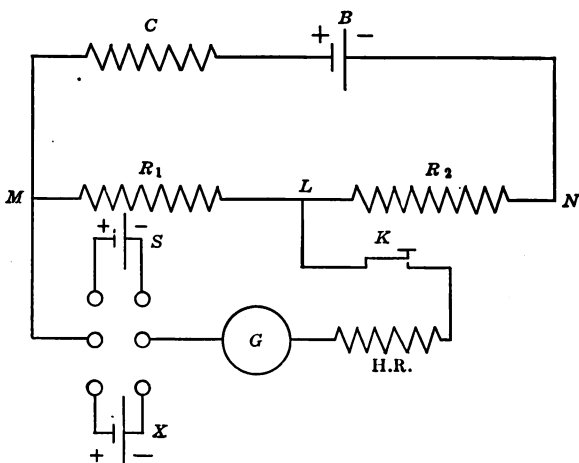


FIG. 26.—Potentiometer constructed from resistance boxes.

are equivalent to a wire of fixed length, and an increase in  $R_1$  accompanied by an equal decrease in  $R_2$  is equivalent to moving the slider of Fig. 25 to the right, while an increase in  $R_2$  and a decrease in  $R_1$  moves it to the left. Balances may easily be obtained, the conditions for which are the same as outlined above. For example, when a balance has been obtained with  $X$  in circuit, we have

$$X = R_1 i. \tag{5}$$

where  $R_1$  is the resistance required for balance and  $i$ , the current flowing through the potentiometer, i.e., through  $CR_1R_2$ . This current, which may be obtained by balancing against the standard cell  $S$ , is given by

$$S = R_1' i \text{ or } i = \frac{S}{R_1'} \tag{6}$$

where  $R'_1$  is the value required for balance in this case. Whence,

$$X = \frac{R_1}{R'_1} S \quad (7)$$

It must constantly be borne in mind that the above relations require that  $i$  should remain constant during the entire process, which will be true only when the sum of the resistances,  $R_1 + R_2 = C$  is unchanged, and the E.M.F. of  $B$  is constant. This arrangement may be made "Direct Reading" if  $i$  is a known decimal fraction of an ampere. This may be accomplished by giving to  $R'_1$  a value having the same significant figures as the E.M.F. of the standard cell, and balancing by varying  $C$ . For example, suppose, as above,  $S = 1.0185$  volts and the boxes used have resistances in the neighborhood of 20,000 ohms. If  $R'_1 = 10,185$  ohms, when a balance has been reached

$$i = \frac{1.0185}{10,185} = \frac{1}{10,000} \text{ ampere,}$$

and the fall of potential across each ohm is  $\frac{1}{10,000}$  of a volt.

Replacing now  $S$  by  $X$  and balancing again, leaving  $C$  undisturbed and keeping  $R_1 + R_2$  constant,

$$X = \frac{R_1}{10,000} \quad (8)$$

**51. Standard Potentiometers.**—In order to avoid the necessity of providing two exactly similar boxes, making the various connections as explained above, and transferring plugs from one to the other, it is convenient to have a single instrument, including all resistances, switches, keys, etc., provided with binding posts, to which the various E.M.F.'s may be connected. A number of such potentiometers are on the market, three of which will be described.

1. *The Leeds and Northrup Potentiometer.*—The arrangement of this circuit, which is the simplest of those to be studied, is shown diagrammatically in Fig. 27, in which the letters correspond, as far as possible, to those used in Fig. 26. The potentiometer circuit proper,  $BNMC$ , consists of 16 coils of 5 ohms each, and a long slide wire  $NO$ , also of 5 ohms. This circuit, in normal operation, carries one fiftieth of an ampere, giving across each coil as well as the slide wire, one-tenth of a volt fall of potential. The circuit, containing the unknown potential is included between the movable contacts,  $T$  and  $L$ . The box  $R_1$  of the previous

diagram is that part of the circuit lying between  $T$  and  $L$ , while  $R_2$  consists of two parts, namely, the right-hand portion of the slide wire, and the resistance to the left of  $T$ . The slide wire, shown in the figure by a single turn, in reality consists of ten turns wound on a marble cylinder and is about .17 feet in length. The fall of potential across each turn is thus .01 volt, and, as the dial circle is divided into 200 parts, the instrument

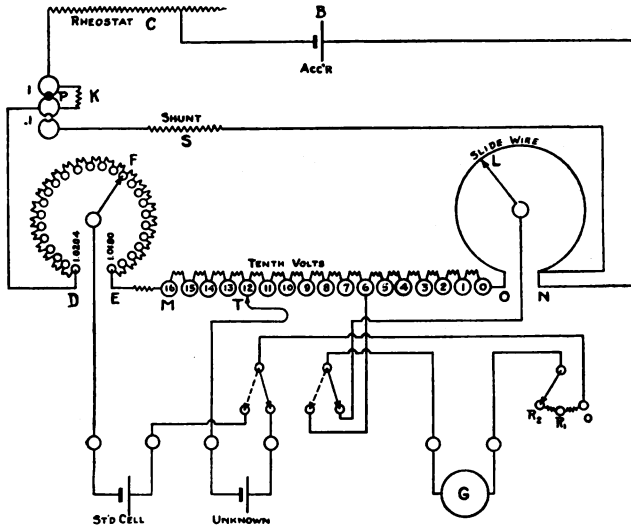


FIG. 27.—Diagram of Leeds and Northrup potentiometer.

reads to directly .00005 volt. By moving the slider  $L$  and the contact  $T$ , the difference of potential may be varied by infinitesimal changes from 0 to 1.6 volts.

The range of the instrument, for small electromotive forces, such as those furnished by thermo-couples, is increased tenfold by means of a shunt. As seen from the diagram, when the plug  $P$  is inserted in the hole marked .1, the shunt  $S$ , which contains a resistance of one-ninth that of the potentiometer proper, is connected across the entire circuit, so that only one-tenth of the normal current flows through the potentiometer proper. In order that the current from the battery  $B$  may remain unchanged a resistance  $K$  is automatically included, thus keeping the resistance of the entire circuit the same. A ready means of standardizing the potentiometer current is furnished by the extra dial  $DE$ , containing 19 coils of such a resistance, that, with the

normal current flowing, the fall of potential across each is .0001 volt. From the .6 post of the tenth volt dial, a permanent lead is brought out, and connected, when the selecting switches are thrown toward the left, through the galvanometer and standard cell to the contact *F*. The fall of potential from the .6 plug to *M* is 1 volt; from *M* through the resistance to *E* is .018 volt, and from *E* to *F* as many ten-thousandths of a volt additional as may be required to equal the E.M.F. of any normal Weston cell within the ordinary range of temperature (1.0180–1.0204 volts).

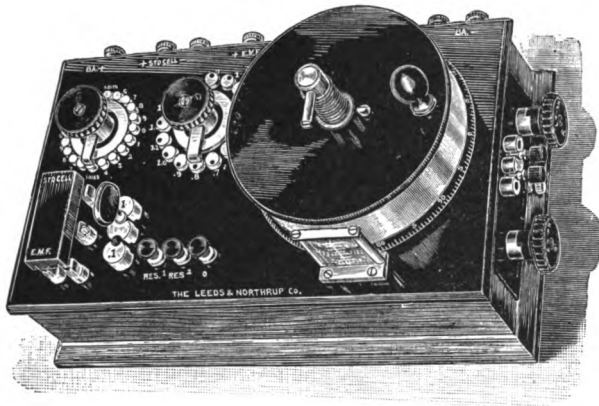


FIG. 28.—Leeds and Northrup potentiometer.

It is thus possible to check the potentiometer current without re-setting the instrument. The operation then is as follows: Set the standard cell dial to correspond to the E.M.F. of the cell, corrected for temperature. Move the selecting switch to the left, set *P* in the hole marked 1, and vary the control resistance *C* (usually mounted at the right-hand end of the instrument) until a balance is obtained. One-fiftieth of an ampere, the normal current is now flowing. Move the selecting switch to the right, thus including the unknown E.M.F., and vary *T* and *L* until the balance is once more obtained, when the unknown may be read directly. If it is less than .15 volt, set *P* in the .1 hole, and balance again, when the reading of the instrument must be divided by 10. The complete instrument is shown in Fig. 28.

2. *The Wolff Potentiometer.*—The fundamental principle of this instrument is shown by the simplified connections of Fig. 29. The result which must be secured by any arrangement is

that the resistance of the potentiometer circuit proper, namely,  $MN$ , must be kept constant, while the resistance across which the auxiliary circuit  $FL$  is connected, must be continuously variable. By moving  $F$  and  $L$ , changes of 1,000 and 100 ohms, respectively, are obtained, without changing the total resistance as is at once obvious. The resistance coils connected by the double sliders are sets with units of 10, 1, and .1 ohms respectively. These double sliders are mounted so as to move together, but are insulated from each other and connected in circuit as

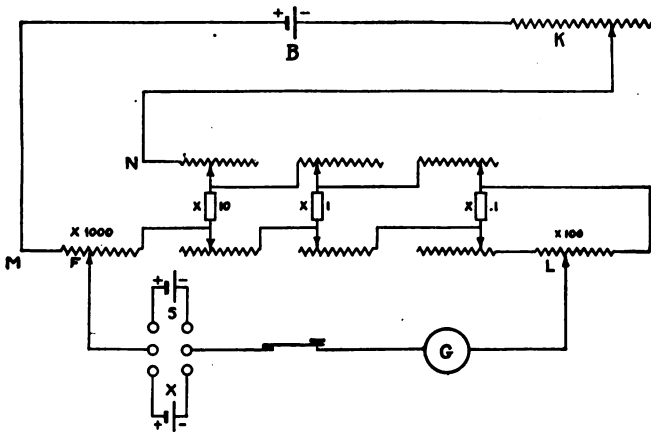


FIG. 29.—Principle of Wolff potentiometer.

shown in the diagram. If the pair at the left is moved one division to the right, it is evident that the resistance between  $N$  and  $L$  is increased by 10 ohms, while that between  $F$  and  $L$  is decreased by the same amount, thus leaving the resistance between  $M$  and  $N$  unchanged. In the same way, the middle pair of sliders produces changes of 1 ohm each between  $F$  and  $L$  leaving  $MN$  unchanged, while the right-hand pair produces changes of .1 ohm each. Shifting any one of these sliders, therefore, is equivalent to moving the slider  $L$  of Fig. 25 by definite amounts.

The actual wiring of the instrument, mounting of the sliding contacts, connections to accessories, switches, etc., are shown in Fig. 30. The control resistance  $K$  is not included in the instrument. Any ordinary resistance box capable of small variations will serve for this purpose. The total resistance of the instrument, as sketched, is 19,000 ohms. When carrying the normal current of one ten-thousandth of an ampere, the difference of

potential across consecutive posts of the first dial is one-tenth of a volt; of the second dial, one-hundredth of a volt; and of the last dial, one hundred-thousandth of a volt, while the maximum voltage directly measurable is one and nine-tenths volts.

In using this instrument, first obtain the E.M.F. of the standard cell, corrected for temperature, and set the small middle dial of the upper row at this value. Set the switch in the upper left-hand corner at *NN*, and the one in the right-hand corner, which includes a high resistance in the galvanometer circuit, at its largest value. Obtain a balance by varying the control resis-

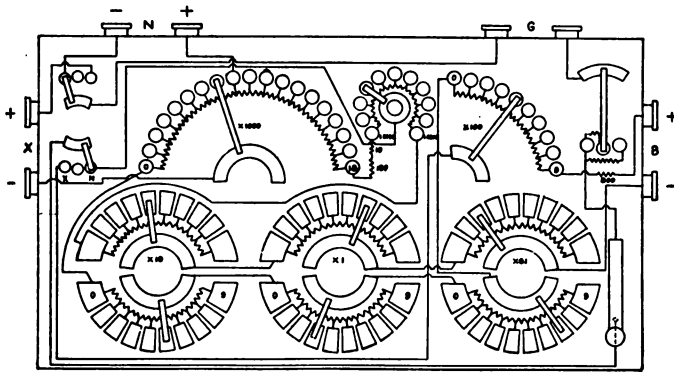


FIG. 30.—Wiring diagram for Wolff potentiometer.

tance, cutting out the galvanometer resistance as a balance is approached. This operation standardizes the current at one ten-thousandth of an ampere. Now switch to *XX* and balance by setting the large dials, when the unknown may be read off directly. In checking the potentiometer current, which must frequently be done, it is not necessary to change the dials from their positions when balanced on the unknown E.M.F.

3. *The Tinsley Potentiometer.*—The working diagram for this instrument, which is unique in that it employs an electrical vernier, is shown in Fig. 31. Seventeen coils, with a resistance of 5 ohms each, connected in series with a short slide wire of .5 ohm, form the potentiometer circuit proper *MN*, while the auxiliary circuit is *FGL*. Attached to a movable arm are two sliding contacts, so spaced that they always rest upon two alternate posts, leaving one post between them as indicated. This pair of contacts is connected to a second series of 10 coils of 1 ohm each.

When the normal current of one-fiftieth of an ampere is flowing through *MN*, the fall of potential between adjacent posts is .1 volt. However, the fall of potential between the posts connected by the pair of contacts to the second series of coils is also .1 volt, since the two coils of the main circuit are now shunted by a resistance equal to their own, giving a resultant resistance between the contacts equal to that of a single main circuit coil. Between adjacent posts of the second series there is accordingly .01 volt fall of potential, and across the slide wire there is also .01 volt potential difference. This instrument, like the Leeds and Northrup, is provided with separate connections for the standard cell,

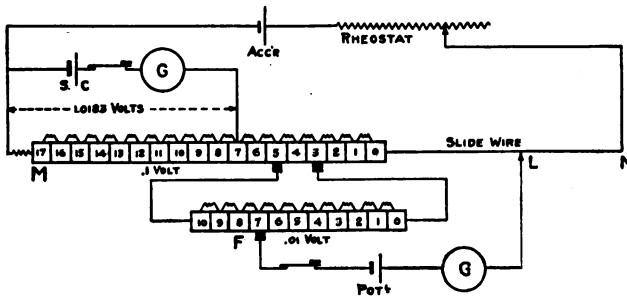


FIG. 31.—Principle of Tinsley potentiometer.

so that it is not necessary to re-set all of the sliders when checking the current through the potentiometer circuit proper. A standard cell lead is permanently attached to post number 7. Across the ten coils between it and post 17 there is, accordingly, 1 volt potential difference, and in series with the main circuit is another coil shown at the left of 17, of such a value that, with the normal current flowing, the fall of potential across it is .0183 volts, and to the other side of this, the second standard cell terminal is attached. Unlike the Leeds and Northrup instrument, this coil cannot be varied to compensate for variations in the E.M.F. of the standard cell due to temperature changes, but the value 1.0183 volts is sufficiently accurate for ordinary purposes.

The wiring connections, switches, etc., are shown in Fig. 32. The control rheostat is included in the instrument, and consists of the dial in the right-hand corner and the slide wire immediately above it. By moving the plug in the upper left-hand corner to the hole marked *X* by .1, the instrument is shunted by a resistance of such a value that all readings should be divided by ten, a

feature of great importance in thermo-couple work. In using the instrument, set the shunt plug in the hole marked *X* by 1, and the two-point switch below the middle dial on *SC*. The first dial must be set so as to shunt none of the coils above the seventh, otherwise, the resistance over which the standard cell is to be balanced will be reduced effectively by one coil. A good rule is to set this dial always at zero when balancing on the standard cell. Obtain a balance by changing first the rheostat and then the slider above it, which is provided with a slow motion screw for the final setting. Use in this connection the key mark

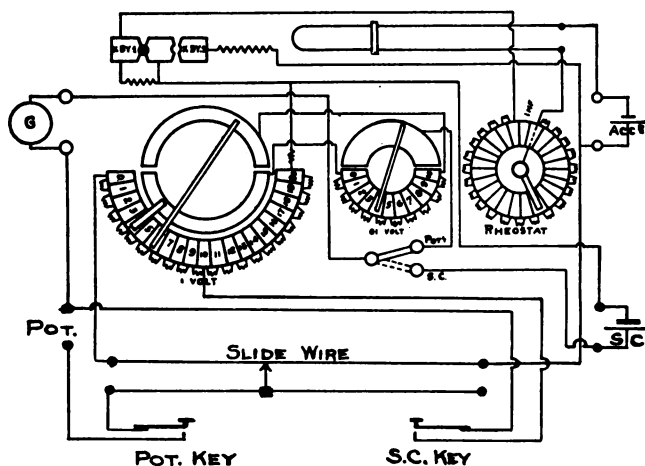


FIG. 32.—Wiring diagram of Tinsley potentiometer.

*SC*. The current is now exactly one-fiftieth of an ampere and the instrument is standardized. To measure the unknown, simply move the two-point switch to *Potl.*, and balance by setting the two dials and the lower slide wire. If the unknown is less than .2 volt, use the shunt as explained above, dividing the reading by 10. In carrying out any measurement, the current through the instrument should be checked frequently.

**52. The Weston Standard Cell.**—While the legal definition of electromotive force is given in terms of the standard current and resistance by means of Ohm's law, nevertheless, in actual practice, the volt is specified in terms of the standard cell. After many years of investigation, the Weston standard cell has been perfected to such an extent that persons in different parts of the



world, may, by following definite specifications, construct cells of this type and be sure of securing E.M.F.'s which agree within less than 1 part in 10,000. This cell is usually set up in an air-tight H-shaped vessel, as shown in Fig. 33, with platinum wires sealed through the bottoms for connection with the electrodes. The positive electrode consists of pure mercury while the negative is an amalgam of cadmium and mercury. These are placed in the bottoms of the tubes, and a solution of  $\text{CdSO}_4$  with a few extra crystals to insure saturation, forms the electrolyte between them. To protect the mercury against contamination by the  $\text{CdSO}_4$  and at the same time prevent polarization, a thick paste, consisting mainly of mercurous sulphate, is placed over the mercury. As the cell operates, the cadmium ions from the  $\text{CdSO}_4$  solution displace some of the ions from the mercurous sulphate paste and mercury is deposited upon the mercury electrode.

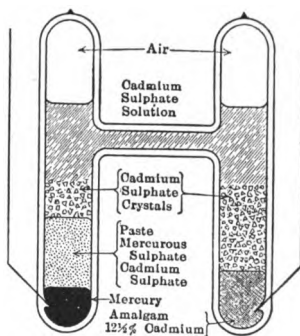


FIG. 33.—Weston standard cell.

One of the advantages of this cell over former types is that its electromotive force changes but very little with the temperature. The electromotive force of a cell which has been set up with care is given, with accuracy sufficient for most purposes, by the equation

$$E_t = E_{20} - 0.0000406 (t - 20^\circ \text{ C.}). \quad (9)$$

That is, the E.M.F. decreases 0.0000406 volt for each degree the temperature is raised above  $20^\circ \text{ C.}$ , and increases by the same amount for each degree below  $20^\circ \text{ C.}$  This quantity is called the temperature coefficient. Since standard cells are never used as a source of current, but merely for balancing potentials or charging condensers, they are made of small size. Those furnished in the laboratory are mounted in a brass tube, with a hard rubber top provided with binding posts and a hole through which to insert a thermometer. The E.M.F. of the individual cells is usually given at  $20^\circ \text{ C.}$ , from which the E.M.F. at the temperature at which they are used may be computed by means of the formula given above. When used in a potentiometer circuit, a high resistance should be included and gradually cut out as a balance is approached.

**53. Experiment 6. Comparison of Cells by the Potentiometer.** *A. Simple Potentiometer.*—Connect the apparatus, as shown in Fig. 26, Art. 50, omitting the control resistance  $C$ , and using for  $R_1$  and  $R_2$  two exactly similar boxes.  $B$  should be a cell of constant E.M.F., preferably a portable storage battery. Obtain from the instructor a standard and several unknown cells whose E.M.F.'s are to be determined. The high resistance marked H.R. need not be known accurately, since its purpose is merely to protect the galvanometer and standard cell from excessive currents when the potentiometer is far from balance. It is well to start this at about 10,000 ohms, gradually reducing it as a balance is approached. Be sure that the double pole double throw switch for connecting  $S$  and  $X$  in circuit is not provided with cross wires, as they would short circuit the cells. To keep  $R_1 + R_2$  constant, as required in the theory, start with all the plugs out of  $R_1$  and all in  $R_2$ , and obtain a balance by transferring them from their places in one box to the corresponding holes in the other.  $R_1 + R_2$  will then always remain equal to the total resistance of one box. To test whether the polarity of the cells is properly arranged in the two circuits, first rock the double pole double throw switch on  $X$ , break the potentiometer circuit at  $B$ , tap the key  $K$  lightly, and note the direction of swing of the galvanometer. Now close again the circuit at  $B$ , remove the wires from the middle posts of the double pole double throw switch, and join them. The galvanometer should swing in the opposite direction on tapping the key. First, secure a balance on  $X$ ; then rock the switch over and balance on  $S$ , afterwards checking your balance on  $X$ , to make sure that the potentiometer current has not changed during the process. Reverse the connections at  $B$ , also on the auxiliary circuit, and proceed as before, taking the average of the two results thus obtained. This is necessary to eliminate errors due to spurious contact and thermal E.M.F.'s within the potentiometer.

*B. Direct Reading Potentiometer.*—Include in the potentiometer circuit the control resistance  $C$ , as shown in Fig. 26. Determine the temperature of the standard cell and its E.M.F. corrected for this temperature. Set  $R_1$  to have the same significant figures as this E.M.F., using the largest multiple possible, and put  $R_2$  equal to the difference between the total capacity of one box and  $R_1$ . Switch  $S$  into the shunt circuit and balance by varying  $C$ . Then rock over on to  $X$  and, leaving  $C$  fixed, balance

by plugging back and forth between  $R_1$  and  $R_2$ , keeping their sum constant. The reading of  $R_1$ , when properly pointed off, gives  $X$  directly. After each balance on  $X$ , the setting on the standard cell should be checked and  $C$  changed, if the current has not remained constant, which, of course, necessitates a new balance on  $X$ . Now reverse terminals as in Part A, and repeat, taking the average of the two results.

**Report.**—1. Give values of E.M.F. for all cells compared, and where temperature corrections are known, reduce to  $20^\circ\text{C}$ .

2. Suppose a balance has been obtained without H.R. in circuit. Now include H.R. How will the balance point be affected? Why?

3. What is the maximum E.M.F. that may be measured by the direct reading potentiometer, as you have used it in this experiment?

**54. The Volt Box.**—In standard potentiometers, operated on normal current, the maximum difference of potential which may

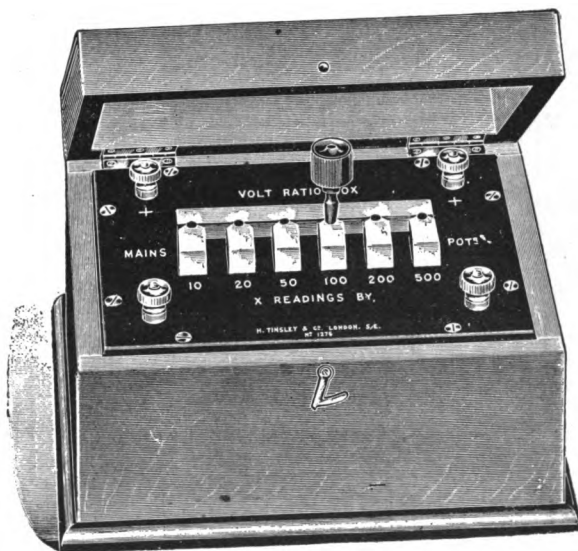


FIG. 34.—Volt box.

be measured directly never exceeds two volts and is usually even less. When it is desired to measure voltages in excess of this value, some means must be provided for accurately dividing the unknown voltage into definite fractions of the total, small enough to be measured by the potentiometer available. This may be

accomplished by means of the "volt box." This consists of an accurately adjusted resistance box, of large range, in which the blocks to which the coils are attached are provided with sockets for receiving traveling plugs. The voltage to be divided is impressed across the terminals and the fraction to be measured is obtained across the traveling plugs, which may be set at any points desired. By Ohm's law, the voltage across the traveling plugs is such a fraction of the total voltage as the resistance between the traveling plugs is of the total resistance. If the resistance of the volt box is 10,000 ohms, the drop across 1,000 ohms is one-tenth of the total; that across 100 ohms, one-hundredth of the total, and so on. It is simpler to use decimal ratios wherever practicable. Special boxes are made in which these ratios are obtained by setting a dial switch or a single plug as shown in Fig. 34.

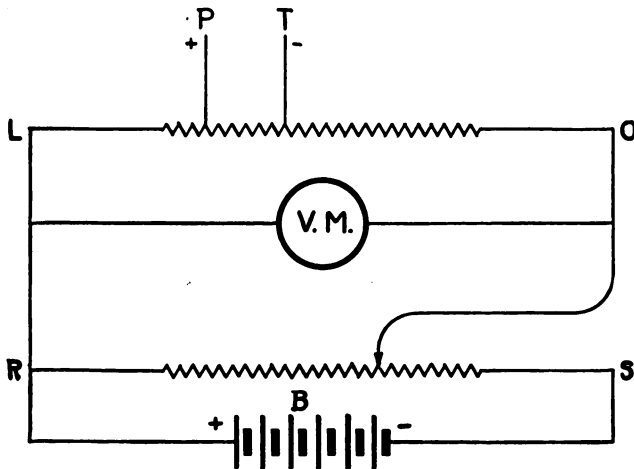


FIG. 35.—Connections for standardizing a voltmeter.

**55. Experiment 7. Calibration of a Voltmeter by Potentiometer and Volt Box.**—The method, in brief, consists in impressing across the terminals of the voltmeter various voltages and measuring these voltages by means of a potentiometer provided with a volt box. The connections for this purpose are shown in Fig. 35. *VM* is the voltmeter to be calibrated; *LO* the volt box; *RS* a high resistance rheostat with a sliding contact for

<sup>1</sup> JANSKY, *Electrical Meters*, chap. V.

KARAPETOFF, *Experimental Engineering*, vol. I, pp. 51-55.

voltage regulation, and *B* a storage battery. *P* and *T* are the terminals from the traveling plugs of the volt-box which are to be attached to the potentiometer. The voltage of *B* should be sufficient to give full scale deflection of the instrument. Use any one of the potentiometers described above, following the directions given for each instrument. After the connections with the potentiometer have been properly made and its current adjusted by balancing against the standard cell, throw the selecting switch to the point marked "unknown." Set the slider of the rheostat *RS* so that the voltmeter indicates about one-tenth full scale deflection, and choose the largest decimal ratio of the volt-box giving a voltage within the range of the potentiometer. Measure this voltage with the potentiometer. In a similar manner check the voltmeter at 8 or 10 points distributed uniformly across the scale. Test the constancy of the potentiometer current frequently by re-balancing against the standard cell. Record voltmeter readings, potentiometer settings, and volt-box ratios. Note carefully the zero reading of the voltmeter before beginning the test and again at the end, after it has been deflected for some time, to see if the springs show any elastic fatigue. With about two-thirds full scale deflection, place the instrument in a vertical position to test the accuracy with which the moving system is balanced. Bring another instrument near this one, and see if there is any effect from external magnetic fields. Tap the instrument gently with the finger to see if the bearing friction is large. Does the pointer swing past its final position when a voltage is suddenly thrown on?

**Report.**—1. Obtain the differences between the readings of the instrument and true voltages, and plot these corrections as ordinates against readings of the instrument as abscissas. Draw in straight lines connecting these points.

2. State your findings regarding the imperfections of the instrument.

3. Would it indicate on alternating voltages?

## CHAPTER V

### MEASUREMENT OF CURRENT

**56. Kelvin's Balance.**—This is an instrument for the measurement of current in which use is made, not of the action between the magnetic field of a current and a permanent magnet, as in the case of galvanometers and ammeters, but of the action between the fields of two currents. It consists of six flat coils placed horizontally, four of which are fixed while the other two, mounted at the ends of a beam pivoted at the middle, are movable. The general arrangement is shown in Fig. 36. The current to be measured passes through all six coils in series, flowing in each in

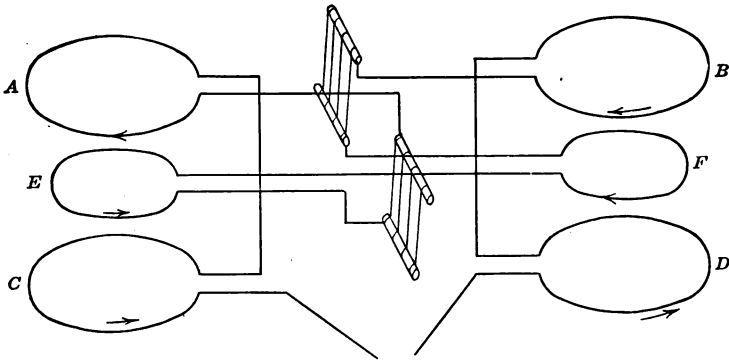


FIG. 36.—Arrangement of coils in Kelvin's balance.

such a direction that *A* and *C* both urge *E* downward, while *B* and *D* urge *F* upward. The force of attraction or repulsion between two coils is proportional to the current in each. Accordingly, when the coils are connected in series the force between them is proportional to the square of the current. Thus, the electrodynamic action between the fixed and the movable coils is such as to produce a torque on the movable ones in the counter clockwise direction proportional to the square of the current. This torque is counterbalanced by a weight which slides along a graduated beam attached to the moving system. An index at each end shows when a balance has been reached. Since the

torque due to the current is proportional to the square of the current, and that due to the weight is proportional to the weight and the length of the lever arm, we have, as the condition for equilibrium,

$$KI^2 = WL \quad (1)$$

where  $W$  is the weight of the slider,  $L$  its distance from the zero position, and  $K$  a constant depending upon the construction of the instrument. Solving

$$I^2 = \frac{W}{K} L \quad (2)$$

or

$$I = \text{const.} \sqrt{L} \quad (3)$$

The constant is generally so given that one must use the doubled square root of the length  $L$ , and, to facilitate observations, tables of these quantities have been prepared. For rough work, however, a fixed scale is mounted directly behind and a little above the movable one, from which the doubled square root may, with fair approximation, be read directly. Since the constant depends upon the weight of the slider, a means is afforded for changing the range. Four weights are usually supplied for which the constants are 0.025, 0.05, 0.1, and 0.2, giving ranges of 1.25, 2.5, 5, and 10 amperes, respectively, since the movable scale has 625 divisions, giving a doubled square root of 50.

As with an ordinary balance, the beam must be in equilibrium for no load, that is, no current flowing through the coils. If the index at the end does not read zero, equilibrium may be obtained by moving a small metal flag attached to the moving system so as to throw more of its weight to one side or the other, as is required. A special device mounted on the base and operated by a handle below the case is provided for this purpose. The movable system is carried by flexible ligaments made up of a number of fine phosphor-bronze ribbons placed side by side. As these are delicate and easily broken, an arrestment is provided which is operated by a milled head at the bottom of the case. Weights should never be changed without first raising the arrestment. Since the balance must be in equilibrium for zero current, no matter which weight is used, there must be a separate counterpoise for each. These consist of brass cylinders, provided with a pin, which are placed in a small horizontal trough at the right-hand end of the moving system, with one end of the pin

passing through the hole in the bottom of the trough. Since the direction of the torque is independent of the direction of the

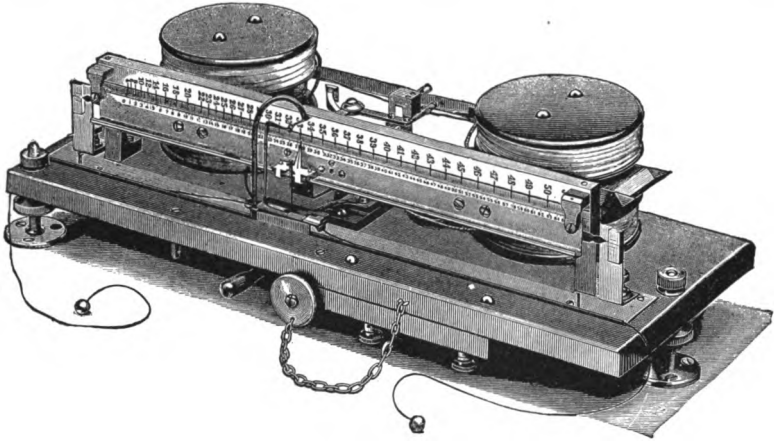


FIG. 37.—Kelvin's balance.

current, the instrument may be used either on direct or alternating currents, indicating in the latter case, root mean square values. Figure 37 shows the usual laboratory form of the Kelvin's balance.

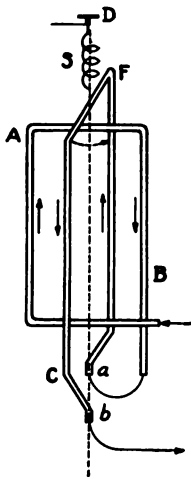


FIG. 38.—Arrangement of coils in Siemens electro-dynamometer.

#### 57. The Siemens Electro-dynamometer.—

This is another current measuring instrument working on the principle of the electro-dynamic action between two coils carrying currents. The coils are rectangular in form and placed perpendicular to one another, as shown in Fig. 38. The movable coil, *CF*, which is placed outside the fixed coil *AB*, is carried by a fine point resting in a jewel and the current is led to and from it by wires dipping into mercury cups at *a* and *b*, situated one above the other in the axis of rotation. One end of a helical spring *S* is attached to the moving coil, while the other is fastened to a milled head *D* carrying an index read from a fixed circular scale. When a current flows through the two coils in series, the movable one tends to set itself parallel to the fixed, but is brought back to its zero position by turning the head *D*, thus



twisting the spring. The torque due to the current is proportional to the square of the current since the coils are in series, while that due to the spring, by Hooke's Law, is proportional to the angle through which it is twisted. Accordingly, we have, as the condition for equilibrium,

$$I^2 = A^2\phi$$

or

$$I = A\sqrt{\phi}$$

where  $A$  is a constant depending upon the size of the coils, number of turns, stiffness of spring, etc, and  $\phi$ , the angle through which the spring is twisted. The range of the instrument is changed by varying the number of turns in one of the coils. The instrument usually has two fixed coils with separate binding posts on the base. Since the magnetic field of these coils is small, that of the earth is appreciable in comparison and may introduce an error. For example, if the earth's field is in the same direction as that of the fixed coil, the instrument will read too high, while if the earth's field is opposite, it will read too low. This error may be eliminated by reversing the currents and taking the average. Since the direction of rotation of the movable coil is independent of the direction of the current, the instrument will indicate on alternating currents as well as direct, giving in the latter case, root mean square values. It may accordingly be calibrated on direct and used on either direct or alternating currents. Figure 39 shows the usual form of Siemens electro-dynamometer.

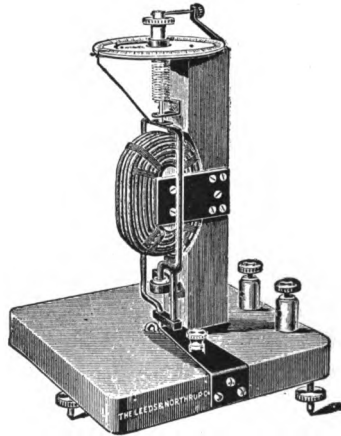


FIG. 39.—Siemens's electro-dynamometer.

**58. Experiment 8. Calibration of an Electro-dynamometer.**<sup>1</sup>—In this experiment, an electro-dynamometer is to be calibrated in terms of a Kelvin balance, which is taken as the standard instrument. Connect the instruments in series on a 20-volt

<sup>1</sup> JANSKY, *Electrical Meters*, chap. VIII.

CARHART and PATTERSON, *Electrical Measurements*, chap. III.

storage battery, including a variable rheostat and an ammeter to observe roughly the currents used. Both instruments must first be leveled and adjusted for zero on no current. Begin with the lowest range of the Kelvin balance. For this use the carriage alone and the smallest counter weight. When the limit of this range has been reached, raise the arrestment, open the case, and push the carriage moving mechanism a little to one side bringing it forward enough for clearance. Place the first additional weight upon the carriage, and the second counter-poise in the trough. Whenever new weights are put in position, the zero must be rechecked. Measure in this way the currents for ten points on the electro-dynamometer, taking them a little closer at the lower end of the scale. Record electro-dynamometer readings, Kelvin balance readings, and number of counterpoise.

**Report.**—1. Compute the current for each setting of the instrument, also the constant  $A$  in equation (5).

2. Plot current as ordinates and settings as abscissas. What is the shape of this curve?

3. What is meant by the root mean square value of an alternating current?

4. Name some other electrical instruments operating on the principle of the electro-dynamometer.

**59. Ammeters and Voltmeters.**<sup>1</sup>—An ammeter, as the name implies is an instrument for measuring the current flowing in a circuit; while a voltmeter, measures the difference of potential or

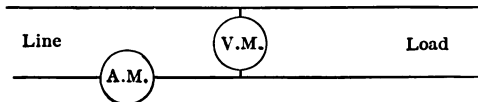


FIG. 40.—Connections for ammeter and voltmeter.

electrical pressure existing between two points. Since the former indicates, at any instant, the rate of flow of electricity through a conductor, it must be placed in series with the circuit, so as to be traversed by the entire current; while the latter, being a pressure gauge, is connected in parallel with the circuit, and carries a very small current, which in general may be neglected. The regular method of connecting these instruments is shown in Fig. 40.

<sup>1</sup> JANSKY, *Electrical Meters*, chap. III.

KARAPETOFF, *Experimental Electrical Engineering*, vol. I, chap. II.  
*Electrical Meterman's Handbook*, chap. V.

While many different kinds of indicating instruments are in use, each having its particular field of application, those generally employed in direct current work are of the "moving coil" type, and are the only ones which will be considered here. The working parts of instruments of this class are the same in both voltmeters and ammeters, the differences between them being only in the method of connection. The instrument proper is, in reality, a low sensibility, portable D'Arsonval galvanometer, consisting of a coil of fine wire, well-balanced, and pivoted between the poles

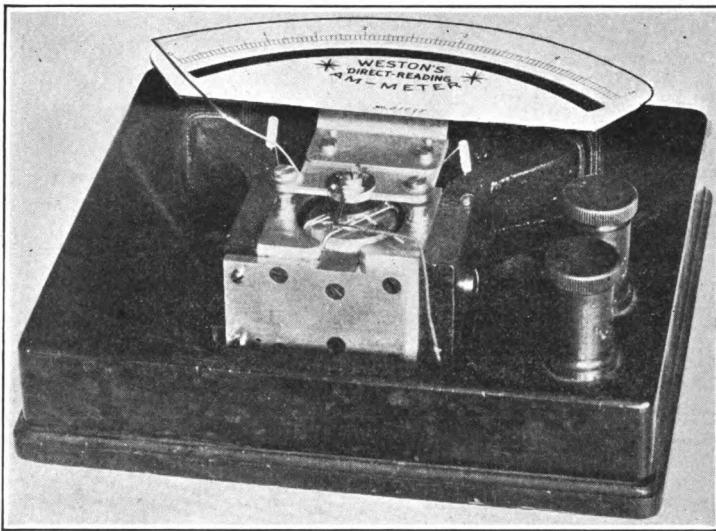


FIG. 41.—Working parts of Weston ammeter.

of a strong, permanent horse-shoe magnet. The magnetic flux through the coil is increased by placing within it a cylindrical iron core, while the air gap is further reduced by pole tips shaped in such a manner as to make the field as nearly radial as possible, with respect to the axis of the coil. In this way, the torque acting upon the coil, when traversed by a current, is independent of its angular position, the condition necessary for equal scale divisions. The current is led to and from the coil by spiral springs, which furnish also the opposing torque. The current sensibility of such an instrument is such that a few thousandths of an ampere, or less, will give a full scale deflection; and since the resistance of the instrument is low, a few millivolts across its terminals will furnish

this current. Figure 41 shows the construction of a Weston ammeter.

When it is desired to construct an ammeter, the instrument  $G$  is provided with a shunt,  $S$ , as shown in Fig. 42. The shunt, which carries the current to be measured, has a resistance (always low) such that it gives, when carrying the maximum current for which it is designed, a fall of potential across its terminals equal to that required for full scale deflection of the instrument. For example, suppose 50 millivolts are required for full scale deflection, and an ammeter reading to 25 amperes is desired; the resistance of the shunt must be

$$R = \frac{.050}{25} = .002 \text{ ohms}$$

By the law of shunts, the current through the instrument (neglected in the above calculation) is proportional to that through the shunt; and if the scale is divided into 25 equal parts, we have an ammeter of the desired range.

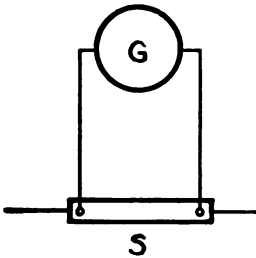


FIG. 42.—Internal connections for ammeter.

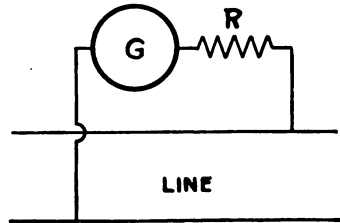


FIG. 43.—Internal connections for voltmeter.

The same instrument may be used as a voltmeter, if, instead of the shunt, it is connected in series with a large resistance  $R$ , Fig. 43, of such a value that, when the maximum voltage to be measured is impressed across the outside terminals of  $G$  and  $R$ , the drop across the instrument is that required for full scale deflection. For example, suppose the instrument, as above, requires 50 millivolts for full scale deflection, that it has a resistance of 10 ohms, and that it is desired to construct a voltmeter reading to 100 volts. By Ohm's law,  $R$ , is given by the following equation:

$$\frac{.050}{99.95} = \frac{10}{R}$$

Whence

$$R = \frac{10 \times 99.95}{.05} = 19,990 \text{ ohms}$$

Since the current through the instrument is proportional to the external voltage impressed, if the scale is divided into 100 equal parts, we have the voltmeter required. In some instruments, e.g., Weston, especially for low ranges, the shunts and series resistances, or multipliers, as they are generally called, are placed within the case and cannot be seen; while in others, e.g., Siemens and Halske, and R. W. Paul, they are mounted outside the case and are detachable. The latter have the advantage of being interchangeable, so that the same instrument, when provided with a series of shunts and multipliers of appropriate values, may serve either as a voltmeter or as an ammeter with any number of ranges for each.

**60. Experiment 9.** *Electrical Adjustment of an Ammeter and a Voltmeter.*—It is the purpose of this exercise to illustrate the fundamental principles of construction and operation of moving coil ammeters and voltmeters. For this purpose, a Weston switch-board type instrument, with transparent case, has been provided with an adjustable external shunt and series resistance. It is to be standardized and tested, first as an ammeter, and then as a voltmeter. In order to accomplish this, it is necessary to know three things concerning the instrument: (1) Resistance; (2) current sensibility; (3) millivolts for full scale deflection.

1. The resistance of the instrument may be obtained directly by means of a Wheatstone bridge. Set the ratio coils Fig. 15 with 100 ohms in the right-hand bank and 10,000 in the left. Be careful to connect the instrument so that the pointer moves forward when operating the bridge.

2. To find the current sensibility of the instrument, which is defined as the current for unit scale deflection, connect it in series with an adjustable known resistance and a cell whose E.M.F. has been determined. In all the tests to be carried out, remember that the instrument is very sensitive, requiring but an exceedingly small current for full scale deflection. Accordingly, a resistance of at least 1,000 ohms should be included before the circuit is closed. Determine the resistances corresponding to five different indications of the instrument distributed uniformly across the scale, and by Ohm's law, compute the current for unit deflection. The E.M.F. of the cell may be obtained by means of a low range voltmeter.

3. The voltage for full scale deflection is given at once by Ohm's

law as the product of the resistance, the current sensibility, and the number of scale divisions.

*Part I. Ammeter.*—It is required to construct an ammeter of range 0–5 amperes, from the instrument and adjustable shunt. From Ohm's Law, find the resistance, which, when carrying 5 amperes, gives a potential drop across its terminals equal to the voltage required for full scale deflection of the instrument. Measure the total resistance of the adjustable shunt by means of the bridge used above, correcting for the leads, and find what length of wire is necessary for the required shunt resistance.

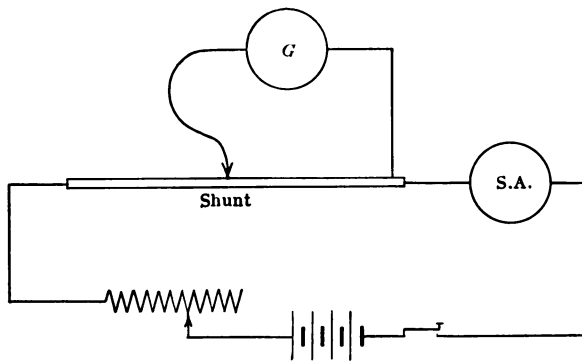


FIG. 44.—Connections for testing improvised ammeter.

Now connect the instrument, as shown in Fig. 44, where *SA* is a standard ammeter and *B*, a storage battery of 6 volts, setting the shunt at the computed value. Check your ammeter against the standard ammeter at 8 or 10 points uniformly distributed across the scale. Now compute, as above, the shunt resistance required in order that your ammeter may have a range of 0–2.5 amperes, and test it in the same manner.

*Part II. Voltmeter.*—It is required to construct a voltmeter of range 0–50 volts, from the instrument and an adjustable series resistance used as a multiplier. From Ohm's law, compute the resistance which, when placed in series with the instrument, will give the potential drop across it necessary for full scale deflection, when 50 volts are impressed across the instrument and multiplier. Connect the apparatus, as shown in Fig. 45, placing in *M* the computed resistance. *B* is a storage battery of 50 volts, *SV* a standard voltmeter, and *PD* a potential dividing rheostat of several hundred ohms, by means of which

any voltage between 0 and 50 may be impressed across the instruments. Check your voltmeter against the standard at 8 or 10 points evenly distributed across the scale.

**Report.**—1. Make a sketch of the instrument describing in detail the essential working parts.

2. Outline the general principles involved in adapting it to measure currents and potential differences.

3. Give in full your data and computations for shunts and multiplying resistances.

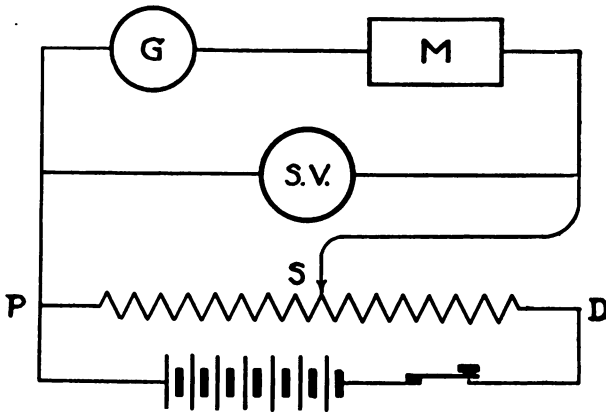


FIG. 45.—Connections for testing improvised voltmeter

4. Give data and curves for your ammeter and voltmeter calibrations.

5. In calculating the resistance of the shunt, in Part I, the current through the instrument was neglected. Compute the error thus made.

**61. Measurement of Current by the Potentiometer.**—Since the potentiometer measures potentials only, current measurements made by it must necessarily be indirect. For this purpose, use is made of a carefully standardized resistance capable of carrying the current to be measured without appreciable heating. The potentiometer measures the fall of potential across its terminals produced by the current, which is then determined by Ohm's law. If the resistance has some decimal value, the value of the current will have the same significant figures as the potential drop across it. Accordingly, if the potentiometer has been made direct reading for voltage, it will indicate currents directly also.

Resistances for this purpose must be provided with two pairs of binding posts, one for current and the other, for potential. The potential leads are soldered securely to the posts between the current terminals and the effective resistance is only that between the points to which they are attached. Errors from imperfect connections are thus eliminated. Such resistances should be placed in an oil bath to keep the temperature constant. The largest resistance giving, for the desired current, a potential difference within the range of the potentiometer should be used.

**62. Experiment 10. Calibration of an Ammeter by Potentiometer and Standard Resistance.**<sup>1</sup>—Connect the apparatus, as shown in Fig. 46. *AM* is the ammeter to be tested, *B* a storage battery of 10 volts, *S* a rheostat for controlling the current, and

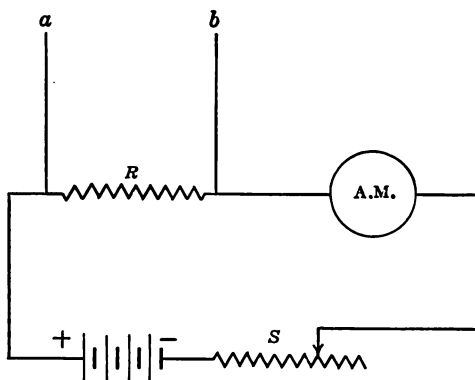


FIG. 46.—Connections for standardizing an ammeter.

*R* a standard oil-cooled resistance provided with current and potential terminals. The leads *ab* are to be connected to the potentiometer. In connecting up the potentiometer and standardizing the current through it, follow the directions for the particular type of instrument given in Chap. IV. After the potentiometer has been adjusted, cause such a current to flow in the ammeter circuit as will produce about one-tenth full scale deflection and measure the fall of potential across *R* by means of the potentiometer. The resistance *R* and the ammeter carry the same current, since no current flows through *a* and *b* at the point of balance. The current through the ammeter is equal to the

<sup>1</sup> JANSKY, *Electrical Meters*, chap. V.

KARAPETOFF, *Experimental Engineering*, vol. I, pp. 51–55.



reading of the potentiometer divided by  $R$ . Since  $R$  has a decimal value, it is merely a question of properly pointing off this indication. In a similar manner, check the ammeter at 8 or 10 points distributed uniformly across the scale. The balance against the standard cell should frequently be tested and any variations in the potentiometer current compensated.

Record ammeter readings, potentiometer settings, and the value of  $R$ . Note carefully the zero reading of the ammeter before beginning the test and again at the end, after the pointer has been deflected for some time, to see if there is any elastic fatigue in the springs. With about two-thirds full scale deflection, place the instrument in a vertical position to test the accuracy with which the moving system is balanced. Bring another instrument near this one to see if there is any effect due to external magnetic fields. Tap the instrument gently with the finger to see if the bearing friction is large. Does the pointer swing past its final indication when a current is suddenly thrown on? Record changes in reading in all of the above cases.

**Report.**—1. Compute the differences between the readings of the instrument and true amperes.

2. Plot these corrections as ordinates against ammeter readings as abscissas. Draw straight lines connecting these points.

3. State your findings regarding the imperfections of the instrument.

4. Would it indicate on alternating currents?

## CHAPTER VI

### MEASUREMENT OF POWER

**63. Wattmeters.**<sup>1</sup>—Whenever a current flows in a circuit, there is a certain amount of energy consumed by the circuit, and any instrument which measures the rate at which energy is consumed is called a wattmeter, from the fact that electrical power is generally measured in watts. Three kinds of wattmeters are in common use; namely, indicating, recording, and integrating. Instruments of the first kind show the power that is being consumed at any instant; those of the second kind make a permanent record on a revolving dial of the power consumption during a given period of time; while those of the third kind show the total energy, that is, the integral of the power times the time, delivered to a circuit during a definite period. Instruments of the first kind only will be considered here, and of the various types in use, only one will be discussed, namely, the electro-dynamometer type.

**64. Use of an Electro-dynamometer for the Measurement of Power.**—In case a steady current is flowing through a circuit, the power is given by the product of the current and the fall of potential across the circuit, or

$$\text{Watts} = \text{Amperes} \times \text{Volts}$$

The watts may, therefore, be measured by simultaneously reading an ammeter and a voltmeter. If, however, a single instrument can be devised which will give indications proportional to both current and voltage, it will automatically indicate their product, and may be calibrated to read watts directly. In the discussion of the electro-dynamometer, it was pointed out that the torque is proportional to the current in both the fixed and movable coils, and, therefore, to their product. Accordingly, if one of the coils can be made to function as an ammeter and the other as a voltmeter, the instrument will be a wattmeter. For this purpose, the fixed coil is made of a few turns of heavy wire and is connected

<sup>1</sup> JANSKY, *Electrical Meters*, chap. X.

KARAPETOFF, *Experimental Engineering*, vol. I, chap. IV.  
*Electrical Meterman's Handbook*.

in series with the circuit like an ammeter, while the movable coil is made of a great many turns of fine wire having a high resistance and is connected across the circuit like a voltmeter and carries a current proportional to the voltage. The torque is proportional, therefore, to amperes times volts, hence, to watts. This is the principle underlying the Weston Indicating wattmeter, the connections for which are shown in Fig. 47. *A* and *B* are series coils consisting of a few turns of heavy wire through which the total current flows, while *C* is a voltage coil of many turns of fine wire. It is connected across the load at the points *H* and *K*, and is mounted so as to turn about an axis through its geometrical center perpendicular to the plane of the paper. Attached to the axle carrying this coil, is a pair of spiral springs, not shown in the

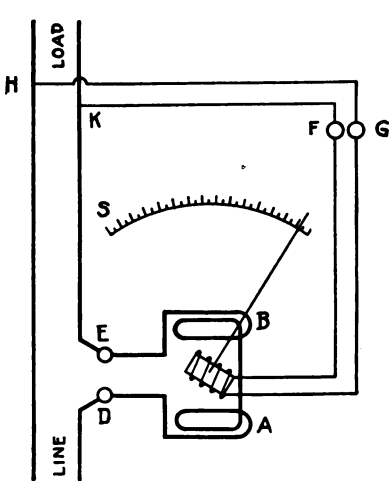


FIG. 47.—Schematic diagram for Weston wattmeter.

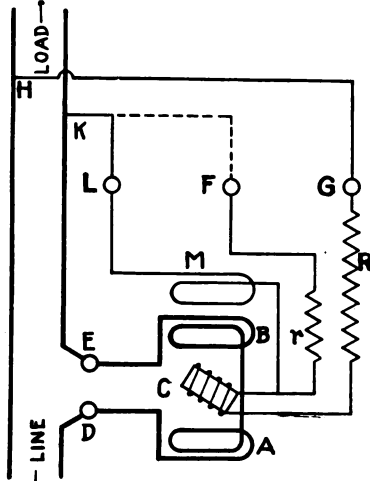


FIG. 48.—Diagram showing compensating and multiplying coils for Weston wattmeter.

figure, whose restoring torque, as the coil is rotated, opposes that due to the electrodynamic action of the currents. They serve also as leads to and from the coil. The scale is so divided that the instrument indicates watts directly.

The readings of such an instrument are subject to an error due to the power consumed by the coils themselves. An inspection of Fig. 47 shows that the current passing through the coils *A* and *B* is the sum of the load current and that carried by the coil *C*, hence the reading must be too large by the  $I^2R$  loss in this coil. If it is attempted to overcome this by connecting the voltage

terminals on the "line" side of the current coils, the registered voltage will be too large by the drop across the current coils thus again making the reading too large. To overcome this difficulty, a compensating coil  $M$  is provided as shown in Fig. 48, which is usually placed inside  $A$  and  $B$  and so connected that its magnetic effect weakens their fields, thus automatically correcting the reading of the instrument. If the wattmeter is to be calibrated by using separate sources of current and potential, this compensation is not necessary, and a separate binding post  $F$  is provided, marked Ind. (Independent) on the instrument. This circuit includes a resistance  $r$  equal to that of the compensating coil, thus making the resistance between  $C$  and  $F$  equal to that between  $C$  and  $L$ . The series resistance  $R$  is used as a multiplying resistance in exactly the same manner as the multiplier in an ordinary D.C. voltmeter. For example, if  $R$  is equal to the resistance of the movable coil, the potential difference across it will be equal to that across the coil, and if the instrument is calibrated without  $R$  in circuit, when  $R$  is included, the readings should be multiplied by the factor two.

**65. Experiment 11. Calibration of a Wattmeter.**—Wattmeters are calibrated on direct currents and may be used on alternating currents as well as direct. Separate sources of current and electromotive force are generally used for purposes of calibration since instruments of large capacity may then be standardized with a comparatively small expenditure of power. Connect the apparatus as shown in Fig. 49, where  $WM$  is the wattmeter which is to be calibrated.  $B$  is ten-volt storage battery furnishing the current which is controlled by the rheostat  $R$  and read by the ammeter  $AM$ .  $C$  is another storage battery furnishing the potential which is controlled by the voltage regulating rheostat  $PS$  and read by the voltmeter  $VM$ . Since the field due to the coils of the instrument is small, extraneous fields, such as those of the earth or large currents, near-by instruments with permanent magnets, etc., may cause errors as large as several per cent. Hence it is necessary, when using this type of wattmeter on direct currents, to reverse both potential and current leads and average the two readings. Make two calibrations. First, hold the current constant and vary the voltage so as to check the instrument at eight or ten points uniformly distributed across the scale. Next hold the voltage constant and vary the current, checking approximately the same points as before.

Record volts, amperes, and indicated watts, both direct and reversed, in all cases. With about two-thirds full scale deflection, bring an instrument with a permanent magnet near the wattmeter and note the effect on the reading. Place the wattmeter pointing in various directions and note any changes due to the earth's magnetic field. Stand the instrument in a vertical position and note any error due to imperfect balancing of the moving system. Change the voltage terminal from the post *F*, marked "Ind." to *L* and note the difference, which is the correction for internal energy consumption.

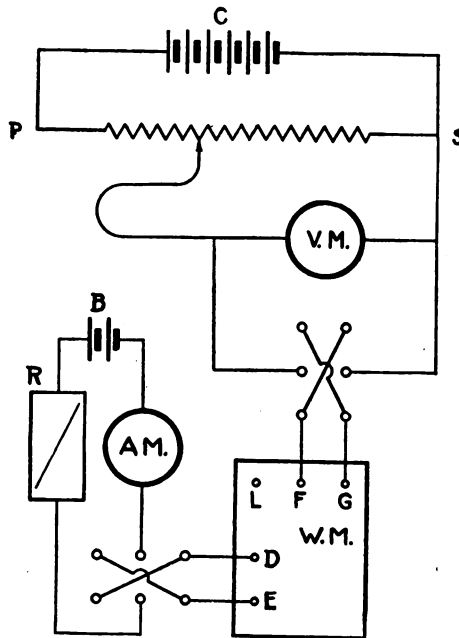


FIG. 49.—Connections for calibrating a wattmeter.

**Report.**—1. Compute true watts from the average products of amperes and volts.

2. Plot corrections as ordinates against wattmeter readings as abscissas. Do the two curves (*a*) with current constant, and (*b*) with voltage constant, coincide?

3. State your findings regarding internal energy consumption, effects of extraneous magnetic fields, balancing of system, etc.

4. Why are the scale divisions in this wattmeter unequal and those of the D.C. voltmeter and ammeter equal?

## CHAPTER VII

### MEASUREMENT OF CAPACITANCE

**66. Condensers.**—When a body is charged with a quantity of electricity  $Q$ , the potential  $V$  which the body acquires is proportional to  $Q$ . With a given charge, however, the potential depends also upon certain conditions of the body such as size, shape, surrounding medium, presence of other charges, etc. The relation between charge and potential is given by the equation

$$Q = CV \quad (1)$$

where  $C$  is a constant depending upon the conditions of the body, and is called the "Capacitance" of the body. It is the ratio of the charge to the potential and is numerically equal to the charge when the potential is unity. The practical unit of capacitance is the farad. A body is said to have a capacitance of one farad when a charge of one coulomb raises its potential by one volt. The farad is too large a unit for practical purposes, however, and it is customary to take the millionth part of this, called the microfarad, as a working unit. Any device by which it is possible to cause a large quantity of electricity to exist under a relatively small potential is called a condenser. Such devices usually consist of thin conducting plates, placed close together, but insulated electrically by thin sheets of some good dielectric material. If a positive charge is placed upon one plate and a negative upon the other, the neutralizing effect of each on the other, due to their close proximity, causes the potential difference between them to be very much reduced over what it would have been if they were far apart.

**67. Grouping of Condensers.**—Condensers, like resistances, may be joined either in series or in parallel and used as a single condenser. Figure 50 represents three condensers joined in parallel. Let  $C_1, C_2, C_3$  represent their individual capacitances,  $q_1, q_2, q_3$  their charges; and  $E$ , the difference of potential across their terminals. Calling  $Q$  the total quantity of electricity stored in the group, which would be obtained if they were discharged, we have

$$Q = q_1 + q_2 + q_3 \quad (2)$$

If  $C$  is the resultant capacitance of the group, we have, from definition,

$$Q = CV = C_1V + C_2V + C_3V \tag{3}$$

or

$$C = C_1 + C_2 + C_3 \tag{4}$$

For condensers connected in parallel, the resultant capacitance is the sum of the individual capacitances of the group. The capacitance of  $n$  similar condensers thus joined is  $n$  times the capacitance of a single condenser. Figure 51 represents three condensers connected in series. As before, let  $C_1, C_2, C_3$  represent

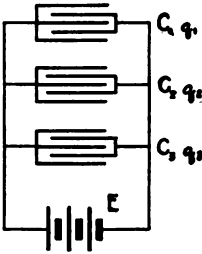


FIG. 50.—Condensers joined in parallel.

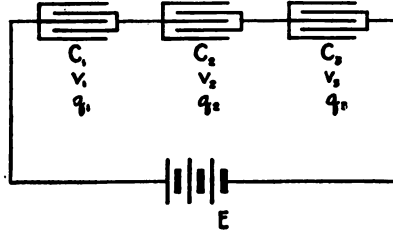


FIG. 51.—Condensers joined in series.

the values of the individual condensers;  $q_1, q_2, q_3$  their charges, and  $v_1, v_2, v_3$  the potential differences across each. It is evident from the figure that

$$E = v_1 + v_2 + v_3 \tag{5}$$

Calling  $C$  the resultant capacitance of the group, and  $Q$  the total charge, we have, from definition,

$$E = \frac{Q}{C} = \frac{q_1}{C_1} + \frac{q_2}{C_2} + \frac{q_3}{C_3} \tag{6}$$

A simple relation exists between these charges. We have tacitly assumed that the condensers were uncharged before connection. Suppose a unit charge passes from the battery to the outer coating of  $C_1$ . A negative charge will then be induced on the inner coating and a positive unit charge repelled from it which will charge the outer coating of  $C_2$  and induce a negative unit charge on its inner coating and so on. The next unit charge from the battery will do the same. It is evident then that the charge for each condenser is the same, no matter what its capacitance and that the total charge which may be obtained from the group on discharge is the same as the charge from any one condenser. That is, the

positive charge on the outer coating of  $C_1$  neutralizes the charge on the inner coating of  $C_3$  and similarly for the other condensers of the group. Thus we have

$$Q = q_1 = q_2 = q_3 \quad (7)$$

and

$$\frac{1}{C} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} \quad (8)$$

For condensers joined in series, the reciprocal of the resultant capacitance is the sum of the reciprocals of the individual capacitances. The resultant capacitance of  $n$  similar condensers so joined is  $\frac{1}{n}$  times the capacitance of a single condenser.

**68. Standard Condensers.**—Standard condensers are made of sheets of tin foil separated by mica, alternate sheets of foil being joined as shown in Fig. 50, and the whole finally imbedded in solid paraffin. Figure 52 shows the connections for

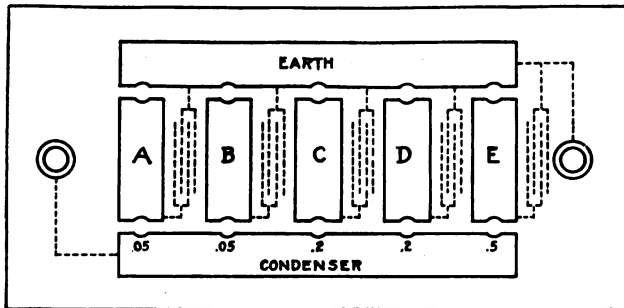


Fig. 52.—Connections for subdivided standard condenser.

one of the subdivided standard condensers used in the laboratory. One side of each of the sections shown by the dotted lines is joined to a heavy bar marked "Earth" and the other sides to one of the blocks. Another bar marked "Condenser" is mounted opposite, and each bar is connected to a binding post. When it is desired to use a certain capacity, e.g.,  $2 MF$ , place a plug in the socket between  $C$  and the lower bar. If  $.7 MF$  is desired, place another plug between  $E$  and this bar. Similarly for the various other possible connections. When a section is not in use, it should be short circuited by placing a plug in the socket between the upper bar and the corresponding block. Care should be taken never to place plugs at both ends of any block as



that would short circuit the entire condenser, possibly injuring apparatus to which it is connected.

Another method of assembling subdivided standard condensers is to join the units, not between the central lugs and one of the bus bars as shown in Fig. 52, but to connect them between the lugs as shown in Fig. 53. Thus between *A* and *B* there is .05 micro-

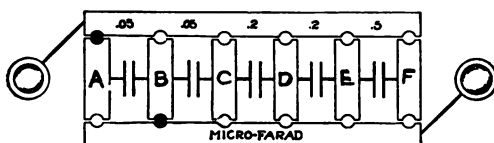


FIG. 53.—Alternate method of connecting condenser units.

farads, between *B* and *C*, .05, etc. One more lug is required in this case. To connect all the units in parallel, plugs are inserted in alternate holes on each side, but staggered. The method has the advantage of permitting series grouping of the units, thus giving a greater number of values of capacitance for a given number of units. A subdivided standard condenser is shown in Fig. 54.

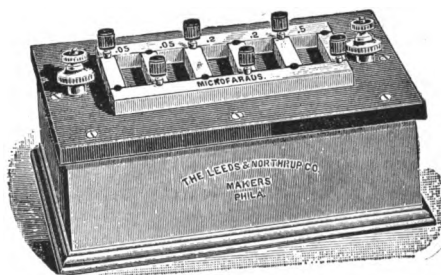


FIG. 54.—Subdivided standard condenser.

**69. Comparison of Condensers.**—The capacitance of an unknown condenser may be found by comparing it with a standard condenser. A ready means of doing this which gives results sufficiently accurate for many purposes is to charge both the unknown and the standard to the same potential difference and discharge each in succession through a ballistic galvanometer. The set-up for this purpose is shown in Fig. 9. Let  $C_1$  be the unknown and  $C_2$  the standard condenser. First insert  $C_1$ , then charge and discharge several times, taking the average deflection

which we will call  $d_1$ . From the definition of capacitance we have, as the charge in the condenser.

$$Q_1 = C_1 V, \quad (9)$$

and, since the deflection of a ballistic galvanometer is proportional to the charge passed through it,

$$Q_1 = C_1 V = K d_1 \quad (10)$$

Now replace the unknown by the standard condenser and charge and discharge as before. In a similar manner, we have

$$Q_2 = C_2 V = K d_2 \quad (11)$$

Dividing equation (10) by (11),

$$\frac{C_1}{C_2} = \frac{d_1}{d_2}. \quad (12)$$

**70. Bridge Method for Comparing Two Condensers.**<sup>1</sup>—A more accurate comparison of two condensers may be made by means

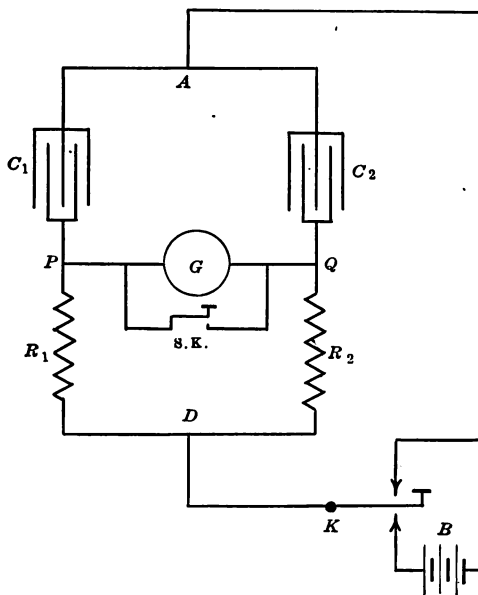


FIG. 55.—Bridge method for comparing two condensers.

of an arrangement similar to the Wheatstone bridge in which the resistances of two of the arms are replaced by the two condensers to be compared, and the current galvanometer is replaced by a

<sup>1</sup> CARHART and PATTERSON, *Electrical Measurements*, pp. 213–220.  
SMITH, *Electrical Measurements*, art. IX.

ballistic galvanometer. The connections are shown in Fig. 55.  $C_1$  and  $C_2$  are two condensers and  $R_1$  and  $R_2$  two variable resistance boxes.  $K$  is a charge and discharge key so connected that, when the blade is pressed down, the battery  $B$  is connected to the bridge, thus charging the condensers through  $R_1$  and  $R_2$  to the potential difference furnished by the battery. When contact is made on the upper point, the battery is disconnected and the condensers are discharged through the resistances. No matter what the values of  $R_1$  and  $R_2$  may be, the points  $P$  and  $Q$  will come to the same final potentials on charge and again on complete discharge, since, when no current is flowing through the resistances there can be no fall of potential across them. However, during the charging and discharging processes there are currents through the resistances and, in general, there will be a momentary difference of potential between  $P$  and  $Q$  causing a deflection of the galvanometer in one direction on charge, and in the opposite, on discharge. By properly adjusting  $R_1$  and  $R_2$ , it is possible to make the potentials at  $P$  and  $Q$  rise and fall at the same rate which is the balance condition for the bridge, from which the relation between the capacitances and resistances may be deduced.

Let  $q_1$  and  $q_2$  = instantaneous charges in  $C_1$  and  $C_2$

Let  $i_1$  and  $i_2$  = instantaneous currents in  $R_1$  and  $R_2$

As in the ordinary Wheatstone bridge, we have

P.D. between  $A$  and  $P$  = P.D. between  $A$  and  $Q$

P.D. between  $P$  and  $D$  = P.D. between  $Q$  and  $D$

whence

$$\frac{q_1}{C_1} = \frac{q_2}{C_2} \quad (13)$$

and

$$R_1 i_1 = R_2 i_2 \quad (14)$$

Differentiating (13) and remembering that  $i = \frac{dq}{dt}$ , we have

$$\frac{1dq_1}{C_1 dt} = \frac{1dq_2}{C_2 dt}$$

or

$$\frac{i_1}{C_1} = \frac{i_2}{C_2} \quad (15)$$

Dividing (14) by (15)

$$R_1 C_1 = R_2 C_2 \quad (16)$$

or

$$\frac{C_1}{C_2} = \frac{R_2}{R_1} \quad (17)$$

It is to be noted that the ratio of the capacitances is the inverse ratio of the resistances, whereas, in the bridge method for resistances, it is the direct ratio.

**71. Experiment 12. Comparison of Two Capacitances by the Bridge Method.**—Connect the apparatus as shown in Fig. 55, using for  $B$  a battery of 40 volts.  $SK$  is a short circuiting key to bring the galvanometer to rest after taking an observation. Use for  $C_1$  a subdivided standard condenser and for  $C_2$  a fixed condenser of about one-half micro-farad capacity. The problem is to check the parts of  $C_1$  in terms of the whole. Set the plugs of  $C_1$  so as to give the maximum available capacitance, and with this as a standard, obtain several balances on  $C_2$ , using different values for  $R_1$  and  $R_2$  in each case. Now, taking this measured value of  $C_2$  as a standard, determine the capacitance of each part of  $C_1$ , making several independent balances for each. In all cases use as large values for  $R_1$  and  $R_2$  as possible.

**Report.**—Tabulate your data in compact form. Your values for the separate parts of  $C_1$  should add up to the total value indicated on the top of the box.

**72. Measurement of Small Capacitance by Commutator.**<sup>1</sup>—The bridge method just described is not suited to the measurement of small capacitances since the charging currents are so minute that the potential drops through the resistances are inappreciable. For the determination of a small capacitance, such as that of an air condenser used in radio work or that between the wires of a transmission line, a direct deflection method may be used in which the condenser is rapidly charged to a known voltage and then discharged through a standardized galvanometer by means of a motor-driven commutator. If the interval between discharges is small compared to the period of the galvanometer, a steady deflection results which is proportional to the average value of the current.

<sup>1</sup> FLEMING and CLINTON, *Proc. Phys. Soc. of London*, vol. 18, 1901-03, p. 386.

Figure 56 shows the principle of the Fleming and Clinton commutator, designed for this purpose, together with the wiring diagram.  $S_1$  and  $S_2$  are slip rings which revolve in a plane perpendicular to the paper while  $S_3$  is a series of posts alternately connected to  $S_1$  and  $S_2$ . When brush 3 rests upon a segment connected to  $S_1$ , the condenser  $C$  is charged to the potential difference of the battery  $B$ , and when 3 touches the succeeding post, the condenser is discharged through the galvanometer. Let  $n$  be the number of discharges per second and  $V$  the E.M.F. of the battery. Then the current through the galvanometer is

$$I = nCV \times 10^{-6} = Fd \quad (18)$$

Where  $C$  is the capacity of the condenser in microfarads, and  $F$ , the figure of merit of the galvanometer, i.e., the current for unit deflection.

In designing a commutator of this type, special precautions must be taken to secure good insulation between posts and sectors. They are generally made with an air gap between posts since metal abraded by friction otherwise embeds itself in a solid dielectric thus giving a direct leakage path from the battery through the galvanometer. A speed counter, mounted on the shaft, indicates the number of revolutions.

**73. Experiment 13.** *Capacitance by the Fleming and Clinton Method.*—Connect the apparatus as shown in Fig. 56 using for  $C$  an air condenser of small capacitance. Drive the commutator at speeds sufficient to give 50 to 100 discharges per second through the galvanometer, and use for  $B$  a battery with voltage large enough to produce a deflection of about 10 cms. Take special precautions to insure good insulation between the galvanometer and battery circuits. Use a number of different speeds and voltages and determine the value of  $C$  by eq. (18). Determine the figure of merit of the galvanometer by the method given in Art. 23.

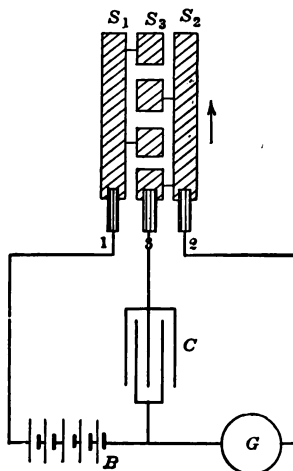


FIG. 56.—Fleming and Clinton commutator.

**Report.**—1. Tabulate observations and results for the series of measurements taken.

2. Check your results by measuring the dimensions of the condenser, and computing its capacity from the formula for the parallel plate condenser

$$C = .0885 \times 10^{-6} \frac{KA}{d} \text{ microfarads} \quad (19)$$

where  $A$  is the area of one of the plates in square centimeters,  $d$  the thickness of the dielectric, and  $k$  the dielectric constant ( $K = 1$  for air).

3. How do you account for the difference between the measured and computed values?

## CHAPTER VIII

### MAGNETISM

**74. General Principles.**—Magnetism is a universal property of matter, since there is no substance which does not experience a ponder-motive action when placed near the poles of a strong magnet, though in many cases the effect is so weak that delicate means are necessary for its detection. Substances may be divided into two groups, in accordance with the manner in which they behave when acted upon by a magnetic pole; those which are attracted by the magnet are called paramagnetic, and those repelled, diamagnetic. It is customary to add a third group, including iron, nickel, and cobalt, which are characterized by the fact that the ponder-motive action upon them is not proportional to the strength of the attracting pole as in the case of ordinary paramagnetic substances, but is much stronger.

**75. Strength of Pole.**—In the early study of magnets, it was noticed that the magnetic property of a body is confined largely to the areas about its ends and corners, and that opposite ends behave differently toward other magnets. The term magnetic pole was given to the regions where the property was most pronounced and has been retained although it has been known for a long time that magnetism is a volume and not a surface phenomenon. *A unit magnetic pole is defined as one which repels an exactly similar pole at a distance of one centimeter in air with a force of one dyne.*

**76. Strength of Field.**—The space surrounding a magnetic pole in which action upon another pole can be detected is called a magnetic field, and is measured, at any particular point, by the force in dynes with which a free unit positive pole is acted upon when placed at that point. *A field of unit strength or intensity is one which will exert a force of one dyne upon a unit pole.* Since field strength is thus measured by force per unit pole, it is a vector quantity; *i.e.*, it possesses both magnitude and direction. Both of these characteristics may be represented by imagining lines drawn in space according to a definite convention; namely,

the magnitude of the field by drawing as many lines per square centimeter as the field has units of intensity, and the direction, by making these lines coincide at every point with the direction in which the unit measuring pole is urged. According to this convention, if a sphere of unit radius is drawn with a pole of strength  $m$  as a center, there must pass through each square centimeter of its surface  $m$  lines, giving a total of  $4\pi m$  lines from the pole. From a unit pole there will emanate according to this convention,  $4\pi$  lines of force.

**77. Intensity of Magnetization.**—Let us imagine an ideal permanent bar magnet, of length  $L$ , and uniform cross section  $A$ , magnetized uniformly and showing, therefore, pole-strength over the ends only. That is to say, the magnetic lines all leave one end, pass in regular curves through the outside space, and enter the other end with no lines entering or leaving on the side, as in any real magnet. Let the strength of pole be  $m$ . The pole strength per unit area,  $\frac{m}{A}$ , is defined as the intensity of magnetization and is generally represented by the letter  $I$ .

**78. Magnetic Moment.**—Imagine the ideal magnet mentioned above placed at right angles to a uniform magnetic field of strength  $H$ . Equal and opposite forces of magnitude  $Hm$  will act upon this magnet producing a couple of strength  $HmL$ . If  $H$  is unity, the magnitude of the couple is  $mL$ , and this quantity, which is exceedingly important in treating problems involving magnets, is called the magnetic moment, and is designated by the letter  $M$ . The moment of any magnet is, then, the torque acting upon it when placed at right angles to a uniform field of unit strength. Another definition of intensity of magnetization in terms of magnetic moment may be obtained as follows: Since the volume of the bar magnet is  $LA$ , we have

$$I = \frac{m}{A} = \frac{mL}{AL} = \frac{M}{V} \quad (1)$$

Intensity of magnetization is thus defined as a volume rather than a surface effect.

**79. Magnetic Induction.**—Let us imagine that, in an infinitely long, uniform magnetic field of strength  $H$ , an iron bar is placed with its axis parallel to the field. The bar becomes magnetized to an intensity  $I$  and is equivalent to the ideal magnet considered above. The number of magnetic lines through the space



occupied by the bar has been increased by the lines of magnetization due to the bar. The total number of magnetic lines through the bar, which is made up of the original lines and the lines of magnetization, is called the magnetic flux, and is generally designated by the Greek letter  $\phi$ . The number of lines per square centimeter through the bar is called the magnetic induction, and is represented by the letter  $B$ . Thus

$$B = \text{Induction} = \frac{\text{Total Flux}}{\text{Area}} = \frac{\phi}{A} \quad (2)$$

The induction  $B$  is defined in the following manner: Imagine a narrow crevasse cut through the middle of the bar at right angles to its axis, and a unit positive pole placed within. The force in dynes upon this pole measures  $B$ . The original field produces a force of  $H$  dynes upon the pole, and since the iron is magnetized to an intensity  $I$ , meaning  $I$  units of pole strength per unit area of the crevasse, from each of which  $4\pi$  lines emanate, we have, as the total lines per square centimeter through the gap or the force in dynes acting upon the unit pole

$$B = H + 4\pi I \quad (3)$$

Lines of induction are continuous throughout the magnetic circuit; that is, they never begin or end but form closed paths, the parts in the air being called lines of force. If, instead of the transverse crevasse we had bored a small hole through the bar parallel to the lines of force and placed a unit magnetic pole within, the force upon it would be the original strength of field  $H$  which has produced the magnetic induction.

**80. Permeability and Susceptibility.**—For many purposes it is convenient to define the magnetic quality of a given material in terms of the relative increase in the number of lines or the intensity of magnetization produced. For this purpose the terms *permeability* and *susceptibility* are used. By permeability is meant the ratio of the induction  $B$  to the field strength  $H$ , and is represented by the Greek letter  $\mu$ . That is,

$$\mu = \frac{B}{H} \quad (4)$$

where  $B$  is the induction produced in a given material when acted upon by a field of strength  $H$ . When it is desired to express the ability of a material to acquire magnetism and to state its condition in terms, not of the total induction, but of its own magnetic lines alone, we use the term *susceptibility*. This is

defined as the ratio of the intensity of magnetization of the specimen to the magnetizing field in which it is placed, and is represented by the Greek letter  $\kappa$ . That is,

$$\kappa = \frac{I}{H} \quad (5)$$

A simple relation exists between these two quantities. Taking the defining equation for induction

$$B = H + 4\pi I \quad (6)$$

and dividing through by  $H$ , we have

$$\frac{B}{H} = 1 + 4\pi \frac{I}{H} \quad (7)$$

or

$$\mu = 1 + 4\pi\kappa \quad (8)$$

**81. Effects of the Ends of a Bar.**—When a bar is magnetized longitudinally by placing it in a magnetic field, the ends become poles which act upon any other pole in the neighborhood, attracting or repelling it according to the relative signs of the poles. If the bar lies in an east-west position, magnetized with a north pole at the west end, a unit north pole lying near the middle of the bar, but outside it, would be urged from west to east or in a direction opposite to that in which the bar is magnetized. If now the unit pole is placed within the bar, the force is in the same direction. Thus the effect of the poles is to produce a field within the bar called a “demagnetizing field” which is opposite to the direction of the field magnetizing it. This effect is greater the shorter the bar is in comparison to its diameter. The actual field producing magnetization is, accordingly, less than the field before the bar was introduced. This phenomenon is allowed for by computing the effective field  $H$  from the equation

$$H = H' - NI \quad (9)$$

where  $H'$  is the original field and  $N$  a constant depending upon the ratio of the length to the diameter of the bar, and is called the “Demagnetizing Factor.” Tables<sup>1</sup> for  $N$  may be found in the more advanced treatises on the subject. The same considerations hold for solenoids, and hence it is necessary, when one wishes a solenoid whose field may be computed readily from its dimensions, to make it long in comparison to its diameter. If one uses a ring solenoid, or a test specimen in the form of a ring,

<sup>1</sup> DU BOIS, *The Magnetic Circuit*, p. 41.

this correction is unnecessary since there are no free poles to produce disturbing effects of this character.

**82. The Magnetic Circuit.**—In treating such phenomena as the conduction of heat and the flow of electricity, one makes use of a general law in which the magnitude of the effect is given as the ratio of a driving force divided by an opposition factor dependent upon the properties of the medium in which the action takes place. For example, the heat current  $Q$ , *i.e.*, the quantity of heat passing per unit time any cross section of a conductor of length  $L$  and cross sectional area  $A$ , when the temperature at the ends are  $t_1$  and  $t_2$ , is given by the expression

$$Q = \frac{t_1 - t_2}{\frac{L}{\tau A}} \quad (10)$$

where  $\tau$  is a constant defining the ability of the medium to conduct heat.  $\tau$  is called the specific thermal conductivity and is numerically equal to the quantity of heat passing through a centimeter cube of the material, per unit time, when a difference of temperature of one degree is maintained across its faces. Similarly, the electrical current flowing in the above conductor when its ends are maintained at electrical potentials  $V_1$  and  $V_2$ , is given by

$$I = \frac{V_1 - V_2}{\frac{L\rho}{A}} = \frac{V_1 - V_2}{\frac{L}{CA}} \quad (11)$$

where  $C = \frac{1}{\rho}$  is called the specific electrical conductivity of the material and is numerically equal to the current flowing through a centimeter cube when unit difference of potential is maintained across its faces. Its reciprocal  $\rho$  is called the specific resistance, and is the resistance of the centimeter cube. This equation is called Ohm's law and is written

$$\text{Current} = \frac{\text{Electromotive Force}}{\text{Resistance}}$$

In an analogous manner it is convenient, for purposes of calculation, to regard the region in which a magnetized state exists as being the seat of a magnetic flow. The magnetic lines of induction are the stream lines along which the flow takes place, and since magnetic lines are closed paths, the lines of flow are closed circuits. Materials are then classified as good or bad magnetic conductors according to the ease with which they are magnetized.

To make the analogy clear, consider a specimen of magnetic material in the form of an anchor ring, wound uniformly with wire through which a current is flowing, as shown in Fig. 57. We wish to compute the total magnetic flux produced in the ring when a given current is flowing.

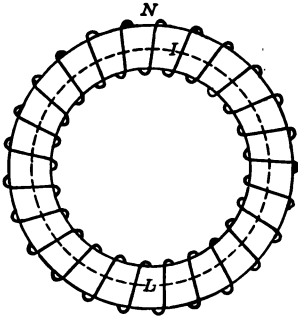


FIG. 57.—The magnetic circuit.

Let  $N$  = total number of turns  
 $L$  = mean length of magnetic lines  
 $A$  = area of cross section of ring  
 $B$  = magnetic induction in ring  
 $\mu$  = permeability  
 $I$  = strength of current

As a direct consequence of the definition of the electromagnetic unit of current, it is shown in elementary textbooks that the work done in carrying a unit magnetic pole once around a current of strength  $I$  E.M.U.'s, is  $4\pi I$  ergs. The field strength within the ring solenoid may be obtained from the fact that the work done in taking a unit pole around this magnetic circuit is

$$\text{Work} = HL = 4\pi NI \quad (12)$$

since the pole is, in reality, carried  $N$  times around the current.  
 Whence

$$H = \frac{4\pi NI}{L} \quad (13)$$

If  $I$  is expressed in amperes instead of electromagnetic units,

$$H = \frac{4\pi NI}{10L} \quad (14)$$

From the above definitions, the expression for the total flux is obtained in the following manner:

$$\phi = BA = \mu HA = \frac{\mu A 4\pi NI}{10L} \quad (15)$$

which may be written in the form

$$\phi = \frac{.4\pi NI}{\frac{L}{\mu A}} \quad (16)$$

The numerator of the right-hand member is of the nature of a driving force, the denominator, an opposition factor depending upon the medium, and their ratio, the effect produced. This

equation is called the "Law of the Magnetic Circuit" and is written

$$\text{Magnetic Flux} = \frac{\text{Magnetomotive Force}}{\text{Reluctance}}$$

**83. Magnetic flux**, which represents the total number of lines of induction, is analogous to flow of heat in calorimetry, and to current in electricity. It forms a closed path which may be spread out over a large area in some places and be concentrated within narrow limits in others. The unit of magnetic flux is called the maxwell and is represented by one magnetic line of induction through the total cross sectional area of the magnetic circuit. Thus, if in a magnetic circuit, there are one thousand lines, the flux is said to be one thousand maxwells. In engineering practice, it is customary to define flux on the basis of the E.M.F. induced in a conductor which cuts it.

*Definition.*—If, in a moving conductor, the induced E.M.F. is one electromagnetic unit, the flux cut per second is one maxwell.<sup>1</sup>

**84. The magnetic induction** is defined as the total flux divided by the area, and is, accordingly, the flux density. The unit of magnetic induction is the gauss.

*Definition.*—Unit induction, or one gauss, exists in a magnetic circuit in which the flux density is one maxwell per square centimeter. Thus

$$\text{Gausses} = \frac{\text{Maxwells}}{\text{Square Centimeters}}$$

**85. Magnetomotive force** may be regarded as the cause of magnetic flux. It is analogous to electromotive force in the electric circuit and is measured in a similar manner. Just as the electromotive force of an electrical circuit is the work required to carry unit electrical charge once around the circuit, so the magneto-motive force in a magnetic circuit is the work required to carry unit magnetic pole once around the circuit. The unit of magnetomotive force is the gilbert.

*Definition.*—If the work required to carry a unit magnetic pole once around a magnetic circuit is one erg, the magnetomotive force is one gilbert.

In case the magnetomotive force is produced by a current in a closed solenoid, as in the above illustration, its value, as given

<sup>1</sup> Note.—The Units for the quantities involved in the magnetic circuit here described were adopted by the International Electrical Congress at Paris, in 1900.

by equation (16) is  $.4\pi NI$ . The product  $NI$  is called the ampere turn, and differs from magnetomotive force only by the constant factor  $.4\pi = 1.26$ . Thus

M.M.F. in Gilberts =  $.4\pi$  Ampere Turns.

Magnetomotive force, being thus measured in terms of work per unit pole, is difference of magnetic potential. Accordingly, if  $H$  is the average value of the magnetic field strength between two equipotential surfaces,  $s$  cms. apart, having magnetic potentials  $M_1$  and  $M_2$ , respectively,

$$H = \frac{M_1 - M_2}{s} = \frac{\Delta M}{\Delta s} \quad (17)$$

where  $\Delta M$  and  $\Delta s$  represent small differences in  $M$  and  $s$ , respectively. Allowing the equipotential surfaces to approach indefinitely close to one another, the limiting value of this ratio gives the actual field strength at a given point. Thus

$$H = \frac{dM}{ds}. \quad (18)$$

Magnetic field strength is the change in magnetic potential per centimeter in the direction of  $H$  or the magnetic potential gradient. The unit of magnetic field strength is called the gilbert per centimeter.

**86. Reluctance** is the resistance a body offers to being magnetized and depends upon the constants of the circuit in a manner similar to resistance in the electrical circuit. As seen from eq. (16), it is directly proportional to the length and inversely proportional to the area and the permeability of the medium. Permeability thus corresponds to specific conductivity, and its reciprocal, corresponding to specific resistance or resistivity, is often called "reluctivity." The unit of reluctance is defined in terms of the law of the magnetic circuit and is called the oersted.

*Definition.*—If, in a magnetic circuit, the flux is one maxwell when the magnetomotive force is one gilbert, the reluctance is one oersted.

Reluctances, like resistances, may be joined in series or parallel to form complex circuits, and laws similar to those for resistances hold.

1. For reluctances joined in series, the total reluctance is the sum of the individual reluctances.

2. For reluctances joined in parallel, the reciprocal of the total reluctance is the sum of the reciprocals of the individual reluctances.

**87. Limitations.**—While the idea of the magnetic circuit is an extremely useful one for purposes of calculation, it must not be regarded as a true physical concept, such as the electrical circuit, but merely as an analogy serving a useful purpose. Among the respects in which the analogy fails are the following:

1. There is no such thing as a magnetic substance in the sense in which we have used it, and hence there can be no magnetic flow.

2. When once the magnetic flux has been established, no energy is required to maintain it, and there is nothing corresponding to the  $I^2R$  consumption of energy in the electric circuit.

3. The reluctance of a circuit containing ferro-magnetic material is not a constant for a given set of physical conditions but varies with the flux, while the resistance of an electric circuit is independent of the current flowing.

4. For ferro-magnetic materials, the reluctance is not a single valued function of the flux, but depends upon the magneto-motive forces to which they previously have been subjected. In other words, there is no analogy, in the electric circuit, to Hysteresis.

**88. Magnetization Curves.**—Para- and diamagnetic substances are characterized by the fact that, under a given set of physical conditions, the permeability remains constant; that is, as the magnetizing field is changed, the induction changes by proportional amounts. This, however, is not true of ferro-magnetic substances. If a piece of unmagnetized iron, for example, is placed in a field which may be varied at will, it is found, starting with  $H = 0$  and gradually increasing it, that the induction  $B$  increases slowly at first, remaining nearly proportional to the field; then increases rapidly, for a certain interval of  $H$ , after which a further increase produces only relatively small increments in  $B$ . The curve showing the values of induction for different magnetizing fields is called the "magnetization curve," and is represented by  $OB$  of Fig. 58. The three parts of the curve, differentiated by rather abrupt changes in slope, are accounted for by assuming that, in the unmagnetized condition, the magnetic axes of the molecular magnets are distributed entirely at random, as many pointing in one direction as in any other; and that the magnetic circuits, of which they form parts,

are small closed curves. Under the action of a weak magnetic field, these molecular magnets are all sprung to a slight extent from their initial positions, giving a resultant component in the direction of the applied field, the amount of deformation being proportional to the field. Thus the part of the curve near the origin is obtained. With a further increase of field, some of these local magnetic circuits are broken, and new alignments formed, giving chains of molecules of considerable length. As each local circuit breaks, becoming part of a chain, neighboring

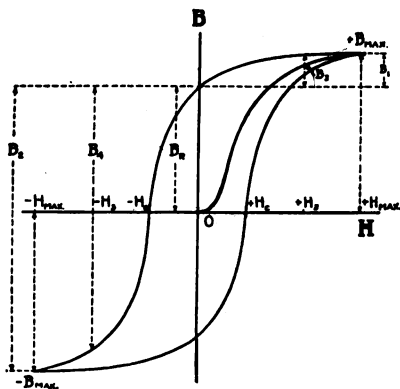


FIG. 58.—Magnetization and hysteresis curves.

groups become unstable, break, and form other chains, thus giving a sort of spontaneous magnetization, resulting in changes in induction much greater than required for proportionality to changes in field. Thus the steep part of the curve is given. As the condition is approached in which all the local groups have been broken up and the molecules placed in complete alignment, the iron is said to become saturated, and further increases in field produce only small changes in induction. So the upper part of the curve which is nearly horizontal is obtained.

**89. Hysteresis.**—If, after the induction has been carried to the point marked  $+B_{\max}$  on the curve of Fig. 58, the magnetizing field is gradually reduced, the induction does not retrace the magnetization curve, but takes on values, for a given field, greater than those for the magnetization curve; and when  $H$  has been reduced to zero, an amount of induction indicated by  $B_R$  still persists. If a reverse field is applied, the induction rapidly falls; and when a certain value,  $-H_c$ , has been reached, the resultant induction is zero; after this, a further negative increase in field to



$-H_{\max}$  gives a reversed value of induction  $-B_{\max}$  equal in magnitude to  $+B_{\max}$ . With a gradual increase in  $H$  to its original positive value,  $B$  assumes values shown by the lower curve of the figure, symmetrical with respect to the origin with the upper one just described. This tendency of any material to persist in a given magnetic state is known as "hysteresis," and the corresponding curve is called the hysteresis curve.  $B_R$  is called the retentivity, and  $H_C$ , the coercive field.

It may be shown that the area of the hysteresis loop is a measure of the energy consumed by molecular friction in each cubic centimeter of material when carried once through a magnetic cycle. For this purpose, let us refer to the ring specimen described in Art. 75, and use the nomenclature there indicated. The method of proof is based upon the fact that, as the current in the magnetizing coil is changed, producing changes of flux in the ring, a counter E.M.F. is induced, against which the magnetizing current must flow. The electrical energy which thus disappears is the energy consumed by hysteresis and reappears in the form of heat within the ring. Let  $i$  represent the instantaneous magnetizing current and let  $dB$  and  $d\phi$  be the changes in induction and flux, respectively, when a change  $di$  occurs in the magnetizing current. If  $dt$  represents the time required for this change to take place, the energy  $dw$  consumed during the change is given by

$$dw = e idt \quad (19)$$

But

$$e = N \frac{d\phi}{dt} = NA \frac{dB}{dt} \quad (20)$$

Therefore

$$dw = NA idB \quad (21)$$

Since

$$H = \frac{4\pi Ni}{L},$$

we have

$$Ni = \frac{HL}{4\pi}. \quad (22)$$

Substituting

$$dw = \frac{HLAdB}{4\pi} = \frac{V}{4\pi} HdB \quad (23)$$

where  $V$  is the volume of the ring. Summing up for the complete cycle, we have

$$\int dw = W = \frac{V}{4\pi} \int_c HdB = \frac{V}{4\pi} (\text{area of loop}) \quad (24)$$

It is thus seen that the area of the loop divided by  $4\pi$  gives the energy lost per cycle per cubic centimeter of material. The shape of the loop varies with the quality of the iron; hard steels have both a high retentivity and coercive force; soft steels, a high retentivity but a low coercive force; while Swedish iron has both a low retentivity and low coercive force. For a given specimen, the area of the loop depends upon the limits of induction. Steinmetz has made an exhaustive study of this relation and has found that the energy lost is proportional to the 1.6 power of the maximum induction. Expressed in symbols,

$$W = KB^{1.6} \quad (25)$$

$K$  is called the Steinmetz coefficient.

**90. Practical Methods.**<sup>1</sup>—For the measurement of magnetic induction, there are three general methods, each of which possess certain advantages as well as disadvantages. They may be classified as follows:

1. The Traction Method.
2. The Magnetometer Method.
3. The Ballistic Method.

The first method consists in measuring the mechanical force required to pull the magnetized specimen away from a massive piece of iron. Since the specimen induces in the block at the point of contact a pole of strength equal and opposite to its own, the force required to separate them is proportional to the square of the intensity of magnetization. In the second method, the specimen is made in the form of a rod or elongated ellipsoid and magnetized by being placed within a long solenoid. Its magnetic moment is determined by observing the deflection it produces upon a small compass needle, called a magnetometer, placed near it. From the magnetic moment, the intensity of magnetization, and hence the induction, may be computed. In the ballistic method, the specimen under test forms the whole or part of a closed magnetic circuit, wound with suitable magnetizing coils, and also a secondary coil, connected to a ballistic galvanometer. Any change in flux induces in the secondary a quantity of electricity which is measured by the ballistic galvanometer and from this quantity the change in flux is computed. From the standpoint of accuracy and ease of performance the

<sup>1</sup> EWING, *Magnetic Induction in Iron*, chap. II.

DUBOIS, *The Magnetic Circuit*, chap. XI.

ballistic method is much to be preferred and is the only one which will be considered here.

**91. Hopkinson's Bar and Yoke.**<sup>1</sup>—This is an application of the ballistic method in which the samples to be tested are in the form of rods, closely fitted into holes in a heavy yoke of soft iron. The arrangement is shown in Fig. 59, where  $YY$  is the yoke and  $CC'$  the specimen under test.  $MM$  are the magnetizing coils and  $F$  the secondary coil. The magnetic lines through the specimen return, half through the upper and half through the lower part of the yoke. Since the cross section of the yoke is large in comparison with that of the specimen, its reluctance

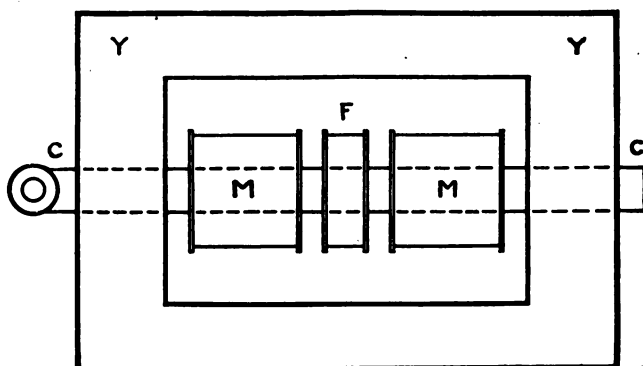


FIG. 59.—Hopkinson's bar and yoke.

may be neglected without appreciable error and the entire reluctance be considered as that part of the bar within the slot. The rod consists of two parts joined at a point a little to the right of  $F$ , one of which is clamped at  $C'$ , while the other may be drawn out by the ring at  $C$ . Springs are attached to the secondary coil  $F$ , generally called the "flip" coil, which runs between guides. While the bar is being subjected to the desired magnetizing field, the part  $C$  is quickly withdrawn, releasing  $F$  which is jerked suddenly out of the field, cutting the entire flux through the specimen. The induction  $B$ , for a given value of  $H$ , is computed in the following manner:

<sup>1</sup> EWING, *Magnetic Induction in Iron*, p. 67-92.  
SMITH, *Electrical Measurements*, chap. X.

- Let  $K$  = constant of the ballistic galvanometer  
 $n_f$  = turns on flip coil  
 $R$  = total resistance of secondary circuit  
 $i$  = instantaneous current in secondary circuit  
 $e$  = instantaneous E.M.F. induced in secondary circuit  
 $d_f$  = deflection of galvanometer  
 $\phi$  = total flux in specimen  
 $A_s$  = area of specimen  
 $N_m$  = magnetizing turns  
 $I_m$  = magnetizing current  
 $L_R$  = length of rod (length of slot in yoke)

The quantity  $Q$  of electricity, expressed in coulombs, discharged through the galvanometer is given by the expression

$$Q = Kd_f = \int idt \quad (26)$$

But

$$i = \frac{e}{R} = \frac{n_f}{10^8 R} \frac{d\phi}{dt} = \frac{n_f A_s}{10^8 R} \frac{dB}{dt} \quad (27)$$

Hence

$$Kd_f = \frac{n_f A_s}{10^8 R} \int_B^0 dB = \frac{n_f A_s B}{10^8 R} \quad (28)$$

Therefore

$$B = \frac{KR10^8}{n_f A_s} d_f. \quad (29)$$

The constant  $K$  of the ballistic galvanometer may be obtained by means of the standard solenoid described in Art. 26. Substituting the value of  $K$  from Eq. 36.

$$B = \frac{8\pi N n A}{10L n_f A_s} \cdot \frac{I}{d} \cdot d_f. \quad (30)$$

The field strength to which the specimen is subjected is given by the regular formula for the ring solenoid

$$H = \frac{4\pi N_m I_m}{10L_R} \quad (31)$$

**92. Experiment 14.** *Magnetization Curves by Hopkinson's Bar and Yoke.*—Connect the apparatus as shown in Fig. 60, where  $C$  and  $Y$  are the bar and yoke, respectively.  $G$  is a ballistic galvanometer and  $DE$  a standard solenoid for calibrating it. Since a considerable range of currents will be required, use two ammeters, one of range 0–15 amperes and the other, a milliammeter connected as shown, where  $S_1$  is a knife switch which should be left closed during all manipulations. Open  $S_1$  when it is

desired to read the millimeter and then only when the 0-15 ammeter indicates a current less than the full scale reading of the millimeter.  $S_2$  is also a knife switch. First compute, by means of eq. (31), the upper and lower limits of current required for field strengths ranging from 1 to 120 gilberts per centimeter.

Before proceeding to test a specimen, it must first be

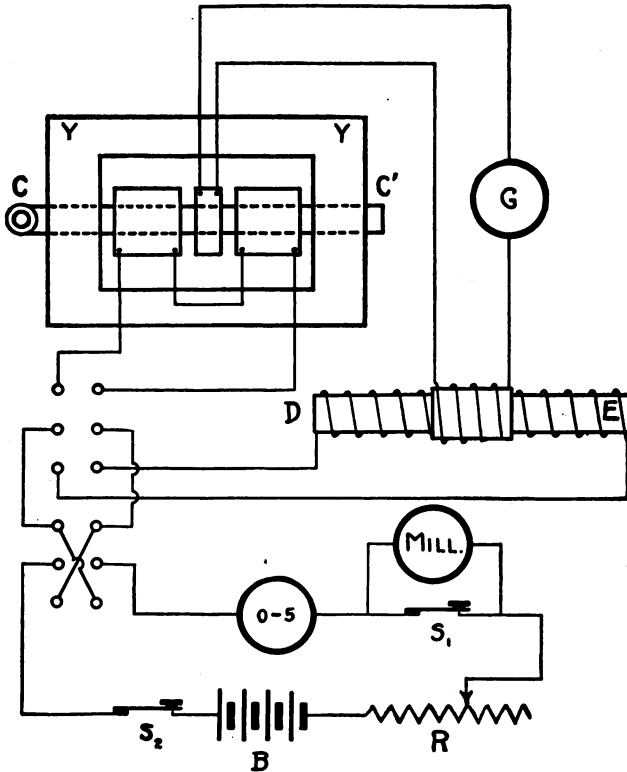


FIG. 60.—Connections for Hopkinson's bar and yoke.

demagnetized. This is done by applying a magnetizing current, somewhat greater than that required for the maximum test field, and reducing it by small steps, reversing the commutator at each step until a current barely readable on the millimeter has been reached. The rate of commutation should not exceed 20 reversals per minute. In this way, the specimen is magnetized first in one direction, and then in the other, each time to a less

extent, until finally all magnetism has disappeared. This should be done with the flip coil out of position or with the secondary circuit broken, to avoid damaging the galvanometer. To test for residual magnetism, flip the coil with no current in the magnetizing coils. A deflection not exceeding a millimeter should be obtained. Next, determine the constant of the galvanometer. To do this, set the double pole double throw switch so as to connect in circuit the primary of the standard solenoid, and, with a steady current of about two amperes flowing, reverse the commutator in such a direction as to cause the galvanometer to swing to high numbers. Make several determinations in this manner, using such values of primary current as will give deflections ranging from 2 to 14 centimeters. It is necessary here to reverse the primary current, not simply to make or break it, since that is the assumption on which the formula for the determination of the constant was derived. Use the average value of the ratio of current to deflection in eq. (30).

Everything is now ready for the test proper. Set the double pole double throw switch again so as to include the magnetizing coils and the rheostat so as to include the maximum resistance. Close the battery circuit and bring the current up to the smallest value computed above. Flip the coil and note the deflection of the galvanometer, which should swing in the same direction as used when determining its constant. Obtain, in this manner, about fifteen points on the magnetization curve, spaced more closely together in the lower part of the field strength range, where the curve rises steeply. Caution.—Points must be taken always with increasing field strength. Do not allow the current to rise too high and then decrease it. Obtain data for the magnetization curves for the samples of iron furnished. Check your galvanometer constant before and after taking each set.

**Report.**—1. Plot magnetization curves for the four samples using  $B$  as ordinates and  $H$  as abscissas.

2. Calculate the permeability for each value of  $H$  and, on a separate sheet, plot permeability as ordinates and field strength as abscissas for each sample.

3. For the maximum field strength, compute the magnetomotive force, total flux and reluctance of the magnetic circuit for each sample, expressing each quantity in its proper units. What is the relation between maxwells and gaussses?

**93. The Rowland Ring.**<sup>1</sup>—In the bar and yoke method described above, errors are introduced due to imperfect magnetic contact between the ends of the rods and the rod and yoke. This objection is overcome by making the specimen in the form of a ring, either turned true in the lathe from a solid block, or built up of sheet stampings. The magnetizing coil is then wound uni-

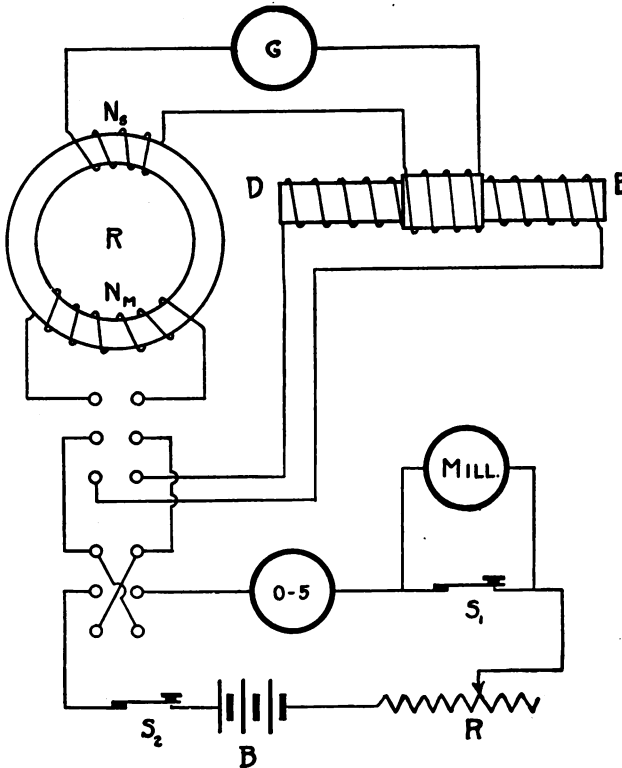


FIG. 61.—Connections for Rowland Ring Method.

formly over the entire magnetic circuit with the secondary wound over the primary. Since the turns on the inner side of the ring are closer together than on the outer, the former part of the ring will be subject to a greater magnetizing force than the latter, and therefore, the thickness of the ring should be small compared to its

<sup>1</sup> EWING, *Magnetic Induction in Iron*, chap. III.

SMITH, *Electrical Measurements*, chap. XII.

ROWLAND, *Phil. Mag.* vol. 46, 1873, p. 151.

diameter, the requisite area being obtained by increasing the height. As the magnetic circuit cannot be broken, it is impossible to obtain any measurement of the magnetic state of a given ring, so the method of observation is limited to measurements of changes of magnetic state produced by definite changes in magnetizing force.

A magnetization curve may be obtained by a series of reversals carried out in the following manner: Suppose the iron to be in an unmagnetized condition. Apply a weak magnetizing field. The induction rises a small amount along the desired magnetization curve. Reverse the magnetizing field. This causes the induction to change along the upper half of a small hysteresis cycle, taking on a value the negative of what it had before the reversal occurred. The change of induction, which is measured by the ballistic galvanometer, is then twice the total induction existing before the reversal. Now increase the field to a somewhat larger value, thus carrying the induction to a higher point on the curve. By again measuring the change of induction on reversal, twice the new value of induction is obtained, and so on for a series of points determining the entire magnetization curve. By this process, the iron is taken around a series of successively larger and larger hysteresis cycles, the apexes of whose corresponding curves lie upon the desired magnetization curve. The induction  $B$ , for a given value of  $H$ , is computed in the following manner:

Let  $K$  = constant of the ballistic galvanometer

$N_s$  = turns on secondary coil

$R$  = total resistance of secondary circuit

$e$  = instantaneous E.M.F. in secondary circuit

$i$  = instantaneous current in secondary circuit

$d_s$  = deflection of galvanometer

$\phi$  = total flux in ring

$A_R$  = cross sectional area of ring

$N_m$  = magnetizing current

$L_R$  = mean circumference of ring

The quantity of electricity  $Q$ , expressed in coulombs, discharged through the galvanometer is given by the expression

$$Q = Kd_s = \int idt \quad (32)$$

But

$$i = \frac{e}{R} = \frac{N_s d\phi}{10^8 R dt} = \frac{N_s A_R}{10^8 R} \frac{dB}{dt} \quad (33)$$



Substituting

$$Kd_s = \frac{N_s A_R}{10^8 R} \int_{-B}^{+B} dB = \frac{2N_s A_R B}{10^8 R} \quad (34)$$

$$B = \frac{KR10^8}{2N_s A_R} d_s. \quad (35)$$

The constant  $K$  of the ballistic galvanometer may be obtained by means of the standard solenoid method, as described in Art. 26. Substituting the value of  $K$  from eq. (36), we have

$$\left( H = \frac{4\pi N n A}{10 L N_s A_R} \frac{I}{d} \cdot d_s \right) \quad (36)$$

The field strength to which the specimen is subjected is given by the formula

$$H = \frac{4\pi N_m I_m}{10 L_R} \quad (37)$$

**94. Experiment 15.** *Magnetization Curves by the Rowland Ring Method.*—Connect the apparatus as shown in Fig. 61.  $R$  is the ring specimen under test, and  $N_m$  and  $N_s$  the primary and secondary windings, respectively.  $G$  is a ballistic galvanometer, and  $DE$  a standard solenoid for calibrating it. Since a considerable range of current will be required, use two ammeters, one of range 0–15 amperes and the other a millammeter, connected as shown, where  $S_1$  is a knife switch which should be left closed during all manipulations. Open  $S_1$  when it is desired to read the millammeter and then only when the 0–15 ammeter indicates a current less than the full scale reading of the millammeter. First, compute by means of eq. (37), the upper and lower fields from .5 to 100 gilberts per centimeter.

Before proceeding to test a specimen, it must first be demagnetized. This is done by applying a magnetizing current somewhat greater than that required for the maximum test field, and reducing it by small steps, reversing the commutator at each step until a current barely readable on the millammeter has been reached. The rate of commutation should not exceed 20 reversals per minute. This should be done with the secondary circuit broken to avoid damaging the galvanometer. Next determine the constant of the galvanometer. To do this, set the double pole double throw switch so as to connect in circuit the primary of the standard solenoid and with a steady current of about 2 amperes, reverse the commutator in such a direction as to cause the galvanometer to swing to high numbers. Make several determinations in this

manner, using such values of current as will give galvanometer deflections ranging from 2 to 14 centimeters. It is necessary here to reverse the primary current, not simply to make or break it, since that is the assumption on which the formula for the galvanometer constant was derived. Use the average value of the ratio of current to deflection in eq. (36).

Everything is now ready for the test proper. Set the double pole double throw switch again so as to include the primary on the ring, and the rheostat  $R$  so as to include the maximum resistance. Close the battery circuit and bring the current up to the smallest value computed above. Bring the galvanometer to rest, reverse the primary current, and note the galvanometer deflection. Now bring the commutator back to its original position, increase the current to a slightly greater value, and read the galvanometer deflection again on reversal. Obtain, in this manner, about 15 points on the magnetization curve, spaced more closely together on the lower part of the field strength range where the rise is rapid. Caution.—Succeeding points must always be taken with increasing field strength. Do not allow the current to rise too high and then decrease it. Obtain data for the magnetization curves for two samples of iron. Check your galvanometer constant before and after taking each set.

**Report.**—1. Plot magnetization curves for the two samples, using  $B$  as ordinates and  $H$  as abscissas.

2. Compute the permeability for each value of  $H$ , and, on a separate sheet, plot permeabilities as ordinates and field strengths as abscissas.

3. For the maximum field strength, compute the magnetomotive force, total flux, and reluctance of the magnetic circuit for each sample, expressing each quantity in its proper units. What is the relation between maxwells and gaussses?

**95. Experiment 16.** *Hysteresis Curves by the Rowland Ring Method.*<sup>1</sup>—Connect the apparatus as indicated in Fig. 61, and observe the precautions regarding use of ammeters, switches, rheostats, etc., indicated in Exp. 15. Instead of starting with zero field and making changes of induction which are symmetrical with respect to the origin, as in the case of the magnetization curve by reversals, start here with the maximum field and make changes of induction by passing first to the retentivity

<sup>1</sup> EWING, *Magnetic Induction in Iron*, chap. V.

TAYLOR, *Physical Review*, vol. 23, p. 95.

point and then away from it. All measurements of induction are accordingly to be made with respect to the retentivity point, and we will, for the moment, regard this point as the origin from which the upper half of the hysteresis curve is to be plotted. The method will be made clear by reference to Fig. 58. Apply first the maximum field, giving  $+B_{\max}$  on the curve. Now reduce the field to zero. The induction changes along the upper part of the curve, and goes to the retentivity point, the actual change being equal to  $B_1$ . Now apply the field  $-H_{\max}$ . The induction changes along the curve from  $B_R$  to  $B_{\max}$ , the actual change in induction being  $B_2$ .  $B_1$  and  $B_2$  are thus located on the curve with  $B_R$  as the origin. An intermediate point, such as  $B_3$  may be obtained by applying again the field  $+H_{\max}$  and slowly reducing to  $+H_3$  without breaking the magnetizing current. If the magnetizing current is now broken, the induction again returns to  $B_R$  and the change, which is measured by the galvanometer deflection, is  $B_3$ . This locates  $B_3$  with respect to  $B_R$ . The corresponding point,  $B_4$  may be obtained by applying the field  $-H_3$  and observing the throw of the galvanometer. In a similar manner, a series of points, corresponding to pairs of positive and negative values of  $H$ , may be obtained and the upper half of the curve plotted with respect to  $B_R$ .

The actual manipulation of switches is as follows: Obtain the constant of the galvanometer as explained in Exp. 14. With the galvanometer circuit broken, set the rheostat to give the maximum magnetizing current. Reverse this current several times through the primary coil of the ring to remove the effects of previous magnetization, and thus make sure that the iron will follow the cycle desired. With maximum current flowing, close the secondary circuit and bring the galvanometer to rest. Break the primary circuit by the switch  $S_2$  and observe the throw of the galvanometer which measures  $B_1$ . Bring the galvanometer again to rest with the secondary circuit closed. Reverse the commutator. Close  $S_2$  and note the deflection of the galvanometer which measures  $B_2$ . Break the secondary circuit, reverse the commutator, bringing the induction back to  $+B_{\max}$ . Reduce the current, without breaking the circuit, to give a value  $+H_3$ . Close the secondary circuit and bring the galvanometer to rest. Break the primary by means of  $S_2$  and the throw of the galvanometer measures  $B_3$ . Bring the galvanometer to rest, reverse the commutator, and close  $S_2$ . The deflection of the galvanome-

ter measures  $B_4$ , the induction corresponding to  $-H_3$ . The other points on the curve are obtained in pairs in the same manner. It is important to notice that before each pair of observations is taken the induction must first be returned to  $+B_{\max}$ , otherwise a different cycle will be carried out for each pair. Obtain in this way at least ten pairs of values for  $B$ , using field strengths ranging from .5 to 30 gilberts per centimeter. It will assist the calculation if deflections corresponding to positive and negative fields are recorded in separate columns. Two samples are to be tested.

The calculation of the values of  $B$  is carried out by the same formula as used in Exp. 4, except here we wish the total change in induction instead of half of it as was the case there. Accordingly the limits of integration in eq. (33) are  $O$  and  $B$  instead of  $+B$  and  $-B$ , giving as our final formula.

$$B = \frac{8\pi NnA}{10LN_s A_r} \cdot \frac{I}{d} \cdot d_s. \quad (38)$$

Before plotting the curve, the origin should be changed from  $B_R$  to  $O$ . This is accomplished by adding  $B_R$  to all values of induction corresponding to positive fields and subtracting all values of induction corresponding to negative fields from  $B_R$ .  $B_R$  is determined from the relation

$$B_R = B_{\max} - B_1 = \frac{B_1 + B_2}{2} - B_1 \quad (39)$$

The lower half of the curve, being symmetrical with the upper, is plotted from these same data, merely changing the signs of all values of  $B$ .

**Report.**—1. Plot the hysteresis curves for the two samples of iron, making the plots as large as convenient.

2. Measure the area of the curves by means of a planimeter, and determine the energy loss per cycle per cubic centimeter. Since it is not convenient to plot  $B$  and  $H$  to the same scale, if unit length along the  $B$  axis represents  $b$  gaussess, and unit length along the  $H$  axis,  $h$  gilberts per centimeter, unit area will represent  $\frac{bh}{4\pi}$  ergs per cc.

3. Compute the Steinmetz coefficient for each sample.

## CHAPTER IX

### SELF AND MUTUAL INDUCTANCE<sup>1</sup>

**96. General Principles.**—Whenever a change occurs in the number of magnetic lines linking any electrical circuit, there is induced within the circuit an electromotive force, which, if the circuit is closed, will cause a current to flow. It makes no difference by what means this change is produced; whether magnets in the neighborhood are moved, currents in adjacent circuits changed, or the current in the circuit itself varied, the nature of the induced electromotive force is the same. The direction of the induced electromotive force is given by a simple rule known as Lenz's law, which may be stated as follows: Whenever a change occurs in an electromagnetic system, the direction of the induced electromotive force is such that the magnetic action of its current opposes the change. For example, if the north pole of a magnet is moved toward a closed helix, the induced current flows in such a direction as to produce a north pole on the end toward the magnet, thus tending to repel it, and vice versa, when it is withdrawn. The magnitude of this induced E.M.F. per turn is given by the expression

$$e = \frac{d\phi}{dt} \quad (1)$$

where  $\phi$  is the total flux passing through the turn at any instant.

If the change of flux through the coil is produced, not by moving toward it a magnetic pole but by changing the current in another coil placed near it, the phenomenon of the induced E.M.F. is called mutual induction. The coil which is producing the change of flux is called the primary and that in which the E.M.F. is induced, the secondary. If the current in the primary of two coaxial coils is rising, let us say in the clockwise direction, on looking along the axis, an application of Lenz's law shows that the current in the secondary is flowing counter-clockwise, while if the current in the primary is decreasing, the secondary current

<sup>1</sup> DUFF, A Textbook of Physics, p. 445.

REED and GUTHE, College Physics, p. 365. STARLING, Electricity and Magnetism, chap. XI.

is in the same direction as the primary. Since the flux through the secondary at any instant is proportional to the current in the primary, we may write for the total E.M.F. in the secondary

$$e = M \frac{di}{dt} \quad (2)$$

where  $i$  is the primary current and  $M$  a constant depending upon the area of the two coils, their number of turns, distance apart, the permeability of the medium surrounding them, etc.  $M$  is called the coefficient of mutual inductance, the unit of which has been named the henry.

*Definition.*—Two coils have one henry of mutual inductance, if, when the primary current is changing at the rate of one ampere per second, the induced E.M.F. in the secondary is one volt.

When the current through any coil is changing, there is a change of flux, not only through any coil in the neighborhood, but also through the coil itself, causing an induced E.M.F. within it. This phenomenon is known as Self Induction. The direction of this E.M.F., considering the coil to be its own secondary, is determined by Lenz's law, as given above; i.e., when the current is rising, the induced E.M.F. is in such a direction as to oppose the current, and when the current is falling, it tends to maintain it. The induced E.M.F. always opposes any change in the current and is called a counter E.M.F. Since the flux through the coil at any instant is proportional to the current, the induced counter E.M.F. is given by

$$e = L \frac{di}{dt} \quad (3)$$

where  $i$  is the current at any instant and  $L$  a constant depending upon the number of turns in the coil, its area, shape, permeability of the surrounding medium, etc.  $L$  is called the coefficient of self inductance and the unit is the henry.

*Definition.*—A coil has one henry of self inductance, if, when the current through it is changing at the rate of one ampere per second, the induced counter E.M.F. is one volt.

Since the henry is a relatively large unit, it is customary in expressing the inductance of ordinary coils, to use a unit only one-thousandth as large, called the millihenry. Variable standards of self and mutual inductance are made by mounting two coils in such a way that their relative positions, and hence their inductive interactions may be changed. If the coils are

connected in circuit separately, one being used as the primary and the other as the secondary, a calibration curve may be made showing the mutual inductance between them for various positions. If, however, they are connected in series and used as a single coil, a variable self inductance is obtained, since the resultant self inductance of two coils, with mutual inductance between them, is given by the formula

$$L = L_1 + L_2 \pm 2M \tag{4}$$

where  $L_1$  and  $L_2$  are the separate coefficients of self inductance. If the coils are mounted in such a manner that advantage may be taken of both positive and negative values of  $M$ , variable self inductances of considerable range may be obtained. Two forms of variable standard are in common use. Figure 62 represents the Ayerton and Perry variable inductor which consists of two coils mounted vertically one of which is fixed and the other movable. The coils are wound on spherical surfaces, and the inner one rotates about a vertical axis. When the planes of the coils are parallel, the resultant self inductance is a maximum or a minimum, according as the mutual is positive or negative. When

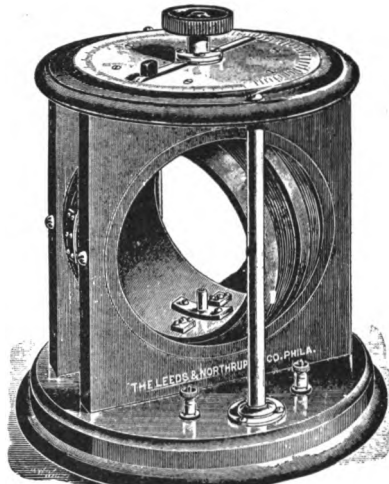


FIG. 62.—Ayerton and Perry variable inductor.

the coils stand at right angles to each other, the resultant self inductance is the sum of the self inductances of the two coils, since the mutual is zero for this position. For other positions of the movable coil, intermediate values are obtained. The relation between resultant self inductance and angular position is nearly linear. Two pointers on the top read, one the angular position of the coil in degrees, the other the self inductance in millihenries. The coils are joined in series by a flexible conductor. Separate binding posts for the coils are usually provided, and, when used independently, the instrument serves as a variable standard of mutual inductance also.

The other instrument is known as the Brook's inductor and is illustrated in Fig. 63. It consists of six coils mounted in pairs in three hard rubber discs, placed one above the other in a horizontal position. The upper and lower disks are fixed and the middle one rotates between them. If the coils are joined in series and connected so that their fields on one side are all directed upward, and on the other side downward, the resultant self inductance is a maximum; but if the middle disk is turned through  $180^\circ$ , the mutual inductance between the fixed and movable coils will neutralize the self inductance and the resultant will be

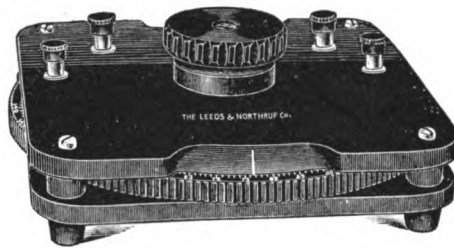


FIG. 63.—Brook's variable inductor.

a minimum. By properly shaping the coils, an approximately linear relation is obtained between angular position and inductance. Separate binding posts enable the coils to be used independently giving also a variable standard of mutual inductance. The instrument is provided with two scales which read respectively self- and mutual inductance in millihenries.

**97. Comparison of Inductances.**<sup>1</sup>—Two coefficients of self inductance may be compared by a bridge method in which the two coils, whose inductances are to be compared, form two arms of the ordinary Wheatstone bridge. Let  $L_1$  and  $L_2$  of Fig. 64 be two inductances having resistances  $R_1$  and  $R_2$ , respectively, and  $R_3$  and  $R_4$  be two non-inductive resistances, and let the bridge be balanced for steady currents, as explained in Art. 31, the condition for which is

$$R_1R_4 = R_2R_3$$

This condition signifies that when the currents,  $i_1$  and  $i_2$  are constant, the potentials at  $C$  and  $D$  are equal, but less than the

<sup>1</sup> CARHART and PATTERSON, *Electrical Measurements*, p. 255.

SMITH, *Electrical Measurements*, p. 197–203.

MAXWELL'S, *Elect. and Mag.*, vol. 2, p. 367.



potential at *A*. If the battery key  $K_1$  is opened, the current ceases to flow and the potentials at *C* and *D* become equal to that at *A*. When  $K_1$  is again closed, the potentials at *C* and *D* on account of the counter E.M.F.'s of self induction in  $L_1$  and  $L_2$  will not necessarily rise at the same rate, although they will come to the same final values. Hence, there may be a short interval of time during which a difference of potential exists between *C* and *D* giving a deflection of the galvanometer if  $K_2$  is closed. By properly adjusting  $L_1$  and  $L_2$  it is possible to cause

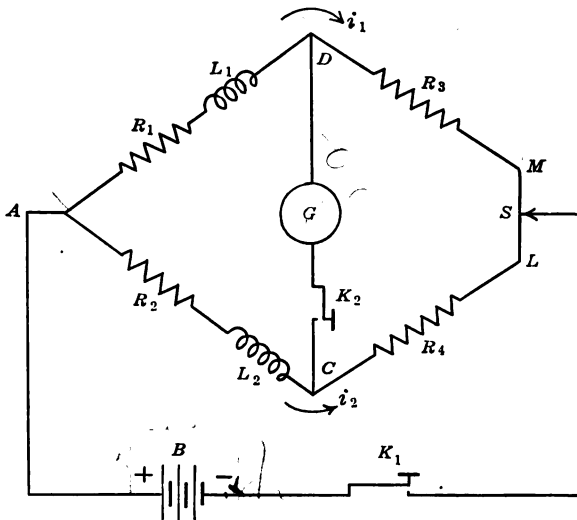


FIG. 64.—Bridge method for self-inductance.

the potentials at *C* and *D* to rise at the same rate when the bridge is balanced for both steady and varying currents. The conditions for such a balance is obtained in the ordinary way, except that the equations must include terms representing the fall of potential due to the counter E.M.F. Equating the difference of potential at any instant between *A* and *D* to that between *A* and *C*, also that between *D* and *S*, to that between *C* and *S*, we have

$$R_1 i_1 + L_1 \frac{di_1}{dt} = R_2 i_2 + L_2 \frac{di_2}{dt} \tag{5}$$

and

$$R_3 i_1 = R_4 i_2 \tag{6}$$

whence

$$R_3 \frac{di_1}{dt} = R_4 \frac{di_2}{dt} \quad (7)$$

Eliminating  $i_2$  and  $\frac{di_2}{dt}$ , we have

$$R_4 R_1 i_1 + R_4 L_1 \frac{di_1}{dt} = R_2 R_3 i_1 + R_3 L_2 \frac{di_1}{dt}. \quad (8)$$

Since  $R_1 R_4 = R_2 R_3$ , the condition for steady current balance, the condition for the varying current or inductive balance is

$$L_1 R_4 = L_2 R_3 \quad (9)$$

or

$$\frac{L_1}{L_2} = \frac{R_3}{R_4} \quad (10)$$

**98. Experiment 17. Comparison of Two Coefficients of Self Inductance by the Bridge Method.**—Connect the apparatus as shown in Fig. 64, where  $L_1$  is the unknown inductance and  $L_2$  a variable standard.  $R_3$  and  $R_4$  may be two ordinary resistance boxes with non-inductively wound coils connected with a slide wire  $LM$  for accurate balancing.  $K_1$  and  $K_2$  should be two ordinary press keys. First, using for  $B$  a battery of about two volts, obtain a steady current balance by closing  $K_1$  first, and  $K_2$  after the current has had time to rise to its final value. Try to keep  $R_3$  and  $R_4$  between one hundred and three hundred ohms. For the inductive balance, use a battery of 20 volts. Close  $K_2$  first and then lightly tap  $K_1$ , never leaving it closed for more than an instant, since the large currents would cause too great a heating of the resistances. The motion of the galvanometer in this case will be a sudden "kick" not a steady deflection. Adjust  $L_2$  until this kick has disappeared. Read the value of  $L_2$  and compute the value of  $L_1$  from eq. (10). The unknown to be determined consists of a spool with two independent windings. Determine the inductance of each separately, then join them in series, and determine the resultant self-inductances with their mutual inductances aiding and opposing, making in all four measurements.

Note.—It may happen that the balance point lies beyond the range of the variable standard, making an inductive balance impossible. When this happens, the ratio  $R_3$  to  $R_4$  must be changed so as to bring the balance point within the required range. Since a steady current balance must always be obtained first, this requires the insertion of a small non-inductive resistance in series with either  $R_1$  or  $R_2$  as the case may demand. For ex-

ample, suppose the inductive kick of the galvanometer decreases as  $L_2$  is increased to its maximum, but cannot be made zero or reversed. The combination of the two balance conditions gives

$$\frac{L_1}{L_2} = \frac{R_3}{R_4} = \frac{R_1}{R_2} \tag{11}$$

If, then, an appropriate resistance is connected in series with  $R_1$  the new steady current balance condition will give a larger ratio of  $R_3$  to  $R_4$  thus making the inductive balance possible. If, on the other hand,  $L_2$  cannot be made small enough, the additional resistance must be placed in series with  $R_2$ .

**Report.**—1. Tabulate your data for the determination of the four inductances as indicated.

2. From the formula  $L = L_1 + L_2 + 2M$ , compute  $M$  from the cases where it is aiding and opposing the self inductance. The agreement of these two values gives a check on the accuracy of your work.

3. How are coils wound so as to be non-inductive?

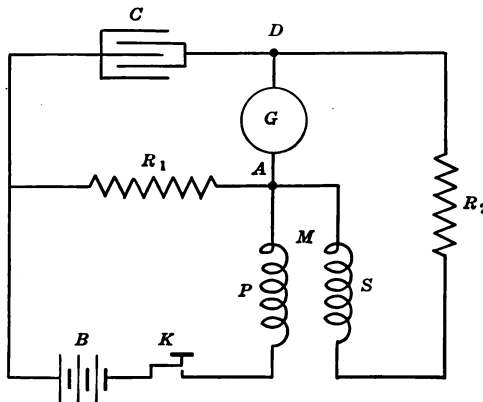


FIG. 65.—Mutual inductance by Carey-Foster method.

**99. Measurement of Mutual Inductances.**<sup>1</sup>—The mutual inductance of two coils may be measured in terms of capacity and resistance by means of a method due to Carey-Foster, in which the quantity of electricity induced in the secondary is balanced against a known charge from a standard condenser. The connections are shown in Fig. 65, where  $P$  and  $S$  are the

<sup>1</sup> CAREY-FOSTER, *Phil. Mag.*, vo. 23, p. 121.

CARHART and PATTERSON, *Electrical Measurements*, p. 268.

SMITH, *Electrical Measurements*, p. 217.

primary and secondary coils of the mutual inductance to be measured,  $C$  a standard condenser, and  $G$  a ballistic galvanometer. The primary circuit is represented by the path  $BPAR_1$ , while the secondary is  $SR_2DA$  including the galvanometer  $G$ . It will be noted that the galvanometer is also included in circuit  $DCR_1A$  containing a standard condenser. When the primary circuit is closed the galvanometer will be traversed by two distinct quantities of electricity: (1) The quantity induced in the secondary coil, and (2) the charge entering the condenser, both of which may easily be computed. If these two quantities are equal and pass through the galvanometer in opposite directions, no deflection will result, which is the balance condition sought.

The quantity  $Q_1$  induced in the secondary coil is the time integral of the secondary current, during the interval required for the primary to rise from zero to its final value  $I$ .

That is,

$$Q_1 = \int idt = \frac{M}{R} \int \frac{di}{dt} dt \quad (12)$$

$$= \frac{M}{R} \int_0^I di = \frac{MI}{R} \quad (13)$$

where  $R$  is the effective resistance of the secondary circuit. The quantity  $Q_2$  of electricity passing through the galvanometer to charge the condenser is given by

$$Q_2 = CV = CR_1I \quad (14)$$

where  $V = R_1I$  is the fall of potential across  $R_1$  which is charging the condenser. Equating,

$$\frac{MI}{R} = CR_1I, \quad (15)$$

or

$$M = CR_1R. \quad (16)$$

Since, at the point of balance, there is no current through the galvanometer, and consequently no fall of potential across it, the effective resistance  $R$  of the secondary circuit includes only  $R_2$  and  $S$ . The final formula then becomes

$$M = CR_1(R_2 + S) \quad (17)$$

If  $C$  is expressed in farads, and the resistances in ohms,  $M$  will be given in henries.

**100. Experiment 18. Mutual Inductance by the Carey-Foster Method.**—Connect the apparatus as shown in Fig. 65, where  $PS$

is a variable mutual inductance whose calibration curve is to be obtained,  $C$  a subdivided standard condenser,  $G$  a ballistic galvanometer of long period, and  $B$  a storage battery of 20 volts. It is necessary that the four wires indicated at  $A$  should actually meet at a common point, so a connector should be used. Since a large voltage is connected directly across  $R_1$  there is danger of burning it, so compute the minimum resistance which may be used, allowing a maximum power consumption of 4 watts per coil. To make sure that the discharges through the galvanometer oppose one another and are of the same order of magnitude, try them first separately; that is, break the circuit at  $C$ , make and break the primary circuit and note the direction of the galvanometer deflection at the make, due to the induced current in the secondary. Now close the circuit again at  $C$ , breaking the secondary at  $R_2$ , and note the deflection at make, which is now due to the charge entering the condenser. If the deflection is in the same direction as before, reverse the connections on either the primary or secondary coil. Close the circuit at  $R_2$  and obtain a balance varying  $R_1$ ,  $R_2$ , and  $C$ . The resistance of the secondary coil may be obtained by means of a post-office box.

**Report.**—1. Plot mutual inductance in millihenries, as ordinates, and positions of coil as abscissas.

2. How would your results be affected if you had interchanged primary and secondary coils? Explain.

## CHAPTER X

### ELEMENTARY TRANSIENT PHENOMENA<sup>1</sup>

**101. Time Constant, Circuit Having Resistance and Inductance.**—When an E.M.F. is suddenly impressed on a circuit containing resistance only, the current rises instantly to a definite value determined by Ohm's law. If, however, the circuit contains inductance as well as resistance, this is not the case, for while the current is being established, it produces within the coil a magnetic flux which links the turns of the coil. Whenever a change occurs in the flux through a coil there is induced within it an E.M.F. in such a direction as to oppose the change which produced it. From the definition of self inductance, the value of this counter E.M.F. is  $L\frac{di}{dt}$  where  $L$  is the coefficient of self inductance. It is thus seen that the impressed E.M.F. is opposed

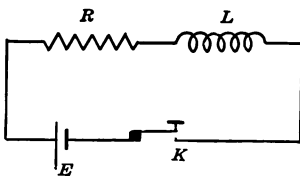


FIG. 66.—Circuit containing resistance and inductance.

by two counter E.M.F.'s; one due to the current flowing through the resistance and the other due to the rising current in the coil. Such a circuit is represented in Fig. 66, where the resistance  $R$  and the inductance  $L$  are shown separately, although they may co-exist in the coil. Let the value of the current,  $t$  seconds after closing the key, be  $i$ . Then by Ohm's law, we have

$$E = Ri + L\frac{di}{dt} \quad (1)$$

This is a differential equation and can not be solved by the ordinary rules of algebra. Dividing through by  $R$  and letting  $I = \frac{E}{R}$  be the final value of the current, we have

$$I = i + \frac{Ldi}{Rdt} \quad (2)$$

<sup>1</sup> BEDELL and CREHORE, *Alternating Currents*  
 PIERCE, *Electric Oscillations and Electric Waves*.  
 STEINMETZ, *Transient Phenomena*.

Separating the variables, we obtain

$$\frac{di}{I - i} = \frac{R}{L} dt \tag{3}$$

Integration of both sides gives

$$-\log (I - i) = \frac{R}{L} t + C \tag{4}$$

where  $C$  is an arbitrary constant whose value may be obtained by substituting corresponding known values for  $i$  and  $t$ . Counting time from the instant the key is closed, when  $t = 0, i = 0$ , and these quantities when substituted in eq. (4) give  $C = -\log I$ . Hence eq. (4) becomes, on replacing  $C$  by its value and rearranging,

$$\log \frac{(I - i)}{I} = -\frac{R}{L} t \tag{5}$$

Taking the antilogarithm of both sides,

$$\frac{I - i}{I} = e^{-\frac{R}{L} t} \tag{6}$$

where  $e$  is the base of the Naperian logarithms. Solving for  $i$ , we have

$$i = I \left( 1 - e^{-\frac{R}{L} t} \right) \tag{7}$$

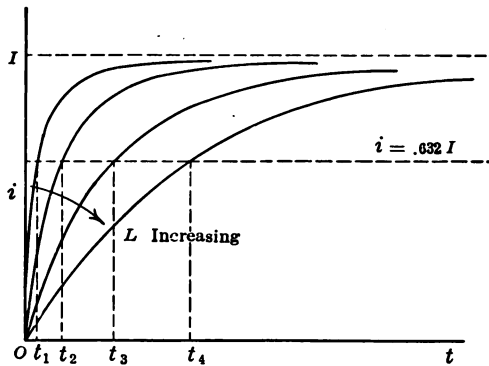


FIG. 67.—Growth of current in a circuit containing resistance and inductance.

The graph of this equation for a series of values of  $L$  with constant  $R$  and  $E$  is shown in Fig. 67. It is seen that when  $L = 0$  the last term of eq. (7) vanishes and the current rises immediately to its final value; but as  $L$  is made larger a longer time is required for it to reach a given fraction of its final magnitude. It is obvious that inductively wound coils might be classified according to the time required for the current to reach a certain specified fraction

of its final values under a constant impressed E.M.F. The most suitable fraction to choose is arrived at in the following way.

If, in eq. (7),  $t = \frac{L}{R}$ , there results

$$i = I\left(1 - \frac{1}{e}\right) = .632 I$$

The quantity  $\frac{L}{R}$  is called the "Time Constant" for the coil and is defined as the time required for the current to reach .632 of its final value under the action of a constant E.M.F. The values  $t_1, t_2, t_3$ , etc., in Fig. 67 represent the time constants for the various values of  $L$ .

**102. Circuit Having Resistance and Capacitance.**—A case

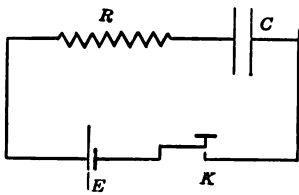


FIG. 68.—Circuit containing resistance and capacitance in series.

quite similar to the one discussed above is that in which an E.M.F. is suddenly impressed upon a circuit containing resistance and capacitance in series. Such an arrangement is shown in Fig. 68. As soon as the key is closed, a current flows through  $R$  and a charge begins to accumulate in  $C$ . This charge at once produces a counter E.M.F., which, added to that due to the current through  $R$ , balances the impressed E.M.F.

The potential difference across the condenser is  $\frac{Q}{C}$  or  $\frac{1}{C} \int idt$ . Accordingly, we may write

$$E = Ri + \frac{1}{C} \int idt. \quad (8)$$

It is more convenient to solve this equation in terms of the instantaneous charge  $q$  in the condenser than of the current through the resistance. Remembering that  $i = \frac{dq}{dt}$  we have, on substitution in eq. (8),

$$E = R \frac{dq}{dt} + \frac{q}{C} \quad (9)$$

Multiplying through by  $C$  and putting  $CE = Q$ , the final charge in the condenser, eq. (9) becomes, on separating the variables,

$$\frac{dq}{Q - q} = \frac{dt}{RC} \quad (10)$$



Integrating both sides of eq. (10), we have

$$-\log(Q - q) = \frac{t}{RC} + K \tag{11}$$

As before,  $K$  is an arbitrary constant of integration which may be evaluated by substituting known values of  $q$  and  $t$  in eq. (11). Counting time from the instant of closing the key, we have, when  $t = 0, q = 0$ . Substituting in eq. (11)

$$K = -\log Q$$

Replacing  $K$  by its value, and rearranging terms, eq. (11) becomes

$$\log \frac{(Q - q)}{Q} = -\frac{t}{RC} \tag{12}$$

Taking the antilogarithm of both sides, we have

$$\frac{Q - q}{Q} = e^{-\frac{t}{RC}} \tag{13}$$

Solving for  $q$ , there results

$$q = Q\left(1 - e^{-\frac{t}{RC}}\right) \tag{14}$$

This equation is analogous to eq. (7) of the previous article and its graph is shown in Fig. 69, for several values of  $R$  with constant

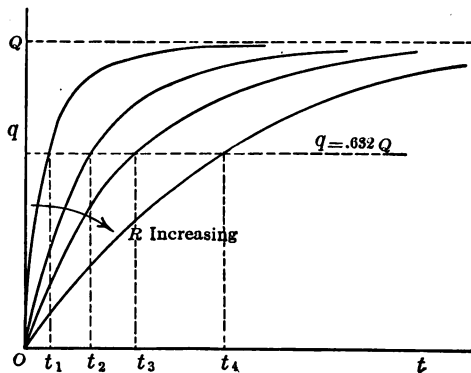


FIG. 69.—Growth of charge for a circuit containing resistance and capacitance.

$E$  and  $C$ . If  $R = 0$ , the condenser becomes charged instantly to its final value  $Q$ , but when a series resistance is included, a definite time is required for the condenser to become charged. Such circuits may be classified according to the time required for the charge to reach a specified fraction of its final value. As before this fraction is arrived at by putting  $t = RC$ .

Eq. (14) then becomes

$$q = Q\left(1 - \frac{1}{e}\right) = .632 Q.$$

The quantity  $RC$  is called the time constant for a circuit containing resistance and capacitance, and is defined as the time required for the charge to reach .632 of its final value. These times are shown for the successive values of  $R$  by  $t_1, t_2, t_3$ , etc., in the figure. The time constant is an important concept in the study of reactive circuits and will be referred to frequently in this text in the discussions to follow.

**103. Circuit Containing Resistance, Inductance and Capacitance. Discharge of a Condenser.**—To describe some of the phenomena peculiar to a circuit containing resistance, inductance

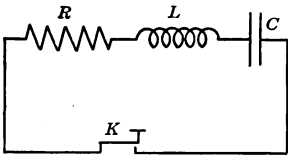


FIG. 70.—Circuit containing resistance, inductance, and capacitance.

and capacitance, it will be supposed that the parts are connected in series as shown in Fig. 70, and that the condenser has been charged by appropriate means. Suppose further that the key has been closed and that it is discharging; also that the instantaneous current is  $i$  and the charge in the condenser is  $q$ . Since

no external E.M.F. is acting, the sum of the differences of potential across the three elements of the circuit must be zero at all times. Accordingly,

$$L \frac{di}{dt} + Ri + \frac{1}{C} \int i dt = 0. \quad (14)$$

Differentiating and dividing through by  $L$  we have

$$\frac{d^2i}{dt^2} + \frac{R}{L} \frac{di}{dt} + \frac{1}{LC} i = 0. \quad (15)$$

Since  $i = \frac{dq}{dt}$ , eq. (14) may also be written

$$\frac{d^2q}{dt^2} + \frac{R}{L} \frac{dq}{dt} + \frac{1}{LC} q = 0. \quad (16)$$

eqs. (15) and (16) are sufficient to completely describe a circuit of this character. Since they are identical, only one of them, e.g., (15), will be discussed.

This is a linear differential equation of the second order with constant coefficients and may be solved in the following manner: Let

$$i = ke^{mt} \quad (17)$$

where  $k$  is an arbitrary constant depending upon the boundary conditions and  $m$ , another constant, depending upon the coefficients of the original differential equation. Differentiating eq. (17) twice and substituting in eq. (15), there results

$$m^2 + \frac{R}{L}m + \frac{1}{LC} = 0. \tag{18}$$

This equation gives the values that must be assigned to  $m$  in order that eq. (17) may be the solution of eq. (15). Solving,

$$m = \frac{-RC \pm \sqrt{R^2C^2 - 4LC}}{2LC} \tag{19}$$

It is thus seen that there are two values of  $m$  which will make eq. (17) a solution of eq. (15). These give what are known as "particular solutions" and the "complete solution" is obtained by adding them together. Accordingly,

$$i = k_1 e^{-\left[\frac{RC - \sqrt{R^2C^2 - 4LC}}{2LC}\right]t} + k_2 e^{-\left[\frac{RC + \sqrt{R^2C^2 - 4LC}}{2LC}\right]t} \tag{20}$$

The solution for  $q$  is identical except that different arbitrary constants will appear. Call them  $k_3$  and  $k_4$ . It is to be noted that the coefficient of  $t$  in the exponential term contains a radical, the quantity under which may be positive, zero, or negative according to the relative values of  $R$ ,  $L$ , and  $C$ . The theory of differential equations shows that the character of the solutions under these circumstances is quite different, and that we have three distinct cases to consider.

Case I.  $R^2C^2 > 4LC$ . *Non-oscillatory Discharge*.—For simplicity, let

$$\tau_1 = \frac{2LC}{RC - \sqrt{R^2C^2 - 4LC}} \text{ and } \tau_2 = \frac{2LC}{RC + \sqrt{R^2C^2 - 4LC}} \tag{21}$$

The solutions of eqs. (15) and (16) may then be written

$$i = k_1 e^{-\frac{t}{\tau_1}} + k_2 e^{-\frac{t}{\tau_2}} \tag{22}$$

$$q = k_3 e^{-\frac{t}{\tau_1}} + k_4 e^{-\frac{t}{\tau_2}} \tag{23}$$

$\tau_1$  and  $\tau_2$  are thus seen to be time constants and it is to be noted that when both inductance and capacity are present, the circuit possesses two time constants instead of one as in the cases previously considered. The arbitrary constants  $k_1$ ,  $k_2$ ,  $k_3$ ,  $k_4$  may be determined in the following way. If time is reckoned from the instant the key is closed, then when

$$t = 0, i = 0, q = Q \tag{24}$$

Substituting these values in eqs. (22) and (23) there results

$$0 = k_1 + k_2 \quad Q = k_3 + k_4 \quad (25)$$

Differentiating eq. (23)

$$i = \frac{dq}{dt} = -\frac{k_3}{\tau_1} e^{-\frac{t}{\tau_1}} - \frac{k_4}{\tau_2} e^{-\frac{t}{\tau_2}} \quad (26)$$

Comparing coefficients in eqs. (22) and (26) we have

$$k_1 = -\frac{k_3}{\tau_1} \text{ and } k_2 = -\frac{k_4}{\tau_2} \quad (27)$$

Substituting the values of  $k_3$  and  $k_4$  from eqs. (27) in (25) and eliminating, the following values are obtained:

$$\begin{aligned} k_1 &= \frac{Q}{\tau_2 - \tau_1} & k_2 &= \frac{Q}{\tau_1 - \tau_2} \\ k_3 &= \frac{Q\tau_1}{\tau_1 - \tau_2} & k_4 &= \frac{Q\tau_2}{\tau_2 - \tau_1} \end{aligned} \quad (28)$$

Substituting these values in eqs. (22) and (23) we have

$$i = \frac{Q}{\tau_2 - \tau_1} \left[ e^{-\frac{t}{\tau_1}} - e^{-\frac{t}{\tau_2}} \right] \quad (29)$$

$$q = \frac{Q}{\tau_1 - \tau_2} \left[ \tau_1 e^{-\frac{t}{\tau_1}} - \tau_2 e^{-\frac{t}{\tau_2}} \right] \quad (30)$$

It is thus seen that the solutions are made up of two exponential curves whose difference is to be taken. In the case of the current, these curves have the same initial ordinates but approach the time axis at different rates because of the different time constants. The solution is shown graphically in Fig. 71, where the dotted curves are the separate exponentials and the full line represents their difference.

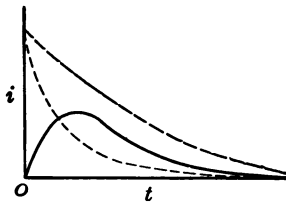


FIG. 71.—Aperiodic discharge of a condenser.

The current starts at zero, rises to a maximum and then slowly dies away.

Case II.  $R^2C^2 = 4LC$ . *Critically Damped Discharge.*—In this case the roots of eq. (18) are identical having the value  $-\frac{R}{2L}$  and the two terms of eq. (22) are the same. This equation cannot be the complete solution for this case since it contains but one arbitrary constant, whereas the complete solution must have two, since the original differential equation is of the second order.

The theory of differential equations<sup>1</sup> shows that for this case the solutions of eqs. (15) and (16) are

$$i = k_1 e^{-\frac{R}{2L}t} + k_2 t e^{-\frac{R}{2L}t} \tag{31}$$

$$q = k_3 e^{-\frac{R}{2L}t} + k_4 t e^{-\frac{R}{2L}t} \tag{32}$$

Imposing the same boundary conditions as before, namely, when  $t = 0$ ,  $i = 0$ , and  $q = Q$ , we have

$$k_1 = 0 \text{ and } k_3 = Q$$

Differentiating eq. (32)

$$i = \frac{dq}{dt} = -\frac{k_3 R}{2L} e^{-\frac{R}{2L}t} + k_4 \left[ e^{-\frac{R}{2L}t} - \frac{R}{2L} t e^{-\frac{R}{2L}t} \right] \tag{33}$$

Applying the first boundary condition to eq. (34) gives

$$k_4 = \frac{k_3 R}{2L} = \frac{QR}{2L}$$

Comparison of coefficients in eqs. (31) and (33) gives

$$k_2 = -\frac{R}{2L} k_4 = -\frac{QR^2}{4L^2} = -\frac{E}{L}$$

The complete solutions accordingly are

$$i = -\frac{E}{L} t e^{-\frac{R}{2L}t} \tag{34}$$

$$q = \left[ 1 + \frac{Rt}{2L} \right] Q e^{-\frac{R}{2L}t} \tag{35}$$

These equations consist of the product of a straight line and an exponential curve, and are similar to the corresponding ones for Case I. If numerical values are substituted, it is found that they rise to higher values and that they are more compressed along the time axis. In fact, the theory shows that for this critical case the discharge takes place in the shortest time possible.

Case III.  $R^2 C^2 < 4LC$ . *Oscillatory Discharge*.—This is the most interesting and important of the three cases. The quantity under the radical sign of eq. (19) then becomes imaginary and the two roots of eq. (18) are complex quantities. Call them

$$m_1 = \alpha + j\beta \text{ and } m_2 = \alpha - j\beta$$

where

$$\alpha = -\frac{R}{2L}, \beta = \frac{\sqrt{4LC - R^2 C^2}}{2LC}, \text{ and } j = \sqrt{-1}.$$

<sup>1</sup> MURRAY. Differential Equations, p. 65.

Equation 20 may then be written

$$\begin{aligned} i &= k_1 e^{(\alpha + j\beta)t} + k_2 e^{(\alpha - j\beta)t} \\ &= e^{\alpha t} [k_1 e^{j\beta t} + k_2 e^{-j\beta t}] \\ &= e^{\alpha t} [k_1 (\cos \beta t + j \sin \beta t) + k_2 (\cos \beta t - j \sin \beta t)] \\ &= e^{\alpha t} [(k_1 + k_2) \cos \beta t + (k_1 - k_2) j \sin \beta t] \end{aligned}$$

Let

$$\begin{aligned} k_1 &= \frac{A - jB}{2} \text{ then } k_1 + k_2 = A \\ k_2 &= \frac{A + jB}{2} \quad k_1 - k_2 = -jB \end{aligned}$$

whence

$$i = e^{\alpha t} [A \cos \beta t + B \sin \beta t]$$

By means of a well known formula of trigonometry this may be written

$$i = k e^{\alpha t} \sin (\beta t + \phi) \quad (36)$$

where

$$k = \sqrt{A^2 + B^2} \text{ and } \phi = \tan^{-1} \frac{A}{B}$$

In a similar manner the solution of eq. (16) for this case may be shown to be

$$q = k' e^{\alpha t} \sin (\beta t + \phi') \quad (37)$$

The four arbitrary constants  $k, k', \phi, \phi'$  are real quantities and may be determined by imposing the same boundary conditions as used above. Substituting in eqs. (36) and (37) the values  $i = 0, q = Q$  for  $t = 0$  respectively they become

$$\begin{aligned} 0 &= k \sin \phi \quad \text{whence } \phi = 0 \\ Q &= k' \sin \phi' \quad k' = \frac{Q}{\sin \phi'} \end{aligned} \quad (38)$$

Differentiating eq. (37) with respect to  $t$

$$\begin{aligned} i &= \frac{dq}{dt} = k' e^{\alpha t} [\alpha \sin (\beta t + \phi') + \beta \cos (\beta t + \phi')] \\ &= k' e^{\alpha t} \left[ \sqrt{\alpha^2 + \beta^2} \sin (\beta t + \phi' + \tan^{-1} \frac{\beta}{\alpha}) \right] \end{aligned} \quad (39)$$

Using again the condition  $i = 0$  for  $t = 0$  we have

$$\tan \phi' = -\frac{\beta}{\alpha} = \frac{\sqrt{4LC - R^2C^2}}{RC}$$

$$\therefore k' = \frac{Q}{\sin \phi'} = \frac{Q}{\sin \tan^{-1} \frac{\sqrt{4LC - R^2C^2}}{RC}} = \frac{\sqrt{4LCQ}}{\sqrt{4LC - R^2C^2}}$$

Comparing the coefficients of the sine terms in eqs. (39) and (36) we have

$$k = k' \sqrt{\alpha^2 + \beta^2} = \frac{2Q}{\sqrt{4LC - R^2C^2}}$$

The complete solutions may now be written

$$i = \frac{2Q}{\sqrt{4LC - R^2C^2}} e^{-\frac{R}{2L}t} \sin \frac{\sqrt{4LC - R^2C^2}}{2LC} t \quad (40)$$

$$q = \frac{\sqrt{4LC}Q}{\sqrt{4LC - R^2C^2}} e^{-\frac{R}{2L}t} \sin \left[ \frac{\sqrt{4LC - R^2C^2}}{2LC} t + \tan^{-1} \frac{\sqrt{4LC - R^2C^2}}{RC} \right] \quad (41)$$

The current and charge are sine functions of the time and are therefore oscillatory in character. The initial amplitude of the oscillations is proportional to the charge given to the condenser

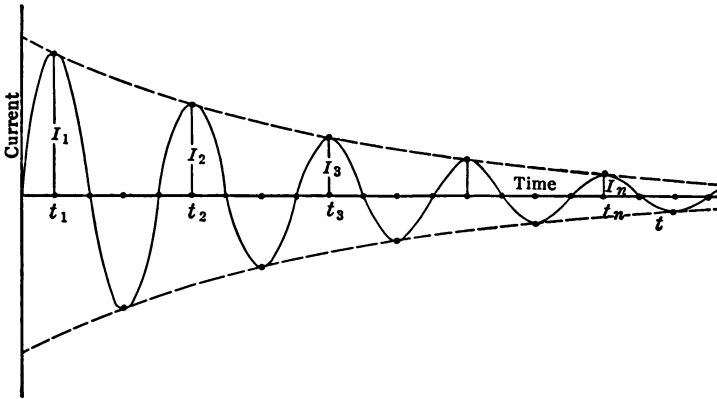


FIG. 72.—Damped sine wave.

and depends also upon the constants  $R$ ,  $L$ , and  $C$  of the circuit. Furthermore, the amplitude is multiplied by an exponential factor which decreases with the time and the oscillations consequently die out. An oscillation of this character is spoken of as a “damped” sine wave. The graph for the current wave is shown in Fig. 72. That for the charge is similar to it except that its phase is ahead of the current by the angle whose tangent is given by the last term in eq. (41). If  $R = 0$ , this angle is  $90^\circ$ .

The period  $T$  of the oscillation is obtained from eq. (40) by the relation

$$\omega = \frac{\sqrt{4LC - R^2C^2}}{2LC} = \frac{2\pi}{T}$$

whence

$$T = 2\pi \frac{2LC}{\sqrt{4LC - R^2C^2}}$$

If  $R^2C^2$  may be neglected in comparison to  $4LC$ , this reduces to the simple expression

$$T = 2\pi\sqrt{LC} \quad (42)$$

**104. Logarithmic Decrement.**—The physical interpretation of the phenomenon just described in mathematical terms is as follows: When the condenser is given a charge, a definite amount of energy,  $\frac{1}{2}C V^2$ , is stored up in it. As it discharges and current flows through the circuit, this energy is in part dissipated by the resistance  $R$  and in part stored up in the electromagnetic field of the inductance  $L$ . At the instant the potential difference across the condenser is zero the energy which has not been dissipated as heat is in the coil has the value  $\frac{1}{2}LI^2$ . This energy, minus that dissipated during the next quarter swing is returned to the condenser charging it in the opposite direction and so on. If the circuit were entirely free from resistance, the oscillations would simply represent interchanges of energy between the condenser and the coil at a frequency twice that of the circuit and would continue indefinitely in much the same manner as a pendulum suspended by frictionless bearings in a vacuum. It is obvious that the greater the rate of energy dissipation, the smaller the number of oscillations. The quantitative method of treating the damping effect is as follows:

Write eq. (40) in the simplified form

$$i = Ie^{-\alpha t} \sin \omega t \quad (43)$$

where

$$I = \frac{2Q}{\sqrt{4LC - R^2C^2}} \quad \alpha = \frac{R}{2L} \quad \omega = \frac{\sqrt{4LC - R^2C^2}}{2LC}$$

Let  $I_1, I_2, I_3, \dots, I_n$  be the successive current maxima as indicated in Fig. 72, let  $t_1, t_2, t_3, \dots, t_n$  be the times at which they occur, and let  $T$  be the period of oscillation. Since

$$\sin \omega t_1 = \sin \omega t_2 = \dots = 1$$

$$I_1 = e^{-\alpha t_1}$$

$$I_2 = e^{-\alpha(t_1+T)}$$

$$I_3 = e^{-\alpha(t_1+2T)}$$

.....

$$I_n = e^{-\alpha(t_1+(n-1)T)}$$



The ratio of the first amplitude to any succeeding one is

$$\frac{I_1}{I_n} = e^{\alpha(n-1)T} \tag{44}$$

In particular, let  $n = 2$ . Then

$$\frac{I_1}{I_2} = e^{\alpha T}$$

It is easily seen that the ratio of any amplitude to the next one succeeding it is constant and is equal to the value just given. Taking the logarithm of both sides

$$\log_e \frac{I_1}{I_2} = \alpha T = \pi R \sqrt{\frac{C}{L}} = \delta \tag{45}$$

The quantity  $\delta$  is called the "Logarithmic Decrement" and is defined as the Naperian logarithm of the ratio of any amplitude to the next one succeeding it in the same direction, and is given in terms of the constants of the circuit by eq. (45). One of the many applications that may be made of this quantity is the determination of the number of oscillations that the circuit will execute before the amplitude is reduced to an assigned fraction of its initial value. For example, between  $I_1$  and  $I_{n+1}$ , there are  $n$  oscillations.

Substituting in eq. (44)

$$\frac{I_1}{I_{n+1}} = e^{\alpha n T} = e^{n\delta}$$

or

$$\log_e \frac{I_1}{I_{n+1}} = n\delta$$

whence

$$n = \frac{1}{\delta} \log_e \frac{I_1}{I_{n+1}}$$

where

$$\frac{I_{n+1}}{I_n} \text{ is the assigned fraction.}$$

**105. Harmonic E.M.F. Acting on a Circuit Containing Resistance, Inductance and Capacitance.**—The equation of E.M.F.'s for this case is

$$L \frac{di}{dt} + Ri + \frac{1}{C} \int i dt = E \sin \omega t. \tag{46}$$

The theory shows that when the second member of a differential equation is different from zero, the complete solution is made up of two parts: (a) the solution of the original differential equation when the second member is put equal to zero, and (b) the par-

ticular integral. Part (a) has already been discussed and it was found to represent a transient phenomenon which quickly dies out. Part (b) corresponds to a "forced" oscillation, and represents a steady state. It is the part in which we are interested in problems of continuous alternating currents.

The student familiar with differential equations will remember that equations of the form of (46) are best treated by means of the differential operator "*D*." To apply this, first differentiate eq. (46) with respect to *t* to remove the sign of integration.

$$\frac{d^2i}{dt^2} + \frac{R}{L} \frac{di}{dt} + \frac{1}{LC} i = \frac{E\omega}{L} \cos \omega t \quad (47)$$

Introducing the operator *D*

$$\left(D^2 + \frac{R}{L} D + \frac{1}{LC}\right) i = \frac{E\omega}{L} \cos \omega t \quad (48)$$

The particular integral which we are seeking is then

$$i = \frac{1}{D^2 + \frac{R}{L} D + \frac{1}{LC}} \frac{E\omega}{L} \cos \omega t \quad (49)$$

The meaning of the "inverse" operator, as the quantity immediately following the equality sign is called, is this: Find a function of *i* such that when operated on by the coefficient of *i* in eq. (48) it gives the right-hand member of that equation. There is a well known short method<sup>1</sup> for treating the case of sines or cosines such as eq. (49). It consists simply in expressing the function of *D* as a function of *D*<sup>2</sup> and replacing *D*<sup>2</sup> by minus the square of the coefficient of the independent variable. Accordingly

$$\begin{aligned} i &= \frac{1}{-\omega^2 + \frac{R}{L} D + \frac{1}{LC}} \frac{E\omega}{L} \cos \omega t = \frac{E\omega}{RD + \frac{1}{C} - L\omega^2} \cos \omega t = \\ &= \frac{E\omega \left[ RD - \left( \frac{1}{C} - L\omega^2 \right) \right]}{R^2 D^2 - \left( \frac{1}{C} - L\omega \right)^2} \cos \omega t = \\ &= \frac{E\omega \left[ RD - \frac{1}{C} - L\omega^2 \right]}{-R^2 \omega^2 - \left( \frac{1}{C} - L\omega \right)^2} \cos \omega t = \end{aligned}$$

<sup>1</sup> See MURRAY, Differential Equations, p. 77.

$$\frac{E\omega^2 R \sin \omega t}{R^2\omega^2 + \left(\frac{1}{C} - L\omega^2\right)^2} + \frac{E\omega\left(\frac{1}{C} - L\omega^2\right) \cos \omega t}{R^2\omega^2 + \left(\frac{1}{C} - L\omega^2\right)^2} =$$

$$\frac{ER \sin \omega t}{R^2 + \left(L\omega - \frac{1}{C\omega}\right)^2} + E \frac{\left(\frac{1}{C\omega} - L\omega\right)}{R^2 + \left(L\omega - \frac{1}{C\omega}\right)^2} \cos \omega t$$

combining into a single sine function

$$i = \frac{E}{\sqrt{R^2 + \left(L\omega - \frac{1}{C\omega}\right)^2}} \sin \left[ \omega t - \tan^{-1} \frac{L\omega - \frac{1}{C\omega}}{R} \right] \quad (50)$$

It is thus seen that the current is a sine function and has the same frequency as the impressed E.M.F. In general, it is not in phase with the E.M.F. but lags behind or leads according as  $L\omega$  is greater or less than  $\frac{1}{C\omega}$ . If  $L\omega = \frac{1}{C\omega}$ , i.e.,  $\omega = \frac{1}{\sqrt{LC}}$ , the current is in phase with the E.M.F. and in this case eq. (50) becomes

$$i = \frac{E}{R} \sin \omega t$$

which is identical with the current equation given directly by Ohm's law for the case when no inductance or capacitance is present. The maximum value of the current is obtained by putting the sine function equal to unity: i.e.,

$$I = \frac{E}{\sqrt{R^2 + \left(L\omega - \frac{1}{C\omega}\right)^2}}$$

By analogy with Ohm's law the denominator is called the "Impedance" of the circuit and the quantities  $L\omega$  and  $\frac{1}{C\omega}$  are called the inductive and capacitive "Reactances" respectively. Reactance produces not only a phase angle between the current and E.M.F. but also reduces the magnitude of the current.

**106. Alternative Method.**—For those unfamiliar with differential equations, an indirect method of obtaining the solution of eq. (46) may be employed. Since an alternating E.M.F. is applied to the circuit, it is reasonable to suppose that the current will also be alternating, that it will have the same frequency as the E.M.F.

and that it may not be in phase with the E.M.F. These assumptions are combined in the following expression

$$i = I \sin (\omega t + \phi) \quad (51)$$

where  $I$  and  $\phi$  are arbitrary constants which are to be determined by substituting eq. (51) in (46) and finding the values which must be assigned to them in order that eq. (46) may be satisfied.

$$\frac{di}{dt} = I\omega \cos (\omega t + \phi) \text{ and } \int idt = -\frac{I}{\omega} \cos (\omega t + \phi)$$

Substituting these values, eq. (46) becomes

$$LI\omega \cos (\omega t + \phi) + RI \sin (\omega t + \phi) - \frac{I}{C\omega} \cos (\omega t + \phi) = E \sin \omega t$$

Since this equation holds for all values of  $t$ , we may write, when

$$\omega t + \phi = 0, LI\omega - \frac{I}{C\omega} = -E \sin \phi$$

when  $\omega t + \phi = \frac{\pi}{2}, RI = E \cos \phi$

Squaring and adding the above expressions,

$$\left[ R^2 + \left( L\omega - \frac{1}{C\omega} \right)^2 \right] I^2 = E^2$$

$$\therefore I = \frac{E}{\sqrt{R^2 + \left( L\omega - \frac{1}{C\omega} \right)^2}}$$

Dividing one by the other

$$-\tan \phi = \frac{L\omega - \frac{1}{C\omega}}{R} \text{ or } \phi = -\tan^{-1} \frac{L\omega - \frac{1}{C\omega}}{R}$$

Substituting these values in eq. (51) we have

$$i = \frac{E}{\sqrt{R^2 + \left( L\omega - \frac{1}{C\omega} \right)^2}} \sin \left[ \omega t - \tan^{-1} \frac{L\omega - \frac{1}{C\omega}}{R} \right]$$

which is eq. (50) above.

**107. Vector Diagrams.**—In the discussion thus far, we have spoken of alternating E.M.F.'s and alternating currents and have used in each case the trigonometric expressions in discussing them. For example the equations

$$e = E \sin \omega t$$

$$i = I \sin (\omega t - \phi)$$

have been used to represent respectively an alternating E.M.F. having a maximum value  $E$  and a frequency  $f = \frac{\omega}{2\pi}$ , and an alternating current of the same frequency with a maximum value  $I$  lagging behind the E.M.F. by a phase angle  $\phi$ .

These may be regarded as being given by the projections on the  $Y$  axis of the vectors  $OE$  and  $OI$  respectively of Fig. 73 which rotate with constant angular velocity in counter clockwise direction, the latter lagging behind the former by the angle  $\phi$ . The vectors  $OE$  and  $OI$  represent the maximum values of the E.M.F.

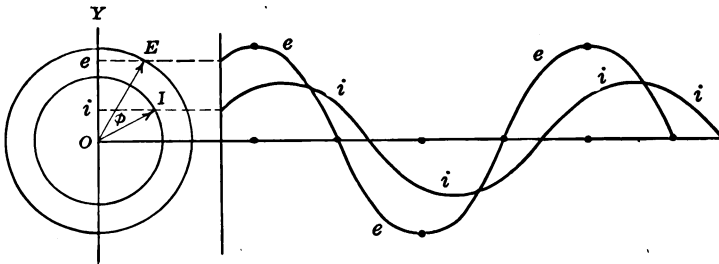


FIG. 73.—Sine waves represented by rotating vectors.

and current. As a special case, consider that of an alternating E.M.F. acting on a circuit having resistance and inductance. The current is given by eq. (50) with  $C = \infty$ , the condition for zero capacitive reactance. Thus

$$i = \frac{E}{\sqrt{R^2 + L^2\omega^2}} \sin\left(\omega t - \tan^{-1} \frac{L\omega}{R}\right) \tag{52}$$

For the maximum value of the current, we have

$$I = \frac{E}{\sqrt{R^2 + L^2\omega^2}} \text{ or } E = \sqrt{R^2 I^2 + L^2 \omega^2 I^2}$$

From the form of the latter expression it is evident that  $E$  has such a value that it may be given as the diagonal of a rectangle whose sides are  $RI$  and  $L\omega I$ , as shown in Fig. 74. The current  $I$  is represented as a vector in phase with  $RI$ , since, from eq. (52), the current lags behind the E.M.F. by an angle whose tangent is  $\frac{L\omega}{R}$ . This is the angle  $\phi$  shown in the figure. If this figure is rotated about the origin  $O$  with an angular velocity  $\omega$  in the positive direction, the projections of the vectors,  $E$ ,  $RI$ , and  $L\omega I$  upon the  $Y$  axis give the instantaneous values of the impressed E.M.F.

and the E.M.F. across the resistance and the inductance respectively.

In a similar manner, a vector diagram may be constructed for a circuit containing resistance, inductance and capacitance in series. For this case the maximum current and phase angle are given respectively by

$$I = \frac{E}{\sqrt{R^2 + \left(L\omega - \frac{1}{C\omega}\right)^2}}$$

$$\phi = \tan^{-1} \frac{L\omega - \frac{1}{C\omega}}{R}$$

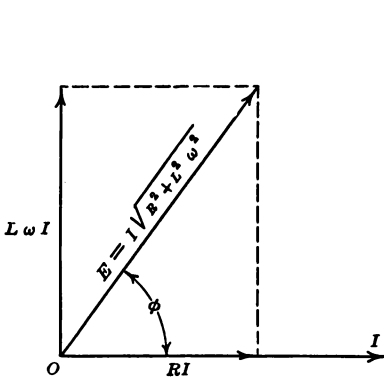


FIG. 74.—Vector diagram for resistance and inductance.

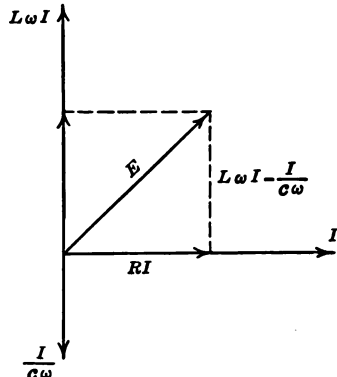


FIG. 75.—Vector diagram for resistance, inductance and capacitance.

The vectors are similar to those of the previous case except for the additional vector,  $\frac{I}{C\omega}$ , which is shown drawn downward in Fig. 75, since in the equation it appears as a quantity subtracted from  $L\omega$ . In the figure,  $L\omega I$  is shown greater than  $\frac{I}{C\omega}$  and the current lags behind the E.M.F. If  $L\omega = \frac{1}{C\omega}$ , the component of  $E$  perpendicular to  $I$  is zero and the current is in phase with the E.M.F. On the other hand when  $\frac{1}{C\omega}$  is greater than  $L\omega$ ,  $\phi$  is negative, and the current leads the E.M.F.

**108. Electrical Resonance.**—In discussing the discharge of a condenser through a circuit containing resistance and inductance, it was shown that when the resistance is less than a certain critical

value, oscillations occur. If such a circuit is acted upon by an alternating E.M.F. whose frequency is the same as the natural frequency of the circuit, alternating currents of large amplitude are set up in the inductance and condenser. This phenomenon is spoken of as electrical resonance and is analogous to the motion of a mechanical system possessing inertia and elasticity, when acted upon by an alternating mechanical force having a frequency corresponding to its own free period. Two distinct cases occur depending upon whether the inductance and capacitance are in series with the E.M.F. or are connected across it in parallel. These are distinguished as "Series Resonance" and "Parallel Resonance" respectively.

**109. Series Resonance.**—This case has been discussed above in some detail. The instantaneous value of the current must satisfy eq. (46) the solution of which is eq. (50). The amplitude of the current is given by

$$I = \frac{E}{\sqrt{R^2 + \left(L\omega - \frac{1}{C\omega}\right)^2}}$$

and it has already been pointed out this is a maximum when

$L\omega = \frac{1}{C\omega}$ , which is the condition for resonance. The current is then given by  $E$  divided by  $R$  as required by Ohm's law. The resonance condition depends upon the relative values of  $L$ ,  $C$  and  $\omega$ ,

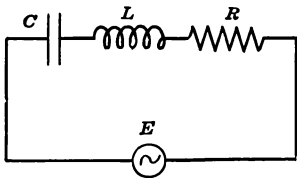


FIG. 76.—Series resonance.

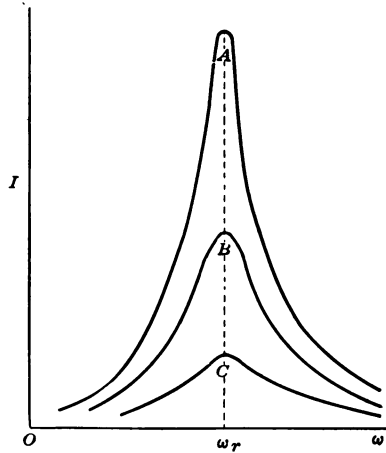


FIG. 77.—Effect of resistance on sharpness of resonance.

and may be brought about by a suitable change of either one of them, the other two being held constant. Bringing a circuit into resonance is generally spoken of as "tuning" it.

The dependence of the current upon the constants of the

circuit may be illustrated by the curves shown in Fig. 77, where the current amplitude is shown as a function of frequency for a short range each side of resonance. The inductance and capacitance are held constant and three different resistances are indicated.  $A$  represents the current at resonance for a small resistance and  $C$  that for a large. It is to be noted that the effect of a change in resistance is much more marked at resonance than at a frequency somewhat removed. This is because at resonance, resistance alone determines the current, while at low frequencies, the capacity reactance  $\frac{1}{C\omega}$  is an important term, but at high frequencies, the inductive reactance  $L\omega$  becomes effective in reducing the current. It is to be noted also, that for low frequencies the current leads the E.M.F., is in phase with it at resonance and lags behind at high frequencies. When the resistance is small, the rate of change of the phase angle in passing through resonance is rapid.

**110. Parallel Resonance.**<sup>1</sup>—When the E.M.F. is introduced in the circuit in such a way that the inductance and condenser are in parallel, the phenomena are strikingly different from those of the series arrangement just described. The connections for this case are shown in Fig. 78. Assuming that the condenser is free from energy absorption, the current through it leads the E.M.F. by ninety degrees, while that through the inductance lags behind by an angle depending upon  $R$ ,  $L$ , and  $\omega$ . The current in the main circuit is the vector sum of these two and in determining it the relative phases of the components must be taken into account. Denoting the currents through the inductance and condenser by  $I_L$  and  $I_C$  respectively, their amplitudes are obtained from eq. (50) as follows

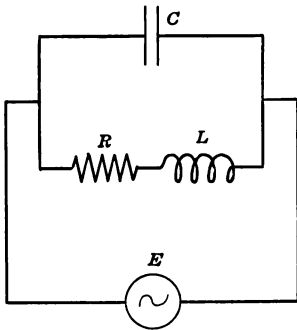


FIG. 78.—Parallel resonance.

$$I_L = \frac{E}{\sqrt{R^2 + L^2\omega^2}} \quad I_C = EC\omega \quad (53)$$

Letting the vector  $OE$  of Fig. 79 represent the impressed E.M.F.,

<sup>1</sup> Circ. 74. U. S. Bureau of Standards, p. 39.



the above currents are given by  $OI_C$  and  $OI_L$  respectively, and the resultant current  $OI$ , is the diagonal of the parallelogram formed by them as sides. The amplitude of the resultant current, by the law of cosines, is:

$$I^2 = I_L^2 + I_C^2 - 2I_L I_C \cos \psi \quad (54)$$

The value of  $\cos \psi$  may be obtained by remembering that the E.M.F. across the coil is made up of two parts: That across the resistance,  $RI_L$ , and that across the inductance  $L\omega I_L$ . The former is in phase with  $I_L$  and the latter, ninety degrees ahead of it. Accordingly

$$\cos \psi = \frac{L\omega I_L}{E} \quad (55)$$

Substituting eqs. (53) and (55) in (54) and combining we have

$$I^2 = E^2 \left[ C^2 \omega^2 + \frac{1}{R^2 + L^2 \omega^2} - \frac{2C\omega L\omega}{R^2 + L^2 \omega^2} \right] \quad (56)$$

Multiplying numerator and denominator of the second term by  $R^2 + L^2 \omega^2$ , eq. (56) may be written

$$I = E \sqrt{\left( C\omega - \frac{L\omega}{R^2 + L^2 \omega^2} \right)^2 + \frac{R^2}{(R^2 + L^2 \omega^2)^2}} \quad (57)$$

Equation (57) is the general expression for the current drawn from the supply. The condition that this current should be in phase with the driving E.M.F. is

$$I^2 = I_L^2 - I_C^2$$

Substituting the values from eqs. (53) and (56) there results

$$C\omega = \frac{L\omega}{R^2 + L^2 \omega^2} \quad (58)$$

The value of  $\omega$  obtained from this equation is not exactly that corresponding to the natural period of the circuit but approximates it closely. If  $R$  is zero, it corresponds exactly. Introduc-

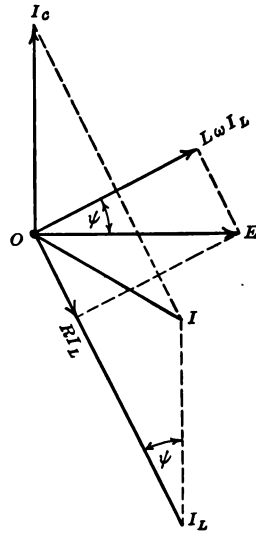


FIG. 79.—Vector diagram for parallel resonance.

ing this condition in eq. (57) it is seen that the current, when in phase with the E.M.F., is

$$I = \frac{ER}{R^2 + L^2\omega^2} \quad (59)$$

It is important to note that for small values of  $R$ ,  $I$  is nearly proportional to  $R$  and that if  $R$  were zero,  $I$  would also be zero. We thus have the extraordinary situation in which the larger the resistance the larger the current. Figure 80 shows the variation of current with frequency in the neighborhood of resonance. It is interesting to note that in the case of series resonance the individual voltages across the condenser and coil exceed the total voltage across the two combined, while in parallel resonance, the current in each exceeds the two combined. The series arrangement gives a low impedance at resonance, while

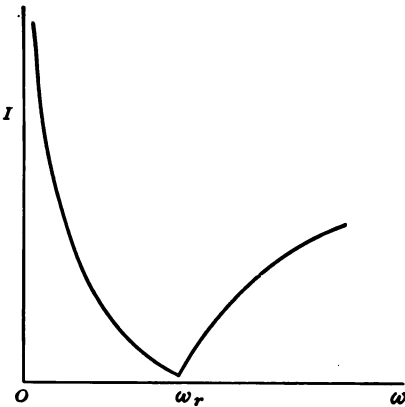


Fig. 80.—Dependence of current on frequency for parallel resonance.

the parallel connection gives a high impedance at this point. For this reason, the latter is frequently inserted in a circuit when it is desired to suppress a particular frequency in a complex wave.

**111. Measurement of Inductance and Capacitance by Resonance.**—The phenomenon of electrical resonance furnishes a convenient method for the determination of inductance and capacitance, particularly when they are small. If two circuits, adjusted to have the same natural periods are placed in inductive relation, and one of them is caused to oscillate, the other will oscillate also by resonance. It was shown on page 136 that the period of an oscillating circuit is given by the expression

$$t = 2\pi\sqrt{LC}.$$

Consequently, the condition for resonance is that the  $LC$  products for the two circuits must be the same or

$$L_1C_1 = L_2C_2 \quad (60)$$

where the subscripts refer to the circuits 1 and 2 respectively. If three of these quantities or one  $LC$  product and either  $L$  or  $C$  are known, the fourth may be computed. In carrying out the measurement it is more satisfactory to use a third circuit as a source of oscillations, and then adjust both the standard and unknown circuits to resonate to it. The inductance and capacitance of the third circuit should be adjustable, but need not be known. The three circuits are shown in Fig. 81. The source circuit is energized by means of the battery  $A$  and an ordinary buzzer  $B$  which serves as an interrupter. When the armature

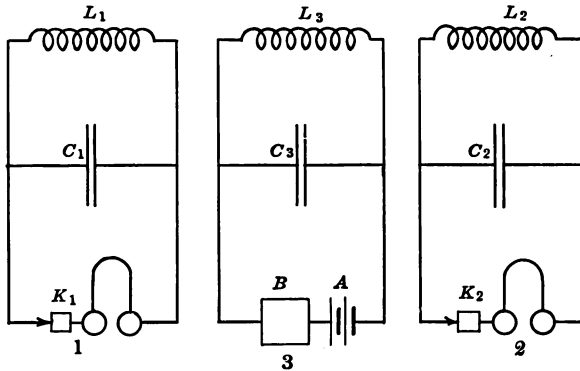


Fig. 81.—Circuits arranged for electrical resonance.

of the buzzer closes the circuit, the battery current flows through the coil  $L_3$  and stores up energy in the electromagnetic field linking its windings. When the armature of the buzzer breaks the battery circuit, this energy is transferred back and forth between  $C_3$  and  $L_3$  until it has been dissipated. A group of damped oscillations is thus established in this circuit for each vibration of the buzzer armature. Similar oscillations but of weaker intensities will be set up in circuits 1 and 2 if they are adjusted to resonate to 3.

If small inductances and capacitances are used the frequency of the oscillations thus produced will be above the audible range, and special means for detecting them must be employed. A convenient method is to use a pair of head phones and a crystal detector such as is commonly employed for the reception of radio signals. Because of the rectifying action of the point-crystal contact the high frequency alternating voltage across the con-

denser will produce a series of high frequency unidirectional pulses in the phone circuit. Because of the distributed capacitance of the phone windings, these are smoothed out into a single pulse which causes a vibration of the diaphragm. The sound in the phones then has the period of the buzzer armature. If a sufficient amount of energy is available, it is best to disconnect the right-hand phone lead shown in the figure, and use only a single wire from the phone through the crystal to the oscillatory circuit. This is particularly important when the condensers are small since the capacity between phone leads may introduce a very appreciable error.

**112. Experiment 19.** *Measurement of Inductance and Capacitance by Resonance.*—Connect the apparatus as shown in Fig. 81, using for  $L_1$  a standard inductance variable by steps, and for  $C_1$  a variable standard air condenser.  $L_2$  should be a single layer coil of uniform windings whose dimensions may easily be measured.  $C_2$  should be an air condenser with plates easily accessible for measurement. First obtain resonance in circuit 2 by varying the frequency of the source. Next obtain resonance in circuit 1 and compute the  $LC$  product. Measure the dimensions of  $C_2$  and compute its capacity from eq. (19) given on page 94. (See also the Appendix.) Determine  $L_1$  from eq. (60). Check your result by computing the inductance of  $L_1$  from dimensions using the formula given in the Appendix.

**113. Effective Value of an Alternating Current.**—If an alternating current is passed through an ordinary D.C. ammeter, no indication will be registered, since such an instrument indicates average values, which in this case is zero. However, if an alternating current is passed through a resistance, heat is liberated, the energy of which is furnished by the current. The reason for the difference in effect in these two cases is that the torque on the moving coil of the instrument is proportional to the current and therefore reverses sign with it, while the heating effect of a current is proportional to its square and is therefore positive no matter what its direction.

It is customary to define the *Effective* value of an alternating current as the equivalent direct current which liberates the same amount of heat in a given resistance per unit time. In deducing the relation between the effective value of an alternating current and its amplitude or maximum value, it is sufficient to equate the heat, in joules, developed by each during the time  $T$

of one complete cycle. Accordingly let  $i = I \sin \omega t$  be the alternating current and  $I_e$  its effective value. When flowing through a resistance  $R$ , the heat liberated by each is

$$\begin{aligned} H &= I_e^2 RT = \int_0^T i^2 R dt = I^2 R \int_0^T \sin^2 \omega t dt \quad (61) \\ &= I^2 R \int_0^T \left( \frac{1}{2} - \frac{\cos 2\omega t}{2} \right) dt \\ &= I^2 R \left[ \frac{t}{2} - \frac{\sin 2\omega t}{4\omega} \right]_0^T = \frac{I^2 RT}{2} \end{aligned}$$

Therefore:

$$I_e = \frac{I}{\sqrt{2}} = .707 I \quad (62)$$

The above process is seen to be equivalent to squaring the instantaneous values of the current, taking the average value of the squares, and then extracting the square root. The effective value accordingly is often spoken of as the "Root Mean Square" value. The same considerations hold for an alternating E.M.F.

**114. Power Consumed by a Circuit Traversed by an Alternating Current.**—Let us suppose that an alternating E.M.F. is impressed upon a circuit which contains reactance as well as resistance so that the current and E.M.F. are not in phase. It is desired to find the power consumed by the circuit. Let the E.M.F. and current be given respectively by the following expressions

$$e = E \sin \omega t; i = I \sin(\omega t \pm \phi) \quad (63)$$

where  $\phi$  is the angle of lag or lead.

The energy  $dH$  consumed in the time  $dt$  is

$$dH = e i dt = EI \sin \omega t \sin(\omega t \pm \phi) dt \quad (64)$$

The energy  $H$  consumed per cycle is

$$\begin{aligned} H &= EI \int_0^T \sin \omega t (\sin \omega t \cos \phi \pm \cos \omega t \sin \phi) dt \\ &= EI \left\{ \cos \phi \int_0^T \sin^2 \omega t dt \pm \sin \phi \int_0^T \sin \omega t \cos \omega t dt \right\} \\ &= EI \left\{ \cos \phi \int_0^T \left( \frac{1}{2} - \frac{\cos 2\omega t}{2} \right) dt \pm \sin \phi \int_0^T \sin \omega t \cos \omega t dt \right\} \end{aligned}$$

Carrying out the integrations and substituting limits the last two integrals vanish and we have

$$H = EI \frac{T}{2} \cos \phi$$
$$\text{Power} = \frac{\text{Energy per Cycle}}{T} = \frac{E I}{\sqrt{2}\sqrt{2}} \cos \phi$$

It is thus seen that the power consumed is the product of the effective E.M.F. and current multiplied by the cosine of the phase angle. Cosine  $\phi$  is called the "Power Factor" and varies from zero to unity.

## CHAPTER XI

### SOURCES OF E.M.F. AND DETECTING DEVICES FOR BRIDGE METHODS

Before discussing the various bridges which are to be employed in the measurement of inductance and capacitance, the student should become familiar with some of the sources of alternating E.M.F. and detecting devices that are available. Inasmuch as the alternating currents for commercial purposes are of frequencies too low to give a tone suitable for telephonic balances, special generators have been devised, a few of which will now be described.

**115. The Sechometer.**—In Exps. 12 and 17 methods were employed for comparisons of capacitance and inductance respectively in which batteries were employed to energize the bridges and the E.M.F.'s due to the reactances were made manifest during the rise and fall of the bridge currents following the closing and opening of the battery circuit key. It was then found that the galvanometer deflected in one direction on closing and in the opposite on opening this key. If some means were available by which the galvanometer leads could be interchanged each time the key is opened and closed, the deflections would always be in the same direction and if the interval between successive operations of the key were small compared to the period of the galvanometer, a steady deflection would result whereby the sharpness of the bridge balance would be greatly increased. The Sechometer is a device which accomplishes this purpose and derives its name from the "Secohm" by which our present unit of inductance, the henry, formerly was known.

It consists essentially of two commutators mounted on the same shaft which may be driven at any desired speed by a motor. The segments are set in such a relation to each other that the galvanometer leads are interchanged by one commutator each time the polarity of the battery is reversed by the other. The connections are shown in Fig. 82. The device must not be driven at too high a speed since sufficient time must be allowed for the establishment of a steady state at each reversal. High speeds

also develop heat at the brush contacts resulting in errors due to thermal E.M.F.'s.

It is well to get an approximate bridge balance by manipulating

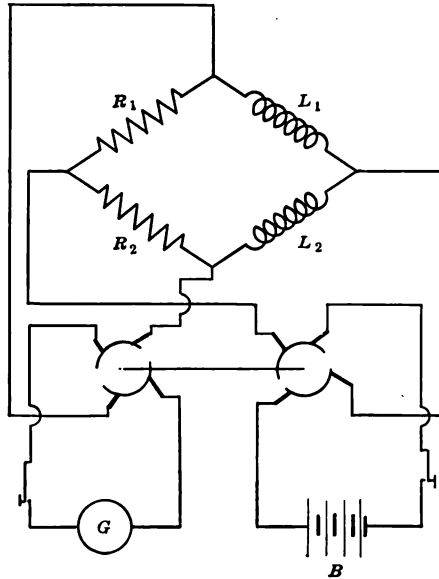


FIG. 82.—Sechometer connections to bridge.

the battery and galvanometer keys with the sechometer stationary and then use it merely to obtain the final setting. The

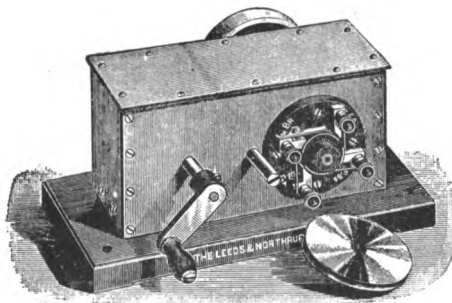


FIG. 83.—The Sechometer.

application of this instrument is equivalent to using a generator giving a square wave form and can, therefore, be used only with bridges which balance independent of the frequency. Figure 83



shows the assembled instrument provided with a crank for hand driving.

**116. The Wire Interrupter.**—The vibrating wire interrupter, shown in Fig. 84, consists essentially of a piano wire stretched between rigid supports *A* and *B*, the tension of which may be varied by the screw *S*. Vibrations are maintained by means of an electromagnet *M*, intermittently energized by a battery *B*<sub>1</sub>. The mercury cup contact *C*<sub>1</sub> interrupts this current when the wire is drawn up, and the device operates in a manner similar to the ordinary buzzer. The battery *B*<sub>2</sub>, which supplies current to the

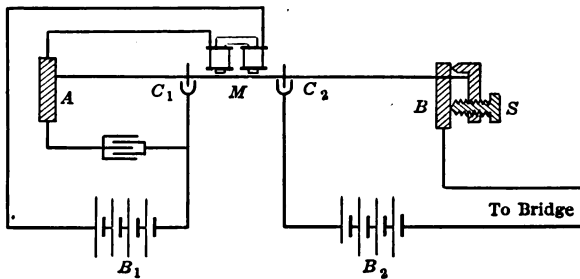


FIG. 84.—Vibrating wire.

bridge, is connected through the contact *C*<sub>2</sub> and this circuit is also closed and opened at the frequency maintained by the wire.

Frequencies ranging from 25 to 150 are easily secured. This device is particularly well suited for use with the vibration galvanometer, since it permits of sharp, easy tuning, and may readily be adjusted to resonance with the galvanometer. Since the vibration galvanometer responds only to the fundamental and not the overtones, the fact that the interrupter gives a square wave form results in no disadvantage and the combination may accordingly be used on bridge circuits which do not balance independent of the frequency and the same results obtained as though a source giving a pure sine wave were employed. If a suitable condenser *K* is shunted across the contact *C*<sub>1</sub> to prevent arcing, the device will operate continuously for hours with little or no attention.

**117. The Motor Generator.**—Another inexpensive source of alternating current is the small motor generator set manufactured by the Leeds and Northrup Company shown in Fig. 85. The generator, which is shown at the right in the figure, is of the

inductor type and has stationary windings for both field and armature circuits. Direct current is supplied to the field coil at the base thus energizing the magnetic circuit which includes the broad toothed wheel carried on the armature shaft of the motor. The reluctance of this magnetic circuit depends upon the position

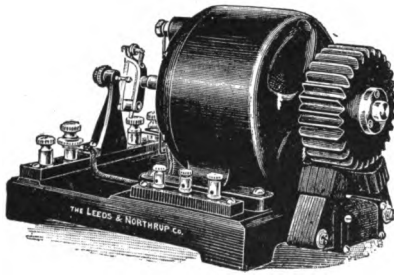


FIG. 85.—Motor generator set.

of the teeth with respect to the pole pieces. When the wheel is driven, the flux through the magnetic circuit fluctuates at a frequency equal to the number of teeth passing the pole tips per second. An alternating E.M.F. is thus induced in the armature windings placed near the pole tips.

By properly choosing the shape of the pole tips and teeth, it is possible to obtain a wave form that is relatively free from harmonics although it is not possible to eliminate them completely. By the use of a suitable filter, good wave forms may be obtained. By means of a specially designed mechanical governor, the speed of the motor may be maintained constant to  $\frac{1}{2}$  per cent.

**118. The Microphone Hummer.**—If it is not necessary to supply the bridge with a constant frequency, a simple microphone hummer furnishes a convenient and inexpensive source of alternating current. Such a circuit is shown in Fig. 86. It consists of a microphone transmitter facing a telephone receiver. The transmitter and receiver circuits are connected in the ordinary way by a telephone transformer. Any stray sound will cause a variation in the microphone current which produces a sound in the receiver. This sound is “fed back” to the microphone which again produces a sound in the receiver and the action is thus continuous, the energy being supplied by the battery. The interval between the application of the sound to the microphone and its return by the receiver after having operated the electrical circuits depends to a large extent upon the time constant of the

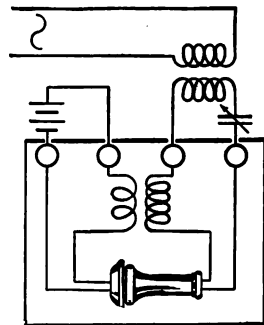


FIG. 86.—Microphone hummer.

secondary or receiver circuit. If the resistance of this circuit is not too large, it may be made oscillatory by the introduction of a condenser as indicated in the diagram. By giving suitable values to the capacitance of this condenser a large range of frequencies may be obtained. Another transformer, the primary of which is in series with the receiver, furnishes a means of making the A.C. power thus generated available for a bridge circuit. A convenient form of this device is manufactured by R. W. Paul of London under the trade name "Kumagen," the appropriateness of which is easily understood. The microphone, receiver, and transformers are contained in a felt lined case which serves to deaden the sound. A condenser is also furnished which is variable in steps chosen so as to give a number of suitable frequencies.

**119. The Audio-oscillator.**—The frequency of the microphone hummer, described above, is somewhat variable depending upon

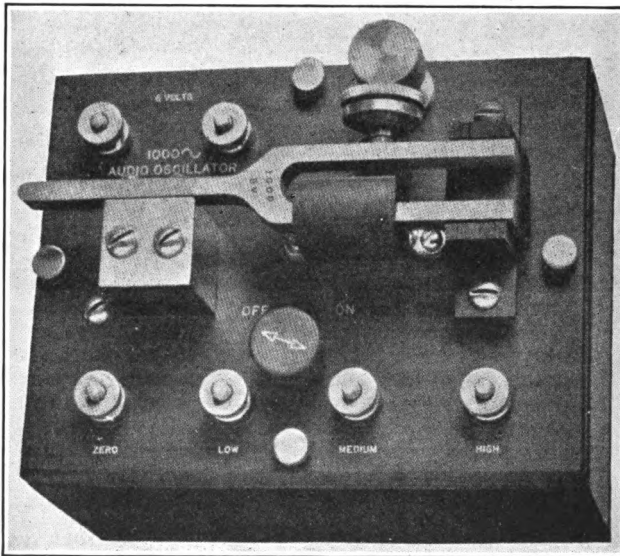


FIG. 87.—Audio-oscillator.

the strength of the driving battery and the load upon the secondary of the output transformer. An adaptation of the underlying principle has been made by Campbell by which this objection is overcome. It consists in operating the microphone button, not by sound waves from a telephone receiver, but by means of a tuning fork whose mechanical period coincides with

the period of the electrical circuit which it energizes. Several different forms are on the market. Figure 87 shows an instrument of this type known as the audio-oscillator, manufactured by the General Radio Co., and Fig. 88 gives the wiring diagram. The "field coil" which is connected directly across the battery serves merely to magnetize the fork and armature core to a point on the magnetization curve near the maximum permeability and this increases the attractive forces of the poles. The battery also sends current through the microphone and primary of the input transformer. When the battery key is closed, the current through

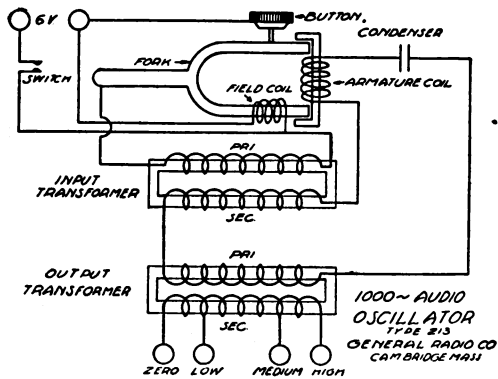


FIG. 88.—Wiring diagram for audio-oscillator.

the primary of the input transformer induces an E.M.F. in the secondary which starts oscillations in the resonating circuit which includes, besides the condenser and primary of the output transformer, the armature coil. This oscillating current changes the attraction between the armature pole tips and the prongs of the fork. Since the secondary circuit is tuned to the period of the fork, the fork resonates to it, thus building up a vigorous vibration. The microphone button, being in contact with the fork, supplies a varying current of this same frequency to the primary of the input transformer and energy from the battery is thus furnished to maintain the oscillations, and carry the load put upon the secondary of the output transformer.

Each transformer coil has a small air gap to prevent distortion, but their magnetic circuits are sufficiently closed to prevent disturbing stray fields. The oscillator is self starting and may be placed at some distance and operated by a key near the bridge. The coils are so wound that a 6-volt battery furnishes ample

power. The device is not designed to furnish more power than that required by a single bridge circuit. If overloaded, the microphone is likely to pack. It is carried by a stiff spring mounted on one prong of the fork and its inertia is sufficient to insure response to vibrations of the fork.

**120. The Vreeland Oscillator.**—None of the sources thus far described produce alternating E.M.F.'s of a purely sinusoidal wave form. There are a number of important bridges which do

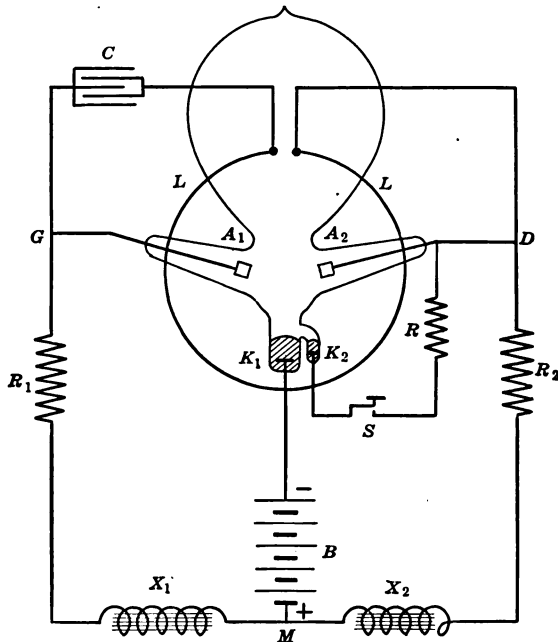


FIG. 89.—Wiring diagram for Vreeland oscillator.

not balance independent of the frequency and when a telephone is used as the detecting device, complete silence can not be obtained with impure wave forms. In such cases, when the fundamental has been balanced out, the overtones are still heard and materially mar the sharpness of setting which would otherwise be possible.

The Vreeland Oscillator is one of the best sources of pure sine waves available. It is, in reality, a mercury arc rectifier operated backwards, the connections for which are shown diagrammatically in Fig. 89. The essential part of the device is a large pear shaped mercury arc tube with two anodes  $A_1$  and  $A_2$  having a common

mercury cathode  $K_1$ . It is well known that the mercury arc will operate only when the mercury electrode is negative. When used as a rectifier, the condenser and deflecting coil are removed and the source of alternating E.M.F. is connected to the terminals  $G.D$ . When  $G$  is positive and  $D$  negative, current will flow from  $A_1$  to  $K_1$  through the battery  $B$ , which is here shown as the load, to  $D$ , and when  $D$  is positive, the path is  $A_2K_1MG$ , these furnishing a current through  $B$  in the same direction as before. The reactances  $X_1$  and  $X_2$  serve to smooth out the fluctuations through the battery.

To understand its operation as an oscillator, let us suppose that the source of  $A.C.$  is removed and that the deflecting coil and condenser are connected to  $G$  and  $D$  as shown in the figure. The battery  $B$  now becomes the source of power. An arc is started between the electrodes  $K_1$  and  $K_2$  by shaking the tube slightly, thus causing the mercury pools to unite and break again. The tube is quickly filled with ionized mercury vapor and the arc spreads to the anodes  $A_1$  and  $A_2$ . The switch  $S$  is then opened thus stopping the arc to  $K_2$ . If the impedance of the two paths  $MD$  and  $MB$  are equal and the tube is symmetrical, the arc will divide equally between the anodes  $A_1$  and  $A_2$  which are thus at the same potential and there is no charge in the condenser. If, however, some irregularity in the tube causes more current to flow momentarily to the anode  $A_1$  it will be at a higher potential than  $A_2$  and a charging current will flow to the condenser through the deflecting coil  $LL$ . This coil, which really consists of two parts, one in front of the tube and the other behind it, is placed so that its magnetic field is perpendicular to the flow through the arc. If the polarity is so chosen that the charging current deflects the arc stream so as to further increase the current to  $A_1$  a very appreciable charge may be given to the condenser. When the condenser discharges, the deflecting action of the current which is now reversed will cause more current to flow to the anode  $A_2$  thus raising its potential above  $A_1$  and charging the condenser in the opposite direction. The deflecting coil serves the double purpose of furnishing a self inductance to form, with  $C$ , an oscillatory circuit, and to automatically deflect the arc streams from one anode to the other to maintain the oscillations. The frequency is given by the expression

$$n = \frac{1}{2\pi\sqrt{LC}}$$

where  $L$  is the inductance of the deflecting coil in henries, and  $C$  the capacitance of the condenser in farads. It is found that such a device, when properly designed, will oscillate at frequencies ranging from 100 to 4,000 cycles per second.

Another coil, placed near the deflecting coils, serves as the secondary of an air cored transformer to supply current to a bridge. It is found that the frequency is but little affected by changes in the load on the secondary. Because of the relatively large coils, the instrument possesses an appreciable stray field and must be placed at some distance from the bridge, to prevent direct induction in the coils which are being studied.

**121. The Electron Tube Oscillator.**—One of the simplest and most effective means of obtaining alternating voltage of any desired frequency is that in which a three element electron tube is used to maintain continuous oscillations in a resonance circuit. The underlying principle is the amplifying action of the tube which will be described in chap. XIV. It will be sufficient for the present purpose to point out that the electron tube consists of a highly evacuated glass container in which are placed a filament and a metal plate with a grid mounted between them. The grid consists of a fairly coarse meshed structure of fine wires. When the filament is heated to incandescence by an electric current, it emits electrons which may be drawn to the plate by a battery connected through an external circuit between the plate and filament. The positive terminal of the battery must be connected to the plate.

Inasmuch as the electrons, to reach the plate, must pass through the meshes of the grid, the number arriving at the plate may be controlled by giving suitable potentials to the grid, and may be stopped entirely, if the grid is sufficiently negative. Inasmuch as the energy required to maintain a given potential on the grid is small, the device acts as an electrical throttle valve, whereby the available energy of the plate circuit battery may readily be controlled. Figure 120 of chap. XIV shows the relation which exists between the plate current and grid volts. The time required for an electron to traverse the distance from filament to plate depends upon the potential of the plate but is of the order of  $10^{-8}$  seconds. Changes in plate current accordingly follow changes in grid volts with remarkable swiftness.

There are many different circuits in which an electron tube may be used to generate sustained oscillations. Figure 90 shows one

of the simplest.  $F$ ,  $G$ , and  $P$  are the filament, grid and plate respectively. The filament is heated by the battery  $A$ , whose current is controlled by the rheostat  $R$ . The battery  $B$  furnishes the potential to draw the electrons from the filament to the plate. The inductance  $L$  and the condenser  $C$  form the oscillatory circuit. To understand the way in which oscillations are sustained, let us suppose that, by closing the switch  $S$ , the establishment of a current through the coil  $L$  has produced a transient

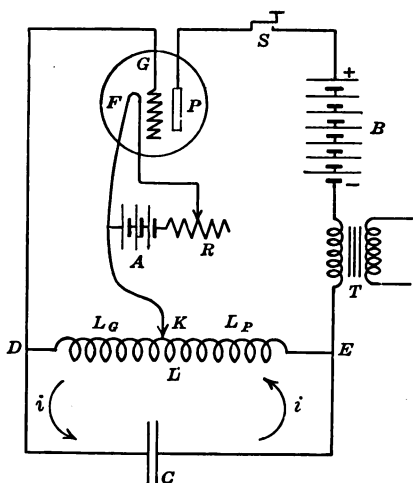


FIG. 90.—Electron tube oscillator.

oscillation in the circuit  $LC$ . This would quickly die out if energy were not supplied to it to compensate for the losses. Suppose that the oscillatory current through  $L$  is in the direction of the arrow and is rising. Due to the self inductance  $L$  there will be an E.M.F. in the coil in the direction  $DE$ . This lowers the potential of the grid with respect to the filament which thus decreases the plate current, flowing through the part  $L_p$ . This decrease in the plate current induces in  $L_p$  an E.M.F. which tends to keep the oscillatory current flowing. A continuation of this reasoning throughout the changes occurring during a complete cycle will show that the variations in plate current always induce in  $L_p$  an E.M.F. tending to drive the oscillatory current in  $L$  in the direction in which it happens to be flowing at any instant. The oscillations would increase indefinitely in amplitude were it not for the fact that the grid volt-plate current characteristic of the tube becomes horizontal at each end.

Frequencies ranging from 1 cycle to several millions per second may be obtained. Alternating current power for bridge work may be obtained either by placing another coil near  $L$  which then serves as the secondary of an air core transformer or by connecting the primary of a telephone transformer in the plate circuit as shown in the figure. The latter is to be preferred since variations in the load have a smaller disturbing effect upon



the frequency than is the case with the former arrangement. The wave form is not as free from harmonics as that obtained from a Vreeland oscillator, and a filter must be used in cases where extreme purity is essential.

DETECTING DEVICES

**122. Telephone Receiver.**<sup>1</sup>—The telephone receiver is one of the most generally useful of the various instruments for detecting the balance condition in a bridge circuit actuated by alternating currents. It consists essentially of a horseshoe magnet upon which is wound a pair of coils carrying the current to be detected, and a soft iron diaphragm mounted near the poles as shown in Fig. 91. The current through the coils magnetizes the core which attracts the diaphragm with a force proportional to the square of the induction produced. The sensitivity of the receiver is increased by using for the core, not a piece of soft iron, but a permanent magnet. The way in which this is brought about may be seen from the following consideration. Let  $B_0$  be the constant induction through the gap due to the permanent magnet, and let the additional induction which is proportional to the current  $i$  in the coils be  $k_1i$ . Then the total pull on the diaphragm is given by

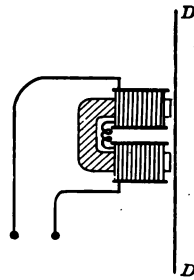


FIG. 91.—Telephone receiver.

$$\text{Pull} = k_2B^2 = k_2(B_0 + k_1i)^2 = k_2B_0^2 + 2k_1k_2B_0i + k_1^2k_2i^2$$

The first term represents the pull due to the permanent magnet alone, the second, that due to the current and magnet combined, while the third is that due to the current alone. If it is desired to have the motion of the diaphragm follow the variations in the current so that its motions may reproduce for the human ear the sound waves acting upon the diaphragm of a distant telephone transmitter, then the receiver must be so designed that the second term is large compared to the last which contains the square of the current. The first term need not be considered since it is independent of the current. The desired effect is attained by making  $B_0$  large compared to  $k_1i$ . Since  $B_0$  enters as a factor in the second term, making it large has the effect of

<sup>1</sup> MILLS, Radio Communication, p. 27.

increasing the motion of the diaphragm and hence of making the receiver, to a certain extent, an amplifying device.

If the third term is not negligible compared to the second, then, although there is a repetition with amplification there is also distortion since the pull which it defines is proportional to the square of the current. The nature of this distortion can be understood by supposing that the current is sinusoidal, e.g.,  $i = I \sin \omega t$ . The last term then becomes

$$k_2 k_1^2 I^2 \sin^2 \omega t = k_2 k_1^2 I^2 \frac{1 - \cos 2\omega t}{2}$$

and it is seen that the distorting pull is made up of two parts:

A constant part  $\frac{k_2 k_1^2 I^2}{2}$  which need not be considered and a pulsating part having twice the frequency of the phone current.

Since the diaphragm of the telephone receiver is an elastic body it will have a frequency of its own and will accordingly respond more vigorously to frequencies which correspond to its natural period, and another source of distortion is thus introduced. For bridge work, however, this fact may be utilized to increase the sensitivity by impressing upon the bridge the frequency to which the telephone resonates. Phones for this particular purpose are constructed in such a way that their resonance frequencies may be varied over a considerable range.

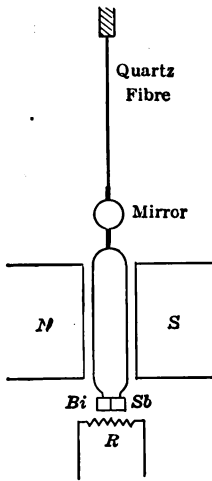


Fig. 92.—Duddell thermo-galvanometer.

**123. Thermo-galvanometer.**—The Duddell Thermo-galvanometer is an adaptation of the Boys' radio-micrometer for the purpose of measuring and detecting small alternating currents. The moving system, shown in Fig. 92, consists of a single turn of silver wire at the bottom of which is a tiny thermocouple of bismuth and antimony. The system is

suspended by means of a fine quartz fibre between the poles of a strong horseshoe magnet and carries a small mirror by means of which its deflections are read with a lamp and scale. Immediately below the thermo-junction is mounted a resistance unit through which the current to be measured is passed. The heat from this current is carried to the thermo-junction by convection

and radiation and causes a current to flow through the low resistance silver loop which is deflected by the electrodynamic action of the field. Since the heating effect is proportional to the square of the current while the thermal E.M.F., for small temperature differences, is proportional to the temperature, the indications of this instrument are roughly proportional to the square of the current.

Several heating units are provided with each instrument and range in value from 1 to 1,000 ohms according to the current sensitivity desired. For low resistances, they are made of fine wire bent back and forth but for the higher values, fine platinized quartz fibres are used. With the latter, current sensitivities of  $10^{-5}$  amperes are obtained. This type of instrument may be calibrated on direct currents and then used to measure alternating currents. Since it is practically free from inductance, the instrument may be used for the measurement of currents of very high frequencies. Because of the low resistance of the moving system it is critically damped electromagnetically, and is usually designed so as to have a period of from three to four seconds. Because of the delicacy of the quartz fibre suspension and the light silver loop, it is not a robust instrument and must be handled with caution. The heating elements are easily burned out and should always be protected by a high resistance which may be reduced to zero when it has been ascertained that safe limits of current will not be exceeded. Sudden changes in temperature cause the zero to drift and the instrument is usually enclosed in a tight wooden case.

**124. Vibration Galvanometer.**<sup>1</sup>—The vibration galvanometer is one of the most useful instruments available for the detection of minute alternating currents of commercial frequencies. To secure suitable sensitivity, advantage is taken of the principle of resonance. That is, the moving system is so adjusted mechanically, that its natural period coincides with that of the alternating current to be detected. Although the instrument shows very little response to direct currents or to alternating currents to which it is not tuned, nevertheless when resonance has been secured, a very appreciable vibration results. The vibrations are indicated by means of a small concave mirror carried on the moving system which focuses the image of an incandescent fila-

<sup>1</sup> LAWS, *Electrical Measurements*, p. 434.

WENNER, *Bull. U. S. Bureau of Standards*, vol. 6, 1909-10, p. 347.

ment on a ground glass scale. When the system vibrates, the image is drawn out into a broad band of light, while very slight motions are detected by a diminution in the sharpness of the line.

One of the chief reasons for the superiority of this instrument is the fact that its response is selective. In many measurements it is necessary to use a pure sine wave, a thing difficult to secure. Since vibration galvanometers may be made with a selectivity

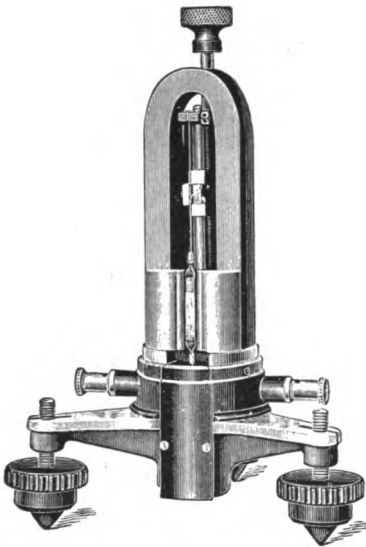


FIG. 93.—Leeds and Northrup vibration galvanometer.

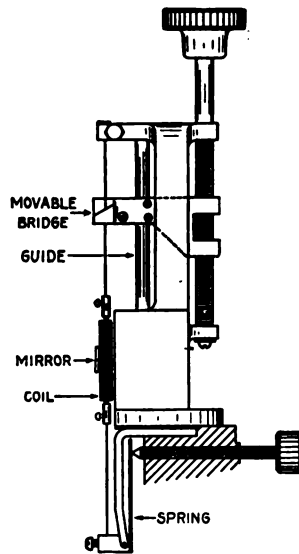


FIG. 94.—Tuning mechanism for Leeds and Northrup vibration galvanometer.

so high that their response to the third harmonic is  $\frac{1}{4,000}$  of that to the fundamental and to the fifth,  $\frac{1}{12,000}$ , impure waves may be employed with very little if any inaccuracy introduced. In fact an interrupter of the vibrating wire type described above, giving a square wave form, may be employed. The current sensitivity of the vibration galvanometer is about the same as that of a good telephone receiver—i.e.,  $10^{-6}$  amperes.

Obviously the instrument may be of either the D'Arsonval or the Thomson type. In Fig. 93 is shown one of the former, or moving coil instruments, while Fig. 94 shows how the moving

system is tuned. The coil is held in position by a taut phosphor-bronze ribbon, the effective length of which is varied by means of the movable bridge carried on the upper screw. By sliding this bridge up or down rough tuning is obtained while fine adjustments are secured by slightly changing the tension of the suspension by means of the lower screw and spring.

Figure 95 shows a Tinsley instrument of the moving magnet type. The vibrating system consists of a small permanent magnet mounted on a taut metallic ribbon behind which is held

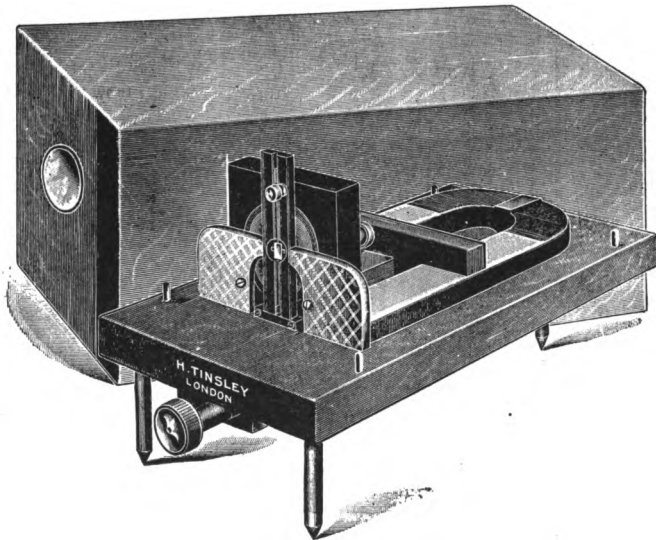


FIG. 95.—Tinsley vibration galvanometer.

the fixed deflecting coil. Specially shaped pole pieces concentrate the field of the large horseshoe magnet on the moving magnet. Since the period of the system is determined largely by the strength of this external field, tuning is obtained by changing this field. This is accomplished by moving the soft iron magnetic shunt along the horseshoe magnet. The milled head shown at the front of the base operates a worm gear which moves the shunt.

**125. Alternating Current Galvanometer.**—The alternating current galvanometer is one of the most sensitive devices available for detecting the balance condition in a bridge supplied with an alternating E.M.F. It is essentially a D'Arsonval galvanometer with the permanent magnet replaced by an electro-

magnet energized from the same A.C. source as that supplying the bridge. It operates upon the electro-dynamometer principle

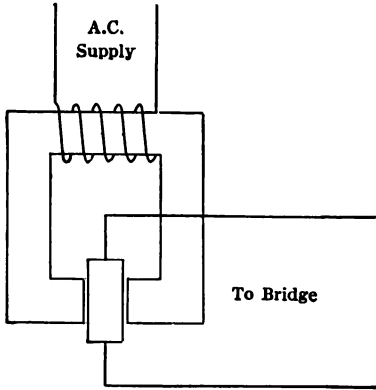


FIG. 96.—Alternating current galvanometer.

and the direction of the torque acting upon the moving coil is independent of the polarity of the supply. Its operation is complicated by the fact that, when connected to the bridge, there are present in the coil two currents, one due to the unbalanced condition of the bridge, and one induced by the alternating flux of the galvanometer field. Since the former is small and disappears at balance, the latter by far overpowers it and must either

be eliminated or made ineffective.

It may be shown in the following manner that when the current induced in the coil is  $90^\circ$  out of phase with the flux through it, the torque is zero.

Let  $\phi = \Phi \sin \omega t$  = instantaneous flux through the coil and  $i = I \sin(\omega t \pm \theta)$  instantaneous current in the coil.

The torque acting upon the coil in a given position at any instant is then

$$\tau = K\Phi \sin \omega t I \sin(\omega t \pm \theta)$$

where  $K$  is a constant depending upon the geometry of the instrument. The average value  $\bar{\tau}$  taken over the time  $T$  of one complete cycle is

$$\begin{aligned} \bar{\tau} &= \frac{K\Phi I}{T} \int_0^T \sin \omega t \sin(\omega t \pm \theta) dt \\ &= \frac{K\Phi I}{T} \int_0^T \sin \omega t (\sin \omega t \cos \theta \pm \cos \omega t \sin \theta) dt \\ &= \frac{K\Phi I}{T} \left[ \cos \theta \int_0^T \sin^2 \omega t dt \pm \sin \theta \int_0^T \sin \omega t \cos \omega t dt \right] \\ &= \frac{K\Phi I}{T} \left[ \cos \theta \int_0^T \frac{1 - \cos 2\omega t}{2} dt \pm \frac{\sin \theta \sin^2 \omega t}{2} \right]_0^T = \frac{K\Phi I}{2} \cos \theta \end{aligned}$$

The resultant torque on the coil is, accordingly, positive or

negative depending upon the sign of  $\theta$  and is zero for  $\theta = \pm \frac{\pi}{2}$ . Since the E.M.F. induced in the coil is  $90^\circ$  out of phase with the flux producing it, the condition stated above is equivalent to saying that the induced current must be in phase with the E.M.F. In other words, the bridge circuit to which the coil is connected must be nonreactive. In certain bridges such as those for comparing two condensers or two inductances this is obviously impossible. The required condition may, however, be met by shunting across the coil an appropriate variable reactance, e.g., an inductance with a variable series resistance in the former case, or a condenser and resistance in the latter.

When the galvanometer is first connected to the bridge, it will be found that, due to the action just described, the coil assumes a very rigid position, including either a maximum or a minimum amount of the field flux. If the former position results, a leading current through the coil is indicated, and a shunt with an inductive reactance must be applied. For satisfactory operation, a certain amount of stability is required to give a constant zero position, so inductive reactance across the coil should predominate. Since the reactance of the bridge is an important factor in determining the rest position of the coil, the galvanometer key must remain closed, and the balance established by opening and closing the supply circuit to the bridge.

The alternating current galvanometer has an important advantage over detecting devices such as the telephone or vibration galvanometer, in that it swings to the right or left according to the phase of the current at the galvanometer corners of the bridge while with the latter, no such effect is possible. Furthermore, if a direct current is supplied to the field, it becomes an ordinary D'Arsonval galvanometer and may be used to determine the steady state balance. Its sensitivity may be made 100 times that of the telephone or vibration galvanometer. It has, however, one distinct disadvantage, in that the deflection depends not only upon the field and current through the coil but also upon the phase angle between them. It can not therefore be calibrated to measure currents. Furthermore, zero deflection indicates either no current, or current  $90^\circ$  out of phase with the field. A simple test for the latter condition is to shift the phase of the field by inserting a resistance in series with the field coil.

## CHAPTER XII

### ALTERNATING CURRENT BRIDGES

**126. General Considerations.**—In order to obtain the reactive effect of an inductance or a capacitance it is necessary that the current through it should be variable. In the early bridge measurements for comparing inductances or capacitances and even for determining an inductance in terms of a capacitance the variable current was obtained simply by closing and opening the battery circuit leaving the galvanometer permanently connected to the bridge. The galvanometer employed was usually of the long period ballistic type. This procedure is open to two objections. First, the sensitivity thus realizable is not great and second it may lead to results which are appreciably different from the effective values of the condensers or coils when employed, as is usually the case, in circuits traversed by alternating currents. For example, the effective value of the self inductance of the primary of a transformer when an alternating current is flowing through it, depends upon the load across the secondary. If measured by the make and break method with a ballistic galvanometer as the detecting device, the result is the inductance of the primary alone independent of the effect of the secondary.

The ballistic galvanometer is an integrating instrument, and a zero deflection does not necessarily mean that no current has passed through it, but that equal and opposite quantities have traversed it. The bridge may have been out of balance each way during the time the current through it was changing. It is, accordingly, much better to use alternating currents through the bridge and employ a detecting device such as the telephone or vibration galvanometer, a zero indication of which indicates that at no time is there a current through it, and that the bridge is balanced at all times.

It will appear in the discussion which follows that, in order for a



bridge with reactive members to be balanced at all times, there are two conditions which must be satisfied. First, the bridge must be balanced for direct currents, "steady state balance," and second, it must be balanced for alternating currents, "variable state balance." These two balance conditions may be interpreted in the equation for the bridge in a simple manner. An expression is deduced, involving one current and its time derivative. The "steady state balance" means that the coefficient of the current term is zero. The "variable state balance" means that the coefficient of the term for the changing current, i.e., the time derivative, is zero. This applies to any bridge for which the balance condition may be reduced to an expression involving only one current and its first time derivative. Such a bridge balances independent of the frequency. If a second time derivative is involved, as, for example, in Trowbridge's bridge and the frequency bridge, the wave form of the current must be assumed, and the bridge no longer balances independent of the frequency. In some instances, the student will find it advantageous to obtain the former by the use of a battery and direct current galvanometer, and later apply an alternator and detector for the variable state balance. After becoming experienced in this type of work, however, both balances may be obtained simultaneously by the use of alternating currents.

**127. Maxwell's Bridge.**<sup>1</sup>—One of the simplest methods for determining an inductance in terms of a capacitance or vice versa is the method known as Maxwell's bridge. It consists of an ordinary Wheatstone's bridge with three non-inductive resistances  $R_1$ ,  $R_2$ , and  $R_3$ , as shown in Fig. 97, while the fourth arm contains the inductance  $L$  to be determined. Let the ohmic resistance of this coil be  $R_4$ . To offset the reactance of the coil  $L$ , a condenser  $C$  is placed across the opposite resistance  $R_1$ . When an alternating E.M.F. is applied to the bridge, the current in the upper half will lead the E.M.F., while that in the lower half lags behind it. Accordingly, if an A.C. galvanometer or other detecting device is connected ahead of the inductance and behind the condenser, the arms of the bridge may be so adjusted that the potential changes at  $D$  and  $E$  are

<sup>1</sup> MAXWELL, *Electricity and Magnetism*, vol. 2, p. 387.

not only equal but also in phase, and no indication of the instrument will result.

The conditions necessary for balance may be obtained in the following manner. Let the instantaneous currents through the various elements be designated as in the figure. By equating

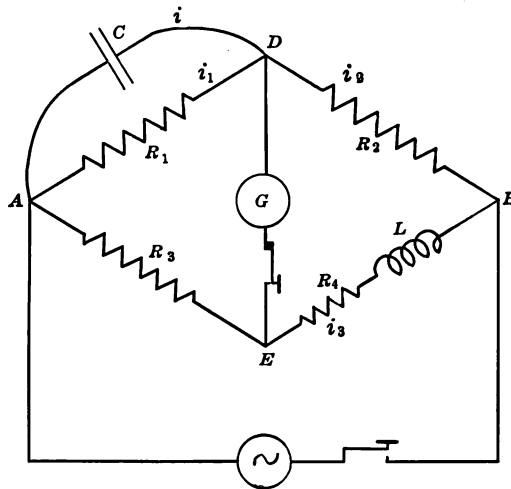


FIG. 97.—Maxwell's bridge.

the fall of potential from  $A$  to  $D$  to that from  $A$  to  $E$ , and the fall from  $D$  to  $B$  to that from  $E$  to  $B$  and noting that  $i_2$  is made up of  $i$  and  $i_1$  the following equations result.

$$i_2 = i_1 + i \quad (1)$$

$$R_1 i_1 = R_3 i_3 \quad (2)$$

$$R_2 i_2 = R_4 i_3 + L \frac{di_3}{dt} \quad (3)$$

$$R_1 i_1 = \frac{1}{C} \int i dt \quad (4)$$

We thus obtain four equations between the four currents. The currents may therefore be eliminated and the relations between  $L$ ,  $C$ , and the  $R$ 's obtained which are necessary for a balance. Eliminating  $i_2$  between eqs. (1) and (3) there results

$$R_4 i_3 + L \frac{di_3}{dt} = R_2 (i_1 + i) \quad (5)$$

Differentiating eq. (4) with respect to  $t$  and solving for  $i$ , also substituting the value of  $i_3$  from eq. (2) in eq. (5), we have

$$\frac{R_4 R_1}{R_3} i_1 + L \frac{R_1 di_1}{R_3 dt} = R_2 \left( i_1 + R_1 C \frac{di_1}{dt} \right) \quad (6)$$

If the bridge has first been balanced for the steady state,  $\frac{R_4 R_1}{R_3} = R_2$ , whence only the terms containing the derivative of  $i_1$  remain. The second condition for balance is obtained by equating the coefficients of the derivatives, whence

$$L = R_2 R_3 C \quad (7)$$

While the theory of this bridge is simple, its application in the laboratory is somewhat tedious in case both  $L$  and  $C$  are fixed. For example, suppose a steady state balance has been obtained, and it is attempted to satisfy eq. (7) by changing  $R_2$  or  $R_3$ . The steady state balance is immediately upset and must again be obtained before the test for the new value of  $R_2$  or  $R_3$  can be made. If  $L$  or  $C$  are continuously variable, eq. (7) may be satisfied without disturbing the steady state balance, and it is in this case that the bridge is particularly useful. An experienced observer however, quickly learns to make both balances simultaneously.

**128. Experiment 20.** *Maxwell's Bridge for Self Inductance.*—Make the connections as shown in Fig. 97 using for  $L$  a continuously variable inductance and for  $C$  a subdivided condenser. As a source of E.M.F., use an alternator giving a frequency from 500 to 1,000 cycles per second, and a pair of head phones as the detector. It may be well to use a battery and ordinary galvanometer to obtain the steady state balance. Connect double pole double throw switches so that each source and detector may be quickly exchanged. For the steady state balance, care must be taken to close the battery key before the galvanometer key. Obtain the variable state balance by changing  $L$ . If the balance does not lie within the range of  $L$ , change either  $C$  or one of the resistances of eq. (7). If the latter is done, a new steady state balance must be obtained.

**Report.**—Plot a calibration curve of  $L$  as a function of its scale readings. Define coefficient of self inductance. If a copper disk were held near the coil so that its face is perpendicular to the axis of the coil would the inductance as measured in this manner be changed? Explain.

**129. Anderson's Modification of Maxwell's Bridge.**<sup>1</sup>—It was pointed out above that the adjustments for balancing Maxwell's bridge are likely to be tedious because each attempt to obtain a variable state balance necessitates a redetermination of the steady state balance. Anderson has suggested a simple device by which the variable state balance may be obtained without destroying that for steady states. The connections are shown in Fig. 98. It will be noted that the condenser *C*, instead of being connected to the point *D* has the resistance *r*, placed in

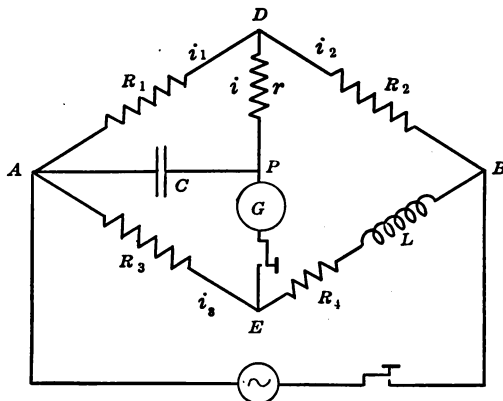


FIG. 98.—Anderson's modification of Maxwell's bridge.

series with it so that its time constant may be varied. Since, in determining the steady state balance, the condenser produces no effect, it may be left in circuit during that process, and the only change introduced is placing *r* in series with the galvanometer. This reduces slightly the sharpness of balance which is of little consequence. The steady state balance may accordingly be made once for all, and the variable state balance obtained by adjusting *r* to the proper value.

The determination of the balance condition is somewhat more complicated and is as follows: Let the instantaneous currents through the various elements of the bridge be designated as before. The points *P* and *E* are now the ones remaining at the same potential. Accordingly,

$$i_2 = i_1 + i \quad (1)$$

$$R_1 i_1 = \frac{1}{C} \int i dt + r i \quad (2)$$

<sup>1</sup> *Phil. Mag.*, vol. 31, 1891, p. 329.

$$\frac{1}{C} \int idt = R_3 i_3 \quad (3)$$

$$R_2 i_2 + ri = L \frac{di_3}{dt} + R_4 i_3 \quad (4)$$

Combining eqs. (1) and (3) with eq. (4), there results

$$R_2(i_1 + i) + ri = \frac{L}{R_3 C} i + \frac{R_4}{R_3 C} \int idt \quad (5)$$

Eliminating  $i_1$  between eqs. (2) and (5) we have

$$R_2 \left[ \frac{1}{R_1 C} \int idt + \frac{r}{R_1} i + i \right] + ri = \frac{L}{R_3 C} i + \frac{R_4}{R_3 C} \int idt \quad (6)$$

Imposing now the condition for the steady state balance, it is seen that the coefficients of the integrals are equal and eq. (6) then becomes

$$\frac{R_2 r}{R_1} + R_2 + r = \frac{L}{R_3 C} \quad (7)$$

Rearranging and using

$$\frac{R_1}{R_2} = \frac{R_3}{R_4}$$

$$L = C \left[ (R_3 + R_4) r + R_2 R_3 \right] \quad (8)$$

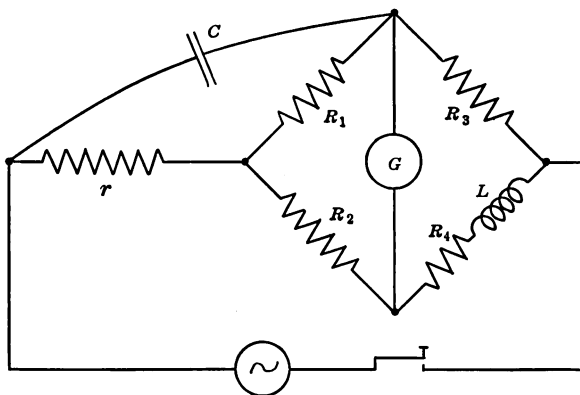


FIG. 99.—Stroude and Oates bridge.

Another change in the arrangement of this bridge has been suggested by Stroude and Oates<sup>1</sup> which is usually an advantage. The general theory of bridges shows that it is always possible to interchange the source of power and the detecting device. Figure 99 shows the connections when this has been done with a slight

<sup>1</sup> *Phil. Mag.*, vol. 6, 1903, p. 707.

change in the arrangement which improves the ease of manipulation. The principal advantage in this method lies in the fact that  $r$  is now in series with the bridge and a correspondingly higher E.M.F. may be used without injuring the resistances. An increase in sensitivity is thus secured. The same balance condition, eq. (8), applies.

**130. Experiment 21.** *Stroude and Oates Bridge for Self Inductance.*—Connect the apparatus as shown in Fig. 99. For power supply and detector use either an audio frequency generator and phones or city A.C. supply and alternating current galvanometer. The latter is particularly well adapted to this bridge. Arrange double pole double throw switches so that a direct current source and ordinary galvanometer may quickly be substituted for making the steady state balance.

As an unknown inductance, use two coils mounted in a fixed position close enough to one another so that mutual inductance exists between them. Measure the inductance of each separately, then connect them in series and measure the resultant inductance with the connections direct and reversed, that is with the mutual inductance first aiding and then opposing the self inductances. Calling  $L_1$  and  $L_2$  the self inductances of the individual coils, and  $L_a$  and  $L_o$  the two together when aiding and opposing respectively, the following equations hold

$$\begin{aligned} L_a &= L_1 + L_2 + 2M \\ L_o &= L_1 + L_2 - 2M \end{aligned} \quad (9)$$

**Report.**—Check your results by solving eq. (9) for  $M$ . Give a physical interpretation for eq. 9.

**131. Trowbridge's Method for Self Inductance.**—In Art. 141 there will be described a method by which an inductance may be measured in terms of capacitance using the two reactances in series in one arm of a bridge. While this arrangement admits of an exceedingly sharp adjustment, the bridge may be balanced for only one frequency for given values of  $L$  and  $C$ . In fact one of its most useful applications is the determination of frequency using reactances of known magnitudes. Trowbridge<sup>1</sup> has shown that if the reactances are shunted with properly chosen resistances the balance condition may be made independent of the frequency while sensitiveness of balance is very inappreciably sacrificed. Such an arrangement is shown in Fig. 100.

<sup>1</sup> *Phys. Rev.*, vol. 23, 1905, p. 475.

Let the currents be designated as indicated in the figure. Then putting, for the moment,  $R_4 = 0$ , the following equations must hold for the balance condition:

$$R_1 i_1 = R_2 i_2 \tag{1}$$

$$R_3 i_1 = R i_4 + r i_6 \tag{2}$$

$$R i_4 = r i_3 + L \frac{di_3}{dt} \tag{3}$$

$$r i_6 = \frac{1}{C} \int i_5 dt \tag{4}$$

$$i_2 = i_3 + i_4 \tag{5}$$

$$i_2 = i_5 + i_6 \tag{6}$$

For simplicity let  $R_1 = R_2$ , then  $i_1 = i_2$ .

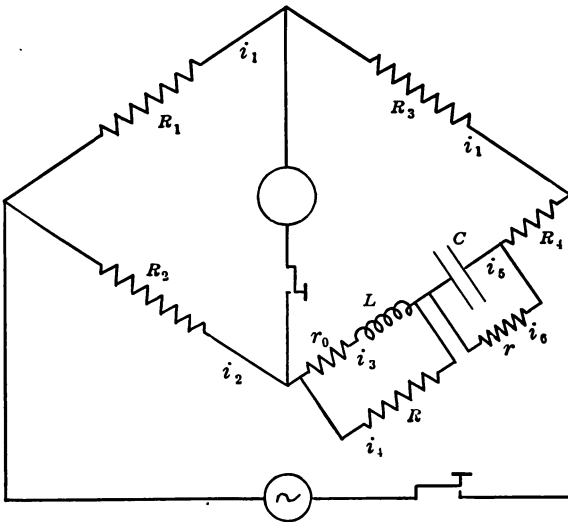


FIG. 100.—Trowbridge's method for self inductance.

Eliminating  $i_6$  between eqs. (2) and (6) we have

$$(R_3 - r) i_1 = R i_4 - r i_5 \tag{7}$$

Again eliminating  $i_6$  between eqs. (2) and (4) and substituting the value of  $i_5$  in eq. (7)

$$(R_3 - r) i_1 = R i_4 - r \left[ R_3 C \frac{di_1}{dt} - RC \frac{di_4}{dt} \right] \tag{8}$$

Substituting the values of  $i_1$  and  $i_4$  in terms of  $i_3$  obtained from eqs. (3) and (5), namely,

$$i_4 = \frac{r_0}{R} i_3 + \frac{L}{R} \frac{di_3}{dt}$$

$$i_1 = i_3 + i_4 = \left( \frac{R + r_0}{R} \right) i_3 + \frac{L}{R} \frac{di_3}{dt}$$

in eq. 8 there results

$$(R_3 - r) \left[ \frac{R + r_0}{R} i_3 + \frac{L}{R} \frac{di_3}{dt} \right] = r_0 i_3 + L \frac{di_3}{dt} - rR_3 C \left[ \frac{R + r_0}{R} \frac{di_3}{dt} + \frac{L}{R} \frac{d^2 i_3}{dt^2} \right] + rRC \left[ r_0 \frac{di_3}{dt} + \frac{L}{R} \frac{d^2 i_3}{dt^2} \right] \quad (9)$$

Collecting terms we have,

$$\left[ (R_3 - r) \frac{R + r_0}{R} - r_0 \right] i_3 + \left[ \frac{(R_3 - r)L}{R} - L + rR_3 C \frac{R + r_0}{R} - rR_0 C \right] \frac{di_3}{dt} + \left[ (R_3 - R) \frac{rCL}{R} \right] \frac{d^2 i_3}{dt^2} = 0 \quad (10)$$

Clearing of fractions,

$$[(R_3 - r)(R + r_0) - Rr_0] i_3 + [(R_3 - r - R)L + rR_3(R + r_0)C - Rr_0C] \frac{di_3}{dt} + (R_3 - R)rLC \frac{d^2 i_3}{dt^2} = 0 \quad (11)$$

Assuming now that  $i_3$  is an alternating current of the form

$$i_3 = I \sin \omega t$$

and substituting this in eq. (11) there results

$$[(R_3 - r)(R + r_0) - Rr_0] \sin \omega t + [(R_3 - r - R)L + rR_3(R + r_0)C - Rr_0C] I \omega \cos \omega t - (R_3 - R)rLC I \omega^2 \sin \omega t = 0 \quad (12)$$

In an ordinary measurement in which  $C$  is expressed in microfarads and  $L$  in millihenries the last term is of the order  $10^{-9}$  and may be neglected without appreciable error. Since eq. (12) holds for all values of  $t$ , we have

when  $t = 0$ ,

$$(R_3 - r - R)L + [rR_3(R + r_0) - Rr_0]C = 0$$

whence

$$L = \frac{[Rr_0 - (R + r_0)rR_3]C}{R_3 - R - r} \quad (13)$$

$$= \frac{[r_0(R - R_3) - RR_3r]C}{R_3 - R - r}$$

when

$$t = \frac{\pi}{2}, (R_3 - r)(R + r_0) - Rr_0 = 0 \quad (14)$$



which is seen to be the condition for a steady state balance. If  $R_3 = R$ , the last term of eq. (12) vanishes, and the expression given by eq. (13) is exact and reduces to

$$L = \frac{RR_3rC}{r} = RR_3C = R^2C \quad (15)$$

The bridge, when used in this manner, is well adapted to the standardization of a variable inductance such as Brooks inductometer but is not well suited to cases in which the values of  $L$  and  $C$  are fixed or variable by steps, since it is impossible to adjust for the variable state balance without upsetting that for steady states. The author has pointed out that this difficulty may be avoided by use of the resistance  $R_4$  as shown in the figure. If identical boxes are employed for  $r$  and  $R_4$  and a steady state balance obtained with  $R_4$  set at a suitable value, then the variable state balance may be obtained by shifting plugs from one box to the other, keeping  $r + R_4$  constant. If an equal arm bridge is used, this has the effect merely of adding to both the upper and lower right hand arms of the bridge the value of  $R_4$ . Eq. (13) then becomes

$$L = \frac{[rr_0(R - R_3 + R_4) - Rr(R_3 - R_4)]C}{R_3 - R_4 - R - r} \quad (16)$$

**132. Experiment 22.**—*Trowbridge's Method for Self Inductance.* Connect the apparatus as shown in Fig. 100 using the telephone and suitable oscillator for detector and energy source respectively. As an unknown use a smoothly variable inductance, and set the four resistances  $R_1$ ,  $R_2$ ,  $R_3$ , and  $R$  at suitable values, e.g., 500 ohms each.  $C$  should be a subdivided standard condenser. Measure the unknown for several settings and plot its calibration curve. Replace the variable inductance by one of fixed value, and measure it, making use of the resistance  $R_4$  as explained above.

**133. Heydweiller's<sup>1</sup> Network for Mutual Inductance.**—In Exp. 18, a method due to Carey-Foster, was used for the measurement of mutual inductance in terms of capacitance. The essential feature of this method consists in balancing the charge of a condenser against the quantity of electricity induced in the secondary of a mutual inductance when a certain current change takes place in the primary. This balance was effected by discharging the two quantities involved in opposite directions through a long period ballistic galvanometer. While this circuit is satisfactory

<sup>1</sup> *Annalen der Physik.*, vol. 53, 1894, p. 499.

when used with the make and break method of excitation, it can not be used with alternating currents since there is no way of adjusting the time constant of the condenser circuit.

This defect was overcome by Heydweiller by the introduction of the resistance  $S$  as shown in Fig. 101 and a very satisfactory method for the measurement of mutual inductance was thus obtained. The resistance  $P$  includes that of the secondary coil whose self inductance is  $L$ . The conditions which must hold

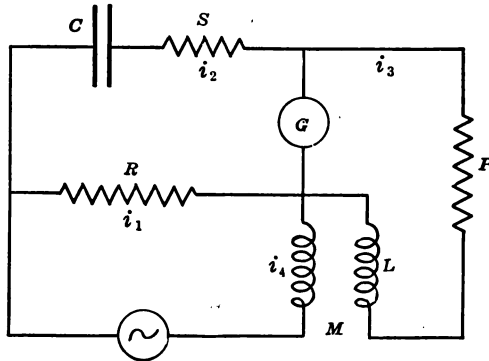


FIG. 101.—Heydweiller's network for mutual inductance.

for zero current through the galvanometer may be obtained as follows. Designating the instantaneous currents through the various resistances as indicated in the figure, we have

$$i_2 = i_3 \quad (1)$$

$$i_4 = i_3 + i_1 \quad (2)$$

$$Ri_1 = \frac{1}{C} \int i_2 dt + Si_2 \quad (3)$$

$$L \frac{di_3}{dt} + Pi_3 = M \frac{di_4}{dt} \quad (4)$$

From eqs. (2) and (4) we have

$$L \frac{di_3}{dt} + Pi_3 = M \left( \frac{di_3}{dt} + \frac{di_1}{dt} \right) \quad (5)$$

From eqs. (3) and (1)

$$i_1 = \frac{1}{RC} \int i_3 dt + \frac{S}{R} i_3 \quad (6)$$

Differentiating eq. (6) and substituting in eq. (5), there results, on collecting terms,

$$\left[ L - M \frac{(R+S)}{R} \right] \frac{di_3}{dt} + \left[ P - \frac{M}{RC} \right] i_3 = 0 \quad (7)$$

Since an alternating E.M.F. is applied to this circuit the current  $i_3$  is also alternating and may be represented by

$$i_3 = I \sin \omega t; \text{ whence } \frac{di_3}{dt} = I \omega \cos \omega t \quad (8)$$

Substituting these values in eq. (7) we have

$$\left[ L - M \frac{(R + S)}{R} \right] I \omega \cos \omega t + \left[ P - \frac{M}{RC} \right] I \sin \omega t = 0 \quad (9)$$

Since eq. (9) holds for all values of  $t$ , we have

when

$$\omega t = 0, L - M \frac{(R + S)}{R} = 0 \text{ or } M = L \frac{R}{R + S} \quad (10)$$

when

$$\omega t = \frac{\pi}{2}, P - \frac{M}{RC} = 0 \quad \text{or} \quad M = PRC$$

It is thus seen that there are two conditions which must be satisfied in order that there should be no deflection of the galvanometer, when an alternating E.M.F. is applied. The second of these is the same as for the original Carey-Foster circuit, which is obtained by putting  $S = 0$ . The impossibility of satisfying the first condition under these circumstances is obvious for then  $M = L$ , an inflexible condition, difficult to satisfy. This circuit, while not strictly a bridge, resembles one in that two balances conditions are necessary.

**134. Experiment 23.** *Heydweiller's Method for Mutual Inductance.*—Connect the apparatus as shown in Fig. 101. For  $M$  use a pair of coils whose relative positions may be varied, and for  $C$ , a subdivided standard condenser. The purpose of the experiment is to determine  $M$  as a function of the setting of the movable coil. As source and detector use either the wire interrupter and vibration galvanometer, or an alternator and telephone. From the known E.M.F. of the source, compute the minimum value of  $R$  in order that the power consumption in it should not exceed 4 watts per coil.

**Report.**—Plot  $M$  as a function of the scale readings of the instrument. In computing  $M$  use the second of eq. (10). Check the accuracy of your results by substituting in the first of these equations and note the constancy of the values for  $L$ . In connecting up the circuit is there any choice as to which coil is used as the primary? Does the mutual inductance of two coils depend upon which is the primary? Explain.

**135. Mutual Inductance by Heaviside's Bridge.**<sup>1</sup>—If one of the arms of a Wheatstone bridge is inductive while the other three are non-inductive it is impossible to obtain a balance since the E.M.F. across the inductive arm will have a component 90 deg. out of phase with the current through it, and the E.M.F.'s at the galvanometer corners of the bridge can never be in phase. It was pointed out by Hughes that if in series with the galvanometer there is connected the secondary of a variable mutual

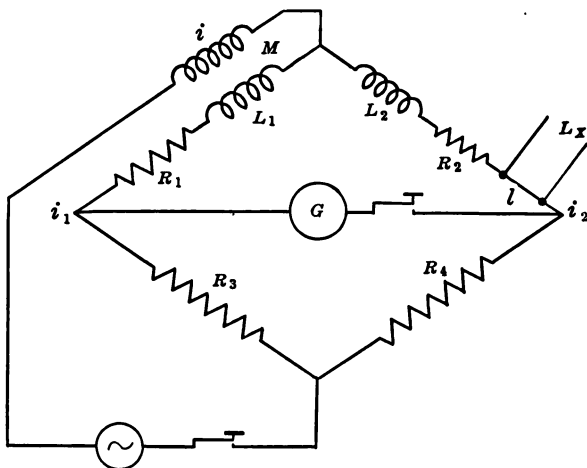


FIG. 102.—Heaviside's bridge for mutual inductance.

inductance, the primary of which is included in the supply circuit, an E.M.F. in quadrature with this current and hence opposite in phase to the E.M.F. due to the self inductance of the bridge coil may be obtained and a balance thus secured.

In discussing this circuit, Heaviside pointed out that a more satisfactory arrangement results if the secondary of the mutual inductance is introduced, not in the galvanometer circuit, but in the arm of the bridge adjacent to that containing the inductance under consideration. The E.M.F. thus induced in  $L_1$  by mutual inductance may be made to compensate the difference in the E.M.F.'s of self inductance in  $L_1$  and  $L_2$ . Such an arrangement is shown in Fig. 102. The balance condition is obtained as follows:

<sup>1</sup> *Phil. Mag.*, vol. 19, 1910, p. 497.

*The Electrician*, vol. 76, 1885-86, p. 489.

Designating by  $i$ ,  $i_1$ , and  $i_2$  the instantaneous supply and bridge currents respectively, the following equations result.

$$i = i_1 + i_2 \quad (1)$$

$$R_1 i_1 + L_1 \frac{di_1}{dt} + M \frac{di}{dt} = R_2 i_2 + L_2 \frac{di_2}{dt} \quad (2)$$

$$R_3 i_1 = R_4 i_2 \quad (3)$$

Eliminating  $i$  between eqs. (1) and (2), we have

$$R_1 i_1 + L_1 \frac{di_1}{dt} + M \left( \frac{di_1}{dt} + \frac{di_2}{dt} \right) = R_2 i_2 + L_2 \frac{di_2}{dt} \quad (4)$$

Substituting in eq. (4) the value of  $i_2$  from eq. (3)

$$R_1 i_1 + \left[ L_1 + M \left( 1 + \frac{R_3}{R_4} \right) \right] \frac{di_1}{dt} = \frac{R_2 R_3}{R_4} i_1 + L_2 \frac{R_3}{R_4} \frac{di_1}{dt} \quad (5)$$

Imposing now the condition for steady state balance, the terms in  $i_1$  vanish, whence

$$L_1 + M \left( 1 + \frac{R_3}{R_4} \right) = L_2 \frac{R_3}{R_4} \quad (6)$$

or

$$M(R_3 + R_4) = L_2 R_3 - L_1 R_4 \quad (7)$$

whence

$$M = \frac{L_2 R_3 - L_1 R_4}{R_3 + R_4} \quad (8)$$

If an equal arm bridge is used, i.e.,  $R_3 = R_4$

$$M = \frac{1}{2} [L_2 - L_1] \quad (9)$$

Campbell has suggested a simple modification of this bridge whereby self inductances may easily be measured in terms of mutual, provided a continuously variable standard of the latter is available. This inductance is introduced at  $l$ , shown short circuited by a link in the figure. A balance is first obtained with the link inserted. Let  $M_1$  be the reading of the variable standard for this setting. Introduce the unknown by removing the link and balance again varying  $R_1$  or  $R_2$  to compensate for the added resistance of the unknown coil. Let  $M_2$  be the new reading of the standard. Then, for an equal arm bridge,

$$\begin{aligned} M_1 &= \frac{1}{2}(L_2 - L_1) \\ M_2 &= \frac{1}{2}(L_2 - L_1 + L_x) \end{aligned}$$

whence

$$L_x = 2(M_2 - M_1) \quad (10)$$

where  $L_x$  is the unknown self inductance to be measured.

A further simplification results if  $L_2$  is a variable inductance, for then the first balance may be obtained by making  $M_1$  zero and adjusting  $L_2$  until it is equal to  $L_1$ . When a second balance has been obtained,  $L_2$  is simply twice the value of  $M$ . Neither  $L_1$  nor  $L_2$  need be known. This method is particularly useful where a number of inductances of the same order of magnitude are to be measured.

**136. Experiment 24. Heaviside's Bridge for Self Inductance.**—Connect the apparatus as shown in Fig. 102, using for  $M$  a variable standard of mutual inductance.  $L_2$  should be a continuously variable self inductance. As a detector, use phones, vibration or A.C. galvanometer with appropriate source. Measure a series of self inductances.

**Report.**—Is there any choice, in this bridge, as to which of the two coils of the mutual inductance is used as the primary? May the leads to the primary be interchanged at liberty? Could a variable state balance be obtained if the unknown were introduced in the arm  $R_4$ ? Explain.

**137. Maxwell's Bridge for Mutual Inductance.**<sup>1</sup>—The simplest, though not the most sensitive bridge for the measurement of mutual inductance is one devised by Maxwell. The method consists in obtaining the mutual inductance of a pair of coils in terms of the self inductance of one of them. The connections are shown in Fig. 103. In the discussion of the Heaviside bridge, Fig. 102, it was pointed out that a balance could be obtained by introducing in the coil  $L_1$  by mutual inductance an E.M.F. which would compensate for the difference in E.M.F.'s in the coils  $L_1$  and  $L_2$ . It might equally well have been said that the E.M.F. in the coil  $L_2$  balances the difference between the E.M.F. in  $L_1$  due to mutual and self inductance. If the relative values of the currents in the primary and secondary of  $M$  are changed these E.M.F.'s may be made equal without the use of the coil  $L_2$ . This is the method employed in the Maxwell bridge, and is accomplished by shunting the entire bridge by the resistance  $R$ .

Indicating the instantaneous currents as shown in the figure, the equations for the balance condition are as follows:

$$i = i_1 + i_2 + i_3 \quad (1)$$

$$R_3 i_2 = R_1 i_1 + L \frac{di_1}{dt} - M \frac{di}{dt} \quad (2)$$

$$R_2 i_1 = R_4 i_2 \quad (3)$$

$$R i_3 = (R_3 + R_4) i. \quad (4)$$

<sup>1</sup> MAXWELL, Electricity and Magnetism, vol. 2, p. 365.

Eliminating  $i$  between eqs. (1) and (2)

$$R_1 i_1 + L \frac{di_1}{dt} - M \left( \frac{di_1}{dt} + \frac{di_2}{dt} + \frac{di_3}{dt} \right) = R_3 i_2 \quad (5)$$

But, from eq. (3)

$$i_2 = \frac{R_2}{R_4} i_1$$

and, from eq. (4)

$$i_3 = \frac{R_3 + R_4}{R} i_2 = \frac{R_3 + R_4}{R} \cdot \frac{R_2}{R_4} i_1$$

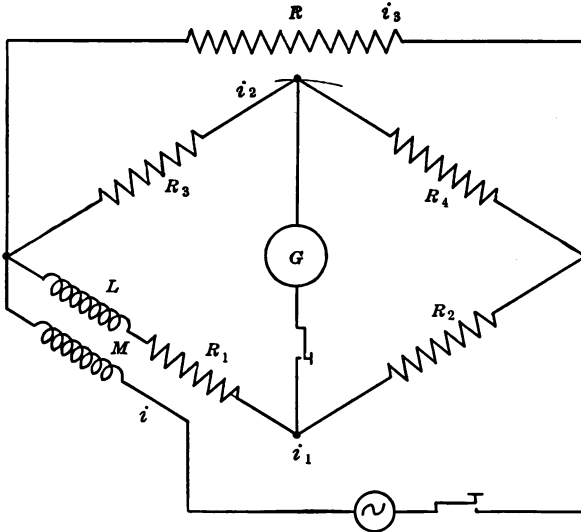


FIG. 103.—Maxwell's bridge for mutual inductance.

Substituting these values in eq. (5) there results

$$R_1 i_1 + L \frac{di_1}{dt} - M \left[ 1 + \frac{R_2}{R_4} + \frac{R_3 + R_4}{R} \cdot \frac{R_2}{R_4} \right] \frac{di_1}{dt} = \frac{R_3 R_2 i_1}{R_4} \quad (6)$$

Imposing the condition for a steady state balance, the terms in  $i_1$  vanish, and we have

$$M \left[ 1 + \frac{R_2}{R_4} + \frac{R_3 + R_4}{R} \cdot \frac{R_2}{R_4} \right] = L \quad (7)$$

Since

$$\frac{R_1}{R_2} = \frac{R_3}{R_4},$$

we have

$$\frac{R_3 + R_4}{R_4} = \frac{R_1 + R_2}{R_2}$$

and eq. (7) may be written

$$M \left[ 1 + \frac{R_2}{R_4} + \frac{R_1 + R_2}{R} \right] = L \quad (8)$$

**138. Experiment 25. Mutual Inductance in Terms of Self Inductance by Maxwell's Bridge.**—Connect the apparatus as shown in Fig. 103 using for  $M$  several pairs of coils with fixed mutual inductances. Operate the bridge either with phones, vibration or A.C. galvanometer, and appropriate source of supply. After the determination of  $M$  for each pair of coils, interchange primary and secondary and check your result.

**Report.**—Is the balance as sharply defined as in some of the bridges previously used? Explain. At the balance point, are the currents in  $R$  and  $R_1$  in phase?

**139. The Mutual Inductance Bridge.**—Figure 104 represents a bridge in which two coefficients of mutual inductance may readily be compared provided one of them is a variable standard. Designating the various parts of the bridge as indicated in the figure, the balance conditions are as follows:

$$R_1 i_1 + L_1 \frac{di_1}{dt} + M_1 \frac{di_1}{dt} = R_2 i_2 + L_2 \frac{di_2}{dt} + M_2 \frac{di_2}{dt} \quad (1)$$

$$R_3 i_1 - M_1 \frac{di_1}{dt} = R_2 i_2 - M_2 \frac{di_2}{dt} \quad (2)$$

Suppose that a variable state balance has been obtained with the secondaries disconnected and the galvanometer joined directly to the points  $A$  and  $B$ . This balance may be facilitated by the introduction of a variable inductance in series with either  $R_1$  or  $R_2$  as the case may require. Under these circumstances eqs. (1) and (2) become the same as those for the simple inductance bridge, namely

$$R_1 i + L_1 \frac{di_1}{dt} = R_2 i_2 + L_2 \frac{di_2}{dt} \quad (3)$$

and

$$R_3 i_1 = R_4 i_2 \quad (4)$$

whence

$$i_2 = \frac{R_3}{R_4} i_1 \quad (5)$$

and

$$\frac{di_2}{dt} = \frac{R_3}{R_4} \frac{di_1}{dt}$$



Substituting in eq. (3) we have

$$R_1 i_1 + L_1 \frac{di_1}{dt} = \frac{R_2 R_3 i_1}{R_5} + L_2 \frac{R_3}{R_4} \frac{di_1}{dt} \quad (6)$$

Imposing the steady state balance, we have

$$\frac{R_1}{R_2} = \frac{R_3}{R_4} \quad (7)$$

and

$$\frac{L_1}{L_2} = \frac{R_3}{R_4}$$

Introduce now the secondary coils as shown in the figure and obtain a balance by adjusting the variable standard. This balance indicates that the E.M.F.'s in the secondary coils are equal and opposite. Since no current flows in the secondary coils, the currents for the primaries which are defined by eqs. (3) and (4) are unchanged. Accordingly, the values for  $i_2$  and  $\frac{di_2}{dt}$  given in eq. (5) may be substituted in eq. (1). Subtracting eq. (3) from eq. (1) then gives

$$\frac{M_1}{M_2} = \frac{R_3}{R_4} \quad (8)$$

This bridge is distinguished from those previously studied in that three balances are necessary. This may seem at first sight to result in an unduly cumbersome method, but experience shows that in reality it is a relatively simple bridge to operate.

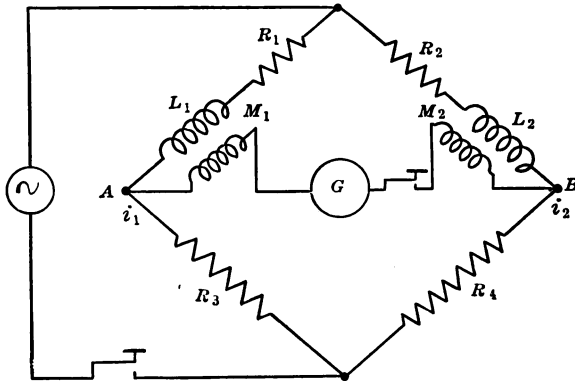


FIG. 104.—Mutual inductance bridge.

**140. Experiment 26.** *Comparison of Two Mutual Inductances.* Connect the apparatus as shown in Fig. 104, using a pair of phones and a suitable source of alternating current. Obtain the

three balance conditions as described above, for several different unknown pairs of coils. Check your results by interchanging primaries and secondaries for each pair.

**Report.**—Explain why it is permissible to introduce an extra inductance in series with  $R_1$  and  $R_2$ . Could this be introduced in  $R_3$  or  $R_4$ ?

**141. The Frequency Bridge.**—In all of the bridges thus far discussed, the balance condition has, in no case, contained a term

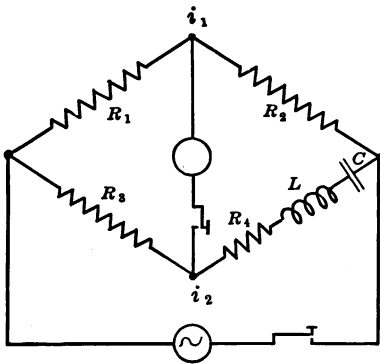


FIG. 105.—The frequency bridge.

depending upon the frequency. The physical significance of this is that these bridges balance independent of the frequency and hence the form of the impressed wave is of little consequence. A bridge will now be studied which, for given values of  $L$  and  $C$ , can be balanced for only one definite frequency. The connections are shown in Fig. 105. Three of the arms are non-reactive, while the

fourth contains an inductance and a condenser in series. Let the instantaneous currents through the upper and lower arms be  $i_1$  and  $i_2$  respectively. The balance conditions are then

$$R_1 i_1 = R_3 i_2 \tag{1}$$

$$R_4 i_2 + L \frac{di_2}{dt} + \frac{1}{C} \int i_2 dt = R_2 i_1 \tag{2}$$

Eliminating  $i_1$ , we have

$$R_4 i_2 + L \frac{di_2}{dt} + \frac{1}{C} \int i_2 dt = \frac{R_2 R_3}{R_1} i_2 \tag{3}$$

Imposing the steady state balance condition, which may be obtained by short circuiting  $C$ , in case a battery and ordinary galvanometer are used,

$$L \frac{di_2}{dt} + \frac{1}{C} \int i_2 dt = 0 \tag{4}$$

Assuming that a pure sine wave of E.M.F. is applied to the bridge, the current through it will also be a sine wave of the same frequency as the source. Let the current  $i_2$  then be given by

$$i_2 = I \sin \omega t$$

Then

$$\frac{di_2}{dt} = I\omega \cos \omega t, \text{ and } \int i_2 dt = -\frac{I}{\omega} \cos \omega t$$

Substituting these values in eq. (4), we have

$$LI\omega \cos \omega t - \frac{1}{C\omega} I \cos \omega t = 0 \quad (5)$$

whence

$$\omega = \frac{1}{\sqrt{LC}}$$

Since  $\omega = 2\pi n$ , where  $n$  is the frequency,

$$n = \frac{1}{2\pi\sqrt{LC}} \quad (6)$$

When two of these quantities are known, the third may be computed. One of the most useful applications of this bridge is the measurement of frequency using a subdivided condenser and a continuously variable inductance. In case a complex wave is applied to the bridge, complete silence in the phones can not be obtained for any value of the  $LC$  product. It will be observed however, that the relative intensities of the fundamental and overtones will be changed as  $L$  is varied and that for a certain setting, the fundamental will disappear while the overtones remain.

In Art. 110, it was pointed that a circuit connected for parallel resonance, possesses a very large impedance for the particular frequency to which it resonances. If now such a circuit is placed in series with the source, and adjusted to resonate to the frequency of the fundamental as above determined, this frequency may be suppressed and that of the strongest overtone measured. Introducing now another resonance circuit in series with the source to suppress this overtone, the next stronger one may be measured and so on. In this way a qualitative analysis of the wave form of the source may be made.

**142. Experiment 27. Bridge Method for Measuring Frequency.** Connect the apparatus as shown in Fig. 105, using for  $C$  a subdivided mica condenser, and for  $L$ , a variable standard of inductance. Determine the frequency of several sources of alternating current, using the phones as a detector. Determine first the fundamental and then place a filter circuit in series with the source to suppress this frequency and measure the frequency for the strongest harmonic. In computing the frequency by eq.

(6), the inductance and capacitance must be expressed in henries and farads respectively.

**Report.**—Compute a constant for the right-hand side of eq. (6) which, when divided by  $\sqrt{LC}$  will give the frequency when  $L$  is expressed in millihenries and  $C$  in microfarads. Compute the inductance, which, when used with a capacitance of 1 microfarad will balance the bridge for a frequency of 60 cycles.

**143. Circuits of Variable Impedance.**—In the bridges studied thus far for the measurement of self and mutual inductance, the assumption has tacitly been made that the only E.M.F.'s induced in the coils are those due to the primary current. For example,

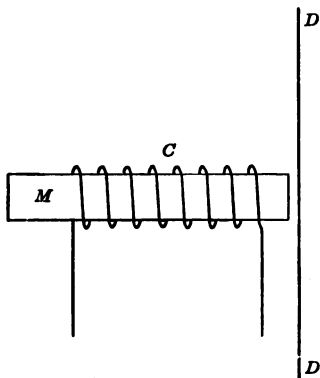


FIG. 106.—Simplified telephone receiver.

in the case of mutual inductance, a varying current in the primary produces an E.M.F. in the secondary proportional to the rate of change of the primary current hence in quadrature with the primary current for the case of a sine wave. For self inductance, the coil is its own secondary, and the same considerations hold as for two coils. The direction of the induced E.M.F. is counter to the driving E.M.F. while the current is rising, and in the same direction when it is falling. The power associated with the

induced E.M.F. at any instant is equal to the product of this E.M.F. and the current. Energy accordingly is alternately stored in the electromagnetic field of the coil and returned to the circuit. The theory shows, in fact, that this occurs at a frequency twice that of the driving E.M.F.

When the circuit is of such a nature that energy is consumed by the coil or parts connected with it in some other manner than by heat developed within the primary coil, the quadrature relationship is destroyed and the impedance of the coil is no longer constant. Among the more important causes of such extraneous energy consumption are hysteresis, eddy currents, and motion of parts. The telephone receiver is an illustration of such a circuit. For simplicity, consider a coil of wire  $C$  wound upon a bar magnet  $M$  near one end of which is placed a flexible iron diaphragm  $D$  as shown in Fig. 106. When an alternating current flows through

$C$ , the residual magnetism is alternately increased and decreased by the current and the diaphragm vibrates with the same frequency as the source. In addition to the Joule heat, represented by  $I^2R$ , developed in the coil, energy consumptions result from the three causes enumerated above in the following manner.

1. *Hysteresis*.—The E.M.F. induced in the coil is proportional to the rate of change of the magnetic flux through it. This flux is produced by the magnetomotive force of the coil, the latter being in phase with the current and proportional to it. Because of the hysteretic lag of flux behind the magnetomotive force, the E.M.F. is no longer in quadrature with the current but has a component counter to the current which results in a continuous energy consumption. The greater the area of the hysteresis loop, the greater the lag of flux behind the current and hence the larger the energy component of the induced E.M.F. The hysteresis loss is proportional to the frequency.

2. *Eddy Currents*.—The magnet  $M$  may be regarded as a secondary coil consisting of a single turn about its own axis having a relatively large cross section and a low resistance. The changing flux through this turn induces in it an E.M.F. in quadrature with the flux and the resulting current is known as a Foucault or eddy current. Because of the small self inductance of this single turn, the eddy current is practically in phase with the induced E.M.F. producing it. The eddy current may in turn be considered as a primary which induces in the coil a quadrature E.M.F. Except for the hysteresis lag, this final E.M.F. in  $C$  is counter to the current because of the double quadrature relationship, and hence introduces a large energy consumption. Viewed from the standpoint of Joule heat developed in the core by the eddy current, this loss is proportional to the square of the frequency, for the induced E.M.F. producing the eddy current is proportional to the frequency and the heating effect of a current is equal to the square of the E.M.F. divided by the resistance.

3. *Motion of the Diaphragm*.—The effect of motion of the diaphragm may be understood by the following considerations. Suppose a sound wave strikes the diaphragm. The varying air pressures cause it to vibrate and in so doing, the air gap between it and the magnet is changed and hence the reluctance of the magnetic circuit of the magnet. This introduces a change in flux through the coil which induces an E.M.F. within it. In

fact this is the principle of the "magneto-phone" which is often employed where accurate reproduction is more essential than energy delivered. As regards the magnitude of the E.M.F. induced in the coil and the phase relation between it and the motion of the diaphragm, it makes no difference whether the motion is produced by a sound wave or by a current through  $C$ . In the latter case, the energy of the wave must be supplied by the current, and the law of conservation of energy requires that the induced E.M.F. due to the motion of the diaphragm must have a component counter to the current to account for this consumption.

If an alternating current of intensity  $I$  is passed through the coil, and the power delivered to the coil is measured by appropriate means, it is found that this is much larger than would be computed from  $I^2R$  when  $R$  is determined by using direct current. On the other hand we may define a resistance  $R_e$  such that

$$\text{Watts} = I^2R_e.$$

$R_e$  is called the "effective" resistance of the coil. It is the resistance of a fictitious coil, free from hysteresis, eddy-current and motional reactions, which consumes the same power with a given current. Again the effective resistance may be written

$$R_e = R + R_H + R_E + R_M$$

where the last three terms represent the parts contributed by hysteresis, eddy currents and diaphragm motion respectively, and, it is customary to speak of the resistance due to hysteresis, eddy currents, etc. In a similar manner, the E.M.F.'s induced in the coil by hysteresis, eddy currents and motion will have components in quadrature with the current, and will change the apparent inductance of the coil, and it is customary, in an analogous manner, to speak of the inductance due to hysteresis, eddy currents, etc.

Kennelly and Pierce<sup>1</sup> have made a detailed study of the motional characteristics of telephone receivers and have shown how their performance in practice may be predetermined from simple measurements. The receiver to be studied was placed in one of the arms of an inductance bridge and its effective resistance and inductance measured for a wide range of frequencies, first with the diaphragm clamped, and again when free to move.

<sup>1</sup> *Proc. Am. Acad. of Sci.*, vol. 48, p. 131, 1912.

The difference between the corresponding values for the same frequency were called "motional resistance" and "motional inductance" respectively. The latter when multiplied by the frequency for which they were determined, gave the "motional reactance" for that frequency. Interesting results were obtained for frequencies near that corresponding to the natural period of the diaphragm. For example, the curve showing the motional resistance as a function of the frequency closely resembles, near the resonance frequency, the curve in optics, showing the variation of the index of refraction with frequency in the neighborhood of an absorption band, while that for motional reactance exhibits a sharp minimum at this point.

**144. Experiment 28.** *Motional Impedance of a Telephone Receiver.*—Connect the apparatus as shown in Fig. 64 substituting for  $L_x$  the receiver to be studied. Use an equal arm bridge making  $R_1$  and  $R_2$  approximately equal to the direct current resistance of the receiver. Energize the bridge with a Vreeland oscillator which has previously been calibrated for frequency, and use a pair of head phones as a detector. Place an electrostatic voltmeter across the output coil of the oscillator and maintain a constant voltage on the bridge throughout the experiment. Determine roughly the natural period of the diaphragm of the receiver by varying the frequency of the oscillator keeping the voltage approximately constant by noting at what frequency the response is loudest. Introduce a small wedge between the diaphragm and the cap to prevent motion and measure the resistance and inductance for a range of frequencies above and below the resonance frequency. Remove the wedge and repeat with the diaphragm moving.

**Report.**—Plot curves showing the variation of resistance and reactance with frequency for both blocked and moving diaphragm. Subtract the former from the latter and thus obtain the "motional" resistance and reactance and plot each as a function of frequency.

**145. Power Factor and Capacity of Condensers.**<sup>1</sup>—In a perfect condenser, that is, one without absorption or leakage, the phase of the current is  $90^\circ$  ahead of the E.M.F. impressed across its terminals. Although many condensers approximate the ideal, it is only with well insulated air condensers that this condition may

<sup>1</sup> GROVER, Bull. U. S. Bureau of Standards, vol. 3, 1907, p. 371.

WIEN, *Wiedemann's Annalen*, vol. 44, 1891, p. 689.

be regarded as actually realized. In condensers having a dielectric made of paper impregnated with paraffine or beeswax there is an appreciable component of the current in phase with the E.M.F. In such a condenser there is a measurable amount of energy absorption which appears as heat in the dielectric, and as far as phase relations are concerned, it may be regarded as a perfect condenser with a small fictitious resistance in series with it. In Fig. 107*a*, let  $C$  represent the equivalent perfect condenser, and  $\rho$  the fictitious series resistance. The vector diagram 107*b* represents the phase relations for such a circuit.  $OE$  is the

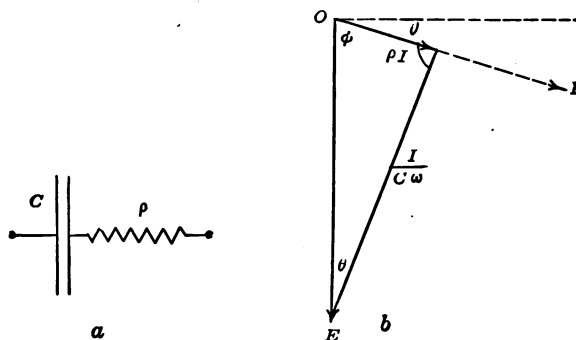


FIG. 107.—Phase diagram for a condenser.

impressed E.M.F. and  $OI$  the current which falls short of the  $90^\circ$  lead by the angle  $\theta$  which is designated as the phase difference of the condenser.  $\phi$  is the phase angle as ordinarily defined and the power factor is then

$$\text{P.F.} = \cos \phi = \sin \theta.$$

It is obvious from the figure that

$$\tan \theta = \rho C \omega \quad (1)$$

A simple bridge method has been devised by Wein by which both the capacitance and the power factor of an imperfect condenser may be simultaneously measured provided there is available for comparison purposes another condenser which shows no absorption. Such a bridge is illustrated in Fig. 108, where  $C_1$  is the perfect condenser and  $C_2$  the one with fictitious resistance  $\rho$  to be studied. In series with these condensers are placed the small finely adjustable resistances  $r_1$  and  $r_2$ . The purpose of these is to bring about equality of phase in the currents through the upper and lower branches of the bridge. It is clear that,



without them, if one of the condensers possesses an equivalent resistance while the other does not, the potential differences from *D* to *B* and *E* to *B* can not be equal and in phase at the same time. Accordingly a perfect balance of the bridge can not be obtained. If, however, a suitable resistance  $r_1$  is introduced in series with  $C_1$  of such a value that the time constant of the arm *DB* equals that of *EB*, this difficulty is obviated. In practice it is generally more convenient to introduce  $r_2$  also and take account of it in deducing the balance conditions.

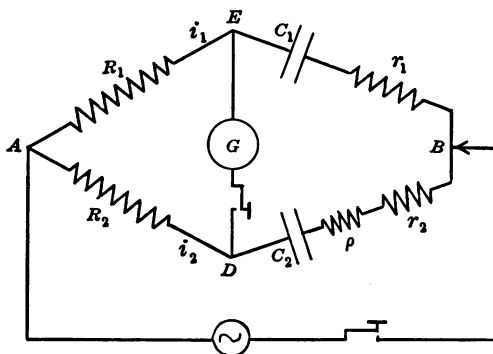


FIG. 108.—Bridge for measuring phase difference of a condenser.

The equations for balance may be derived in the following manner, calling  $i_1$  and  $i_2$  the instantaneous currents in the upper and lower arms respectively.

$$R_1 i_1 = R_2 i_2 \tag{2}$$

$$\frac{1}{C_1} \int i_1 dt + r_1 i_1 = \frac{1}{C_2} \int i_2 dt + (\rho + r_2) i_2 \tag{3}$$

Eliminating  $i_2$  we have

$$\frac{1}{C_1} \int i_1 dt + r_1 i_1 = \frac{R_1}{R_2} \frac{1}{C_2} \int i_1 dt + (\rho + r_2) \frac{R_1}{R_2} i_1 \tag{4}$$

Imposing the condition for a steady balance, namely

$$\frac{R_1}{R_2} = \frac{r_1}{r_2 + \rho} \tag{5}$$

there results

$$\frac{C_1}{C_2} = \frac{R_2}{R_1} \tag{6}$$

The phase difference  $\theta$  may be obtained as follows:

Combining eqs. (5) and (6) we have

$$\frac{C_1}{C_2} = \frac{r_2 + \rho}{r_1} \quad (7)$$

Multiplying numerator and denominator on the left by  $\omega$  and clearing of fractions, there results

$$C_1\omega r_1 = C_2\omega(r_2 + \rho) \quad (8)$$

Referring to Fig. 107*b* and solving eq. (8)

$$\tan \theta = C_2\omega\rho = C_1\omega r_1 - C_2\omega r_2 \quad (9)$$

**146. Experiment 29. Measurement of Phase Difference and Capacitance of a Condenser.**—Connect the apparatus as shown in Fig. 108.  $C_1$  is a standard mica condenser whose phase difference is regarded as negligible, and  $C_2$  is a telephone condenser with paraffine paper dielectric whose phase difference and capacitance are to be determined as a function of the frequency. The resistances  $r_1$  and  $r_2$  are small in value and should be joined by a slide wire for fine adjustment. As a source of power use an oscillator giving a pure wave form whose frequency may be varied over a considerable range, such as the Vreeland, with phones as detector. In obtaining a balance, set  $r_2 = 0$  and get as good silence as possible. Introduce such a value of  $r_1$  as makes the best improvement, then change  $R_1$  or  $R_2$  and again adjust  $r_1$  and so on until complete silence is reached. Keep  $r_2$  as small as possible. Make a series of balances using as wide a range of frequencies as may be obtained from the oscillator.

**Report.**—Plot capacity and phase difference of the unknown condenser as a function of the frequency. Show that in a perfect condenser the current leads the E.M.F. by  $90^\circ$ . Define *Power Factor*.

**147. Resistance of Electrolytes.**—The measurement of the resistance of an electrolyte offers special difficulties not encountered in determining the resistance of metallic conductors. This is due to the fact that current is carried through a solution by virtue of the migration of ions, a double procession in opposite directions. These are deposited on the electrodes, where secondary chemical reactions often take place. In general, the deposits on the electrodes set up counter E.M.F.'s in the cell which affect the measurements in the same manner as added resistance. Obviously then an electrolytic resistance can not be measured by a Wheatstone bridge employing direct currents.

If an alternating current is used this effect is eliminated since the counter E.M.F. is with the bridge current during one half of the cycle and opposite to it during the other.

In case an electrolyte is measured in which a gas is formed at one of the electrodes a further complication is introduced since the cell behaves as though it contains capacitance. This results from the fact that a gas layer separates the liquid from the electrode thus forming a condenser. Since the gas layer is, in general, very thin, a capacitance of considerable magnitude may

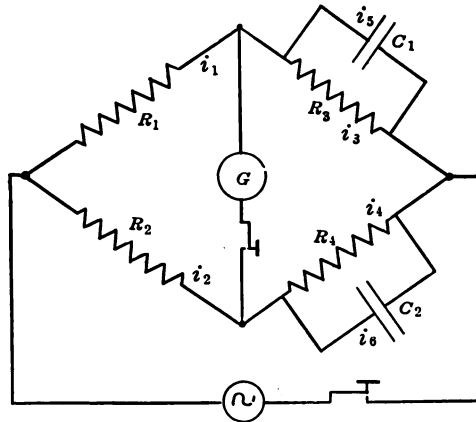


FIG. 109.—Bridge for electrolytic resistance.

result. The cell then behaves like a condenser and resistance in parallel, and it must be so regarded when connected in one of the arms of a bridge. The resistance in the adjacent bridge arm must also be shunted by a condenser else a balance can not be obtained. Such a bridge is shown in Fig. 109, where  $R_4$  and  $C_2$  represent the resistance and capacitance of the electrolytic cell, and  $R_3$  and  $C_1$  its counterpart in the adjacent arm. Designating the currents as indicated in the figure, we have

$$i_1 = i_3 + i_5 \tag{1}$$

$$i_2 = i_4 + i_6 \tag{2}$$

$$R_1 i_1 = R_2 i_2 \tag{3}$$

$$R_3 i_3 = R_4 i_4 \tag{4}$$

$$\frac{1}{C_1} \int i_5 dt = R_3 i_3 \tag{5}$$

$$\frac{1}{C_2} \int i_6 dt = R_4 i_4 \tag{6}$$

Eliminating  $i_5$  between eqs. (1) and (5) and  $i_6$  between eqs. (2) and (6) there results

$$i_1 = i_3 + C_1 R_3 \frac{di_3}{dt} \quad (7)$$

$$i_2 = i_4 + C_2 R_4 \frac{di_4}{dt} \quad (8)$$

Substituting in eq. (8) the values of  $i_2$  and  $i_4$  from eqs. (3) and (4) and eliminating  $i_1$  between the resulting equation and eq. (7) we have

$$i_3 + C_1 R_3 \frac{di_3}{dt} = \frac{R_2}{R_1} \cdot \frac{R_3}{R_4} i_3 + C_2 R_3 \frac{R_2 di_3}{R_1 dt} \quad (9)$$

Imposing now the condition for steady state balance, *i.e.*,

$$\frac{R_1}{R_2} = \frac{R_3}{R_4} \quad (10)$$

we have

$$\frac{C_1}{C_2} = \frac{R_2}{R_1} \quad (11)$$

In carrying out measurements of the resistance of solutions, the design of the electrolytic cell is a matter of considerable

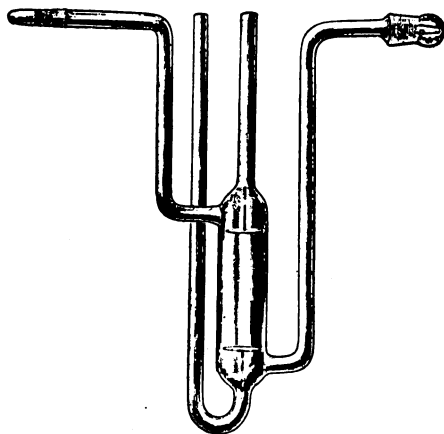


FIG. 110.—Cell for measurement of electrolytic resistance.

importance. It has been found that different electrolytes require different types of cells and even for the same electrolyte a given cell is not always suited to wide ranges of concentration. For example, polarization may occur in some cases unless the electrodes are platinized, and in other cases platinized electrodes

appear to act catalytically and assist chemical action. Again platinized electrodes may, because of their spongy nature, absorb so much of the electrolyte as to cause errors in measurement when used later with solutions of a different nature or concentration.

Figure 110 shows a cell designed by Dr. Washburn and manufactured by the Leeds and Northrup Co. The electrodes are of platinum and are mounted by sealing their supporting wires into tubular glass stems. These wires project through the seals and connections with them are made by filling the stems with mercury. Side tubes, above and below the electrodes respectively, are attached for filling and washing out the cell. These tubes are bent so as to form supports for holding the cell in a suitable bath for maintaining a constant temperature.

**148. Experiment 30. Resistance of Electrolytes.**—Connect the apparatus as shown in Fig. 109, placing the solution in a cell specially designed for the purpose. Energize the bridge with the Vreeland oscillator and detect the balance with a telephone receiver. Determine the resistance of a series of solutions furnished by the instructor. Measure the dimensions of the cell and the distance between electrodes and compute the specific resistance of each solution.

**Report.**—Explain why a bridge can not be balanced using direct currents when it contains an electrolytic cell. What is the essential difference between metallic and electrolytic conduction?

## CHAPTER XIII

### CONDUCTION OF ELECTRICITY THROUGH GASES<sup>1</sup>

**149. Electrons.**—When a high tension discharge passes between electrodes sealed into a partially evacuated vessel, the gas becomes luminous showing a series of highly colored glows which are often very beautiful. If the pressure is sufficiently reduced, a series of streams appears, proceeding in straight lines from the cathode. These streams are known as “cathode rays,” and are found to be independent of the position of the anode, and often penetrate regions occupied by other glows in the tube.

The researches of modern physics have shown that these rays are streams of discreet particles of negative electricity, called “electrons.” Their properties do not depend upon the material of the electrodes nor the nature or presence of the gas through which the discharge takes place. They may be produced from all chemical substances, and consequently must play an important part in the structure of matter. The velocities with which they move through the tube vary from one-thirtieth to one-third that of light. The ratio of the charge of an electron to its mass is constant and is equal to  $1.77 \times 10^7$  electromagnetic units per gram. The charge of an electron is  $1.5 \times 10^{-20}$  electromagnetic units and the mass is about  $\frac{1}{1,800}$  that of the hydrogen atom. The radius of an electron is estimated, at  $1.9 \times 10^{-13}$  cms., which is about  $\frac{1}{50,000}$  that of the atom. For many years the mass has been regarded as purely electromagnetic in character; that is, while exhibiting inertia, it shows no gravitational attraction in the sense possessed by ordinary matter. Recently, however, certain experimental and theoretical evidence has been produced which makes it appear likely that this cannot be entirely the case.

<sup>1</sup> CROWTHER, Ions, Electrons and Ionizing Radiations.

McCLUNG, Conduction of Electricity through Gases and Radioactivity.

MILLIKIN, The Electron.

THOMSON, Discharge of Electricity through Gases.

TOWNSEND, Electricity in Gases.

Many attempts have been made to discover evidence of quantities of electricity smaller or larger than the electron, but none smaller have ever been found. In fact, when quantities comparable to the electron have been isolated, they have always proved to be exact integral multiples of it. The evidence points to the conclusion that electricity is atomic in structure and that the smallest possible element is the electron, which thus constitutes our natural unit of electricity. Electric currents through conductors, as we know them in every day practice, are simply streams of electrons through or between the atoms and molecules making up the conducting body.

**150. Conductivity of Gases.**—A gas in its normal state is one of the best insulators known. This may be shown by mounting a gold leaf electroscope inside an inclosed space, and allowing only a small rod carrying a polished knob, for the purpose of charging, to project out. If the support carrying the electroscope is well insulated from the container, the electroscope will remain charged for a long time, showing that the air or whatever gas surrounds the electroscope is a poor conductor of electricity.

If, however, X-rays are allowed to shine through the enclosure, or if a small quantity of some radio-active substance such as thorium or radium is placed inside it, or again if the products of combustion of a flame are drawn through it, it is then found that the gold leaves collapse quite rapidly, indicating that the gas has lost its insulating properties. That the leakage has taken place through the air and not across the insulating support may be shown by using a second chamber connected with the electrometer enclosure by a glass tube, and introducing the X-rays, the radio active substance or other agent into this, and then drawing the air thus acted upon into the first chamber. The same effects are observed. However, if glass wool is introduced in the connecting tube, or if the air is passed between two insulated plates connected to a battery before entering the electrometer chamber, it is found that its insulating properties are restored. Experiments of this sort as well as many others of an entirely different nature have shown that the conduction of electricity through gases is due to carriers of electricity, and that the carriers are of two distinct types, positive and negative; the former are similar to the carriers of electricity through solutions and are called positive ions, while the latter are either negative ions or electrons.

**151. Structure of the Atom.**—To explain the phenomena of the conductivity of gases, it is necessary first to make a brief statement concerning the structure of the atom. While our knowledge is far from complete, it is well established that the atom consists of a nucleus of positive electricity, about which revolve in closed orbits, electrons, in much the same way that the planets revolve about the sun, and that the relative dimensions of electrons, nucleus and orbits are about the same as in the solar system. The number of electrons present in a given atom has been estimated in various ways, and while the results are not entirely in agreement, it is probable that it is the same as the atomic number, that is, its number in the list of elements arranged in order of ascending atomic weights. The atomic number, except for the case of hydrogen, is approximately half its atomic weight. Since the atom as a whole is neutral, it is necessary that the positive nucleus should have a charge equal to  $ne$ , where  $e$  is the charge of the electron and  $n$  the number of electrons. The shape of the orbits, the law of force between nucleus and electron, and even the conditions of stability are problems which have not yet been solved, but are now being attacked from many angles.

When external agencies such as X-rays, ultra violet light, radiations from radio active materials, etc., act upon a gas, it is found that the atomic structure is broken up. One or more electrons may be torn away from the system leaving it with an excess of positive electricity. We thus have present in the gas positive ions and negative electrons. The gas is then said to be ionized, and the means by which this condition is brought about is called the "ionizing agent." If two electrodes are introduced, and a difference of potential is maintained between them, the electrons move to the positive electrode, and, entering it, pass on through the external metallic circuit. The positive ions, on the other hand, move to the negative electrode and receive electrons from it, thus becoming again neutral molecules. Unless an ionizing agent acts continuously, the current through the circuit will persist only until the ions and electrons have been removed from the gas.

**152. The Ionization Current.**—Suppose now that an ionizing agent is acting continuously upon a gas in an ionization chamber, as an arrangement such as that just described is called. At first it might be supposed that if the agent acts long enough all of



the atoms would be ionized. This, however, is not the case; for, due to their undirected heat motion, ions and electrons collide, and recombine. When the rate of recombination is equal to that of ionization, a steady state is reached where only a definite fraction, usually a very small number, of the total number of molecules are in the ionized state. If the difference of potential between the plates is varied, and the current between them is measured and plotted as a function of voltage, it is found that the current increases with the voltage almost linearly at first, in accordance with Ohm's law; but for higher voltages, the curve is concave downward and when a certain voltage has been reached, no further increase in current can be obtained, unless the voltage is raised to very large values. The constancy of the current is due to the fact that all of the ions and electrons produced are swept out by the field. This current is spoken of as the "saturation current," from the similarity between the shape of this curve and the magnetization curve for iron. The voltage at which the horizontal part of the curve begins is called the "saturation voltage."

If the distance between the electrodes is increased, it might, by analogy with metallic conductors, be thought that the saturation current would be reduced because of the increased path the ions and electrons must travel. It is found, however, that the current is actually increased. This is because there is a larger number of gas molecules subjected to the action of the ionizing agent, and hence more carriers are produced. Again, it is found that if the pressure of the gas is increased, the ionization current is increased. Both of these facts show that the saturation current through a gas is proportional to the mass of the gas between the electrodes.

**153. Ionization by Collision.**—If the voltage between the plates of the ionization chamber is increased to sufficiently large values, the saturation current does not remain constant indefinitely, for fields may be reached at which the current again begins to rise, slowly at first and then very rapidly, finally resulting in a disruptive spark accompanied by the passage of a current of considerable magnitude. The field required for this increased current depends upon the distance between electrodes, their size and shape, and the nature and pressure of the gas. For air at atmospheric pressure and spherical electrodes of moderate dimensions, e.g., 1 cm. diameter, it is of the order of 10,000 volts per

centimeter. It diminishes, however, as the pressure is reduced, and is most conveniently studied at pressures below 10 millimeters of mercury.

This increase in current is due to the fact that ions are produced by collisions taking place between neutral molecules and ions as well as electrons already existing in the gas. The mechanism of this process is somewhat obscure, but it is clear that a definite amount of energy is required to disrupt a neutral atom. The kinetic energy of motion of the ions and electrons depends upon how far they have moved under the accelerating field before being stopped in the same way that the energy of motion of a freely falling body depends upon the distance through which it has fallen before being arrested. Thus, as the pressure of the gas is reduced, the average length of free travel is greater and the acquired energy available for ionizing purposes is increased. The conductivity of a gas therefore increases as the pressure is reduced. Since, however, the conductivity depends upon carriers which come originally from neutral molecules, the conductivity can not increase indefinitely with decrease of pressure, for the effect of the decreased available supply will eventually be felt. An optimum pressure therefore exists at which the increased range for acceleration is just balanced by the decreased supply of molecules. For air, this pressure is of the order of a few tenths of a millimeter of mercury. A further decrease in the pressure results in a rapid increase in the resistance of the gas. If a perfect vacuum could be obtained, the free space between electrodes would be a perfect insulator. While this is, of course, impossible, it is, nevertheless, easy with modern methods of evacuation to obtain pressures so low that no appreciable discharge can be detected with the highest fields available in the laboratory.

**154. Experiment 31. Resistance of a Discharge Tube.**—The apparatus consists essentially of a discharge tube, as shown in Fig. 111, about fifteen inches in length through the ends of which are sealed wires attached to electrodes of relatively large area. It is connected to a high vacuum pump by means of which the pressure may be reduced to any desired value. A manometer and McLeod gauge are also joined to the tube to measure the pressure.

Connect a small high tension transformer across the tube to supply the voltage for the discharge. Place an electrostatic

voltmeter across the tube and an A.C. milliammeter in series with it. The impressed voltage may be controlled by a series resistance in the primary circuit. Starting at one atmosphere, reduce the pressure until a current of 10 or 15 milliamperes is obtained through the tube. Measure the required voltage. Take a series of readings at various pressures measuring the voltage

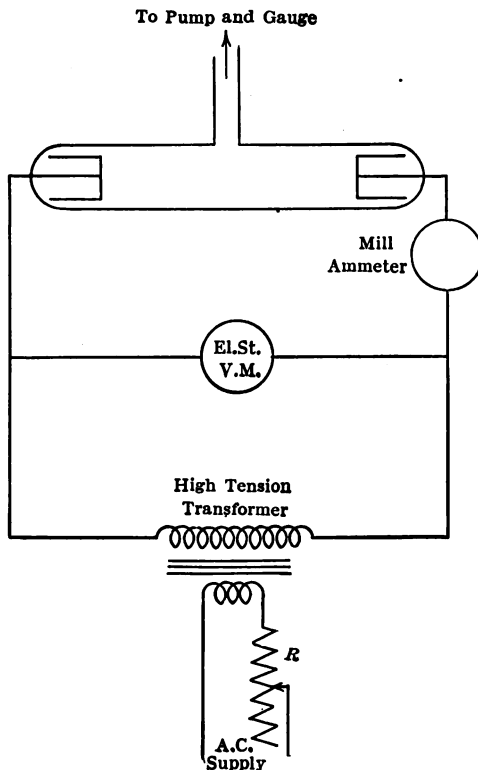


FIG. 111.—Resistance of discharge tube.

required to maintain a definite predetermined current. Compute the resistance of the tube by Ohm's law. Repeat the experiment using twice this current.

**Report.**—Plot a curve showing the resistance of the tube as a function of pressure. Why must the current be held constant in this experiment? Explain the operation of the McLeod gauge.

**155. Phenomena of the Discharge Tube.**—If electrodes are mounted at the ends of a tube such as shown in Fig. 112, con-

taining air at ordinary pressures and a sufficiently high voltage is impressed between them, the phenomenon first observed is the ordinary spark similar to that between the electrodes of a static machine. If, however, air is gradually removed, the sparks become less violent, and fine streamers of bluish color are observed. As the pressure is further reduced, these streamers broaden out and fill the entire tube, and a pink color appears at the anode. With further exhaustion, the pink color extends some distance from the anode and dark spaces appear in the region of the cathode. When the pressure has been reduced to

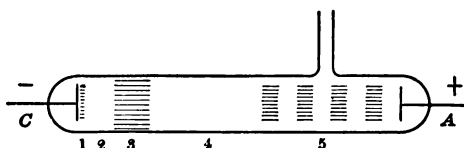


FIG. 112.—Luminous regions of discharge tube.

about half a millimeter of mercury, the discharge assumes a very characteristic appearance. Closely surrounding, but not quite touching the cathode, is a thin layer of luminosity known as the *cathode glow*. Next to this is a region, from which no light is observed, called the *Crooke's dark space*, and beyond this is a rather broad region of luminosity known as the *negative glow*. Following this is another non-luminous region, called the *Faraday dark space*. Between this dark space and the positive electrode is a region called the *positive column*, which may be seen as a continuous band of light or, under certain conditions of current and voltage, as a series of light and dark striae. The positive column seems to be definitely associated with the anode, for if the tube is increased in length or bent into a curve, the positive column increases or bends with it, while the other parts of the discharge remain fixed and are thus shown to be associated with the cathode. These luminous regions are indicated in Fig. 112.

If the pressure is still further reduced, the striae of the positive column become fewer in number and wider in extent and finally disappear. The regions associated with the cathode also become larger and, with the disappearance of the positive column, the dark spaces fill nearly the entire tube. With sufficient exhaustion, the Crookes dark space completely fills the tube, and the voltage required for a passage of current becomes

very high. At this stage, the walls of the tube fluoresce brilliantly with colors depending upon its chemical composition, being bluish for soda, and bright green for German glass. If the exhaustion is carried far enough, the tube becomes a non-conductor of electricity.

**156. Theory of the Discharge.**<sup>1</sup>—Since no external ionizing agent is acting, it is obvious that the discharge is maintained by ions produced by collision, and the varied distributions of the luminous regions indicate that the electric fields and the velocities of the carriers can not be uniform throughout the tube. It has not yet been definitely determined whether luminescence arises from ionization of neutral molecules or whether it accompanies the recombination of an ion and an electron to form a neutral molecule. At the present time, the evidence seems to favor the latter hypothesis. Another widely accepted view is that when a molecule has been shaken up by collision with an ion or electron to such an extent that its electronic orbits are badly distorted, but not disrupted, light emission accompanies its return to the equilibrium state. On the latter theory, luminous regions do not necessarily coincide with regions of ionization. Some of the more important phenomena characterizing the several regions enumerated above are the following.

1. *Cathode Glow.*—The field strength in this region is large and often the greater part of the entire potential difference occurs in this limited space. The magnitude of the fall in potential depends upon the nature of the gas and the material of the electrode, ranging from 470 volts for water vapor to 170 volts for argon with platinum electrodes. If metals such as magnesium, sodium, or potassium are used, much smaller values are obtained because of the greater ease with which these substances emit electrons. The large potential gradient here is caused by the accumulation of positive ions in front of the cathode. Because of the greater mobility of electrons, they rapidly move away from this region thus leaving a preponderance of positive ions. The ionization is caused by collision of the positive ions either with gas molecules or the cathode itself.

2. *Crookes Dark Space.*—It was pointed out above that a certain amount of energy is required to produce ionization. The electrons from the cathode glow must move through a certain

<sup>1</sup> CROWTHER, *Ions, Electrons, and Ionizing Radiations*, chap. VI.

TOWNSEND, *Electricity in Gases*, chap. XI.

difference of potential before they possess the requisite kinetic energy for this purpose. The Crookes dark space represents this distance for it is here that electrons, liberated in the cathode glow, are acquiring the necessary energy of motion to produce the ionization of the negative glow. It is, in general, a rough measure of the mean free path of the electrons. No ionization occurs in this region and the current is carried almost exclusively by the electrons.

3. *Negative Glow*.—The luminosity of this region is due to ionization by electrons from the Crookes dark space. The positive ions produced here move slowly out of the negative glow into the Crookes dark space and their presence reduces the potential gradient to such an extent that electrons, originating in the negative glow, do not gain sufficient speed to produce ionization; and hence, after those entering from the Crookes dark space have been stopped by the ionization process, no further ionization occurs.

4. *Faraday Dark Space*.—The current in this region is due largely to electrons which enter it from the negative glow. Because of the accumulation of electrons in the negative glow, the potential gradient through the Faraday dark space and even up to the anode is quite large. The electrons are accordingly accelerated through this dark space and when they have attained velocities sufficient for ionization, the positive column commences.

5. *Positive Column*.—The potential gradient is practically constant throughout this region and ionization by collision may take place all the way, resulting in a uniform column of light. Ordinarily, however, there are local accumulations of positive ions, which result in a decrease in the potential gradient with a consequent reduction in the acceleration of the electrons. There are then regions in which the velocities are too small to produce ionization and the striae commonly observed, result. Under these circumstances, the positive column is, to a certain extent, a repetition of the phenomena of the Crookes dark space, and the negative glow.

**157. Investigation of the Field Strength at Various Points in the Discharge.**<sup>1</sup>—The potential at any point in a tube may be determined by inserting an auxiliary electrode. A small platinum wire is most frequently used for this purpose. If the region happens to be one of high potential, the wire will attract to it positive ions until its potential is the same as that of its surround-

<sup>1</sup> GRAHAM, *Wied. Ann.*, vol. 64, 1898, p. 49.

ings, which is then indicated by an electrometer to which the wire is attached. Accurate results can be obtained by this method only when there is a plentiful supply of ions of both signs. For example, suppose the wire is introduced near the anode, where only electrons are present. The forces of the field will cause electrons to strike the wire until it is so highly charged negatively that no more can reach it because of repulsion, and the wire thus has a negative potential considerably in excess of the region in which it is placed. If positive ions also were present, they would be drawn to the wire until its potential is the same as the surrounding region.

If two test electrodes are used, the field strength at various points through the discharge may be determined by measuring the potential difference between them and dividing by their distance apart. Except for regions close to the electrodes, where only one type of ion is present, this method gives reliable results. Because of the mechanical difficulty of moving a pair of test wires through a tube with fixed electrodes, it is more convenient to use a tube with fixed test wires  $tt$  and moveable electrodes as shown in Fig. 113. The anode  $A$  and cathode  $C$  are held at a fixed distance apart by means of a glass rod  $d$  with flexible leads connecting to the seals through the tube. A small lug of iron  $I$  is acted upon by a magnet so that the electrodes may be moved along the tube, placing the test wires at any desired part of the discharge.

**158. Experiment 32.** *Measurement of Field Strength in the Discharge through Air.*—Connect the apparatus as shown in Fig.

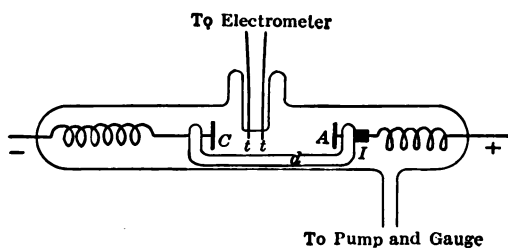


FIG. 113.—Tube for measuring potential gradients.

113, using as a source of power either a battery of flash light cells or a motor generator set giving an E.M.F. of about 1,000 volts. Include a graphite resistance in series with the tube to prevent arcing when the conductivity is high. Measure the difference of potential between the test electrodes by means of an electrom-

eter which has been checked against a standard voltmeter. Start the pump and note the character of the discharge from the highest pressure at which a current can be maintained to the best vacuum that the pump will give. An E.M.F. of 1,000 volts is not in general sufficient to start the discharge although it will maintain it, once it is going. To start it connect a small spark coil across the tube with an air gap in series to prevent shorting the generator or battery through the secondary of the coil. Determine the field strength at various points through the discharge for two pressures (a) the highest at which a uniform discharge can be maintained, (b) one at which the discharge has the characteristic appearance shown in Fig. 112. Measure the pressures by means of a McLeod gauge, and the voltage across the tube by an electrostatic voltmeter.

**Report.**—Indicate by sketches the character of the discharge for several different pressures. Plot field strength as a function of distance from the cathode for the two cases studied. Plot voltage as a function of distance from cathode. Obtain the latter from the area under the field strength—distance curve.

**159. Cathode Rays.**—It was pointed out above that when the pressure in a discharge tube has been reduced to a certain value, e.g., a hundredth of a millimeter of mercury, the character of the discharge is entirely changed from that represented by Fig. 112. The positive column shrinks back and disappears entirely and the Crooke's dark space occupies the entire volume of the tube. The glass now shows a bright fluorescence, green or blue, depending upon its composition. This fluorescence is due to bombardment by electrons shot out from the cathode or the region immediately in front of it. They travel in straight lines perpendicular to the cathode, and possess many interesting properties. For example, if they strike a piece of platinum foil, it may be heated to incandescence by their bombardment, or if they impinge upon substances such as willimite, calcium tungstate, barium platino-cyanide, etc., they cause them to fluoresce brilliantly. These streams of electrons are called cathode rays.

The fact that they possess a negative charge may be demonstrated by placing two parallel plates within the tube between which there exists a difference of potential. A stream of cathode rays passed between them will be deflected away from the negatively charged plate toward the positive. Again, if a magnetic field is introduced across the tube, the stream will be deflected



*Rela y m = v.c.t.*

at right angles both to their motion and to the field in the manner required by the ordinary rules of electrodynamic action for currents.

**160. Velocity and Ratio of the Charge to the Mass of an Electron.**<sup>1</sup>—The fact that an electron, when moving through a magnetic field, is acted upon by a force at right angles both to its motion and the direction of the field may be used to determine the ratio of the charge to the mass of an electron and the velocity with which it moves. Apparatus arranged for this purpose is shown in Fig. 114. A vacuum chamber C is constructed from a brass tube from which there projects a smaller tube A also of

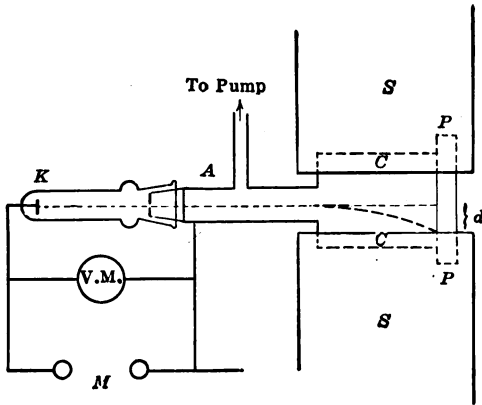


FIG. 114.—Apparatus for measuring  $\frac{e}{m}$ .

brass. The end of A is tapered and fitted to one end of a ground glass joint. The other end of the glass tube is closed and carries the cathode K. A piece of plate glass P, on the inner side of which has been placed a thin coating of fluorescent material such as calcium tungstate closes the vacuum chamber. The end of the smaller tube A contains a brass plug through which has been bored, with a jeweler's drill, a very fine hole.

When a suitable vacuum has been obtained, a discharge produced between A and K by a static machine M causes a stream of electrons to pass from K to A, the individual electrons of which move in straight lines normal to K. All but those lying in a

<sup>1</sup> TOWNSEND, *Electricity in Gases*, p. 453.

CROWTHER, *Ions, Electrons and Ionizing Radiations*, p. 92.

DUFF, *A Text Book of Physics*, p. 492.

very narrow beam, defined by the hole through  $A$ , are stopped but those passing through, enter the chamber  $C$  and produce on  $P$  a bright fluorescent spot. If now the solenoid is energized, the magnetic field causes a deflection of the beam and the spot is moved a distance  $d$  perpendicular to the plane of the paper, (shown in the plane of the paper in Fig. 114).

If the magnetic field is uniform, the path of an electron is circular, since the force, in this case, is constant in magnitude, and is, always at right angles to the motion. The magnitude of the force may be obtained as follows: Let  $l$  be the length of path of an electron through the magnetic field. When it has traversed the distance  $l$ , a quantity of electricity  $e$  has been transported through this distance and may be replaced by a steady current of strength  $i$  defined by  $i = \frac{e}{t}$ , where  $t$  is the time required for the electron to travel the distance  $l$ . The theory of electrodynamics gives, for the force acting on a conductor of length  $l$ , carrying a current  $i$ , the expression

$$F = H il = H \frac{el}{t} = Hev \quad (1)$$

where  $v$  is the velocity with which the electron moves.

Since the electron moves in a circle, whose radius we will call  $R$ , the force given by eq. (1) must balance the centrifugal force. Accordingly, we have

$$Hev = \frac{mv^2}{R} \quad (2)$$

where  $m$  is the mass of the electron. The velocity  $v$  is acquired while the electron moves through the difference of potential  $E$  maintained between the anode and cathode by the static machine. Since there is no potential difference between  $A$  and  $P$  it travels this distance with constant velocity. The kinetic energy acquired in moving from  $K$  to  $A$  is equal to the loss of potential energy over this distance. From the law of conservation of energy and the definition of potential difference, we have

$$Ee = \frac{1}{2}mv^2 \quad (3)$$

Eliminating successively  $v$  and  $\frac{e}{m}$  from eqs. (2) and (3) there results

$$\frac{e}{m} = \frac{2E}{R^2H^2} \text{ and } v = \frac{2E}{RH} \quad (4)$$

The radius of curvature  $R$  is obtained from the sagitta formula

$$R = \frac{l^2}{2d} \quad (5)$$

The magnetic field strength  $H$  is computed from the dimensions of the solenoid and the current through it by the formula

$$H = \frac{4\pi NI}{10L}$$

where  $N$  is the number of turns on the solenoid and  $L$  its length. The accelerating potential  $E$  is measured by an electrostatic voltmeter.

**161. Experiment 33.** *Measurement of  $\frac{e}{m}$  and Velocity for an Electron in a Cathode Ray.*—Connect the apparatus as shown in Fig. 114. Start the static machine and pump the vacuum chamber until a green fluorescence is seen near the anode  $A$ . Should this color appear at  $K$  the leads to the static machine should be reversed. A bright spot will appear at  $P$ . Energize the solenoid and determine the current required for a suitable deflection  $d$ . In taking observations, reverse the solenoid current and measure  $2d$ . It will be found that by varying the vacuum, different voltages may be maintained across the discharge while the static machine is driven at a constant speed. With the two halves of the solenoid as close together as possible, take a series of observations using different accelerating voltages, and deflecting fields and determine  $\frac{e}{m}$  and  $v$ . The fact that the parts of the solenoid must be separated to permit the entrance of the discharge tube introduces a non-uniformity in the field. To determine this error, take a series of observations, keeping the accelerating potential and the solenoid current constant and increase the separation of the solenoid parts from the smallest amount up to 10 cms., and plot the apparent values of  $\frac{e}{m}$  and  $v$  as a function of the separation. The intercept of this curve, when extrapolated to zero separation gives the correction to be applied to the results obtained above. Since the value of  $\frac{e}{m}$  is usually given in electromagnetic units per gram, it is necessary to express  $E$  and  $H$  in eq. (4) in that system.

**Report.**—Plot the correction curve called for above and apply to average values of  $\frac{e}{m}$  and  $v$ . Compute the velocity of an elec-

tron which has fallen through the following differences of potential using your value for  $\frac{e}{m}$ : 300, 3,000, 30,000 volts. Compute the time required for an electron to move from  $K$  to  $A$  for some one of the conditions actually used in this experiment. If the charge on an electron is  $4.77 \times 10^{-10}$  electrostatic units, compute the number of electrons passing per second across a plane in a wire through which a current of one ampere is flowing.

**162. Radio-active Substances.**<sup>1</sup>—If the region surrounding any radio-active substance such as uranium, radium, thorium, etc., is examined by appropriate means, it is found that these substances emit definite radiations which have very unusual properties. These radiations, for example, are able to darken a photographic plate, to convert an insulating gas into a conductor, and to cause a fluorescent screen to emit light. Moreover, they are different from ordinary light in that they are able to penetrate many substances usually regarded as opaque. It has been found that each radio-active substance is a definite chemical element and that its activity is due to a spontaneous decomposition or disintegration of its atoms. Furthermore, when certain of the rays are emitted, there is a definite reduction in the atomic weight of the substance, which naturally leads to the view that the atoms of these substances are made up of complex systems which have the same intrinsic character and differ from one another only in their order of arrangement or degree of complexity. Three distinct types of radiation have been found which are designated as  $\alpha$ ,  $\beta$ , and  $\gamma$  rays.

**163. The Alpha Rays.**—These rays are distinguished from the others by the fact that they are easily absorbed on passing through gases or thin sheets of metal and that their action on a photographic plate is weak. On the other hand, they are very effective as a means for ionizing a gas, and they cause fluorescent substances to emit light. If a screen upon which they are acting is examined by a microscope, it is found that the illumination is not uniform but is made up of a large number of separate flashes as though the screen were under bombardment. In fact it has been found that  $\alpha$  rays are discrete particles shot out

<sup>1</sup> CROWTHER, Ions, Electrons and Ionizing Radiations, chap. XI.

McCLUNG, Conduction of Electricity through Gases and Radioactivity. Part II.

DUFF, A Text Book of Physics, p. 502.

from radio-active substances and it is possible by suitable experimental arrangements, to photograph their zig-zag courses as they make their way through a gas, abruptly deflected by some of the gas molecules, and stopped by others.

If a beam of  $\alpha$  particles is shot at right angles to an electric or a magnetic field, the path is curved in much the same manner as the cathode ray stream described above, except that the deflection is much smaller in magnitude due to their larger mass and is in the opposite direction, indicating that they are positively charged. By making use of electric and magnetic deflections, the value  $\frac{e}{m}$  of the ratio of the charge to their mass and the velocity with which they are emitted, have been measured. The results show that  $\frac{e}{m}$  is the same for all  $\alpha$  particles, no matter what their source and is equal to 4,823 electromagnetic units per gram, and that the velocities range from  $1.5 \times 10^9$  to  $2.2 \times 10^9$  cms. per sec.

The ratio of the charge to the mass for the hydrogen ion in electrolysis is twice that for the  $\alpha$  particle, and at first sight it might be supposed that the latter is a hydrogen molecule consisting of two atoms. However, it has been found that the charge carried by the  $\alpha$  particle is twice that of the hydrogen ion, and hence its mass must be four times that of the hydrogen atom. Since the particle is atomic in size and is of the same order of magnitude as the atom of helium whose atomic weight is 3.96, the most natural assumption is that it is an atom of helium with twice the electric charge of the hydrogen ion. This hypothesis is supported by the fact that both chemical and spectroscopic analyses show conclusively that helium is always present where radio-active transformations are taking place.

**164. The Beta Rays.**—The  $\beta$  rays are distinguished from  $\alpha$  rays in several important respects. In the first place, they have a far greater penetrating power. While the  $\alpha$  rays are completely stopped by a sheet of aluminum foil  $\frac{1}{10}$  mm. in thickness,  $\beta$  rays still produce noticeable effects after passing through sheets 100 times this thickness. Again, they are much more easily deflected by a magnetic field. The deflection of the  $\alpha$  rays is appreciable only in the largest fields available, and even then special methods have to be employed. The  $\beta$  particles, on the other hand, travel in circles of large curvature when moving at

right angles to fields of ordinary magnitudes. The direction of the deflection shows that they carry a negative charge, and all the evidence indicates that they are identical with the cathode rays of the ordinary discharge tube, i.e., electrons.

By subjecting  $\beta$  rays to the deflecting action of electric and magnetic fields combined, the values of  $\frac{e}{m}$  and the velocities with which they are emitted may be measured. It has been found that while the former is the same as for the cathode-ray particles, the velocities of emission are considerably higher than those observed in discharge tubes, ranging from  $6 \times 10^9$  to  $2.8 \times 10^{10}$  cms. per second. The latter is very close to the velocity of light,  $3 \times 10^{10}$  cms. per second.

A careful study has been made by Kaufmann of the value  $\frac{e}{m}$  for the particles as a function of velocity, and it was found that  $\frac{e}{m}$  is not constant, but decreases as the speed increases. This can be explained only by assuming that  $e$  decreases or that  $m$  increases as the velocity becomes larger. The evidence furnished by other lines of study indicates that the charge of the electron is one of the fixed constants of nature, and therefore it is concluded that the mass of the electron depends upon its velocity. Theoretical considerations have shown that the apparent mass of an electron is due wholly, or in part, to the motion of its electric charge. In fact, for a number of years, the view was held that the mass of the electron is entirely electromagnetic in character, but some very recent work indicates that this can not be the case entirely.

**165. The Gamma Rays.**—The nature of the  $\gamma$  rays is very different from that of the  $\alpha$  and  $\beta$  rays. They are distinguished by the fact that they possess very much greater power of penetration. In fact they may easily be detected after passing through several cms. of iron. Though subjected to the most powerful electric and magnetic fields available, they show no deflection, and can not therefore carry an electric charge. They cause a fluorescent screen to emit light, and affect a photographic plate. When passed through gases they produce ionization, and, in fact, are usually detected by this action.

Searching investigations have shown that they are similar in character to X-rays, that is, electromagnetic waves of very short wave length. The similarity of the relation of  $\beta$  rays to cathode

rays and  $\gamma$  rays to X-rays is very close. When the target of an X-ray tube is struck by a rapidly moving electron, the electronic orbits of one of the atoms of the former undergoes some sort of rearrangement; that is, they change over from one stable configuration to another possessing a different amount of potential energy, and a train of X-rays is emitted. The emission of the X-ray occurs as the result of suddenly stopping a high speed electron. Similarly, when a radio-active substance emits a  $\beta$  particle, sending it forth with a velocity comparable to that of light, a rearrangement of the electronic orbits also occurs, which is accompanied by the emission of the  $\gamma$  ray. The  $\gamma$  rays thus accompany the rapid acceleration of electrons. The fact that  $\gamma$  rays are always present when  $\beta$  rays are emitted supports this view. Measurements have shown that the wave length of the  $\gamma$  rays is somewhat shorter than that of the most penetrating X-rays.

**166. Radio-active Transformations.**—Careful investigations of the phenomena accompanying the emission of the rays just described, show that radio-active substances are distinguished from ordinary ones in that they are constantly undergoing changes of character, never observed in ordinary materials. Each substance is entirely distinct from the other, and has its own characteristic physical and chemical properties. However, instead of enduring indefinitely as is the case with ordinary elements, such as copper, iron, gold, etc., each radio active substance has a definite, measurable period of existence, after which it disintegrates and becomes a new chemical substance, and it is during these processes of transformation, that the emission of rays occurs.

All molecules are made up of atoms which consist of positive nuclei with electrons rotating about them in closed orbits. The electrons are held in their orbits by the electric attractions existing between them and the nucleus while the atoms are held together by the electric forces between their parts, or the magnetic forces due to the circulating electrons. This complicated structure becomes unstable for some reason or another, and an  $\alpha$  or a  $\beta$  particle or both is emitted. After a rearrangement of the remaining particles, a new state of stable equilibrium ensues, giving a new substance of different physical and chemical properties. As an illustration, take the substance radium. Although the individual molecules do not have the same periods of existence, the life of an average molecule is 2,000 years. At the end of this time, it emits an  $\alpha$  particle, and the residue is called radium

emanation. The emanation persists for a period of 3.75 days when it gives off another  $\alpha$  particle, and becomes radium *A*. In this form it lasts for 3 minutes, then again emits an  $\alpha$  particle and becomes radium *B*. This state persists for 26 minutes when it gives off a  $\beta$  particle accompanied by a  $\gamma$  ray and becomes radium *C*, and so on. The entire series has been carefully worked out, starting with uranium, going through ionium and the various phases of radium, and thorium to those of actinium. The duration of the different phases ranges from a few minutes to  $10^{10}$  years. Some of the transformations are apparently not accompanied by the emission of any rays. These transformations are explained by supposing that the ray is present but possesses such a low velocity as to be unable to ionize a gas and is therefore not detected.

It is important to note that each time an  $\alpha$  particle is emitted the atomic weight decreases by 4, i.e., the atomic weight of helium. Furthermore, the last radio active product, radium *F*, or polonium, has an atomic weight equal to that of lead, and possesses the properties of ordinary lead.

It is easy to conjecture that each of the chemical elements as we know them, has been derived from one higher in the scale of atomic weights by the emission of one or more  $\alpha$  particles, and that transformations are going on continuously but at a rate so slow as to escape detection by methods at present available.

**167. Experiment 34. Ionization by Radio-active Substances.**—The apparatus for this experiment is shown in Fig. 115. It consists of an ionization chamber made entirely of metal. The radio-active substance, in the form of a powder is spread over the plate *A* which may be moved up or down. An insulated plate *D* is connected to an electrometer *E* mounted in another chamber and connected with the ionization chamber by a removable brass tube. The electrometer is charged by means of a battery *B* of small dry cells by pressing down the wire *W* which must be insulated from the container. When the rays from the radio-active substance pass up through the metal gauze *G* they ionize the air between *G* and *D*. Either electrons or positive ions, depending upon the sign of the charge on *D* and *E* are drawn toward *D* and neutralize this charge. The deflections of the electrometer are read by means of a long focus microscope provided with an eye piece having a graduated scale. The time required for the gold leaf of the electrometer to fall through one division is inversely proportional to the ionization current.



It is necessary first to determine the rate of discharge of the ionization chamber and electrometer due to leakage alone. For this purpose, cover up the radio active substance by a close fitting metallic plate  $P$ . Charge the electrometer by connecting it for an instant to the battery by means of  $W$ , and note the time required for the gold leaf to fall one division. Take several readings and average. This leakage is due partly to imperfect insulation, and partly to  $\gamma$  rays which penetrate the metal cover.

Remove the shield  $P$ , charge the electrometer as before, and with  $A$  near the bottom of the chamber, determine the rate of

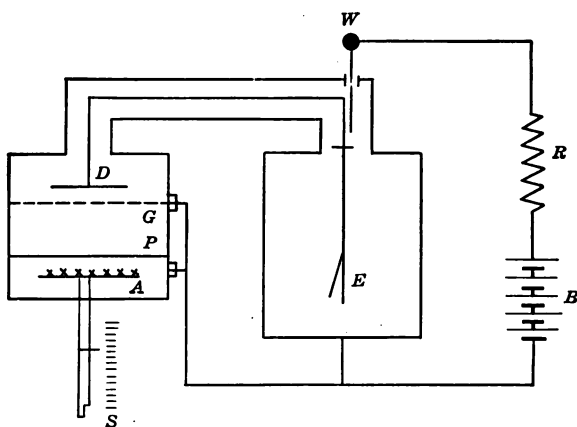


FIG. 115.—Apparatus for ionization studies.

discharge as above. The difference between these two rates is a measure of the ionization produced by the  $\beta$  rays from the radio active substance, provided the distance  $AC$  is greater than 10 centimeters, the range of the  $\alpha$  particles. Take a series of observations determining the rate of leak each time raising  $A$   $\frac{1}{2}$  cm. until a marked increase in the rate of leak is observed. This indicates that the  $\alpha$  rays have penetrated the space between the gauze and  $D$ . Take readings each millimeter until the rate has become nearly constant again. Continue until the plate  $A$  is as high as it can be raised.

**Report.**—Plot inverse time of leakage against distance between  $A$  and  $D$ . Draw horizontal lines representing the leakage current, and that due to the currents produced by both  $\beta$  and  $\alpha$  ray ionization.



## CHAPTER XIV

### ELECTRON TUBES<sup>1</sup>

During the last decade, the electron tube has had a development little less than phenomenal. Because of the multiplicity of its uses, e.g., as detector, amplifier, oscillator, modulator, etc., it finds many applications not only in the art of radio communication but also in engineering work and the general research laboratory. No student of electrical engineering or physics can afford to be unacquainted with this device, and it is the purpose of the present chapter to set forth and illustrate the fundamental principles upon which it operates.

**168. Free Electrons.**—It is customary to distinguish an insulator from a conductor by saying that in the former, electrons are held in their orbits about the positive nuclei with forces so great that they can be dislodged, if at all, only by exceedingly large fields while in the latter, the attracting forces are so weak that they are easily torn from their positions of equilibrium and move about through the body. The idea of such easily disruptable atoms is held by some to be inconsistent with the rigid mechanical properties of metals, and the ease with which electrons move through conductors is explained by saying that while the forces holding atoms together are very large, nevertheless, due to the closeness of approach during collisions, the nucleus of one atom may attract an electron of another with so great a force in the opposite direction that the electron is nearly in equilibrium, and a slight field may cause it to leave its original atomic system and enter that of a neighboring one. The one from which it escaped would be left with an excess positive charge and might, in a similar manner, capture an electron from another atom. According to this view, electrons move through a conductor, not by zig-zag paths between molecules, but by passing through the molecules, and forming distinct parts of the atomic structures

<sup>1</sup> RICHARDSON, Emission of Electricity from Hot Bodies.  
VAN DER BIJL, Thermionic Vacuum Tube.  
MORECROFT, Principles of Radio Communication.  
LAUER and BROWN, Radio Engineering Principles.

on the way. Because of the many collisions taking place in consequence of thermal agitation, the large number of electrons required to explain observed currents is easily accounted for.

**169. Electron Emission.**—From the fact that electrons move thus freely from one part of a conductor to another, going either between the molecules or through them, and pass readily out of one conductor in to another in contact with it, it might be inferred that they could also be drawn easily out of a conductor into a vacuous space. It is found, however, that this is not the case, and that special means must be used to cause them to thus emerge. For want of a better explanation, it has been assumed that there exists at the surface of a conductor, a force which tends to keep the electrons within the body. The exact nature of this force is unknown, but recent developments regarding the structure of the atom tend to support the view that such a force really exists. If this is true, a certain amount of work must be done on the electron to move it out of a body against this attracting force.

One of the ways in which electrons may be dislodged from a metal is by the application of electromagnetic radiation of very short wave length. For example, if ultraviolet light falls upon an insulated piece of zinc, it acquires a positive charge, or, if originally charged to a negative potential, it loses this charge and becomes positive. This is explained by saying that the electrons within the atoms of the metal absorb energy from the incident light waves and are stimulated to vibrate with amplitudes so great that they possess energy sufficient to overcome the surface forces and escape into the surrounding space with velocities which depend upon the energy of the light wave and that lost in moving against the surface attraction. This is known as the *photo electric effect*, and while it is most pronounced in zinc it is found to exist to a greater or less extent in all metals. Another way in which electrons may be dislodged from a body is by bombardment with other electrons. Certain metals, notably copper and nickel, when struck by electrons having sufficient energy of motion may emit as many as twenty other electrons for each one striking. This is known as secondary emission, and has been made use of in a number of electron devices.

The most effective way to get electrons out of a body is to heat it. The explanation of this effect is as follows: Since the

body possesses temperature, its molecules must be in motion and the average kinetic energy of the molecules is a measure of the temperature. The electrons being free to move about within the body must also possess undirected motion of thermal agitation from impact with the molecules. In fact it is generally supposed that they are in thermal equilibrium with the molecules, that is, the average value of their kinetic energies is the same as that of the molecules. Since kinetic energy is  $\frac{1}{2} mv^2$ , and the mass of an electron is very much less than that of a molecule, it follows that the velocities of the electrons must be many times larger than those of the molecules. The temperature accordingly need not be very high (dull red) before an appreciable number of electrons will possess sufficient energy of motion to overcome the surface force of attraction and escape into the surrounding space. If the emitting body is insulated, it will take on a positive charge because of the loss of electrons. If the body is in a closed vessel so that the electrons can not move far away, some of them will be drawn back into it, and an equilibrium condition will be established in which the number emitted is equal to the number falling back. The number of electrons emitted per unit time is given by the formula<sup>1</sup>

$$N = A\sqrt{Te}^{-\frac{b}{T}}$$

where  $T$  is the absolute temperature of the body,  $e$ , the base of the Napierian logarithms, and  $A$  and  $b$  are constants depending upon the nature of the substance, its size, shape, and certain other characteristics.

**170. The Two-element Electron Tube.**—This is a device in which application of thermionic emission is made for the rectification and control of currents. It consists of a filament  $F$  which may be made of tungsten or of platinum coated with oxides of barium, strontium or calcium and a plate  $P$  mounted within an enclosure which has been exhausted to a very high vacuum. The filament may be heated to any desired temperature by a battery  $A$  as shown in Fig. 116. Another battery  $B$  is connected between the plate and the filament in such a way as to make  $P$  positive with respect to  $F$ . On heating the filament, electrons pass out into the enclosure, and, were it not for the battery  $B$ , would fill the space with a definite density depending upon the temperature

<sup>1</sup> RICHARDSON, *Phil. Trans. (A)* vol. 201, 1903, p. 543.

of the filament, and an equilibrium state would be reached in which the number returning to the filament is equal to that of those leaving it. The battery  $B$  produces an electric field which causes electrons to move from the filament to the plate, which they enter and pass through the external metallic circuit and return to the filament. They constitute an electric current which, according to common parlance, is said to flow into the plate and out of the filament. The passage of electrons through the vacuous space between the electrodes is called the "space current." The magnitude of the space current is limited by two important considerations which may be made clear by the following experiments.

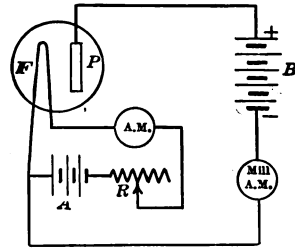


FIG. 116.—Two element electron tube.

**171. Voltage Saturation.**—Suppose that the temperature of the filament is held constant at a value somewhat less than that required for normal operation of the tube. Let the voltage of the battery  $B$  be gradually increased from zero to some specified value, and let the space current be measured and plotted as a

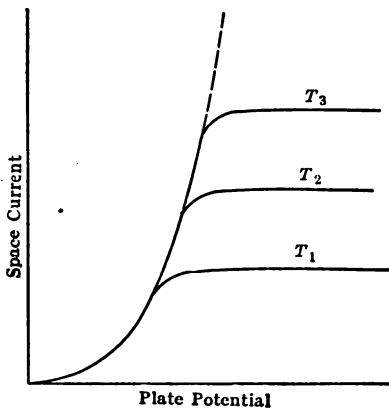


FIG. 117.—Voltage saturation curves.

function of  $B$ . It will be found that for small values of plate potential the space current gradually increases as shown by the curve of Fig. 117, marked  $T_1$ , but that it soon stops rising and remains constant, no matter how much the voltage is increased. This limitation of the current is due to the fact that there is available at the filament only a finite number of electrons which depends upon its temperature as

shown by eq. (1). When the voltage is sufficient to draw to  $P$  all the electrons which are emitted at a given temperature, the maximum current for that temperature is reached, and no increase in voltage, however great, can further increase the current. If now, the experiment is repeated using a higher filament

temperature, the lower part of the curve will be the same as in the previous case. When such a voltage is reached that the available electrons are all drawn to the plate, the current again becomes constant but this time at a higher value, as shown by  $T_2$  of the figure. In this way a series of curves may be obtained which are coincident at their lower extremities but become horizontal at definite values of voltage for each filament temperature.

The constant current which results when all the available electrons are used is somewhat inappropriately called the "saturation current" from the similarity of shape between these curves and the magnetization curves of iron, in which the knee of the curve is called the saturation point. The voltage required to produce the saturation current at any temperature is called the "saturation voltage" for that temperature. The saturation current is thus a measure of the total electron emission at a given temperature.

**172. Space Charge.**—From the experiment just described, it might be inferred that the rate of electron emission is the only

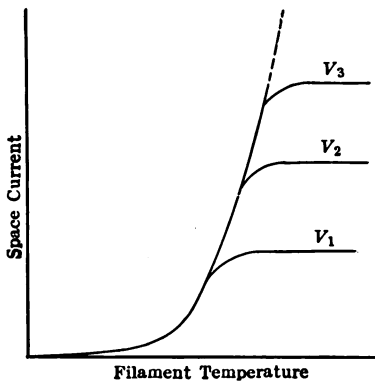


FIG. 118.—Effect of space charge.

limitation to the magnitude of the space current and that if filaments of sufficient areas were provided, currents of any magnitude could be obtained. That this is not the case is shown by the following experiment.

Suppose now the voltage of the battery  $B$  is held constant and the space current measured as the temperature of the filament is changed. Starting with the filament cold, it will be found that the space current is zero, since no electrons are emitted. In fact for most filament materials, there will be no space current, measurable with ordinary instruments, until the filament is hot enough to show a dull glow. When this point has been reached, it is found that the space current rises rather rapidly with increasing filament temperature. This increase in space current does not continue indefinitely for a temperature is soon reached above which the space current remains constant as shown by the curve

marked  $V_1$  of Fig. 118. Even though the temperature of the filament is raised to the melting point, the space current remains constant. If, however, the experiment is repeated using a larger voltage for the battery  $B$ , it is found, on starting again with the filament cold, that the relation between the space current and filament temperature is the same as in the previous case for low temperatures. At a certain temperature, however, the space current again becomes constant but has a larger value than before, and takes place at a higher filament temperature. This is shown by the curve  $V_2$  of the figure. Repeating with a still higher voltage, the curve  $V_3$  is obtained.

The limitation of the space current in this case is due to the action of the electrons which constitute it. Consider an electron which has just emerged from the filament. If it were the only electron between the filament and the plate, it would be acted upon by an electric field which depends only upon the difference of potential between the filament and the plate. If however, there exists between this electron and the plate a second electron, the force on the first electron will be less than in the previous case since it is repelled by the second electron. The fact that the second electron may be in motion makes no difference so long as its velocity is less than that of light. If, now, there is a swarm of electrons of sufficient number between the filament and plate, their repelling action on freshly emitted electrons will just balance the attraction of the positively charged plate and there is no tendency for them to move, until some of those near the plate have entered it and thus reduced the number in the swarm. Electrons from the filament will then enter the swarm keeping the number between filament and plate constant, thus giving the steady space current observed. If the plate voltage is raised, it will require a larger number of electrons in the space to neutralize this increased potential gradient. Furthermore, electrons will be drawn out of the swarm more rapidly thus requiring a larger number to enter it to maintain equilibrium and the space current is thereby increased.

From the explanation just given, it may be inferred that the maximum space current which can be obtained for a given difference of potential between filament and plate depends upon the shape, dimensions and spacing of the electrodes. For a tube having a cylindrical plate of radius  $r$ , and a straight filament

placed along its axis, the current per unit length of filament is given by the expression<sup>1</sup>

$$i = \frac{2\sqrt{2}}{9} \sqrt{\frac{e}{m}} \frac{V^{3/2}}{r} \quad (2)$$

where  $V$  is the difference of potential between filament and plate and  $\frac{e}{m}$  is the ratio of the charge to the mass of the electron.

Substituting numerical values for  $\frac{e}{m}$ , and expressing  $V$ ,  $i$ , and  $r$  in volts, amperes and centimeters this becomes

$$i = 14.65 \times 10^{-6} \frac{V^{3/2}}{r} \quad (3)$$

The two element tube finds its chief application as a rectifier and is often called the "Kenotron." Current can flow only when the plate is positive with respect to the filament. When the plate is negative, filament electrons are driven back into it as fast as they are emitted, and so long as the plate is cold, none are emitted there. Consequently there can be no reverse current. The tube is thus a perfect rectifier for any voltage within the limits of the mechanical and dielectric strength of the parts of which it is made. It ceases to function as a rectifier however, if the plate becomes too hot for it also then becomes a source of electrons. Even at relatively low voltages, electrons acquire velocities of many thousand miles per second in passing from filament to plate and thus strike it possessing very appreciable amounts of kinetic energy which is converted into heat by bombardment. In fact this effect is made use of in heating the plates to "outgas" them during the evacuation process.

**173. Experiment 35. Characteristics of the Two Element Electron Tube.**—Connect the apparatus as shown in Fig. 116, using for  $B$  a battery of flash light cells or a motor generator set giving an E.M.F. of about 500 volts. The purpose of this experiment is to obtain the two sets of characteristic curves for the Kenotron rectifier illustrated in Figs. 117 and 118. Ascertain from the instructor the normal filament current for the tube, and using this and two smaller ones take plate potential-space current characteristics for each, varying plate potentials from 0 to 500 volts. Determine also the filament current—space current characteristics for three different values of plate potential.

<sup>1</sup> LANGMUIR, *Gen. Elec. Rev.*, 1915, p. 330.



**Report.**—Plot the two sets of curves as indicated. Explain what is meant by voltage saturation and space charge. From formula 3 compute the dimensions of a tube that would carry one quarter of an ampere with a difference of potential of 500 volts.

**174. The Three-element Electron Tube.**—In the discussion of the two-element tube the dependence of space current upon filament temperature and plate potential was described, and it was pointed out that its principal application is in the rectification of high voltage alternating currents. By changing the temperature of the filament, thus regulating the supply of available electrons it also serves as a means of controlling currents. In this way, it acts as an electrical valve which may be opened or closed to any desired fraction of its current carrying capacity. Since, however, filament temperatures do not respond immediately to changes in heating current, this action is sluggish, and it can not be used in this way to produce current variations that are at all rapid.

It has been found that the space current may be controlled with remarkable ease by the introduction between the filament and plate of a third electrode in the form of a grid or mesh of fine wires through which the electrons must pass on their way from filament to plate. Such an arrangement is shown in Fig. 119. If a difference of potential is established between the filament and grid by means of the battery *C*, the grid tends to accelerate or retard the electrons of the space current according as it is positive or negative with respect to the filament. It thus counteracts or increases the effect of the space charge. The operation of the three-element tube may be best described by means of the curve of Fig. 120, which shows the relation between the plate current and the grid volts and is known as the "static characteristic." If the grid is disconnected from the circuit, the tube behaves as the ordinary two-element device in which the space current is limited either by electron emission of the filament or by space charge. Assuming there is available a sufficient supply of electrons so that the space charge is the controlling factor, a negative potential placed upon the grid adds to the retarding action of the space charge, and the plate current is reduced, and may even be made zero, if the grid is sufficiently negative. Again, if the grid is positive, it neutralizes to a certain extent the effect of the space charge, causing an increase of the space current. The space current can not continue increasing indefinitely, for even though

the space charge were completely neutralized by positive charges on the grid, the current would be limited by the electron supply at the filament. This accounts for the horizontal part of the static characteristic. If a higher voltage is applied to the plate, the characteristic curve is not changed in shape, but is shifted toward the left. This is because larger negative grid voltages are required to reduce the space current to a given value.

This method of controlling the space current has a number of advantageous features. In the first place, it requires the expenditure of exceedingly small amounts of energy. If the grid is negative with respect to the filament, no electrons strike it and consequently no current flows through the battery *C*, hence the only energy drawn from it is that required to charge the condenser formed by the grid and filament, which is negligible in most cases. If, however, the grid is positive with respect to the filament, a few electrons strike it and a current is drawn from *C* which then supplies energy to the tube. If, however, the grid wires are very fine, this current may be made quite small even though relatively large positive potentials are impressed on the grid. The battery *B* may be one of high voltage and the space current will therefore have large amounts of power associated with it. Accordingly, by the expenditure of small amounts of power in the grid circuit, large amounts of power in the plate circuit may be controlled, and the device constitutes a relay having a large energy ratio.

In the second place, the response of the plate current to changes in grid potential is exceedingly quick, almost instantaneous. If the time required for an electron to travel from the filament to the plate is computed by eq. (3) of chap. XIII, it is found that for an ordinary tube with moderate plate voltages it is of the order of one hundredth of a millionth of one second. This then is the order of the time lag to be expected. For this reason it may be regarded as a relay with no moving mechanical parts and is therefore without inertia in its action.

Again, there exists for a considerable range, a linear relation between grid potential and plate current so that the variations in plate current are faithful reproductions of the changes in grid potential and thus the device is a distortionless amplifier.

**175. Experiment 36.** *Static Characteristics of a Three-element Electron Tube.*—Connect the apparatus as shown in Fig. 119. Use for the filament battery *A*, a set of storage cells, furnishing

from 10 to 20 volts depending upon the size of the tube to be tested. Ascertain from the instructor the normal heating current for the filament, and be careful that this is not exceeded at any time during the test. If the filament is of the oxide coated type, it should be operated at a dull red heat, but if it is a tungsten wire, bring it up to about the same brightness as the ordinary vacuum incandescent lamp. *B* may be a battery of flash light cells giving 500 volts or a motor generator set. For *C* use a battery of flash light cells giving about 60 volts. Bring the filament up to normal temperature, and apply a plate voltage of  $\frac{1}{3}$  normal. Apply a sufficient negative voltage to the grid

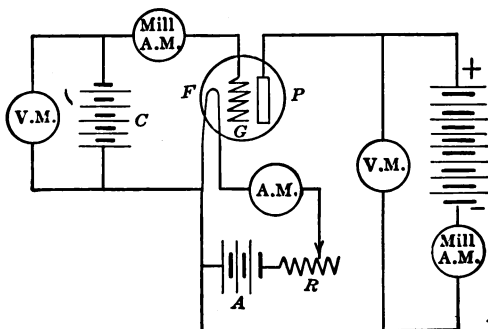


FIG. 119.—Three element electron tube.

to reduce the plate current approximately to zero. Raise the grid volts by steps to zero and positive values and note the grid and plate currents for each setting. Repeat for several values of plate voltage up to and including normal.

**Report.**—Describe the three element electron tube and outline its principal operation features. Plot the static characteristic for the plate voltages studied, also the grid current as a function of grid volts. Sometimes a negative grid current is obtained. How can this be explained?

**176. Amplification Factor.**—The fact that the three-element tube may be used as a relay has been referred to several times, and it is necessary to define accurately what is meant by this statement. By a relay, is meant any device by which a small amount of energy may be used to turn on and off or control a much larger source of energy. In the case of the electron tube, the source of energy is the plate battery and the grid is the gate by which it is controlled. Considering now the plate and grid

circuits, it is obvious that we may be interested in the relative values of either the power, the currents, or the voltages existing in these circuits, and that we may accordingly refer to either the power amplification, the current amplification, or the voltage amplification. The meaning of the first two of these expressions is obvious; for example, by power amplification is meant the ratio of the change in power drawn from the plate battery to the change in power supplied to the grid, and a corresponding meaning is given to current amplification.

However, in the ordinary use of the tube, the voltage of the plate battery remains constant, and the meaning of the voltage amplification factor is not so evident. The significance of this

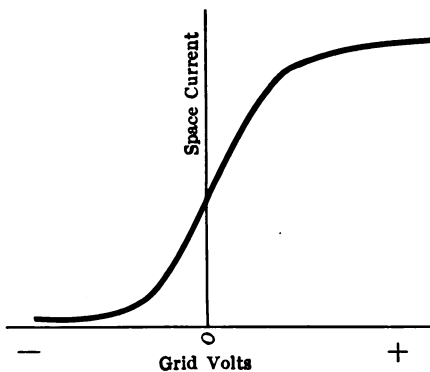


FIG. 120.—Characteristic for three element electron tube.

term can perhaps be understood by reference to a series of static characteristics as represented in Fig. 121, where the dependence of space current upon grid volts for a series of plate potentials, at 50 volts intervals, is shown. Suppose, for example, the plate voltage is 100 and the grid volts zero. The space current is then 10 milliamperes. It is desired to increase the space current

to 20 milliamperes. This may be done either by raising the plate voltage to 150 or the grid voltage to 5. Thus an increase of 5 volts on the grid produces the same change in the space current as an increase of 50 volts on the plate. The voltage amplification factor in this case is said to be 10, since one volt on the grid is equivalent to 10 volts on the plate.

A working equation connecting these quantities may be deduced as follows. It was shown in eq. (2) that for the two-element tube, the plate current is proportional to the  $\frac{3}{2}$  power of the plate voltage, i.e.,  $I_p = aV^{3/2}$ , where  $a$  is a constant. Since a change in grid voltage is more effective by a certain factor, which we will call  $k$ , in producing a change in plate current than a change in the plate voltage, it follows that the plate current in a given tube on which there is acting a plate voltage  $E_p$ ,

and a grid voltage  $E_g$  is just the same as though it were a two-element tube with a plate voltage  $E_p + kE_g$ . The expression for the current then becomes

$$I_p = a(E_p + kE_g)^{3/2} \quad (4)$$

Since eq. (2) refers to the case in which there is an abundance of electrons at the filament and the current is limited only by the space charge, eq. (4) holds only for the left-hand part of the characteristic, i.e., up to the bend.

Referring to Fig. 121, it is seen that the static characteristics all have a point of inflection, and that for a considerable portion each side of this point, the curve is nearly a straight line. If the

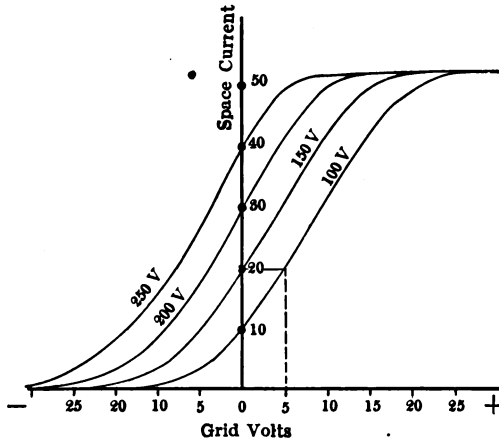


FIG. 121.—Dependence of static characteristics upon plate potential.

tube is used as a distortionless amplifier, it is necessary that the range of applied grid volts should not appreciably exceed the linear part. In this case, the simplified equation

$$I_p = a(E_p + kE_g) \quad (5)$$

may be used in which  $a$  is the filament to plate conductance of the tube, and is the slope of the linear part of the characteristic. If  $E_g$  is sufficiently negative, the plate current is zero. Calling this value  $E_{g0}$ , we have

$$k = -\frac{E_p}{E_{g0}} \quad (6)$$

It is obvious that the amplification for a given tube depends upon the spacing of the grid wires. If these wires are far apart,

a definite change of voltage is not as effective in controlling the electron flow as though the meshes were smaller. As a matter of fact, the amplification factor is inversely proportional to the distance between grid wires. Again, if the grid is close to the filament so that it acts upon the electrons before they have gained appreciable speeds, it is more effective than if it is near the plate. Thus, if it is desired to construct a tube with a large voltage amplification factor it should have a grid with a fine mesh mounted close to the filament. Tubes having amplification factors as large as 100 have been constructed, but in actual practice factors from 10 to 20 are more common.

A simple method for obtaining the amplification factor of a tube is to impress upon the plate a certain positive potential and then apply to the grid a negative potential sufficient to reduce the plate current to zero. The ratio of the plate and grid potentials is then the amplification factor of the tube for this particular plate voltage. It is found in practice that the amplification factor of a tube is not constant but varies with the plate and grid potentials used. This is due to the fact that the average distribution of electrons between the plate and filament changes with the potentials on the grid and plate which in effect, changes their relative positions. By taking, in this manner, measurements over a series of values of plate voltage a fair idea of the behavior of the tube may be obtained.

While the method just described yields results sufficiently accurate for many purposes, it has nevertheless one serious error. Unless the tube is very carefully designed, it does not have a sharp "cut off." That is, the characteristic curve does not proceed straight down to the axis, but slopes off and approaches it gradually. The actual negative grid potentials required to reduce the plate current to zero are much larger than would be obtained by continuing the straight portion of the characteristic until it intercepts the horizontal axis. In actual use, this intercept value is the one which is effective. A dynamic method in which this error is eliminated has been devised by Miller.<sup>1</sup> His circuit is shown in Fig. 122. The tube is connected in the ordinary way with a telephone receiver in the plate circuit, and potentials supplied to the plate and grid by the batteries *B* and *C* respectively. By properly adjusting the values of these voltages, the tube may be set at any point on the characteristic

<sup>1</sup> J. H. MILLER, *Proc. Inst. of Radio Engineers*, vol. 12, 1918, p. 171.

curve. Included in the grid and plate circuits are the resistances  $R_1$  and  $R_2$  across which is connected the secondary of a telephone transformer  $T$ . When an alternating current is supplied to the primary of this transformer, small alternating voltages, i.e., the resistance drops across  $R_1$  and  $R_2$ , are introduced into the grid and plate circuits respectively. It is obvious from the connections that when the additional voltage on the plate is positive that on the grid is negative and vice versa. By changing the relative values of  $R_1$  and  $R_2$  the ratio of these voltages may be

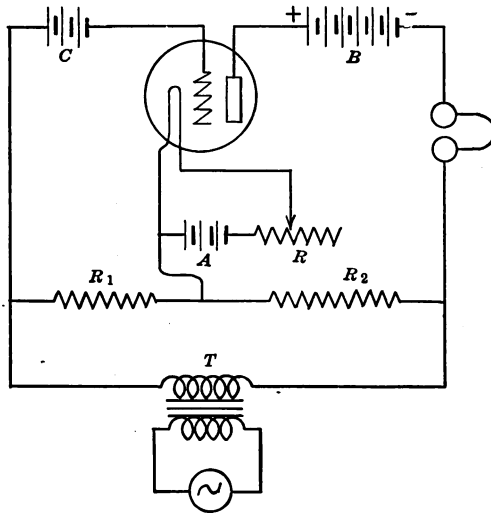


FIG. 122.—Dynamic method for amplification factor.

made to have any desired value. If it is such that the added grid potential just balances that added to the plate, there will be no change in the steady plate current and consequently no sound in the phones. The amplification factor  $k$  is then the ratio of  $R_2$  to  $R_1$ . The advantage of this method is that it measures the amplification factor while the tube is operating in the same manner as when actually used in practice. The dependence of the amplification factor upon the plate and grid volts may thus be easily and quickly obtained.

**177. Experiment 37. Amplification Factor of a Three-element Electron Tube.**—Connect the apparatus as shown in Fig. 122, using for  $P$  a pair of high resistance head receivers. The source  $B$  should furnish a voltage equal to the maximum for which the tube

is designed, and if a power tube is under test, may be a high voltage generator.  $C$  should consist of a battery of small flash light cells. The  $A. C.$  supply should have a frequency high enough to give a good clear note in the phones, and the voltages across  $R_1$  and  $R_2$  should be low enough so that the operating point moves only a small amount along the static characteristic curve. Make two tests. First hold the grid volts at some predetermined value, and measure the amplification factor for a series of plate voltages ranging from a small value up to the maximum for which the tube is designed. Next hold plate volts at normal value and measure the amplification factor for a series of values of grid volts. Check the results of the first series by the static method explained above. That is, for each different plate voltage, find the negative grid potential required to reduce the plate current to zero.

**Report.**—Plot curves showing the dependence of the amplification factor upon both the plate and grid potentials by the dynamic method, and upon plate potentials for the static method. How do you account for the differences between these curves?

**178. Internal Plate Resistance of a Three-element Electron Tube.**—Following the amplification factor, the next most important characteristic of an electron tube from the standpoint of operation is perhaps its internal impedance. It is a well known principle of electrical practice that the impedance of a device should equal that of the circuit on which it operates. Accordingly, in designing a tube to operate on a particular circuit or conversely in adjusting a circuit to fit the tube which is supplying power to it, it is necessary to know the plate to filament impedance of the tube. The mechanism by which the vacuous space offers resistance may be understood by the following consideration. When a current flows through a conductor, heat is developed within it. This energy is furnished by the driving electric field which urges the electrons along through the conductor. Resistance, in this case, is due to a direct interference with the motion of electrons. As a consequence of this view of the nature of resistance, it might at first be thought that a perfect vacuum would be a perfect conductor of electricity since there is nothing to interfere with the free motion of electrons. That this however, is not the case is at once evident when one remembers that relatively large voltages are necessary to cause small currents



to flow through the ordinary electron tubes, even when the conditions are far removed from those of current saturation. Moreover, the fact that it is easy to heat the plate red hot by the passage of current, indicates that it is accompanied by a consumption of energy.

When an electron is emitted by the heated filament, it finds itself in the electrostatic field existing between filament and plate, and it is at once accelerated toward the plate. Since the electron possesses mass, it necessarily gains kinetic energy as it moves toward the plate. This energy is abstracted from the electric field which accelerates it. When the electron strikes the plate, it possesses a velocity of the order of several thousand miles per second even under moderate potential differences. At the plate it is suddenly brought to rest and its kinetic energy of motion is converted into heat energy of the molecules of the plate. While the tube does not possess resistance in quite the same way that an ordinary metallic conductor does, it, nevertheless, consumes energy when a current passes, and it is customary to speak of its resistance and to define it on the basis of the energy it consumes. Thus, if  $I$  is the current flowing through the tube, and  $W$  the watts consumed by it, its resistance  $R$  is defined to be such that

$$W = I^2R \quad (7)$$

Since this is the same equation as holds for the power converted into heat by the ordinary conductor, we may determine the resistance of the tube by the voltage required to furnish a given current through it. An application of Ohm's law to corresponding values of plate volts and plate current as read from the static characteristics shows that the resistance of a tube is not constant but depends upon the values of both the plate and grid potentials, and also upon the electron emission from the filament in case saturation voltages are used. It is necessary therefore to define the resistance of the tube for a particular point in the characteristic curve. This is done by saying that the resistance of the tube is the ratio of the change in plate volts to the change in plate current produced by it, when this change is made vanishingly small. That is

$$R = \frac{dE_p}{dI_p} \quad (8)$$

Thus the resistance is the reciprocal of the slope of the plate potential, plate current characteristic. Since this curve is seldom

taken in practice,  $R$  may be obtained from the plate current-grid potential characteristic by remembering that

$$E_p = kE_g \tag{9}$$

whence

$$dE_p = kdE_g \tag{10}$$

Therefore

$$R = k \frac{dE_g}{dI_p} \tag{11}$$

The internal plate resistance is then the product of the amplification factor and the reciprocal of the slope of the plate current-grid potential characteristic.

While this method is satisfactory for many purposes, it is open to the objection that it requires a determination of the amplification factor  $k$ . A dynamic null method has been employed by Ballantine<sup>1</sup> in which the resistances may be measured

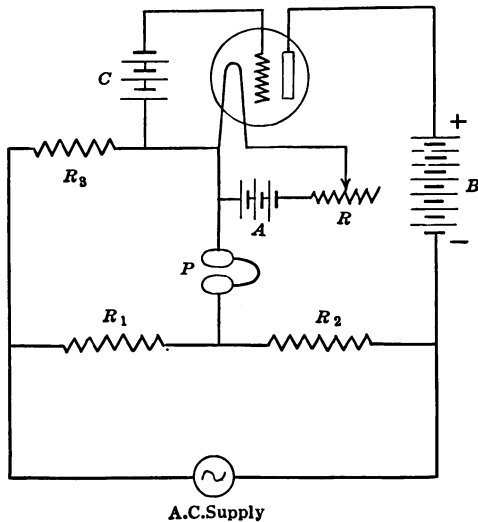


FIG. 123.—Connections for measuring resistance of tube.

directly. The connections for this circuit are shown in Fig. 123. It will be noted that the arrangement is essentially a Wheatstone bridge in which the plate to filament path through the tube is one of the arms. Because of the battery  $B$  a steady current flows through all four arms of the bridge and also through the phones. The phones, however, respond only to the variable currents

<sup>1</sup> BALLANTINE, *Proc. Inst. Radio Engineers*, vol. 7, 1919, p. 129.

furnished by the A.C. supply. The resistance thus measured will be those defined by eq. (8).

**179. Experiment 38. Plate-filament Resistance of an Electron Tube.**—Connect the apparatus as shown in Fig. 123. As a source of alternating voltage use any oscillator giving a good clear note furnishing an E.M.F. of about 10 volts. The resistance  $R_3$  should be of the same order of magnitude as the tube under test, i.e., several thousand ohms. Ascertain the normal plate voltage for the tube, and make a series of measurements of internal resistance varying the grid volts over a considerable range, both positive and negative. Repeat using plate voltages three-quarters, one-half and one-quarter normal. Disconnect the tube from the bridge and determine its static characteristic for normal plate voltage.

**Report.**—Plot internal resistance as a function of grid volts for the four series of observations. Plot the static characteristic and check your results by the first method described. The amplification factor may be obtained by extending the straight portion of the characteristic and taking its intercept on the horizontal axis as the value of the grid volts necessary to reduce the plate current to zero. See Art. 176.

**180. The Tungar Rectifier.**—In the case of tubes operated on a pure electron discharge, it is possible, at best, to obtain currents of but a fraction of an ampere, and these only by the employment of several hundred volts. While such tubes are satisfactory for the rectification of high voltage currents they are, nevertheless, unsuitable for cases in which several amperes at low voltage are required, as, for example, charging storage batteries from ordinary city lighting circuits. For this purpose, a satisfactory tube, known as the tungar rectifier has been developed by the General Electric Co.<sup>1</sup> It is a two-element tube, the cathode of which is a heated tungsten filament in the form of a helix, while the anode is a conical piece of tungsten mounted about 3 mm. from the filament. Instead of a vacuum, the tube contains pure argon at a pressure of 8 or 10 cms. of mercury.

The purpose of the argon is to furnish positive ions which neutralize the space charge encountered in pure electron tubes, and thus to reduce by many fold the voltage required to maintain the current. Furthermore the positive ions take part in trans-

<sup>1</sup> *Gen. Elec. Rev.*, vol. 19, No. 4, 1916, p. 197.

porting electricity between the electrodes and thus materially increase the carrying capacity of the tube. In the early attempts to utilize positive ions, it was found that many gases have injurious effects. For example, in the presence of oxygen, the electron emission of tungsten is cut down to a small fraction of what it is in high vacuum. Again, many gases unite with the heated filament forming compounds, which are highly volatile at normal operating temperatures and thus cause it to disintegrate. Furthermore, when a gas is present in only small amounts, the mean free path of the positive ions may be so great that they acquire velocities sufficient to chip off particles of the filament softened by heating, and thus hasten its disintegration. By use of an inert gas such as argon, the first two difficulties are overcome and by shortening the mean free path by using relatively high pressures, the speeds are so reduced by frequent collisions that the disintegration by bombardment is insignificant.

In order to avoid the formation of volatile compounds it is necessary that the argon be very pure, and in the early tubes great pains were taken to secure this. It has been found possible to mount within the tube, usually on one of the filament leads, substances which react chemically with the impurities, which thus keep the argon in a pure state. For the larger sized tubes, a graphite anode mounted on a tungsten support is often used, and the purifying agent may then be introduced in the anode. As impurities are given off from the electrodes or interior walls, the drop across the arc increases, liberating more heat at the anode, which thus causes vapors to be given off by the purifying agent and in this way the argon is maintained in a state of high purity.

After the arc has once been started, the filament may be kept heated by positive ion bombardment after the heating current has been shut off. In this case, the arc confines itself to a very limited portion of the filament. This spot wastes away more rapidly than the rest of the filament and the life of the tube is materially shortened when operated in this way. For the larger sized tubes, i.e., those with a current capacity of 20 to 40 amperes, a fine tungsten point is independently mounted close to the filament. This may be heated to a high temperature by using it as anode with the filament as cathode. If the connections are then shifted, this hot point may be used as the cathode against the regular anode, its temperature being maintained by positive

ion bombardment as just explained. The filament serves then as a starting device only and the tube has an exceedingly long life. Since relatively large amounts of power are consumed by the filament current, it might be expected that the latter method of operation would result in a material increase in efficiency. This is not the case, since the voltage across the arc rises when the filament current is cut off, and the resulting increase in energy consumption in the arc itself practically balances the saving effected in the filament. Commercial sets are usually made for the purpose of charging automobile storage batteries with a maximum E.M.F. of 60 volts directly from 110 volt alternating current circuits. To avoid losses in controlling rheostats, a step down transformer is mounted within the case to reduce the A.C. voltage to the desired value before rectifying it. A separate low voltage winding is included for heating the filament.

**181. Experiment 39. Study of the Tungar Rectifier.**—For simplicity of operation, obtain the characteristic curves by the

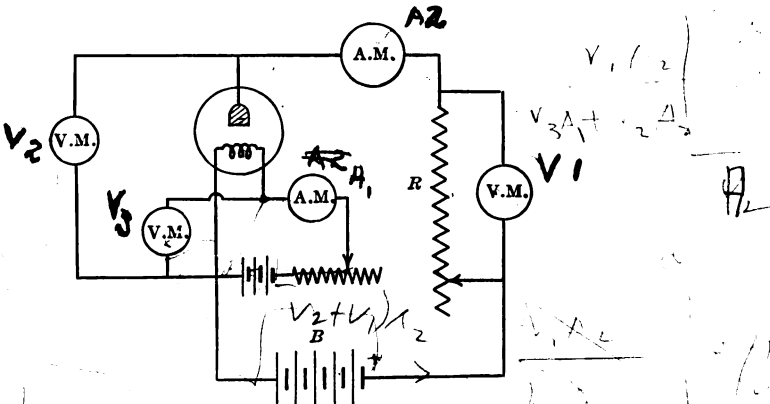


FIG. 124.—Connections for tungar rectifier.

use of direct currents. Mount the tube in a special socket and connect it in circuit as shown in Fig. 124. Ascertain the normal heating current for the filament and be careful not to exceed this value. With this arrangement four curves are to be taken: (a) The volt-ampere characteristic for the arc; (b) the efficiency of the rectifier with external filament heating current; using 30 volts on the plate; (c) the efficiency of the rectifier with filament heated by positive ion bombardment, 30 volts on plate, and (d) same as (b) using 60 volts on plate. In all cases vary the arc

current by means of the rheostat  $R$  through as wide ranges as the arc will permit. The power consumed by  $R$  is taken as the load or useful output of the device. Next place the tube in the socket of the regular rectifier set and make an efficiency run using the 110 volt A. C. circuit as a source of power. Measure the input by means of a wattmeter and the output by the volt-ampere product for the load rheostat  $R$ . Vary the load amperes through

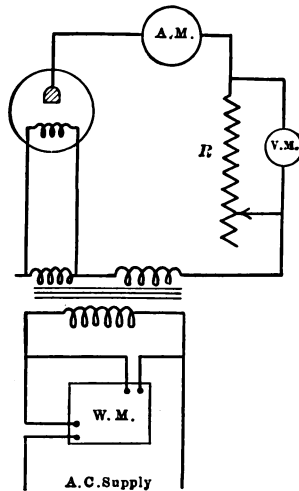


FIG. 125.—Connections for rectifier mounted in commercial set.

as wide a range as possible. The connections for this test are shown in Fig. 125. Before starting the test open up the housing for the set and study carefully the internal connections.

**Report.**—Plot the volt-ampere characteristic for the tungar rectifier, also the various efficiency curves as a function of the load current. Is there any similarity between the volt-ampere characteristics for the tungar rectifier and that of the ordinary carbon arc.

## CHAPTER XV

### PHOTOMETER<sup>1</sup> AND OPTICAL PYROMETER

**182. Intensity of Radiation.**—The brightness of light, as estimated by the eye, is not capable of precise measurement, since it depends to a large extent upon the color of the light and the sensitiveness of the eye which receives it. Accordingly, the only consistent way in which intensity may be specified is in terms of energy. Proceeding on this basis, the intensity of waves, whether they are those of sound, light or of any other type, is measured by the amount of energy passing per second through a square centimeter of area at right angles to the direction of propagation. If there is no loss in the medium, and if the medium contributes nothing to the intensity, the same quantity of energy will persist in a given wave no matter how far it travels, or how the dimensions and form of the wave front may change as it advances.

The variation of intensity with distance from the source depends upon the shape of the wave front, or what amounts to the same thing, the number of dimensions in which the wave spreads out. For example, if the wave front is plane, as in the case of a sound wave travelling along a speaking tube, or the beam from a searchlight, the wave front maintains a constant area, and the intensity is independent of the distance from the source. Again, if a pebble is dropped in the lake, waves travel outward in circles and are propagated in two dimensions. In this case the energy remains constant in a circle which increases as the distance from the center and the intensity varies inversely as the distance from the source. In the case of spherical

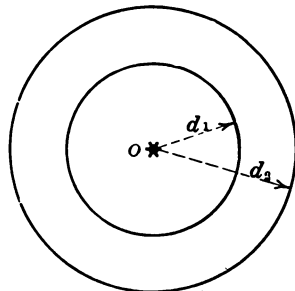


FIG. 126.—Propagation of spherical waves.

<sup>1</sup> DUFF, Text Book of Physics, arts. 259, 637–639, 724.

KARAPETOFF, Experimental Electrical Engineering, arts. 205–211.

NUTTING, Outlines of Applied Optics, p. 169.

waves with which we are particularly concerned here, the energy emitted per vibration of the source is confined within a spherical shell whose thickness is that of one wave length, and this remains constant as the wave advances. Let  $O$ , Fig. 126, be a source from which waves are sent out in all directions. Let  $S$  be the strength of the source, i.e., the amount of energy emitted per second. Also let  $d_1$  and  $d_2$  be the radii of a given wave at two different distances from the source and let  $I_1$  and  $I_2$  be the corresponding intensities. Then

$$S = 4\pi d_1^2 I_1 = 4\pi d_2^2 I_2 \quad (1)$$

whence

$$\frac{I_1}{I_2} = \frac{d_2^2}{d_1^2} \quad (2)$$

Thus the intensity varies inversely as the square of the distance from the source.

**183. The Photometer.**—An instrument for the comparison of two sources of light is called a photometer. While the eye is unable to estimate absolute intensities at all accurately, it is, nevertheless, quite sensitive to differences in illumination.

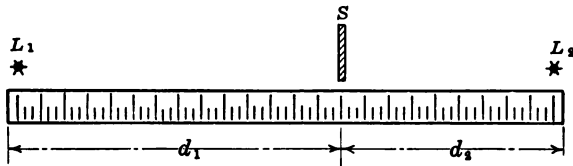


FIG. 127.—Principle of the photometer.

Accordingly, if light from two different sources is allowed to fall upon a screen in such a way that the areas of the separate illuminations are adjacent, equality in the two intensities may be determined by the disappearance of the line of demarkation between them. An instrument for this purpose may be arranged as shown in Fig. 127 by mounting two lamps  $L_1$  and  $L_2$ , which are to be compared, at the ends of a bench provided with a scale along which runs a carriage supporting a screen of white paper. The central portion of this screen is impregnated with paraffine which renders it semitransparent. This spot appears darker than its surroundings if viewed by reflected light, but it is brighter in transmitted light. If, however, the intensity of illumination is the same on both sides, the spot disappears since the amounts transmitted in the two directions are equal.



If  $S_1$  and  $S_2$  are the strengths of the two sources and  $d_1$  and  $d_2$  their respective distances from the screen, then by eq. (1) the illumination on each side of the screen is given by

$$I = \frac{S_1}{4\pi d_1^2} = \frac{S_2}{4\pi d_2^2} \tag{3}$$

$$\frac{S_1}{S_2} = \frac{d_1^2}{d_2^2} \tag{4}$$

If one of the sources, e.g.,  $S_2$  is a standard lamp,  $S_1$  may be computed.

**184. The Lummer-Brodhun Photometer.**—A comparator considerably more sensitive than the grease spot screen just described has been developed by Lummer and Brodhun. The special

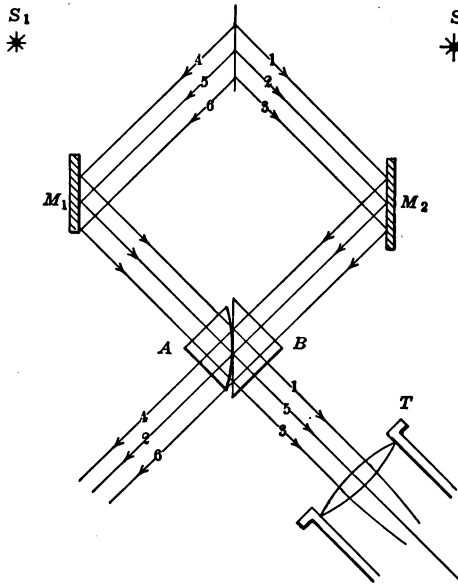


FIG. 128.—Lummer-Brodhun photometer.

feature of this instrument is the optical device for simultaneously viewing the two sides of the comparison screen  $W$ , as shown in Fig. 128. Light from each side is reflected by two mirrors or prisms  $M_1$  and  $M_2$  so as to enter the optical system  $AB$ . This consists of two totally internally reflecting prisms placed back to back. The reflecting surface of one is plane, while that of the other is spherical with a small portion ground flat. The flat surface of the latter is placed in optical contact with the former.

Light entering either of these prisms and striking the contact surface will be transmitted, but light striking any portion of the reflecting surfaces backed by air will be totally internally reflected. Light emerging from the prism  $B$  consists of two parts, that from the contact portion of the two prisms and that from the surrounding area. The former comes entirely from the left-hand side of  $W$  while the latter is from the right-hand side. If a telescope is placed at  $T$  and focused on the contact area of the two prisms, the central portion appears brighter or darker than the surroundings according as the illumination of the left- or the right-hand side of  $W$  is more intense, but the entire field appears uniformly illuminated when a balance is secured.

A convenient form of laboratory instrument is one in which a single socket, to receive in succession the unknown and standard lamps, is mounted at a fixed distance from the comparison box. On the other side is a movable socket containing a small six volt lamp for comparison purposes. The distance of this lamp from the screen is read by an index registering on a fixed scale. A slow motion device is also provided. The process consists then in placing the unknown lamp in the fixed socket and obtaining a balance by moving the comparison lamp to or from the screen until the line of demarkation between the outer and central positions of the field of the telescope disappears. The lamp is then replaced by the standard and a balance again obtained. The screen should be reversed and readings taken in each position and averaged to eliminate differences in reflecting power of the two sides. The equation for computing the strength of the unknown lamp may be derived as follows:

Let  $S$ ,  $U$ , and  $C$  be the candle powers of the standard, the unknown, and comparison lamps, respectively; let  $d_s$  and  $d_u$  be the distances of the comparison lamp from the screen when balanced against the standard and unknown, and let  $D$  be the fixed distance of both standard and unknown from the screen. Then, for the two balances, the following equations hold:

$$\frac{U}{C} = \frac{D^2}{d_u^2} \qquad \frac{S}{C} = \frac{D^2}{d_s^2}$$

Dividing one equation by the other, we have

$$\frac{U}{S} = \frac{d_s^2}{d_u^2} \qquad (5)$$

Care must be taken to maintain the same voltage on the comparison lamp throughout the test.

**185. Experiment 40.** *Study of Incandescent Lamps.*—The purpose of this experiment is to determine, as a function of the voltage upon which they are operated, the candlepower, wattage consumption, watts per candlepower, and resistance of four lamps differing as widely as possible in design. Each lamp, including the comparison lamp, should be provided with a voltmeter and a control rheostat. An ammeter should be placed in series with the unknown. Use five different voltages between 90 and 130. Do not operate the lamps at the higher voltages longer than is necessary for making the observations. The standard lamp should be operated only at the voltage for which it is rated. Make several settings for each observation using the screen in both the direct and reversed positions.

**Report.**—Describe the Lummer-Brodhun photometer and plot the four curves indicated for each lamp. Why does a tungsten lamp reach full brilliancy more quickly after closing the switch than a carbon? Why does the gas-filled lamp have a higher efficiency than a vacuum lamp?

#### THE OPTICAL PYROMETER<sup>1</sup>

**186. General Principles.**—It is a matter of common experience that when a body is heated to a high temperature it emits light and also that the intensity of this emitted radiation varies rapidly with the temperature of the source. For example, a small change in the voltage across an incandescent lamp produces a relatively large change in the brightness of the filament. Measurements show that a body at 1,500° C. emits more than one hundred times as much as it does at 1,000° C., and if the temperature is raised to 2,000° C., the radiation is increased more than two thousand fold. This fact is often made use of in the measurement of temperatures, and pyrometers operating on this principle have the marked advantage that it is not necessary to heat any part of the measuring apparatus to the temperature of the body being studied. This is particularly important for work above 1,600° C., for there is no substance which retains its temperature measuring properties uniform when subjected to such extreme heats. Again, the products of combustion in furnaces contaminate any pyrometric material introduced, thus necessitating frequent recalibrations.

<sup>1</sup> LECHATELIER and BURGESS, *Measurement of High Temperatures*, pp. 237-243, 291-303, 325-327, 336-337.

GRIFFITHS, *Methods of Measuring Temperature*, pp. 113-118.

The radiation method of measuring temperatures, however, is complicated by the fact that incandescent bodies differ materially as regards both the intensity and quality of the light which they emit. For example, the radiation from iron or carbon is much greater than that from such substances as magnesia or polished platinum at the same temperature. If a pyrometer were calibrated by measuring the radiation from one substance and then used to measure the temperature of another possessing different radiating properties large errors would result in many cases.

This difference in radiating properties has led to the use of "black bodies" as standard radiators and absorbers. A black body is defined as one which absorbs all the radiation falling upon it, and it therefore neither reflects nor transmits any radiation. It also has the property, when heated, of emitting radiation whose intensity is a function of temperature only and depends in no way upon the physical constants of the material of which it is made. Further, the intensity of the radiation from a black body at a given temperature is greater than that from any other body at the same temperature.

**187. Black Body Furnace.**—Experimentally, a black body is very closely approximated by a hollow opaque inclosure with a small opening. If the internal area of the inclosure is large compared to the opening, radiation falling upon it enters the inclosure and is reflected diffusely back and forth so many times, that it is practically all absorbed before any can emerge. Again, if the walls are heated uniformly to any temperature, the radiation emerging from the opening has been reflected back and forth so many times that it no longer has properties characteristic of the material of the walls. Such a body is at the same time a perfect absorber and a perfect emitter. The radiation from a crack or other small opening in an ordinary furnace is nearly black body radiation, so also is that from the inside of a narrow wedge formed by folding a thin metallic ribbon into a very flat *V*.

A black body, satisfactory for experimental purposes, is made by winding a porcelain tube with thin platinum foil through which a heating current may be passed. The center of the tube is closed by a porcelain disk and between this and the end, through which observations are made, is arranged a series of diaphragms, also of porcelain, whose apertures increase in diameter successively toward the end. These minimize the disturbing effects of air currents and increase the number of internal reflec-

tions which the radiation must make before it emerges. To protect the internal tube from external disturbances and reduce the heat losses to a minimum, it is surrounded by another tube upon which is wound a second heating coil of some alloy such as nichrome or therlo. Outside of this is a series of several additional tubes with air spaces between them, the outer one usually being surrounded by powdered magnesia. By properly adjusting the heating currents through the two coils, any desired temperature up to 1,600° C. may be maintained with a high degree of constancy. The temperature of the black body is usually measured by a platinum, platinum-rhodium thermocouple, the junction of which is supported by two small holes through the central disk, with the insulated leads passing out through the rear of the furnace.

**188. Distribution of Energy in the Spectrum.**—If one measures the total energy emitted by a black body, he finds that it increases rapidly as the temperature is raised. The law connecting black body radiation with temperature was first stated by Stefan and later deduced theoretically by Boltzmann. It is

$$E = ST^4 \quad (6)$$

where  $E$  is the total energy radiated,  $T$  the absolute temperature, and  $S$ , a constant which is approximately  $5.6 \times 10^{-5}$ , ergs per square centimeter per second. Although this law is rigidly true only for a black body it is found to hold approximately for most surfaces, the constant  $S$  being different for each.

If the radiation from a black body is separated out into a spectrum and the energy associated with each wave length is measured, it is found that not only is there a continuous change in the amount of energy as we go from one wave length to another, but also that the distribution of energy among the wave lengths changes as we vary the temperature. Figure 129 gives the distribution of energy among the wave lengths for a series of temperatures. It will be noted that as the temperature is raised, the energy in each wave length increases but not in the same proportion. Also that the wave length containing the maximum energy decreases as the temperature is raised. This is in accord with the common observation that, starting with low temperatures, a body appears at first dull red, then yellowish or cherry red, and finally becomes "white hot" as extreme temperatures are reached. Wien has shown that the wave length for maximum

energy and the absolute temperature are connected by the simple law

$$\lambda_{\max} T = \text{const.} \quad (7)$$

He has also shown that the distribution of the energy among the wave lengths at a given temperature, as illustrated by Fig. 129, follows very closely the law

$$E_{\lambda} = c_1 \lambda^{-5} e^{-\frac{c_2}{\lambda T}} \quad (8)$$

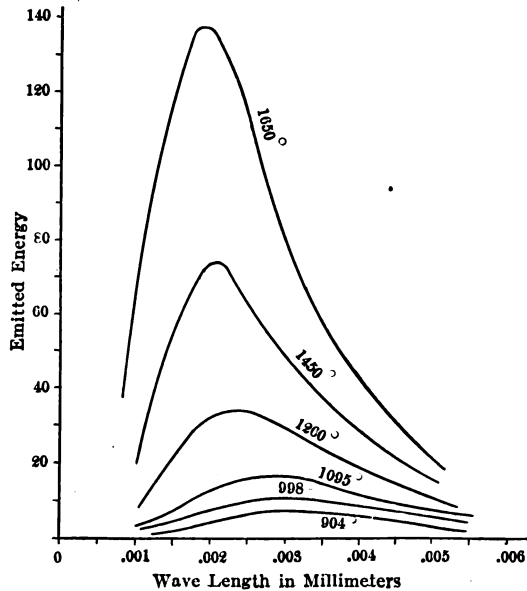


FIG. 129.—Energy distribution for a black body.

where  $E_{\lambda}$  is the energy in the wave length interval  $\lambda$  to  $\lambda + d\lambda$ ;  $e$  is the base of the Napierian logarithms;  $T$  the absolute temperature, and  $c_1$  and  $c_2$  are constants. For other radiating surfaces, it is found that  $E_{\lambda}$  follows very closely the above law but different constants must be used.

**189. Application to Pyrometry.**—It is obvious that any of the three equations just given might be used to measure temperatures. It is found, however, that eq. (8) is most suitable, and when it is applied, only one wave length is used, or at least only those lying within a very restricted range. This equation lends itself more easily to calculation if it is put in the form:

$$\log_e E_{\lambda} = k - \frac{c_2}{\lambda T} \quad (9)$$

where

$$k = \log_e c_1 - 5 \log \lambda.$$

Let  $E_1$  and  $E_2$  be the energies for a particular wave length radiated at the temperatures  $T_1$  and  $T_2$ , respectively. Substituting these values in eq. (9) and subtracting, we have

$$\log_e \frac{E_1}{E_2} = \frac{c_2}{\lambda} \left( \frac{1}{T_2} - \frac{1}{T_1} \right) \tag{10}$$

If  $T_2$  is a standard temperature and  $T_1$  an unknown, then by measuring  $E_1$  and  $E_2$  or their ratio, by appropriate means,  $T_1$  may be computed. Solving eq. (10) for  $T_1$  and using common logarithms,

$$T_1 = \frac{c_2}{\lambda} \frac{1}{\frac{c_2}{\lambda T_2} + 2.303 \log_{10} \frac{E_2}{E_1}} \tag{11}$$

**190. The Optical Pyrometer.**—One of the most convenient forms of the optical pyrometer is that devised by Holborn and

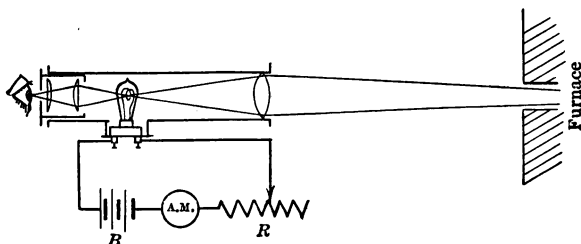


FIG. 130.—Holborn and Kurlbaum optical pyrometer.

Kurlbaum. It consists of a telescope in the focal plane of which is mounted a small six volt lamp with either a carbon or tungsten filament, as shown in Fig. 130. When the telescope is focused on the furnace and the filament is lighted, there is seen, on looking into it, a field of uniform illumination with a fine line extending across it. If the filament is hotter than the furnace, it appears as a bright line across a dark background; but if the furnace is hotter, there is seen a dark line across a bright background. If filament and furnace are at the same temperature, the line disappears and the field is uniform throughout. The eye is very sensitive to differences of brightness and a difference of two degrees between furnace and filament may easily be detected. Current for the filament is furnished by a storage battery, controlled by a

rheostat and measured by an ammeter. The indications of the pyrometer are thus in terms of the filament current. If the furnace is held in turn at a series of known temperatures and the filament currents for balance obtained, a calibration curve may be plotted showing temperature as a function of current.

A number of improvements in the original form of the Holborn-Kurlbaum pyrometer have been made by Mendenhall.<sup>1</sup> One of them is a method by which such an instrument may be calibrated over a wide range using only one standard temperature. This is accomplished by holding the temperature of the furnace constant and rotating between it and the pyrometer a sectored disk which allows only a known fraction of the energy to enter the telescope. This is equivalent to reducing the temperature of the furnace. Suppose the fraction of the energy transmitted is  $R$ . Then  $E_1 = RE_2$ . Substituting this value in eq. (11), we have, for the apparent temperature of the furnace,

$$T_1 = \frac{c_2}{\lambda} \frac{1}{\frac{c_2}{\lambda T_2} + 2.303 \log_{10} \frac{1}{R}} \quad (12)$$

By using a series of sectors, for example with  $R$  equal to  $\frac{1}{2}$ ,  $\frac{1}{4}$ ,  $\frac{1}{8}$ , etc., a series of apparent temperatures are obtained, and the filament temperatures corresponding to each may be determined. This gives a calibration for the instrument for ranges below the standard temperature actually maintained in the furnace. The necessary narrow wave length band is secured by mounting behind the eyepiece a disk of red glass of special quality. The instrument also may be used to measure temperatures above that of the standard by using the sectored disk when taking observations on the unknown temperature, thus reducing it to an apparent lower temperature within the calibration range just determined. For example, if an unknown temperature is observed through a sector of transmission ratio  $R$  and is found to be the same as the standard temperature  $T_2$  then the unknown temperature is obtained from eq. (11) by putting  $E_2 = RE_1$  which gives

$$T_1 = \frac{c_2}{\lambda} \frac{1}{\frac{c_2}{\lambda T_2} + 2.303 \log_{10} R} \quad (13)$$

In a similar manner a calibration curve may be computed for a given sector extending the range of the instrument to any desired

<sup>1</sup> MENDENHALL, *Phys. Rev.*, vol. 35, 1910, p. 74.



value. For this purpose, it is only necessary to substitute for  $T_2$  in eq. (13) the value of temperature corresponding to each particular current read off from the original calibration curve. These computed values of  $T_1$  plotted against the corresponding values of filament current give the calibration curve for the instrument when used with the sectors to measure unknown temperatures.

It should be borne in mind that the Wien radiation law upon which this method is based holds only for black body radiation, and that the method of calibration just described makes use of a black body as a source of radiation. If it should be used to determine the temperature of some other body such as a heated filament or strip of metal not within an enclosure, its indications will be the temperature of a black body which would emit the same amount of energy at the particular wave length used in the calibration. Since no other body emits more energy at any wave length than a black body at the same temperature, and most substances emit less than a black body, the reading of the optical pyrometer will, in general, be too low. The reading obtained is called the "black body temperature." Mendenhall and Forsythe<sup>1</sup> have made an extended study of the differences between the "black body" and "true" temperatures of a great many substances with the result that the optical pyrometer may now be very generally used to determine actual temperatures. A few of their values for carbon and tungsten are given below:

| Black body temperature | Corresponding true temperature |                    |
|------------------------|--------------------------------|--------------------|
| Degrees Centigrade     | Tungsten, Degrees C.           | Carbon, Degrees C. |
| 1,000                  | 1,068                          | 1,012              |
| 1,200                  | 1,273                          | 1,222              |
| 1,400                  | 1,486                          | 1,430              |
| 1,600                  | 1,700                          | 1,638              |
| 1,800                  | 1,910                          | 1,847              |
| 2,000                  | 2,126                          | 2,056              |
| 2,200                  | 2,345                          |                    |
| 2,400                  | 2,565                          |                    |
| 2,600                  | 2,783                          |                    |
| 2,700                  | 2,890                          |                    |

<sup>1</sup> MENDENHALL and FORSYTHE, *Astrophysical Jour.*, vol. 37, 1913, p. 389.

**191. Experiment 41.**—Connect the apparatus as shown in Fig. 130. Ascertain the heating currents to be used through the two windings of the furnace and take care that they are never exceeded, particularly through the inner platinum winding. Find out, also, the maximum current allowable for the filament of the pyrometer lamp. Fill the vessel containing the cold junction of the thermocouple with cracked ice to maintain it at  $0^{\circ}$  C. Measure the E.M.F. of the thermocouple with a low resistance potentiometer, special instructions for which are given in chap. IV. A calibration curve is furnished with the thermocouple. Focus the eyepiece of the telescope on the lamp filament and as soon as the furnace is warm enough to permit it, focus the telescope so that the inner circle of the furnace is distinctly seen. As the furnace heats up, determine its temperature with the thermocouple and balance the pyrometer every few minutes.

When a temperature of  $1,200^{\circ}$  C. has been reached, reduce the heating current through both windings and allow the temperature to rise slowly to about  $1,300^{\circ}$  C. and then hold the furnace constant at this value. When holding the temperature constant, it is best to leave the potentiometer setting fixed and keep the galvanometer balanced by adjusting the heating current rheostat. When a steady state has been secured, make several settings of the pyrometer. Then introduce the  $\frac{1}{2}$  sector and with the motor running, again make several settings on this apparent temperature. Repeat, using the  $\frac{1}{4}$ ,  $\frac{1}{10}$ ,  $\frac{1}{30}$ ,  $\frac{1}{60}$ , and  $\frac{1}{120}$  sectors. Check the settings with no sector between each replacement to insure constancy of conditions. Two observers are required for this experiment, one to manipulate the pyrometer, and one to hold the furnace temperature constant. Measure the temperature of the filaments of several incandescent lamps of different types and candle power using such a sector that the current through the pyrometer lamp lies within the range covered by the calibration.

**Report.**—Compute the effective temperatures below the standard temperature secured by the various sectors by use of eq. (12). Use for  $c_2$  the value 14,350 and for the wave length 0.658. The standard temperature is that in degrees absolute at which the furnace was held constant and is obtained from the calibration curve for the thermocouple. The computed values of  $T_1$  are also in degrees absolute. Plot temperatures below that of the furnace.

Plot calibration curves for values above that of the furnace for the  $\frac{1}{10}$ ,  $\frac{1}{30}$ , and  $\frac{1}{120}$  sectors, by use of eq. 13. To do this, read from the first curve the values of  $T$  for a series of values of filament currents. Substitute these values of  $T_2$  in eq. 13 using for  $R$  the appropriate ratio. These values of  $T$ , when plotted against the currents, give the calibration curve for a given sector for the high range.

Read from these curves the black body temperatures of the lamps measured and by use of the tables given above, determine their true temperatures in degrees centigrade.

If the temperature of the sun is about  $6,000^\circ \text{C.}$ , find the size of sector opening necessary to measure it on the instrument used.

## APPENDIX

### CALCULATION OF INDUCTANCE AND CAPACITANCE

In designing electrical apparatus and in checking the results of bridge measurements it is often advantageous to determine the inductance of coils by calculation from their dimensions and number of turns. In connection with its work in establishing primary units of inductance, the United States Bureau of Standards made an exhaustive study of the formulas for this purpose, and, besides extending those available at the time, developed a number of new ones. A comprehensive collection of inductance formulas, together with numerical examples, is given in the *Bulletin* of the Bureau of Standards, vol. 8, 1912, pp. 1 to 237. This publication is known also as Scientific Paper 169. In another publication, "Radio Instruments and Measurements," Circular 74, there is given a series of simplified formulas which yield results accurate to one-tenth of one per cent.

Three formulas, taken from Circular 74, are given below. They apply to the coils most commonly used in every day practice. Lengths and other dimensions are expressed in centimeters, and the inductance calculated is given in microhenries. One henry =  $10^3$  millihenries =  $10^6$  microhenries =  $10^9$  C.G.S. electromagnetic units. It is assumed that the coil is placed in air or other medium whose permeability is unity, and that no iron is in the vicinity.

*I. Single Layer Coil or Solenoid.—Nagaoka's Formula.*

$$L = \frac{0.03948a^2n^2}{b}K \quad (1)$$

where  $n$  = number of turns of coil

$a$  = radius of coil, i.e., axis to center of any wire

$b$  = length of coil, i.e., number of turns times distance between centers of adjacent turns.

$K$  is a correction factor made necessary by the demagnetizing action of the ends of the coil and is a function of  $\frac{2a}{b}$ . Its value may be read from Table I. If the coil is very long compared to

its diameter,  $K = 1$ . Formula (1) takes no account of the size or shape of the cross-section of the wire and assumes that the diameter of the wire is small compared to the dimensions of the coil, and that the coil is compactly wound.

TABLE I.—VALUES OF  $K$  FOR USE IN FORMULA I

| Diameter Length | $K$    | Difference | Diameter Length | $K$    | Difference | Diameter Length | $K$    | Difference |
|-----------------|--------|------------|-----------------|--------|------------|-----------------|--------|------------|
| 0.00            | 1.0000 | -0.0209    | 2.00            | 0.5255 | -0.0118    | 7.00            | 0.2584 | -0.0047    |
| .05             | .9791  | 203        | 2.10            | .5137  | 112        | 7.20            | .2537  | 45         |
| .10             | .9588  | 197        | 2.20            | .5025  | 107        | 7.40            | .2491  | 43         |
| .15             | .9391  | 190        | 2.30            | .4918  | 102        | 7.60            | .2448  | 42         |
| .20             | .9201  | 185        | 2.40            | .4816  | 97         | 7.80            | .2406  | 40         |
| 0.25            | 0.9016 | -0.0178    | 2.50            | 0.4719 | -0.0093    | 8.00            | 0.2366 | -0.0094    |
| .30             | .8838  | 173        | 2.60            | .4626  | 89         | 8.50            | .2272  | 86         |
| .35             | .8665  | 167        | 2.70            | .4537  | 85         | 9.00            | .2185  | 79         |
| .40             | .8499  | 162        | 2.80            | .4452  | 82         | 9.50            | .2106  | 73         |
| .45             | .8337  | 156        | 2.90            | .4370  | 78         | 10.00           | .2033  |            |
| 0.50            | 0.8181 | -0.0150    | 3.00            | 0.4292 | -0.0075    | 10.0            | 0.2033 | -0.0133    |
| .55             | .8031  | 146        | 3.10            | .4217  | 72         | 11.0            | .1903  | 113        |
| .60             | .7885  | 140        | 3.20            | .4145  | 70         | 12.0            | .1790  | 98         |
| .65             | .7745  | 136        | 3.30            | .4075  | 67         | 13.0            | .1692  | 87         |
| .70             | .7609  | 131        | 3.40            | .4008  | 64         | 14.0            | .1605  | 78         |
| 0.75            | 0.7478 | -0.0127    | 3.50            | 0.3944 | -0.0062    | 15.0            | 0.1527 | -0.0070    |
| .80             | .7351  | 123        | 3.60            | .3882  | 60         | 16.0            | .1457  | 63         |
| .85             | .7228  | 118        | 3.70            | .3822  | 58         | 17.0            | .1394  | 58         |
| .90             | .7110  | 115        | 3.80            | .3764  | 56         | 18.0            | .1336  | 52         |
| .95             | .6995  | 111        | 3.90            | .3708  | 54         | 19.0            | .1284  | 48         |
| 1.00            | 0.6884 | -0.0107    | 4.00            | 0.3654 | -0.0052    | 20.0            | 0.1236 | -0.0085    |
| 1.05            | .6777  | 104        | 4.10            | .3602  | 51         | 22.0            | .1151  | 73         |
| 1.10            | .6673  | 100        | 4.20            | .3551  | 49         | 24.0            | .1078  | 63         |
| 1.15            | .6573  | 98         | 4.30            | .3502  | 47         | 26.0            | .1015  | 56         |
| 1.20            | .6475  | 94         | 4.40            | .3455  | 46         | 28.0            | .0959  | 49         |
| 1.25            | 0.6381 | -0.0091    | 4.50            | 0.3409 | -0.0045    | 30.0            | 0.0910 | -0.0102    |
| 1.30            | .6290  | 89         | 4.60            | .3364  | 43         | 35.0            | .0808  | 80         |
| 1.35            | .6201  | 86         | 4.70            | .3321  | 42         | 40.0            | .0728  | 64         |
| 1.40            | .6115  | 84         | 4.80            | .3279  | 41         | 45.0            | .0664  | 53         |
| 1.45            | .6031  | 81         | 4.90            | .3238  | 40         | 50.0            | .0611  | 43         |
| 1.50            | 0.5950 | -0.0079    | 5.00            | 0.3198 | -0.0076    | 60.0            | 0.0528 | -0.0061    |
| 1.55            | .5871  | 76         | 5.20            | .3122  | 72         | 70.0            | .0467  | 48         |
| 1.60            | .5795  | 74         | 5.40            | .3050  | 69         | 80.0            | .0419  | 38         |
| 1.65            | .5721  | 72         | 5.60            | .2981  | 65         | 90.0            | .0381  | 31         |
| 1.70            | .5649  | 70         | 5.80            | .2916  | 62         | 100.0           | .0350  |            |
| 1.75            | 0.5579 | -0.0068    | 6.00            | 0.2854 | -0.0059    |                 |        |            |
| 1.80            | .5511  | 67         | 6.20            | .2795  | 56         |                 |        |            |
| 1.85            | .5444  | 65         | 6.40            | .2739  | 54         |                 |        |            |
| 1.90            | .5379  | 63         | 6.60            | .2685  | 52         |                 |        |            |
| 1.95            | .5316  | 61         | 6.80            | .2633  | 49         |                 |        |            |

*II. Multiple Layer Coil.*—For a long coil with few layers, the inductance is given by

$$L = L_s - \frac{0.01257n^2ac}{b}(0.693 + B_s) \quad (2)$$

where  $L_s$  = inductance of mean single layer given by formula (1)

$n$  = number of turns of the coil

$a$  = radius of coil measured from the axis to the center of cross-section of the winding

$b$  = length of coil = distance between centers of turns times number of turns in one layer

$c$  = radial depth of winding = distance between centers of two adjacent layers times the number of layers.

$B_s$  = correction given in Table II in terms of the ratio  $\frac{b}{c}$ .

TABLE II.—VALUES OF  $B_s$  FOR USE IN FORMULA II

| $b/c$ | $B_s$  | $b/c$ | $B_s$  | $b/c$ | $B_s$  |
|-------|--------|-------|--------|-------|--------|
| 1     | 0.0000 | 11    | 0.2844 | 21    | 0.3116 |
| 2     | 0.1202 | 12    | 0.2888 | 22    | 0.3131 |
| 3     | 0.1753 | 13    | 0.2927 | 23    | 0.3145 |
| 4     | 0.2076 | 14    | 0.2961 | 24    | 0.3157 |
| 5     | 0.2292 | 15    | 0.2991 | 25    | 0.3169 |
| 6     | 0.2446 | 16    | 0.3017 | 26    | 0.3180 |
| 7     | 0.2563 | 17    | 0.3041 | 27    | 0.3190 |
| 8     | 0.2656 | 18    | 0.3062 | 28    | 0.3200 |
| 9     | 0.2730 | 19    | 0.3082 | 29    | 0.3209 |
| 10    | 0.2792 | 20    | 0.3099 | 30    | 0.3218 |

*III. Short Circular Coil with Rectangular Cross Section.*—For a coil having a shape such as shown in Fig. 131, the inductance is given by a formula due to Stefan. It is deduced on the assumption that the wire is rectangular in cross-section, and that the insulating space between turns is negligible. Further, the axial and radial dimensions of the winding are supposed to be small compared to the mean radius of the coil.

Let  $a$  = the mean radius of the winding measured from the axis to the center of the cross-section

$b$  = the axial dimension of the cross-section

$c$  = the radial dimension of the cross-section

$d = \sqrt{b^2 + c^2}$  = the diagonal of the cross-section

$n$  = number of turns of rectangular wire.

There are two cases depending upon the relative values of  $b$  and  $c$ .

Case 1.  $b > c$ .

$$L = 0.01257an^2 \left[ 2.303 \left( 1 + \frac{b^2}{32a^2} + \frac{c^2}{96a^2} \right) \log_{10} \frac{8a}{d} - y_1 + \frac{b^2}{16a^2} y_2 \right] \quad (3)$$

Case 2.  $b < c$ .

$$L = 0.01257an^2 \left[ 2.303 \left( 1 + \frac{b^2}{32a^2} + \frac{c^2}{96a^2} \right) \log_{10} \frac{8a}{d} - y_1 + \frac{c^2}{16a^2} y_3 \right] \quad (4)$$

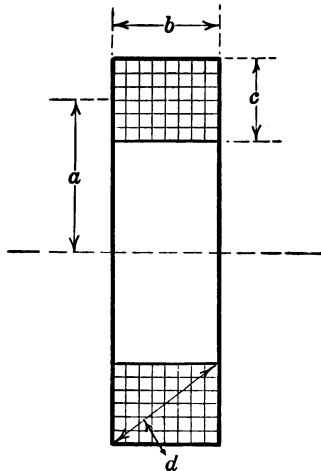


FIG. 131.—Multiple layer coil with winding of rectangular cross section.

The constants  $y_1$ ,  $y_2$ , and  $y_3$  depend upon relative values of  $b$  and  $c$ , and are given in Table III. The ratio of these quantities is always to be taken so as to give a proper fraction; i.e., in formula (3), use  $c/b$ , and in formula (4), use  $b/c$ . In eq. (3),  $y_1$  is the same function of  $c/b$  that it is of  $b/c$  in eq. (4).

TABLE III.—CONSTANTS USED IN FORMULAS (3) and (4)

| $b/c$ or $c/b$ | $y_1$  | Difference | $c/b$ | $y_2$ | Difference | $b/c$ | $y_3$ | Difference |
|----------------|--------|------------|-------|-------|------------|-------|-------|------------|
| 0              | 0.5000 | 0.0253     | 0     | 0.125 | 0.002      | 0     | 0.597 | 0.002      |
| 0.025          | .5253  | 237        |       |       |            |       |       |            |
| .05            | .5490  | 434        | 0.05  | .127  | 5          | 0.05  | .599  | 3          |
| .10            | .5924  | 386        | .10   | .132  | 10         | .10   | .602  | 6          |
| 0.15           | 0.6310 | 0.0342     | 0.15  | 0.142 | 0.013      | 0.15  | 0.608 | 0.007      |
| .20            | .6652  | 301        | .20   | .155  | 16         | .20   | .615  | 9          |
| .25            | .6953  | 266        | .25   | .171  | 20         | .25   | .624  | 9          |
| .30            | .7217  | 230        | .30   | .192  | 23         | .30   | .633  | 10         |
| 0.35           | 0.7447 | 0.0198     | 0.35  | 0.215 | 0.027      | 0.35  | 0.643 | 0.011      |
| .40            | .7645  | 171        | .40   | .242  | 31         | .40   | .654  | 11         |
| .45            | .7816  | 144        | .45   | .273  | 34         | .45   | .665  | 12         |
| .50            | .7960  | 121        | .50   | .307  | 37         | .50   | .677  | 13         |
| 0.55           | 0.8081 | 0.0101     | 0.55  | 0.344 | 0.040      | 0.55  | 0.690 | 0.012      |
| .60            | .8182  | 83         | .60   | .384  | 43         | .60   | .702  | 13         |
| .65            | .8265  | 66         | .65   | .427  | 47         | .65   | .715  | 14         |
| .70            | .8331  | 52         | .70   | .474  | 49         | .70   | .729  | 13         |
| 0.75           | 0.8383 | 0.0039     | 0.75  | 0.523 | 0.053      | 0.75  | 0.742 | 0.014      |
| .80            | .8422  | 29         | .80   | .576  | 56         | .80   | .756  | 15         |
| .85            | .8451  | 19         | .85   | .632  | 59         | .85   | .771  | 15         |
| .90            | .8470  | 10         | .90   | .690  | 62         | .90   | .786  | 15         |
| 0.95           | 0.8480 | 0.0003     | 0.95  | 0.752 | 0.064      | 0.95  | 0.801 | 0.015      |
| 1.00           | .8483  | .....      | 1.00  | .816  | .....      | 1.00  | .816  |            |

IV. Coil of Round Wire Wound in a *Channel of Rectangular Cross-section*. If the insulation is not too thick, eqs. (3) and (4) give a very close approximation for the case in which ordinary round wire is used. When the percentage of the cross-section occupied by the insulating space is large, the following correction must be added to these formulas.

$$\Delta L = 0.01257an^2 \left[ 2.303 \log_{10} \frac{D}{d_0} + 0.155 \right] \quad (5)$$

where  $D$  = distance between centers of adjacent wires  
 $d_0$  = diameter of the bare wire.

#### CALCULATION OF CAPACITANCE

The following formulas<sup>1</sup> may be used to calculate the capacitance of condensers of the common forms. The dimensions of the condensers are measured in centimeters, and the capacitance is given in micro-microfarads. In these formulas, no correction

<sup>1</sup> *Cir.* 74, U. S. Bureau of Standards, p. 235.



is made for the curving of the electrostatic field at the edges of plates, etc., and it is assumed that the distance between plates is small compared to their linear dimensions.

*V. Parallel Plate Condenser*

$$C = 0.0885K \frac{S}{T} \quad (6)$$

where  $S$  = surface area of one plate

$T$  = thickness of dielectric

$K$  = dielectric constant ( $K = 1$  for air, and for most substances, lies between 1 and 10).

If, instead of a single pair of plates, there are  $N$  similar plates with dielectric between them alternate plates being connected in parallel,

$$C = 0.0885K \frac{(N - 1)S}{T} \quad (7)$$

*VI. Variable Condenser with Semi-circular Plates*

$$C = 0.1390K \frac{(N - 1)(r_1^2 - r_2^2)}{T} \quad (8)$$

where  $N$  = total number of plates

$r_1$  = outside radius of the plates

$r_2$  = inside radius of the plates

$T$  = thickness of dielectric

$K$  = dielectric constant

This formula gives the maximum capacitance, i.e., when the movable plates are entirely within the spaces between the fixed plates. As the movable plates are rotated out, the capacitance decreases in direct proportion to the angle through which they are turned.

*VII. Isolated Disk of Negligible Thickness*

$$C = 0.354d \quad (9)$$

where  $d$  = diameter of the disk

*VIII. Isolated Sphere*

$$C = 0.556d \quad (10)$$

where  $d$  = diameter of the sphere

*IX. Two Concentric Spheres*

$$C = 1.112K \frac{r_1 r_2}{r_1 - r_2} \quad (11)$$

where  $r_1$  = inner radius of outside sphere

$r_2$  = outer radius of inner sphere

$K$  = dielectric constant of material between spheres.

*X. Two Coaxial Cylinders*

$$C = 0.2416K \frac{l}{\log_{10} \frac{r_1}{r_2}} \quad (12)$$

where  $l$  = length of each cylinder

$r_1$  = inner radius of outer cylinder

$r_2$  = outer radius of inner cylinder

$K$  = dielectric constant of material between cylinders.

## INDEX

- A**
- Alpha rays, 212  
Alternating current galvanometer, 165  
Ammeter, 74  
    adjustment of, 76  
    calibration of, 80  
Ampere turn, definition of, 102  
Amplification factor of electron tube, 227  
    dynamic method for, 231  
Anderson modification of Maxwell's bridge, 129  
Atom, structure of, 200  
Audio-oscillator, 155
- B**
- Ballantine, dynamic method for resistance of electron tube, 234  
Battery test, 53  
Beta rays, 213  
Black body, 244  
    temperatures corrected to true, 249
- C**
- Campbell, measurement of inductance, 181  
Carey-Foster bridge for resistance, 42  
    method for mutual inductance, 124  
Cathode glow, 205  
    rays, 208  
Checking devices for ballistic galvanometer, 33  
Comparison of cells, 63  
Condensers, capacitance of, 86  
    comparison of, 89  
    grouping of, 87  
    measurement by Fleming and Clinton commutator, 93
- D**
- Crooke's dark space, 205  
Current, measured by electro-dynamometer, 72  
    Kelvin balance, 70  
    potentiometer, 79
- D**
- Damped sine wave, 135  
Decrement, logarithmic, 136  
Demagnetizing factor, 96  
Discharge of condenser, aperiodic discharge, 131  
    critically damped discharge, 132  
    oscillatory discharge, 133  
    through gases, theory of, 205  
Duddell thermo-galvanometer, 162
- E**
- Effective value of an alternating current, 148  
Electrodynamometer, Siemens, 72  
Electrolytes, resistance of, 194  
Electrons, 198  
Electron tubes, 218  
    amplification factor of, 227  
    as oscillator, 159  
    characteristics for, 228  
    impedance of, 234
- F**
- Faraday dark space, 206  
Fleming and Clinton commutator, 92  
Fluxmeter, Grassot, 31  
Forsythe and Mendenhall, corrections for black body temperatures, 249  
Frequency bridge, 186
- G**
- Galvanometer, description of, 17  
    ballistic galvanometer, theory of, 25

- Galvanometer, constant of, 24  
 current galvanometer, 19  
 D'Arsonval galvanometer, 18  
 figure of merit, 22  
 Thomson galvanometer, 17
- Gamma rays, 214
- Gauss, definition of, 101
- Gilbert, definition of, 101
- Graham, potential gradient in discharge tubes, 206
- Grover, phase angle of condensers, 191
- H
- Heaviside's bridge for inductance, 180
- Heydweiller's network for mutual inductance, 177
- Holborn and Kurlbaum's optical pyrometer, 247
- Hopkinson's bar and yoke, 107
- Hysteresis, 104  
 measurement of, 114
- I
- Impedance, 139
- Inductance, 117  
 calculation of, 252  
 coefficients of, 118  
 comparisons of, 120  
 standards of, 119
- Induction, magnetic, 96
- Insulation resistance, measurement of, 46
- Intensity of magnetization, 96
- Internal resistance of cells, 50  
 condenser and ballistic galvanometer method for, 52  
 voltmeter ammeter method for, 51
- Ionization, theory of, 151
- K
- Kaufmann, variation of  $\frac{e}{m}$  with velocity, 214
- Kelvin current balance, 70
- Kelvin current balance, 70 double bridge for resistance measurement, 40  
 galvanometer, 17
- Kennelly and Pierce, motional impedance, 190
- Kenotron, 224
- Keys, 2
- Kumagen, 155
- Kurlbaum, optical pyrometer, 247
- L
- Lummer-Brodhun photometer, 241
- M
- Magnetic circuit, 99  
 shields, 18
- Magnetism, general principles, 94
- Magnetization curves, 103
- Maxwell, definition of, 101
- Maxwell's bridge for mutual inductance, 169
- Mendenhall, use of optical pyrometer, 248  
 correction for black body temperatures, 249
- Microphone hummer, 154
- Miller, amplification factor of electron tubes, 230
- Motional impedance, 191
- Motor generator, 153
- Multipliers for voltmeter, 77
- Mutual inductance bridge, 184
- N
- Nagaoka's inductance formula, 252
- Negative glow, 206
- Notebooks, 6
- O
- Oersted, definition of, 102
- Ohm's law, 35
- P
- Permeability, magnetic, 97
- Phase angle of condensers, 191
- Photo-electric effect, 219
- Photometer, 240

- Pierce and Kennelly, motional impedance, 190  
 Pohl's commutator, 2  
 Polarization of cell, 54  
 Positive column, 206  
 Post-office box, 38  
 Potentiometer, description of, 55  
   Leeds and Northrup, 58  
   Tinsley, 62  
   Wolff, 60  
 Power, measurement of, 82  
   factor, definition of, 150  
   of condensers, 191  
 Pyrometer, optical, 243
- R
- Radiation, intensity of, 239  
 Radioactive substances, 212  
 Reactance, 139  
 Resistance, specific, 35  
   measurement of high resistance, 46  
   of low resistance, 40  
   temperature coefficient of, 36  
 Resistances for current measurements, 80  
 Resonance, electrical, 142  
   parallel resonance, 144  
   series resonance, 143  
 Rheostats, 3  
 Root mean square value of an alternating current, 149  
 Rowland ring, 111
- S
- Saturation current, 201  
 Sechometer, 151  
 Siemen's electro-dynamometer, 72  
 Sine wave, vector representation of, 141  
 Space charge, 222  
   current, 221  
 Specific resistance, 35  
 Spectrum, distribution of energy in, 245  
 Standard cell, E.M.F. of, 11  
   temperature coefficient of, 12
- Stefan Boltzman law, 245  
 Steinmetz coefficient, 106  
 Stroude and Oate's bridge, 173  
 Susceptibility, 97  
 Switchboard, 5  
 Switches, 2
- T
- Telephone receiver, 161  
 Temperature coefficient of resistance, 36  
   standard cell, 12  
 Thermo-galvanometer, Duddell, 162  
 Time constant of circuit containing resistance and inductance, 126  
   and capacitance, 128  
   inductance and capacitance, 131  
 Tinsley potentiometer, 62  
 Trowbridge's bridge, 174  
 Tungar rectifier, 235
- U
- Units, systems of, 7  
   electromagnetic, 8  
   electrostatic, 8  
   practical, 9  
   rationalized practical, 13  
   ratios of, 12
- V
- Variable impedance circuit, 188  
 Vibration galvanometer, 163  
 Volt box, 67  
 Voltmeter, adjustment of, 74  
   calibration of, 68  
 Vreeland oscillator, 157
- W
- Wattmeters, description of, 82  
   compensation of, 83  
   calibration of, 84  
 Wein, phase angle of condensers, 191  
 Wein's law, 246  
 Weston instruments, 75  
   standard cell, 64  
 Wheatstone bridge, 36  
 Wire interrupter, 153  
 Wolff potentiometer, 60











This book may be kept

**30 FOURTEEN DAYS**

from last date stamped below. A fee of **TWO CENTS** will be charged for each day the book is kept over time.

89074766387



B89074766387A

|        |  |  |  |
|--------|--|--|--|
| DEC 50 |  |  |  |
| DEC 51 |  |  |  |
| DEC 52 |  |  |  |
| DEC 53 |  |  |  |
| DEC 54 |  |  |  |
| DEC 55 |  |  |  |
| DEC 56 |  |  |  |
| DEC 57 |  |  |  |
| DEC 58 |  |  |  |
| DEC 59 |  |  |  |
| DEC 60 |  |  |  |
| DEC 61 |  |  |  |
| DEC 62 |  |  |  |
| DEC 63 |  |  |  |
| DEC 64 |  |  |  |
| DEC 65 |  |  |  |
| DEC 66 |  |  |  |
| DEC 67 |  |  |  |
| DEC 68 |  |  |  |
| DEC 69 |  |  |  |
| DEC 70 |  |  |  |
| DEC 71 |  |  |  |
| DEC 72 |  |  |  |
| DEC 73 |  |  |  |
| DEC 74 |  |  |  |
| DEC 75 |  |  |  |
| DEC 76 |  |  |  |
| DEC 77 |  |  |  |
| DEC 78 |  |  |  |
| DEC 79 |  |  |  |
| DEC 80 |  |  |  |
| DEC 81 |  |  |  |
| DEC 82 |  |  |  |
| DEC 83 |  |  |  |
| DEC 84 |  |  |  |
| DEC 85 |  |  |  |
| DEC 86 |  |  |  |
| DEC 87 |  |  |  |
| DEC 88 |  |  |  |
| DEC 89 |  |  |  |
| DEC 90 |  |  |  |
| DEC 91 |  |  |  |
| DEC 92 |  |  |  |
| DEC 93 |  |  |  |
| DEC 94 |  |  |  |
| DEC 95 |  |  |  |
| DEC 96 |  |  |  |
| DEC 97 |  |  |  |
| DEC 98 |  |  |  |
| DEC 99 |  |  |  |
| DEC 00 |  |  |  |

Terry.

LL

.T27

Advanced laboratory

.5

practice in electricity and

LL

.T27

.5

**STORAGE**

LIBRARY

89074766387



b89074766387a